

**COMPLETE INDEX**  
for  
**PERPETUAL TROUBLE SHOOTER'S MANUALS**  
Volumes I, II, III, IV, V, VI, VII, VIII, IX, and X  
and  
**"HOW IT WORKS"**  
*Special Section of Volume X*

by  
**John F. Rider**


**404 Fourth Avenue**

**New York 16, N. Y.**

*Copyright 1939 by John F. Rider*

**Printed in the United States of America**
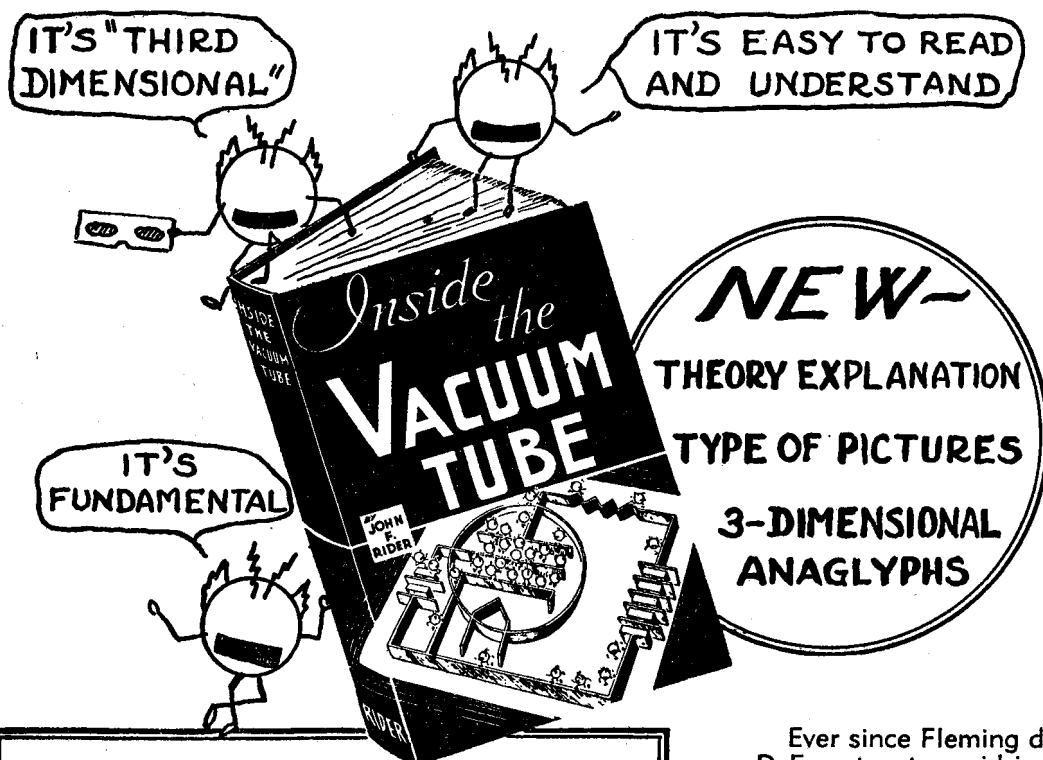
# A New Book Explaining Vacuum Tubes in a Different Way



## Contents

### CHAPTERS

1. INTRODUCING THE ELECTRON
2. ELECTRON EMISSION
3. MOVEMENT OF CHARGES
4. SPACE CHARGE AND PLATE CURRENT
5. FUNDAMENTALS OF TUBE CHARACTERISTICS
6. THE DIODE
7. THE TRIODE
8. STATIC CHARACTERISTICS OF TRIODES
9. TRIODE DYNAMIC CHARACTERISTICS AND LOAD LINES
10. DYNAMIC TRANSFER CHARACTERISTICS
11. VOLTAGE AMPLIFICATION
12. THE TETRODE AND PENTODE VACUUM TUBES
13. THE CATHODE CIRCUIT
14. POWER AMPLIFIERS
15. MISCELLANEOUS VACUUM TUBES

Ever since Fleming discovered his "valve" and DeForest put a grid in it, thousands upon thousands of pages have been written on how and why the vacuum tube functions. Here is a new approach—one which affords the clearest understanding of the subject. The presentation is aimed for the man who is starting out in radio and who desires not only a solid grounding in the theory, but also a good working knowledge of tubes. At the same time it is a perfect refresher for the man who studied the subject long ago.

Throughout the book, which covers diodes, triodes, screen-grid tubes, and pentodes, the aim is to give the reader a clear physical picture of exactly what is happening within the tube—inclusive of the development of characteristic curves of all kinds. The anaglyphs giving a three-dimensional picture of phenomena heretofore seen in only two dimensions, are an innovation in radio texts. Two-colored spectacles are provided with the book for viewing these anaglyphs. Like the text—the illustrations are new—they live—show action—thereby simplify the explanation of tube behavior.

**424 Pages — Hard Covers**  
**Price \$4.50**



# HOW IT WORKS

## Special Section of Volume X RIDER'S MANUAL

### CONTENTS

	PAGE		PAGE
<b>TELEVISION—HOW IT WORKS</b> .....	3	<b>Average Brightness and D-C Restorer</b>	
Comparison with Sound Broadcasting .....	3	Circuits .....	38
Scanning .....	4	D-C Restorer Circuits .....	39
The Picture Tube .....	8	Brightness Control .....	41
The Camera Tube .....	11	Grid Leak-Condenser Restorer .....	41
Scanning and Synchronization .....	13	The Contrast Control .....	42
Flicker and Hum on the Raster .....	14	<b>Synchronizing Circuits</b> .....	42
Scanning Waveform .....	14	Sync Separator Circuit .....	43
Overall View of a Television System .....	15	Horizontal and Vertical Sync Selectors .....	44
<b>The Television Signal</b> .....	16	<b>Deflection Circuits</b> .....	45
Signal and Sync Pulses .....	18	Electromagnetic Circuits .....	45
RMA Standard Television Signal .....	19	Blocking Oscillator .....	46
Range of Frequencies in Video Signal .....	20	Width and Height Controls .....	47
The Modulated Wave .....	22	Damping Tube .....	47
Channel Make-up .....	23	Electrostatic Deflection .....	48
<b>Television Receiver Circuits</b> .....	24	<b>Power Supplies</b> .....	48
<b>R-F and Oscillator Circuits</b> .....	26	<b>Antennas and Installation</b> .....	50
High-Frequency Section of Belmont X-466..	27	<b>FREQUENCY MODULATION</b> .....	52
High-Frequency Section of DuMont 180-183..	28	Advantages .....	52
<b>I-F Circuits</b> .....	28	How Noise is Reduced .....	52
<b>Video I-F Circuits</b> .....	30	What the Limiter Does .....	53
Video I-F Circuit in Andrea 1F5 .....	31	Special Detector Used .....	53
Video I-F Circuit in RCA TRK-12 .....	32	How the Discriminator Detects .....	54
<b>Video Second Detector Circuits</b> .....	34	The G.E. GM-125 Receiver .....	54
Video Second Detector in DuMont 180-183..	34	Alignment .....	55
Video Second Detector in RCA TRK-12 ....	34	<b>WIRELESS RECORD PLAYERS</b> .....	55
<b>Video AVC Circuits</b> .....	35	General Service Notes .....	56
Video AVC in RCA TRK-12 .....	36	<b>FACSIMILE RECEIVERS</b> .....	57
Video Amplifiers .....	37	<b>SERVICING BY SIGNAL TRACING</b> ..	58

## PREFACE

1939 witnessed the start of commercial exploitation of modern television. With two stations in operation, one at each end of the continent and other stations under construction in a number of the larger centers of population, television received a very definite stimulus. As a matter of fact, a number of different makes of television receivers are being demonstrated here in New York, with the NBC station W2XBS as the source of signals.

It therefore is only natural that television receivers be included in Rider's Manual Volume X and concurrently with the appearance of these service notes, we feel that an explanation of the subject of television transmission and reception should be a part of this "How It Works" section.

In this discussion you will find not only an explanation of the "how" of television but also a breakdown of some of the circuits to be found in the commercial television receivers contained in Rider's Volume X. Inasmuch as a certain amount of standardization in television transmission has been accomplished, the facts given herein will be found of interest at least for several years to come.

The presentation of facts is by no means complete. To cover the subject fully would take volumes. However, we feel that what is here presented is the actual "meat" and will be sufficient to give an insight to the *modus operandi* of television.

You also will find some facts pertaining to another development in transmission, one with myriad possibilities, namely frequency modulation. At present only a few receivers suitable for the reception of such signals are in use, but if what the originators say is true, we can look forward in the years to come to a general transition from the present amplitude-modulated form of transmission to the frequency-modulated form of transmission, with a corresponding radical change in receivers.

COPYRIGHT, 1939, BY JOHN F. RIDER

---

*Printed in the United States of America*

# TELEVISION—HOW IT WORKS

No COMMENTS can be made on advances in the radio art during the past year without recognizing that after many years of development, television has finally reached the stage where servicemen can no longer afford to ignore its existence. In some parts of the country television is already an accomplished fact; hundreds of receivers have been installed and sold, and all signs point toward the gradual expansion of television facilities into sections which do not have coverage at the present time.

Recognizing, then, that the radio serviceman's job is being extended to include not only radio servicing as we know it today, but also the servicing of television receivers, this section explaining the fundamentals of television is being offered in the belief that it will be of help to many of you in dealing with the problems introduced by television. Throughout you will find that it is written from the viewpoint of the man who is called upon to install and service television receivers; and yet, although there is this emphasis on the practical aspects of television, you will find that an essential amount of theory is included. Lest any of you feel that this inclusion of what might be called "theoretical" material is unnecessary, it should be pointed out that television is an extremely complicated subject, much more so in fact than is radio, and that television receivers cannot be serviced efficiently by any one who does not understand the principles underlying the operation of the system. The different situations which can arise are so numerous that it is indeed impossible to list them, to explain the reasons for each,

and in the case of faulty operation to locate the source of the trouble. As in radio servicing, so it is in television servicing: a thorough understanding of the fundamental principles of operation is invaluable.

Fortunately for the radio serviceman, the advent of television does not mean that an entirely new field must be learned. The more you study television, the more you will come to realize that television embodies every principle that has ever been used in radio—and more besides. You will marvel at the ingenuity of television engineers in using the same old time-proved principles of radio, in adapting these to the needs of television, and in discovering new principles and new techniques wherever the available ones were inadequate. Thus, for example, you will find the simple diode rectifier being used in clipping circuits, in d-c restoring circuits, in video detector circuits, and in many other applications. If you understand how the diode rectifier operates, then you will recognize in each one of these "new" circuits an old friend. True, it will take some time before you become familiar with the need for these circuits and the specific modifications to achieve certain results, still you will be amply repaid for the effort in the new opportunities which television offers to the trained serviceman and technician.

## Comparison with Sound Broadcasting

Just as it is the problem of radio broadcasting to recreate sound at places distant from the actual sound, so it is the problem of television to recreate a scene at

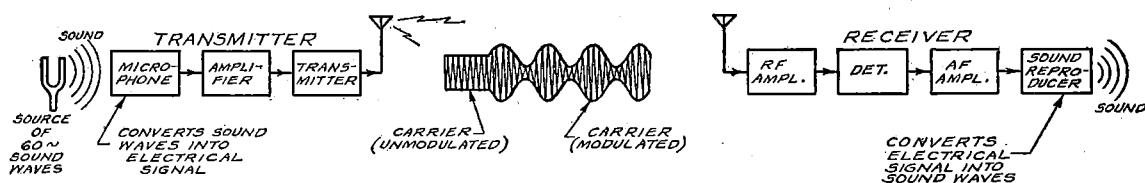


FIG. 1A—SOUND TRANSMISSION SYSTEM

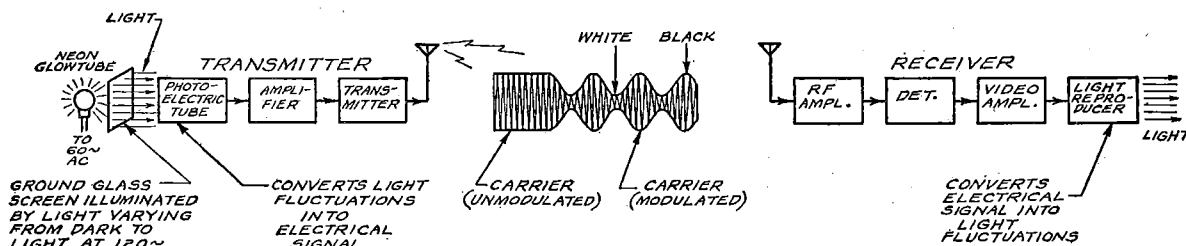


FIG. 1B—TELEVISION TRANSMISSION SYSTEM

FIGS. 1A, 1B.—A television system uses an arrangement similar to that employed in sound broadcasting. Note that in the television system the photoelectric tube replaces the microphone and the light reproducer replaces the speaker.

places distant from the original scene. In the case of sound broadcasting, as Fig. 1A shows, sound vibrations produced by, let us say, a tuning fork are picked up by a *microphone* which converts these vibrations into corresponding electrical vibrations. This electrical signal, which now carries an electrical image of the sound vibrations, is amplified, used to modulate the carrier, the radio wave is radiated, picked up by the receiver, amplified, detected and finally, as you know, the electrical impulses (similar in shape to those which were originally produced by the microphone) are used to actuate the speaker which in turn recreates the original sound.

Fig. 1B shows that a system very similar to this is used in television and that in general a very close resemblance exists between sound broadcasting and television. To simplify the explanation at the present time, we assume that only a very small part or element of a scene is being televised. For example, we might allow the light from a neon tube operated from the 60-cycle power line to fall on a small piece of ground glass. The illumination on the ground glass would then change from dark through various shades of brightness and back again to dark, and repeat this cycle 120 times per second. (Note that the rate is 120 cycles because both positive and negative cycles cause the neon tube to illuminate the screen.) In the same way that sound broadcasting uses a *microphone* to convert the sound pressure variations into electrical variations, so the heart of any television broadcasting system is the "*television camera*" which converts the time-variations in illumination of the scene into corresponding electrical variations. In the simple illustrations we have chosen, because only a single small area is being televised, an ordinary photoelectric cell can serve as the television camera.

Once the varying light values have been changed into corresponding electrical values by the television camera, the process of transmitting the information

follows exactly the same procedure as in the case of sound broadcasting. Note that the carrier is modulated in the same way, and that it remains stationary in amplitude during the period before the screen is illuminated. Once the neon tube is turned on and illuminates the screen, the amplitude of the carrier varies in proportion to the amount of illumination. Note that the maximum amplitude of the carrier corresponds to a black image, and that the image gets progressively lighter as the amplitude of the carrier is decreased. In passing we might say that this is called negative modulation about which we shall have a great deal more to say later on.

For the present, the important thing to note is the similarity between the two systems, the one for transmitting information on light values, and the other for transmitting information on sound values. At the output of the television receiver, we of course have an important change. Whereas the output of the sound receiver is a speaker which converts the electrical impulses into corresponding sound impulses, the output of the television receiver is a "*picture tube*" or other device which converts the electrical impulses into corresponding light values.

We see then, that the sound system and the television system are identical with the exception that the television camera is substituted for the microphone and the picture tube for the loudspeaker. We might also mention here that in the RCA television system, the trade-mark name "Iconoscope" is used for the television camera tube and the trade-mark name "Kinescope" is used for the picture tube. As will be explained in detail later on, the Iconoscope consists of a very large number of minute photoelectric cells which create an *electrical* picture of the scene being televised, while the Kinescope consists of a cathode-ray tube on the screen of which is built up a visible image.

## SCANNING

No doubt you have noticed by this time that in comparing television with sound broadcasting we limited ourselves to televising the simplest type of object, one which was uniformly illuminated over its entire area. We then showed that the two systems are identical provided that the television camera replaces the microphone and the picture tube replaces the loudspeaker. Unfortunately, however, television is not as simple as this or television would have "arrived" many years ago. In television, we are confronted with the problem of conveying information on the light value not at one point but at every point over the com-

plete area of the scene being televised. Thus, the scene must be broken up into a great many elements or elemental areas and information on the light values over each one of these elements must be conveyed to the receiver and finally to the picture tube. And not only must this information be conveyed, but it must be reassembled in the correct order at the receiver and the corresponding light value reproduced for every one of the many elements into which the image has been broken down.

As a matter of fact, this process of breaking down a picture into a great number of elements is nothing

new but is as old and as fundamental as the process of seeing itself. For, in viewing a scene, the image is carried to the brain by the eye over a huge network of transmission lines which tells the brain the intensity and the color of the light at every point in the field of vision. Because the number of elements into which the retina of the eye breaks down the scene is so great, we are not conscious that the picture is made up in this way but receive the impression that the picture is perfectly blended or continuous.

Some of you will be surprised to know that even photographs are made up of elementary particles even though they too appear to be continuous upon casual inspection. Actually the light and dark parts of a photograph are the result of the presence of black particles of silver which vary in number over the area of the picture. Where the picture is dark, these particles of silver are more numerous than where the picture is light. Because these particles are so small they are not ordinarily visible. We might note in passing that where photographs are to be enlarged appreciably so-called fine-grain film and special developers are used so that the individual grains or particles will not become visible.


#### Number of Elements Required

It is important for an understanding of television to appreciate how the number of particles or areas into which a picture is broken up affects the type and quality of the reproduction which is obtained. As we should expect from the preceding discussion the quality of the picture will be improved as the number of elements is increased. In order to compare the effect of breaking up a picture into a varying number of elements, let us consider the two reproductions shown in Fig. 2a and Fig. 2b. These are reproductions of the same photograph, the only difference being the number of elements into which the picture is divided. If you examine these figures closely, you will see that they are composed of a large number of black dots of different sizes, and that Fig. 2b contains a larger number of dots than Fig. 2a. As a matter of fact, in printing as well as in the processes of seeing and photography, it is necessary for the picture to be broken down into a series of small areas before it can be printed. The engraver in making his halftone, places a fine mesh screen in front of his camera so that the image is broken down into a series of dots, the actual size of any one dot depending upon the amount of light on the area which the dot represents. Where the picture is dark, the size of the corresponding dot is large, and where the image is light the size of the black dot is correspondingly small. The number of dots into which Fig. 2a is broken down is 50

per inch, while Fig. 2b is broken down into 100 per inch.

The great improvement effected by breaking down the picture into a larger number of dots or elements is clearly apparent in the superiority of Fig. 2b over Fig. 2a. Because of the larger number of elements, the former presents more detail, appears finer, more blended and more continuous than the picture with the fewer number of elements.

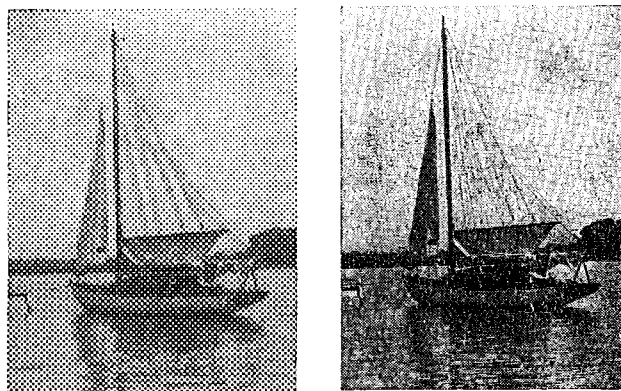The actual number of elements into which a picture



FIGS. 2a, 2b.—Fig. 2a is a halftone reproduction of a photograph using a 50 screen; in Fig. 2b greater detail is obtained by using a 100 screen.

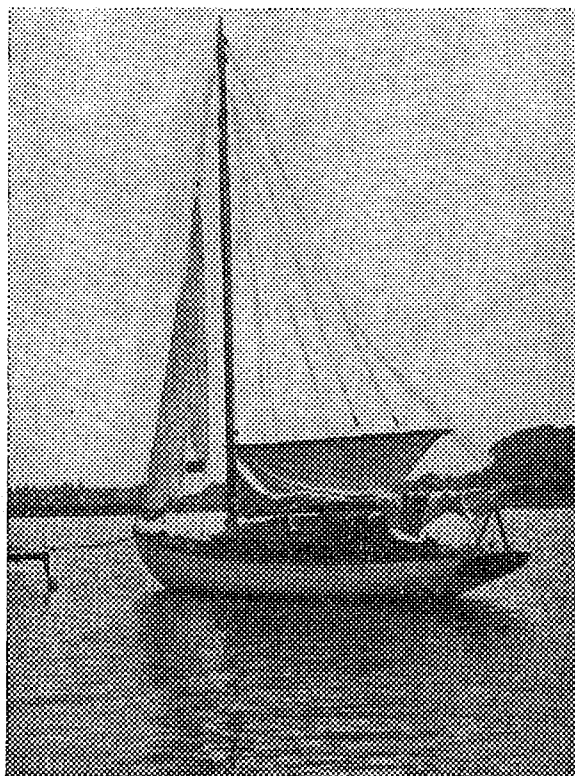


FIG. 3.—Fig. 2b enlarged to twice its original size. Note that this illustration can be viewed from twice the distance and still the same detail will be seen as in Fig. 2b.

must be divided depends upon several factors: the fineness of detail which it is desired to reproduce, the distance from which the picture is viewed and the size of the picture. Fineness of detail, as we have seen, requires a large number of elements for a given portion of a scene. In addition, the more closely the picture is viewed, the smaller must be the individual elements. This is necessary so that the individual elements will appear to the eye to merge into smooth lines and shades. If a picture of a given scene is enlarged, either the total number of elements must be increased, or the picture must be viewed from a greater distance. Figs. 2a and 2b illustrate the first two factors, fineness of detail and viewing distance. Fig. 3, which shows Fig. 2b *enlarged* to twice its original size, illustrates the third factor. Fig. 2b contains 100 dots per inch; Fig. 3 contains only 50 dots per inch. Each contains the same *total* number of elements, therefore the *fineness of detail* is the same in each. Because Fig. 3 has *larger* dots, it must be viewed from a greater distance. This consideration is important in television, since the total number of lines into which the scene is divided is the same at all times. Therefore, large pictures should be viewed from a greater distance than small ones to get the same effect.

An idea of the number of elements needed to reproduce fine details can be obtained from Fig. 2b. This has 100 dots or "elements" per inch in an area 1.5 by 2 inches, giving  $150 \times 200 = 30,000$  total elements, or 10,000 elements per square inch. Television pictures may be considered to contain about 224,000 elements, regardless of picture size. Although this does not work out to be so great a number per square inch on large picture-tube screens, the fact that the scene is usually in motion compensates for some loss of detail. A point to remember about television is that increasing the number of elements increases the frequency bandwidth which must be transmitted. Thus there are technical and economic limitations to the degree of detail that may be provided.

We can now begin to appreciate the complexity of the problem with which television is confronted. For not only must information on the light value of each one of many thousands of elements be transmitted to the receiver, but also information as to the order or sequence in which these light values must be assembled to form the picture. To make the problem even more complex, all this information must be transmitted in approximately 1/30th of a second in order to prevent blurring due to movement in the scene and in order to make way for the next picture impression or "frame." In this respect the problem of television is more difficult than that of facsimile, since in the latter a still picture is transmitted and the time con-

sumed may be ten minutes or more instead of 1/30th second.

### Need for Scanning

By this time we have seen that to make television possible, the picture must be broken down into a large number of elements and information transmitted on the light value at each one of the elements. At the receiver this information is reassembled in the proper space relationship to form the original picture. How to transmit this information is the next problem.

Previously we saw that using a conventional system of radio we could transmit information on the light value at any *one* element of a scene by using a photoelectric cell pickup to convert the light value to an electrical value, and that this process was essentially the same as that of sound broadcasting and involved essentially the same transmitting and receiving equipment. This was shown and explained in Fig. 1. The first thought that arises is this: Why not use individual channels of the type shown in Fig. 1b to transmit information on the light values at each one of the points into which the picture is divided? But then, this would require some 100,000 individual pickups and transmission systems each of which would be similar to the system of Fig. 1b. Quite obviously such a system would be far too complex and expensive to be practicable, even if other problems of great difficulty at the receiving end did not exist.

Another more promising solution, which is the one that is used in all television systems today, works on the basic idea of transmitting information on the light value of one element at a time. In this way the picture is covered or "scanned" in a systematic way until finally the image is said to be completely scanned when information on the light values at every point in the picture has been obtained. In this way the need for more than one channel is avoided. However, the information must still be reassembled in the proper order at the receiving end before the picture can be obtained.

Scanning a scene is sometimes compared with the manner in which we read a printed page. For instance as you read this page your eyes start at the upper left-hand corner of the page and successively sweep to the right-hand side while examining every letter on the line; when the first line has been completed the eye snaps over rapidly to the left hand side, jumps down one line, and in the same way, examines every letter on the second line as it progresses at a uniform rate toward the right. This procedure continues until finally the eye reaches the last letter on the lower right-hand side of the page, at which time we can consider that the whole page has been scanned.

This same procedure is used when a television camera scans a scene which is to be televised. The only difference is that the television camera breaks down the scene into finer elements than the letters of a page and that the camera produces electrical impulses which vary in proportion to the amount of light on each element of the scene being scanned.

The following simple example will help to clarify the fundamental principles and requirements involved in scanning. Suppose we wish to reproduce by television the pattern shown at the left of Fig. 4. Let us assume in this example that a television camera (consisting essentially of a photoelectric cell with the proper lens equipment) is available which can be focused so as to pick off the light values on any one of the squares into which the picture has been divided. Let us also assume that we have a mechanical arrangement for moving the camera both horizontally and vertically so that it will scan the object. That is, it is possible to start with the camera focused on element 1 and to move it at a uniform rate across the screen until it reaches element 6. At this point the camera snaps back rapidly to element 7 at the beginning of the second line and moves at a uniform rate along the second line until it reaches element 12. The camera then returns very rapidly to the left and starting at element 13 on line 3 it scans the third line. In this manner the procedure continues until the entire pattern is scanned. Note that at any one instant the camera receives light only from the particular element at which it is aimed and focused and produces an electrical impulse which is proportional to the amount of light reflected by this element.

So much for the scanning at the transmitting end where the picture is being televised. At the receiving end let us assume that we have a projector which

projects a narrow pencil of light on the screen equal in area to one of the square elements. This projector like the camera can be moved horizontally and vertically so that the light can be focused on any part of the screen. Suppose further that the electrical impulses from the television camera are fed to the projector and arranged to control the intensity of the light emitted by the projector in accordance with the amount of light registered by the camera at any particular instant.

Under these conditions before a picture can be obtained at the receiver, the motion of the camera at the scene being televised and the motion of the projector at the receiver must be properly coordinated or "synchronized." This means that the television camera and the projector must go through the same movements together, that the projector must at all times be focused on exactly the same element in the picture as that on which the camera is focused. In the figure we have assumed a sort of mechanical linkage between the camera and the projector to accomplish this; actually no such mechanical linkage is possible in television and we shall see later that electrical *synchronizing pulses* are used to control the camera at the transmitting end and the projector (or picture tube) at the receiver, so that both the scene being televised and the image which is being reproduced at the receiver are scanned in unison—so that the scanning is *synchronized*.

In the picture shown the image has been scanned only as far as element 13; element 14 is about to be scanned. As a result the image at the receiver is totally dark beyond this point since the lower elements have not yet been scanned and hence have not yet been illuminated. We shall explain later on that the observer sees the complete image at one time even

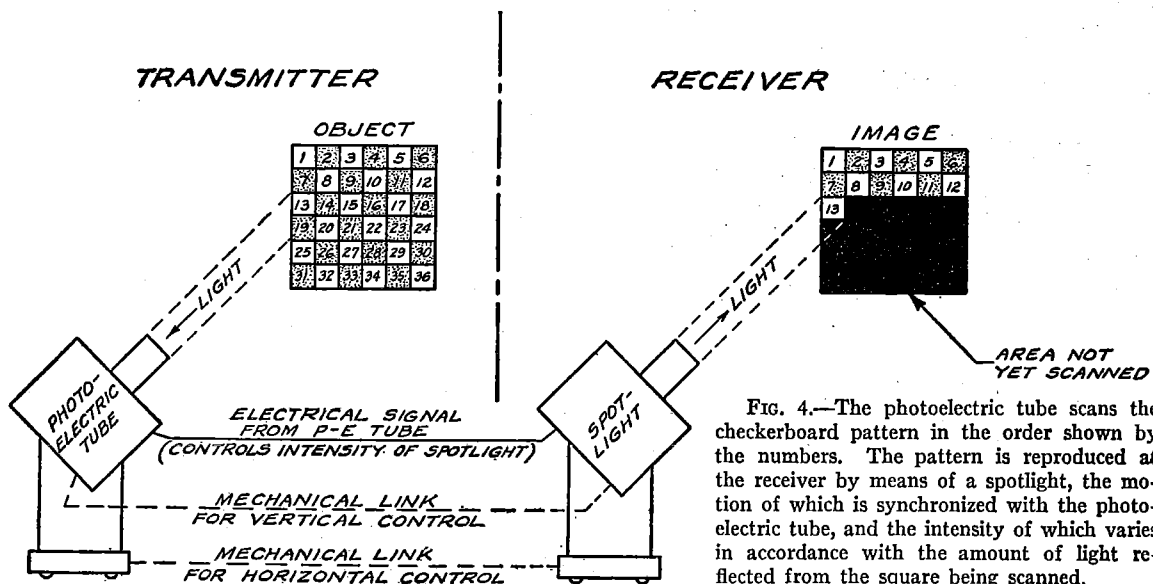


FIG. 4.—The photoelectric tube scans the checkerboard pattern in the order shown by the numbers. The pattern is reproduced at the receiver by means of a spotlight, the motion of which is synchronized with the photoelectric tube, and the intensity of which varies in accordance with the amount of light reflected from the square being scanned.

though only one element of it is receiving light at any particular instant. This is because the entire scanning process is repeated some thirty or more times a second, and the eye tends to see the image after it is no longer illuminated.

We can now summarize the requirements which must be met before a scene can be transmitted by television:

1. The scene must be systematically scanned by the television camera which interprets the light values at every element of the scene in terms of corresponding electrical values.
2. The image must be scanned at the receiving end

according to the same systematic plan used by the television camera and the intensity of the light emitted by the light source in tracing the image must vary at every instant in accordance with the amount of light which the camera is receiving at that instant.

3. At every instant the camera and the light tracing the image must be synchronized so that the identical portion of the image is being traced out which corresponds to the element of area being scanned by the camera.

4. This scanning procedure or process must be completed over and over again at a rate of at least 30 times per second so that as far as can be determined by the eye a continuous image of the scene is formed.

## THE CAMERA TUBE AND THE PICTURE TUBE


We have already seen that a complete television system, like a complete broadcasting system, requires a pickup at the transmitter and a reproducer at the receiver, and that the pickup is a photoelectric tube and the reproducer is a cathode-ray tube similar to those used in oscillographs. To avoid confusion of trade names let us call the pickup a "camera tube" (it "takes" the television picture) and the reproducer a "picture tube" (it reproduces the picture). Since we want to get a good general idea of how a television system works, we shall consider both these tubes here, although the serviceman in the field will naturally come in contact with only the picture tube.

### The Picture Tube

Essentially the television picture tube is similar to the familiar cathode-ray oscillograph tube, so that those who have read Rider's "The Cathode-Ray Tube at Work" will have a good basis for understanding television picture tubes. For those who have not we will review the subject here.

Let us assume that television (video) signals are coming into a receiver; as we have said before, the amplitude of these signals is proportional to the light reflected by the object being televised. We want to use these signals to produce a picture. In sound work we know that the signals can be made to move the diaphragm of a loudspeaker, thus producing sound waves similar to the original. The picture tube, then, must be capable of converting the electrical video signals into *light* to produce a picture. It is a property of certain substances called fluorescent materials that they will glow when they are struck by a beam of electrons, and that the more electrons striking such a substance at a given instant, the brighter will be the glow. A picture tube, then, can be made if we have a source of electrons, means for controlling their motion and their quantity, and a fluorescent screen.

The external appearance of some typical picture tubes is shown by the photograph, Fig. 5. These are glass vacuum tubes specially shaped to withstand the high pressure exerted by the surrounding air, due to the high vacuum within the glass envelope. Servicemen should remember this, and handle picture tubes with great care. Even scratching the glass or careless handling may cause them to *collapse* as violently as if they exploded! The white appearance of the large end of these tubes is caused by the film of fluorescent

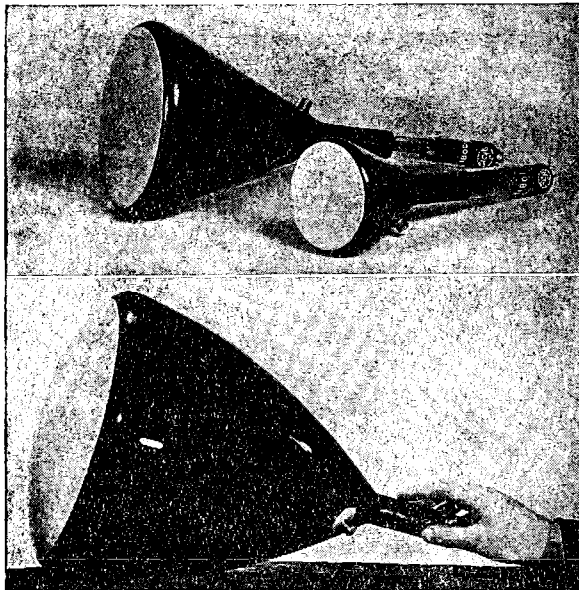

Courtesy RCA Mfg. Co.

FIG. 5.—The left-hand Kinescope shown above has a 9-inch screen and the smaller has a 5-inch screen. Below is a 12-inch Kinescope.




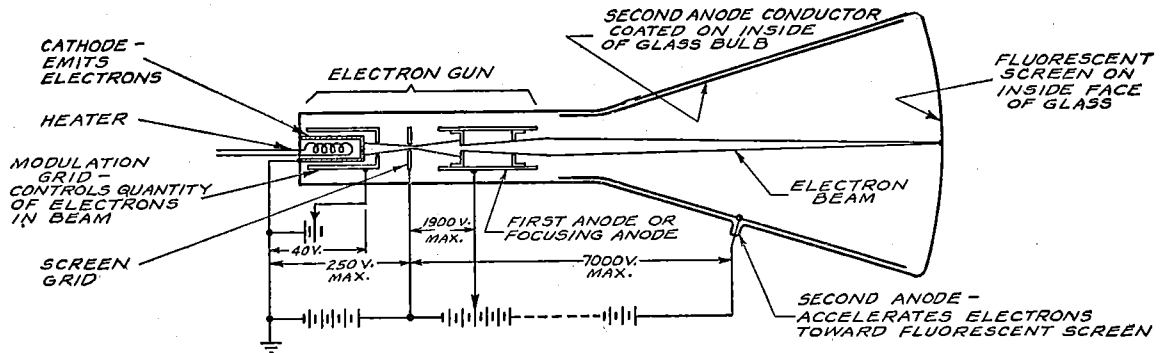


FIG. 6a.—The different elements of a picture tube are designated in the above sketch with typical voltages shown. Fig. 6b on the right shows a common schematic representation; where K is the cathode; G, the modulation grid; S, the screen grid; F, the focusing anode, and A, the second anode.

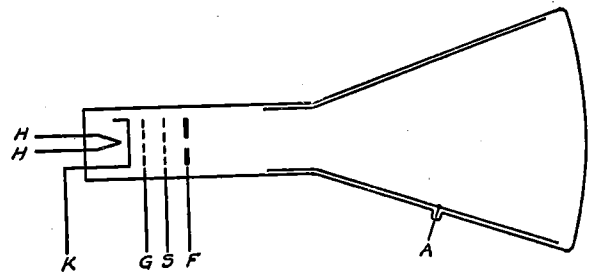

material deposited on the inside surface; this, of course, is where the television pictures are built up.

A cross-sectional view of a picture tube is shown in Fig. 6. As in the usual radio tube, the heater causes the cathode to emit electrons and the second anode (like the plate of the ordinary tube) strongly attracts them, giving them a high velocity. The modulation or control grid regulates the number of electrons which pass through it in a given time. In the picture tube are some additional elements such as a focusing anode, which forms the electrons into a narrow beam so that they will strike the fluorescent screen in a small round spot; in some tubes a screen grid is inserted between the modulation grid and the focusing anode to prevent the focusing action from affecting the modulating action. Fig. 6a shows the general arrangement of parts inside the tube, and Fig. 6b shows a common way of representing these in schematic form.

With the parts so far mentioned, the tube can produce a beam of electrons which will hit the center of the fluorescent coating on the inside of the picture tube and produce a small spot of light which can be seen through the glass end. We can focus this spot by varying the potential on the first (focusing) anode, and we can vary its brightness by applying a suitable potential to the modulation grid. The more negative the modulation grid becomes relative to the cathode, the dimmer the spot becomes; the less negative the grid, the brighter the spot. It now remains to provide some means for moving this spot rapidly enough over the fluorescent screen to give us a complete picture . . . in other words to provide scanning.

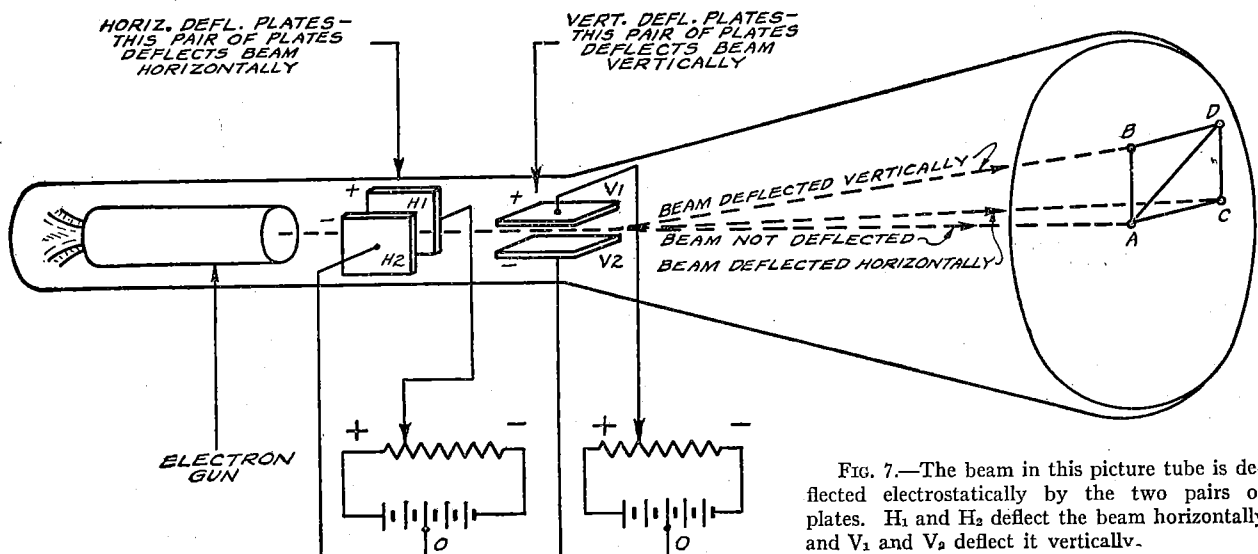


FIG. 7.—The beam in this picture tube is deflected electrostatically by the two pairs of plates.  $H_1$  and  $H_2$  deflect the beam horizontally and  $V_1$  and  $V_2$  deflect it vertically.

Two methods of deflecting the electron beam are now commonly used: *electrostatic* deflection and *electromagnetic* deflection. The first of these methods, which is probably the simplest to understand, takes advantage of the familiar fact that particles of matter having like charges of electricity repel each other, while particles having unlike charges attract each other. Since the electron beam consists of negative charges, we see immediately that the beam can be deflected by means of suitably shaped electrodes which are charged either positively or negatively as the case may require. In picture tubes, as in oscillograph tubes, this is done by building into the tube two pairs of metallic plates, arranged approximately as shown in Fig. 7.

The figure shows that plates  $H_1$  and  $H_2$  are parallel to each other but in a plane at right angles to plates  $V_1$  and  $V_2$ . If no potential is applied to any of these plates, the electron beam will pass straight along the axis of the tube and cause a spot to appear on the screen at A. Now if we leave plates  $H_1$  and  $H_2$  alone, but make plate  $V_1$  positive with respect to plate  $V_2$ , plate  $V_1$  will tend to attract the negative electrons which make up the beam, thus causing the beam to bend, so that it strikes the screen at a new point, say at point B. We have thus deflected the beam upward in a vertical direction a distance AB. Similarly, if we leave  $V_1$  and  $V_2$  alone, but make  $H_1$  positive with respect to  $H_2$ ,  $H_1$  will deflect the beam horizontally to the right until we get a spot at a point such as C.

If we combine these effects, by making both  $V_1$  and  $H_1$  positive at the same time, the beam will bend sideways and upwards, causing the spot to appear at D. If the potentials of  $V_1$  and  $H_1$  have been the same as used in the first two tests, D will be located so that the distance AD is the hypotenuse of a right triangle whose sides are equal to AB and AC. Naturally, if  $V_2$  is made positive with respect to  $V_1$ , the beam will be deflected vertically downward, and if  $H_2$  is made positive with respect to  $H_1$ , the beam will be deflected horizontally to the left. The whole process of electrostatic scanning is simply a matter of varying the potentials on the deflecting plates in the picture tube so that the spot on the screen traces out the desired picture according to a regular plan. In a later section, we shall study the details of the plan actually used.

The second method of deflecting the electron beam is called *electromagnetic deflection*, because coils of wire carrying current act on the beam the way a magnet would. See Fig. 8a: The magnetic lines of flux from a permanent magnet pass from the north pole (N) to the south pole (S); the electron beam passes between the poles. If the magnet were not present, the beam would produce a spot at point A on the screen. When the magnetic field acts on the beam as in Fig. 8a, however, the beam is deflected vertically upward to produce a spot at point B. Compare this effect with that produced by the electrostatic field in Fig. 7, and you will notice that in Fig. 7 the electron beam was deflected *in the direction of the lines of elec-*

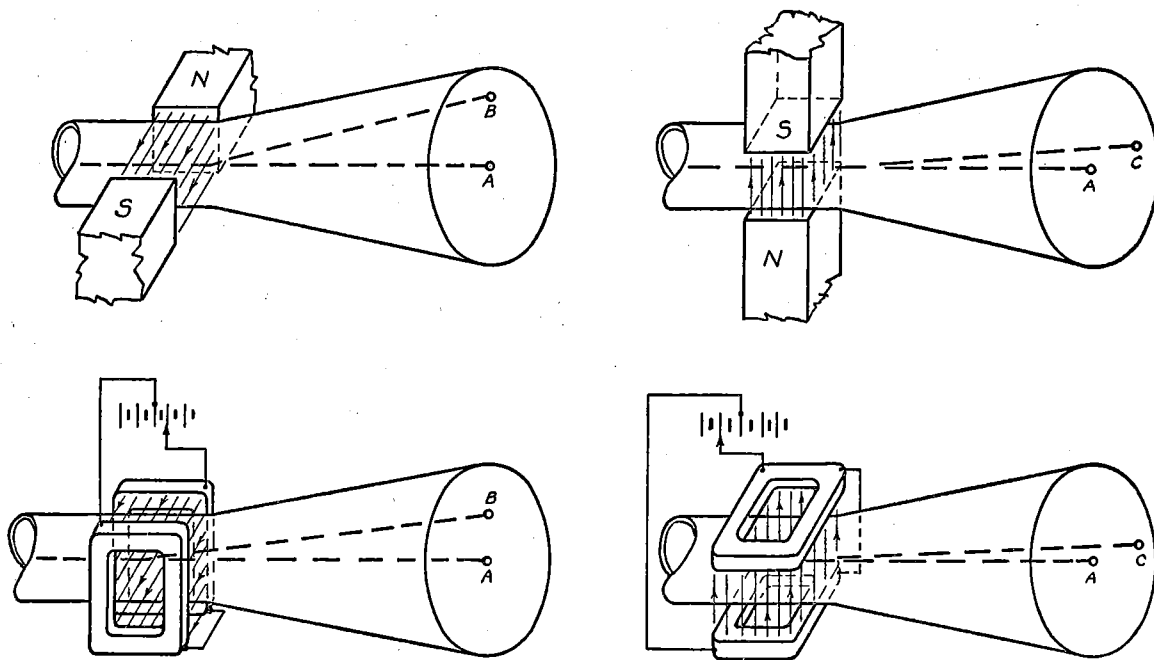


FIG. 8.—The magnetic deflection coils in Figs. 8c and 8d provide a magnetic field similar to that of the permanent magnets in Figs. 8a and 8b above. Note that the beam is deflected at right angles to the lines of force.

*trostatic flux* existing between plates  $V_1$  and  $V_2$ , whereas in the case of magnetic deflection, the beam is deflected *at right angles to the lines of magnetic flux*. Thus in Fig. 8b the beam is deflected horizontally to the right, when another magnet is introduced whose influence is at right angles to the one shown in Fig. 8a.

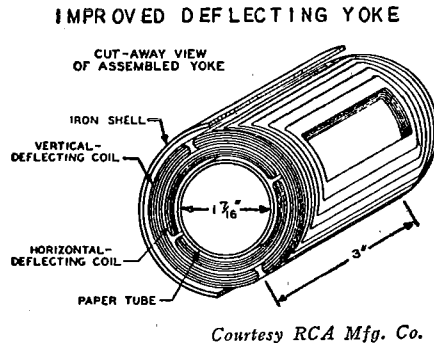


FIG. 9.—The magnetic deflecting yoke contains the horizontal and vertical deflection coils which are designated in the above sketch.

Of course, a permanent magnet gives a steady field and would therefore produce a constant deflection, whereas in television we must be able to vary the extent of the deflection from zero to maximum in various directions. Since we can also produce a magnetic field by passing a current through a coil, and in addition, can vary the strength of the field by varying the current, we use coils for electromagnetic deflection, as shown in Figs. 8c and 8d. Two pairs of coils are used, and these are often combined in a single compact cylindrical unit called a "deflecting yoke." Fig. 9 shows a partial cutaway view of an RCA deflecting yoke.

A point to remember about deflection systems is that when one tube has *electrostatic* deflection, a change of voltage on the deflecting plates is required to move the beam, whereas in *electromagnetic* deflection, a change of current through the deflecting coils is required.

### The Camera Tube

Whereas the picture tube contains a fluorescent screen to convert an electric current into light, the camera tube contains a photosensitive screen to convert light into an electric current. The RCA type of camera tube, called the Iconoscope, the type in general use in this country at the present time, is illustrated in Fig. 10. The essential parts of this tube are shown in the cross-sectional view in Fig. 11: these are the mosaic, the signal plate, the collector and the electron gun. The important accessories external to the tube are the lens, the deflecting yoke, and the load resistor.

The mosaic consists of millions of individual photo-sensitive globules like metallic droplets deposited on one side of a thin sheet of mica. Each globule is like a minute island on the mica, so that the globules are insulated from each other. On the other side of the mica there is a layer of conducting material . . . the signal plate. Because the globules are separated from the signal plate by the mica, the mosaic consists of a myriad of mica-dielectric condensers, all having one plate in common. Fig. 12 shows in a general way what the mosaic looks like when viewed from the edge and enormously magnified. The collector ring is a metallic coating applied in the form of a ring around the inside of the tube and also extended down the neck of the tube near the electron gun.

Briefly the action of the Iconoscope is as follows: An optical image of the scene to be televised is focused on the mosaic by the lens. The electron gun projects



FIG. 10.—Light images formed on the plate of the Iconoscope, the camera tube, are transformed into electrical energy by a scanning electron beam.

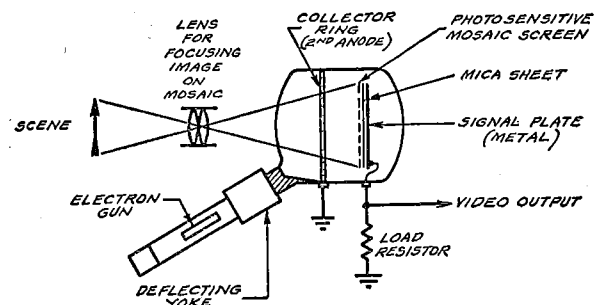


FIG. 11.—The elements of the Iconoscope can be identified in this sketch.

a stream of electrons over the mosaic, scanning it under control of the deflecting yoke, as already described in connection with the picture tube. The electron beam in traversing the mosaic causes a succession of voltages to appear on the signal plate which are proportional to the distribution of light in the image of the scene. The resultant current which flows in the load resistor causes a voltage drop. This constitutes the *video signal*. This signal is then amplified and used to modulate the television transmitter.

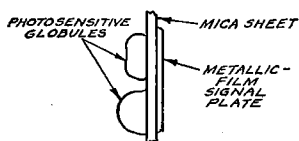


FIG. 12.—An enlarged view of how the photosensitive mosaic is arranged with respect to the signal plate of a picture tube.

The following more detailed description of the action of the Iconoscope is presented for those interested. When a scene is focused on the mosaic, each photosensitive globule emits electrons in proportion to the amount of light falling upon it; the more light that falls on a given area the more electrons are emitted from that area. This process is called "photoemission." Since a loss of electrons means a more positive charge, photoemission sets up a variety of different charges over the surface of the mosaic in accordance with the distribution of the light it is receiving. So far no video signal has been produced because the globules are insulated from the signal plate.

Since the path from the mosaic to the signal plate is through a condenser, the only way to get a signal across is to produce a sudden *change* of potential. In the Iconoscope type of camera tube, this change of potential is produced by the action of the electron beam from the gun. (The necessary orderly scanning action from left to right and top to bottom is provided by suitable currents through the deflecting yoke, as in the case of a magnetically deflected picture tube.) In order to understand the effects produced by this scanning beam, let us first consider three possible conditions on the surface of the mosaic *before* scanning. It has been found that the ordinary Iconoscope mosaic in *total darkness* (black scene) assumes a potential of  $-1.5$  volts relative to the collector ring. When strong light (white scene) falls on a portion of the mosaic, a considerable number of electrons are lost by photoemission, and the potential is changed from, say,  $-1.5$  volts to  $0$  volts. Illumination of medium intensity (gray scene) may cause the potential to change from  $-1.5$  volts to  $-0.8$  volt. These potentials of the mosaic, then, may be approximately as follows for

these portions of the mosaic: black area,  $-1.5$  volts; gray area,  $-0.8$  volt; white area,  $0$  volts.

The electrons in the scanning beam travel so rapidly that when they strike a surface such as the Iconoscope mosaic, they knock off a great many electrons, more, in fact, than even bright light does. This kind of action is called "secondary emission." So many electrons are thus lost by secondary emission, that the portion of the mosaic directly under the action of the scanning beam is driven to a *positive* potential of  $+3$  volts. Each portion of the mosaic is driven to  $+3$  volts *during the instant the scanning beam acts upon it* and this  $+3$ -volt potential is reached *regardless of the light conditions prevailing . . .* a black area goes to  $+3$  volts as well as a white or gray area. Although the *peak* potential reached by every area as the scanning beam passes over it is the same, the *change in potential* which this area undergoes at this time *will depend on the illumination* it has received. Thus the black area will change from  $-1.5$  to  $+3$  volts, a change of  $4.5$  volts; the gray area will change from  $-0.8$  to  $+3$  volts, a change of  $3.8$  volts; the white area will change from  $0$  to  $3$  volts, a change of  $3$  volts. It is this sudden *change of potential* which is induced on the signal plate that causes the video signal current to flow through the load resistor. The *difference between the changes* for black, gray and white areas is what indicates the difference in the illumination over the mosaic surface as it is scanned, and this difference is proportional to the distribution of light over the mosaic.

The important things to notice here are: (1) that we get a video signal across the load resistor (Fig. 11) only when a *change of potential* is produced on the mosaic, and that this is accomplished by the scanning beam; and (2) that the resultant *video signal is proportional to the light coming from the scene being televised*, the signal being of *maximum* amplitude for black portions of the scene, *minimum* amplitude for white portions.

The collector ring (2nd anode) serves to accelerate the electrons in the scanning beam, and also to collect some of the electrons emitted from the mosaic. In Fig. 11 you will notice that this element is grounded; it is, however,  $500$  to  $1000$  volts *positive* with respect to the cathode of the electron gun, because the gun is at a corresponding potential *negative* with respect to ground. This will not be the last time that you *will* find television tubes with elements at very high negative potentials, and the possibility of such circuits existing must always be borne in mind as a safety measure.

## SCANNING AND SYNCHRONIZATION

In previous sections we discussed (1) the necessity for scanning both the camera tube and the picture tube, (2) the essential requirement that these operations must be synchronized, and (3) the devices which make it possible to control the motion of the electron beam in these tubes. In this section we shall describe the details of the path of the scanning beam on the tube screen, the waveshapes necessary to produce this path and some of the problems which arise in connection with scanning.

### The Scanning Pattern

As we have already mentioned, the usual scan is from left to right and from top to bottom. In certain cases this order must be reversed, but the principle is the same. In Fig. 13 is shown a simplified diagram of a scanning pattern; this is often called a "raster." The rectangular diagram formed by the light lines connecting points A, B, C and D represents what we may call the "picture space." The width of this rectangle (AB) is drawn so as to be  $4/3$  times the height (AC); this is the proportion used in motion pictures. The ratio of width to height is called the "picture aspect ratio" and its value of  $4/3$  is one of the proposed RMA television standards. On a picture tube, the heavy lines ab, cd, etc., are caused by the fluorescent glow which occurs as the electron beam moves from point a to point b (in the direction of the arrow on line ab). You will notice that points a and A coincide, while point b is slightly below point B. In fact, *all* the lines in Fig. 13 slant downward. This slant is necessary to provide the *vertical* (top-to-bottom) part of the scanning process. In fact, the left-to-right component of scanning is called "horizontal scanning" or "line scanning"; the top-to-bottom component is called "vertical scanning" (also called "frame scanning" or "field scanning," for reasons which will be clear later on). This slant-line system of scanning is used because the characteristics of the electrical circuits which provide scanning make it impossible to scan in a series of truly horizontal lines, with an abrupt vertical drop at the end of each line.

After the beam reaches point b it is deflected back along the dotted line bc to start a new line, cd. On the picture tube the line bc would be much fainter than line ab because the *time* allowed for the beam to move from b to c is only about one-tenth the time allowed for it to travel from a to b. Lines like ab, cd, etc. are called "line traces"; lines like bc, de, etc. are called "line retraces" or "line flybacks."

Here some questions may arise: Why does the motion of the spot across the screen appear as a line? Why is the flyback dimmer than the trace? The eye is responsible for these effects. Any one who has ever swung a flashlight or a "sparkler" in a circle must have noticed that as the speed of the swinging is increased, the individual spot of light merges into an apparently continuous circle of light. The velocity of the scanning spot across the picture tube screen is so rapid (several thousand miles per hour) that the eye cannot distinguish the spot from a continuous streak. This property of the eye is called "persistence of vision."

The difference in brilliance between the trace and the flyback is due to the fact that the brilliance of the fluorescence produced on the picture-tube screen depends on the *time* during which the electron beam acts upon it. Although in both cases the actual time is very short, the *difference* in time (about 10 to 1) does result in a very marked difference in brilliance.

A complete set of lines such as shown in Fig. 13 is called a "frame." This particular frame is completed when the spot reaches point l; it then returns to point a to start a new frame. A frame like that shown in Fig. 13 is said to be built up by "progressive scanning" (the lines follow each other in a continuous chain). Six complete lines (retraces are not counted) are shown in this figure; a complete technical description of this figure would be: "A six-line frame (or raster) produced by progressive linear scanning." Of course, so few lines as we have shown would be insufficient to give a good picture, and a very great many more are actually used. In order to give the eye the illusion of motion, many complete frames must be

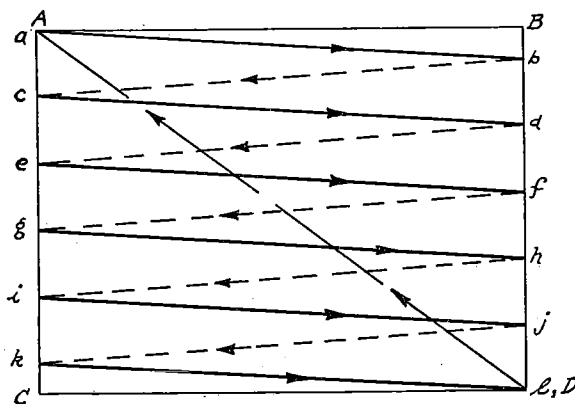


FIG. 13.—A simple progressive scanning pattern in which the picture is scanned in a series of lines which start at the upper left and slope down to the right.

traced out every second. The standard American procedure is to trace 30 complete frames every second; each frame consists of 441 lines.

### Flicker and Hum on the Raster

It has been found that if the raster is bright a *flicker* will be observed when the number of frames per second (frame frequency) is less than a certain critical value. Although a satisfactory illusion of motion might be produced by about 12 frames per second, as many as 48 frames per second may be required to remove objectionable flicker. The more frames per second a television transmitter sends out, each having a large number of lines, the higher the modulation bandwidth required. One way to keep the bandwidth down is to send twice as many frames per second, each frame having half the number of lines. But a large number of lines is necessary for detail in the picture. It was therefore decided to divide the total number of lines in each frame between two rasters (called "fields"), each containing half the total number of lines required to make up a frame. These fields, transmitted at the rate of 60 per second, get rid of the flicker effect. The required number of lines per frame is supplied by sending the odd-numbered lines along with one field and the even-numbered lines along with the following field. The fields are transmitted so rapidly that as far as the eye can see, all the necessary lines appear in their proper positions on the raster simultaneously.

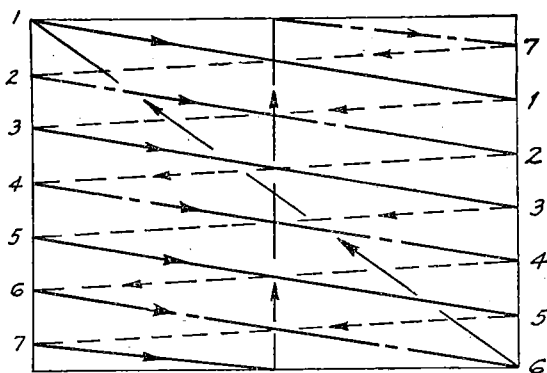


FIG. 14.—An interlaced scanning pattern in which the odd and even lines are scanned on successive fields.

The method of scanning just described is called "interlaced scanning," and is the system now in use. A simplified pattern of a frame produced by interlaced scanning is shown in Fig. 14. The general principles are the same as for progressive scanning; in fact, each *field* is itself progressively scanned. The lines transmitted during the first field scan, referring to Fig. 14, are lines 1, 3, 5 and the first half of line 7. The beam is then deflected to the top of the picture

space to begin the second field. During the second field, line 7 is completed and lines 2, 4 and 6 are traced, thus completing the entire seven-line frame in two steps. (As in Fig. 13, the arrows show the direction of travel of the beam spot.) The use of an odd number of lines has been found advantageous in interlaced scanning; this method is called "odd-line interlacing." American practice calls for 220.5 lines in each field, making 441 total lines per frame. Sixty fields are transmitted each second, giving a field frequency of 60 per second.

The frame frequency chosen depends upon the a-c power-line frequency; it must be an even multiple or submultiple thereof. The reason for this is that if there is some hum present in the deflecting circuits, a certain amount of distortion will appear in the picture. If this distortion appears to be stationary, and is not excessive, it can probably be tolerated. On the other hand if the distortion moves so that the picture appears to have moving ripples in it, even slight distortion is most objectionable. By making the frame frequency an even submultiple of the power-line frequency, this type of hum pattern can be rendered stationary. Since most American power lines use 60-cycle a.c., the frame frequency chosen was 30 per second. (In England, with 50-cycle a.c., the frame frequency is 25.)

### Scanning Waveform

In describing the picture tube, we showed that the beam can be deflected by applying suitable potentials to the deflecting plates or suitable currents through the deflecting coils. The nature of these voltages and currents depends on the kind of deflection to be produced. In Fig. 14 is shown the kind of deflection required in television scanning. The trace deflection required is a steady motion from left to right along a line slanting slightly downward to the right; the retrace travels from right to left along a line slanting downward to the left. We found out that such a motion will occur when both sets of deflecting plates or coils are in operation simultaneously. Thus in scanning, two deflection circuits are acting at once, one moving the beam horizontally (horizontal deflection circuit), the other moving it vertically (vertical deflection circuit).

The shape of the voltage (or current) wave which has to be applied to the deflecting plates (or coils) to produce the desired scan is shown in Fig. 15. At (a) is shown the waveform for horizontal or line scanning; at (b) the waveform for vertical or field scanning. Notice that the time of the line wave is equal to the time of the field wave divided by the number of lines per field ( $1/60$  second divided by

220.5 =  $1/13230$  second). Also notice that the line retrace is allowed only about  $1/6$  the time allowed to the line trace; the field retrace is allowed  $1/13$  the time of the field trace. The total time-intervals allowed for these waves indicate that the line-scan fre-

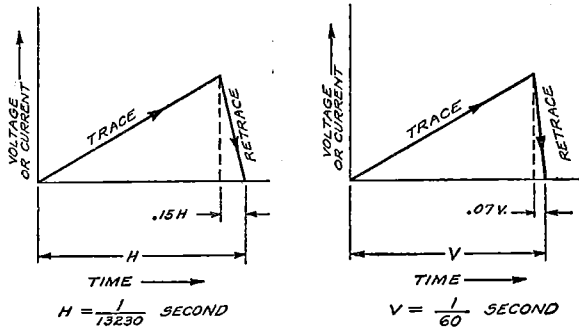


FIG. 15.—At the left is shown the sawtooth waveform required for horizontal scanning. A similar waveform, but of much lower frequency, is required for vertical deflection; it is shown at the right.

quency is 13,230 cycles and the field-scan frequency is 60 cycles. These waveforms are called sawtooth waves; circuits for generating them are described in a later section.

### Overall View of a Television System

We are now in a position to obtain a bird's eye view of a complete television system. Such a step is advisable at this time because of the complexity of the system and the desirability of not losing sight of the function of the principal parts in the maze of detail associated with all the individual elements of the system.

Fig. 16 shows the general role played by each of the major units of a television system in causing the picture of the televised scene to appear on the screen of the picture tube. Referring to this illustration, you will note that the camera tube is focused on the scene to be televised with the result that an image of the scene is formed on the photoelectric mosaic of the camera tube. In this way each point of the mosaic

takes on a voltage which is proportional to the light value associated with this point of the image. In order to transmit this information, the electron beam of the camera tube completely scans the image on the photoelectric surface 30 times in each second. As a result of this the video portion of the television signal is produced in which the electrical variations correspond with the light variations on the screen of the camera tube.

In order to fulfill the requirements of synchronization, the need for which has already been explained, a synchronizing signal (abbreviated "sync" signal) is applied to the camera tube deflecting circuits so that the scanning of the electron beam is at all times under the timing control of this sync signal.

At the same time this sync signal must also form a part of the television signal which is broadcast in order that the scanning at the picture tube in the receiver can be kept in synchronism (in step) with the scanning at the camera tube. For this reason you will note that the sync circuit also feeds the same sync signal to the video amplifier, and as a result the complete signal contains information not only on the light values but also the necessary control signals to synchronize the scanning at the picture tube with that at the camera tube.

The complete television signal is amplified by the video amplifier circuits in the transmitter and fed to the modulating circuits of the transmitter where it modulates the high-frequency radio wave which serves as the carrier. According to the present frequency allocations assigned by the Federal Communications Commission, the carrier frequencies used lie within the range between 44 and 108 megacycles, with the lower values being in greater use. The reasons for the use of carrier frequencies in the ultra-high frequency range and the actual make-up of the signal will be discussed later in detail.

The signal which is radiated by the transmitting antenna is picked up by the receiving antenna and fed to the television receiver. The television signal is

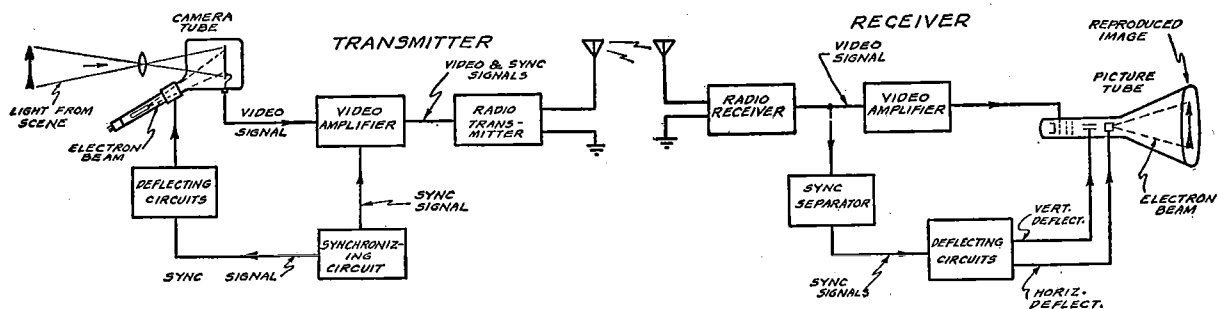


FIG. 16.—The principal elements of a complete television system. Note the provision made for synchronizing the scanning at the picture tube with that at the camera tube.

amplified in this receiver which incidentally is almost invariably of the superheterodyne type. After sufficient amplification the signal is demodulated in the second detector of the receiver and the video and sync signals are recovered. The video amplifier following the detector further amplifies the signal which is finally impressed on the control grid of the picture tube. The fluctuations of voltage on the control grid of the picture tube cause the intensity or brightness of the scanning spot to vary in accordance with the amount of light on that element in the scene which at that particular instant is being scanned by the electron beam of the camera tube.

The receiver contains separate circuits for deflecting the beam of electrons horizontally and vertically so as to accomplish the scanning of the image at the picture tube. In general these circuits are similar to those used to deflect the electron beam at the camera tube. To insure absolute synchronization between the scanning at the picture tube and that at the

camera tube, the receiver contains circuits (called sync separator circuits) for separating the synchronizing pulses from the complete television signal. As is noted in the figure, these impulses are applied to the deflection circuits in the receiver and keep the two scanning beams—the one in the camera tube at the transmitting end and the other in the picture tube at the receiving end—in perfect synchronism. In this way the image of the scene is traced out by the moving spot of light on the screen of the picture tube.

In the above description we have omitted a consideration of the sound broadcasting which almost invariably is a part of the television broadcast. For the present, it will be sufficient to understand that the sound is transmitted and received in the same way as a conventional sound broadcast even to the extent that an entirely separate carrier is used to carry the modulation of the sound accompanying the television broadcast.

## THE TELEVISION SIGNAL

One of the most important factors delaying the commercial introduction of television in this country was the necessity for establishing definite standards. You can appreciate that standards are of tremendous importance in television—and in this respect television is unlike radio—because of the close relationship which exists between the design of the receiver and conditions at the transmitting end. Thus the manner in which the image is scanned and the manner in which the synchronizing information is conveyed influence both the design and operation of the receiver.

To avoid the danger of establishing transmitting standards which would tend to prevent progress in television, the entire problem in all its aspects was investigated by the television committee of the Radio Manufacturers Association—the RMA. After several years of careful study, the standards were arrived at which are the basis of television in the United States today. It is believed that these standards have been made flexible enough to permit gradual improvements without requiring radical changes in receivers now being distributed and sold. Thus improvements which will be made will probably be improvements in the present basic system rather than radical changes in the system itself. The primary contribution of the present RMA standards is that they have started television out along the path which appears to hold the greatest promise for the future.

### The Video Signal

We are now in a position to consider more fully the nature of the signal which is used to transmit the television image. Up to this point we have explained in a general way that this signal contains the electrical image of the scene being televised and in addition contains the information required to synchronize the scanning at the camera tube with that at the picture tube. We will now go into greater detail as to the structure of this signal because of the bearing which it has on the operation and servicing of television receivers.

It will be helpful in understanding the nature of the television signal to review briefly the audio signal used in sound broadcasting and later to compare the two. In Fig. 17a is shown a typical sound or audio signal. As you know, the amplitude of this audio signal represents the intensity (loudness) of the sound, and the number of cycles per second represents the frequency (pitch) of the sound. During periods when the sound intensity is zero, the amplitude of the sound wave is of course zero; on the other hand, during periods when the sound intensity is high, this is represented by a proportionate increase in the amplitude of the signal. An important characteristic which you should note is that in a sound wave, the amplitude of the wave has both positive and negative peaks and extends equally in both directions from the zero axis.



A typical video or picture signal, that is, the electrical signal which represents the variations in brightness over the elements of a scene, is shown in Fig. 17b. The horizontal line in the left-hand portion of the signal shown represents the signal voltage produced by an *unilluminated* or *black* portion of the scene, which is called the "black level." In discussing video signals this black level is used as a reference from which the light values corresponding to all other signal voltages are measured. The reason for this is apparent from inspection of the rest of Fig. 17b, which represents various signal voltages corresponding to parts of the scene reflecting varying degrees of brightness. Note that as the brightness of the scene increases from black, the voltage of the video signal decreases, and that in any case the picture brightness never results in a signal voltage greater than the black level. The black level is therefore a suitable reference, because its voltage is fixed and easily reproduced. "White" would not be a suitable reference because the signal voltage corresponding to "whitest white" depends upon the maximum intensity of illumination available.

A video signal in which the signal voltage decreases (from the black level) as the picture brightness increases toward white is said to have a "negative picture polarity." The signal of Fig. 17b, as we have seen, is of this type. If we call the black-level voltage zero volts in Fig. 17b, all other shades of brightness will produce negative voltages, the whitest part of the scene having the greatest negative voltage. A signal having negative picture polarity is used to mod-

ulate the television carrier in present-day American television. Of course it is perfectly possible to have a video signal in which the signal voltage increases as the picture brightness increases; in this case the signal is said to have a "positive picture polarity." In fact we shall see later on, in considering receiver circuits, that the signal undergoes a reversal of polarity in passing through each stage of the video amplifier.

The important difference between the audio signal and the video signal is that the *video signal is always located on only one side of the black reference level*, whereas the audio signal contains variations on both sides of the zero-signal level. The video signal is therefore a pulsating voltage with a d-c component, not an a-c wave like the audio signal.

Let us now consider the video signal in greater detail. Fig. 18a shows the output of the camera tube for two successive lines of the image. At the same time Fig. 18b shows these two lines as they appear on the scanning pattern or raster. Starting at a, the beginning of the field, the beam traces the first line a-c; referring to the signal (Fig. 18a) it can be seen that the image is black at a, changes gradually to a brilliant white at b, and finally changes gradually to black at the end of the line c.

During the retrace time c-d, the signal level is maintained at a uniform black level as shown by c-d on Fig. 18a. This "black" interval during which the retrace is carried out is called the "horizontal blanking period," and the pulse c-d is called the "horizontal blanking pulse," or the "horizontal blanking pedestal."

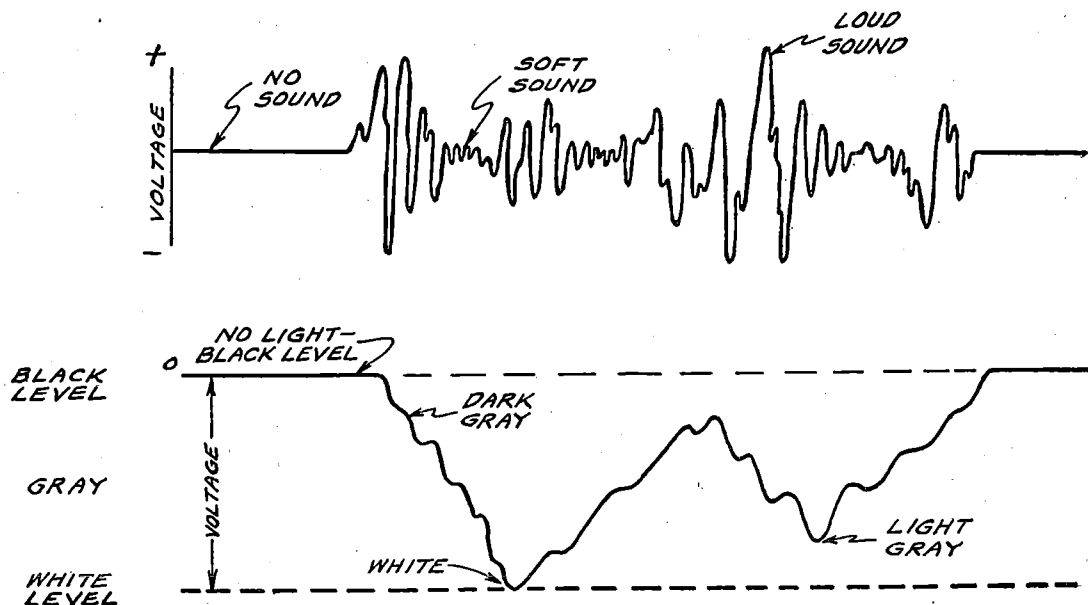


FIG. 17a, 17b.—Comparison between a sound and video signal. In the video signal black is represented by a fixed level, and various shades of brightness by voltages which are displaced proportionately from the black reference level.

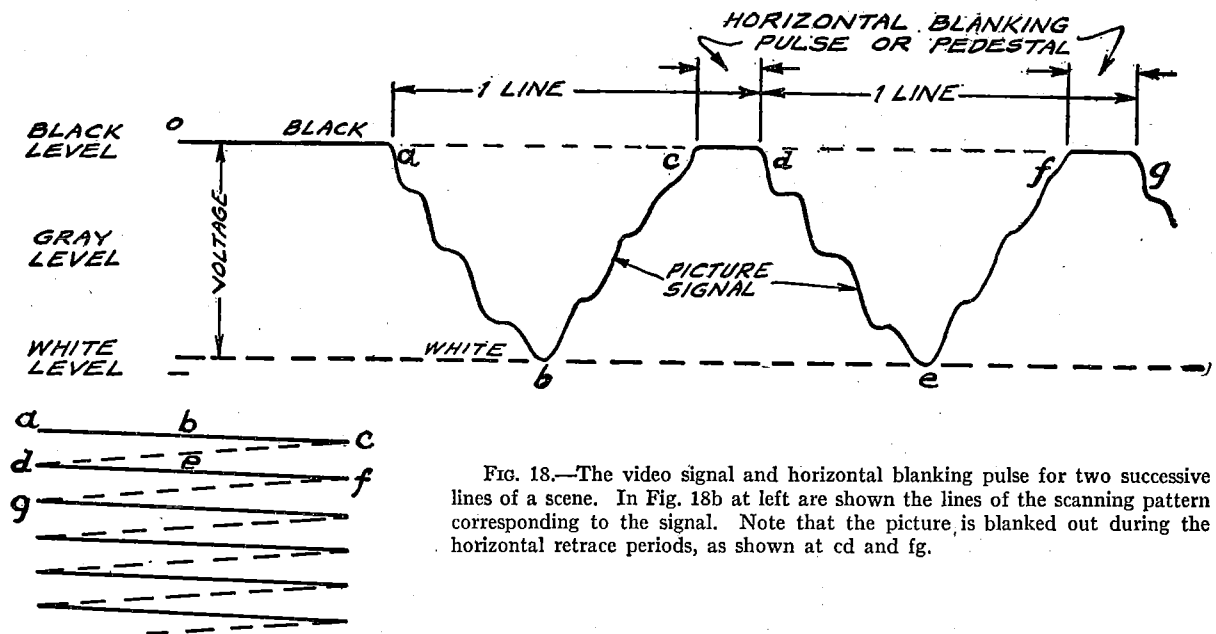


FIG. 18.—The video signal and horizontal blanking pulse for two successive lines of a scene. In Fig. 18b at left are shown the lines of the scanning pattern corresponding to the signal. Note that the picture is blanked out during the horizontal retrace periods, as shown at cd and fg.

As we shall see later in more detail, the pedestal performs two functions: (1) It blacks out the return trace so that it will not appear on the screen of the picture tube and (2) it provides a platform on which the horizontal synchronizing pulse is erected. Note that the second scanning line d-e-f is essentially the same as the first line and again the line is terminated on the signal wave by a blanking pulse f-g. In this way the entire field is scanned and the picture signal corresponding to the light and dark variations of the field is produced.

### Signal and Sync Pulses

In the previous section we showed the video signal without discussing the modifications which must be made in the signal in order to provide the necessary synchronization. We shall now describe how this synchronizing information is added to the signal.

Consider the video wave shown in Fig. 19. This shows the wave for the last two lines of the field, just preceding the vertical retrace period during which the beam returns to the upper portion of the field. Starting at the left of the figure, the first thing you will note is the addition of a pulse which is erected on top of the horizontal blanking pulse; this is called the "horizontal sync pulse." As we shall see later in the discussion of receiver sync circuits, this small rectangular pulse provides the means which keeps the horizontal line or scanning oscillator in the receiver in synchronism with the scanning at the camera tube. An important thing to note is that this sync pulse is located in the "blacker-than-black" region so that the screen of the picture tube is kept dark during the period of the horizontal retrace. Thus the portion of the signal more positive than black is used for synchronizing information, whereas the voltage more neg-

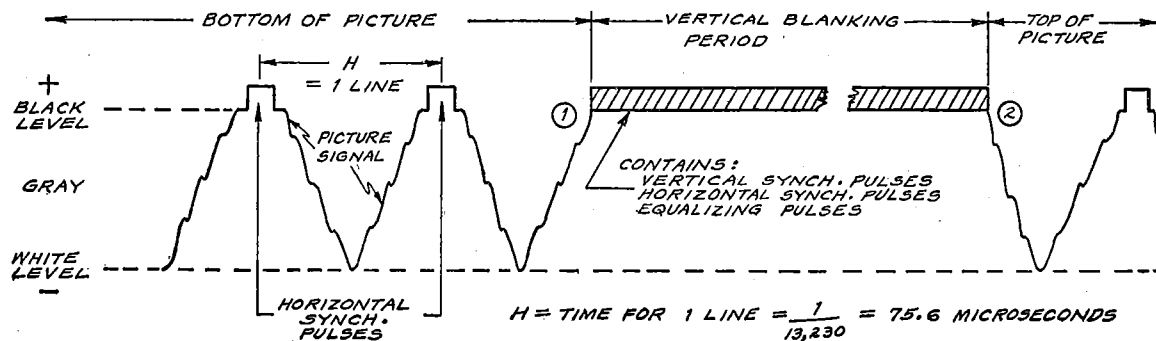


FIG. 19.—The video signal, showing the last two lines of a field followed by a vertical blanking period. Horizontal sync pulses have been erected on the horizontal pedestals and during the vertical blanking period the vertical sync pulse is transmitted.

active than the black level is used for the picture information. It is also important to observe that this line-synchronizing pulse appears at the end of each line so that constant synchronization of the line oscillator is maintained.

At the end of the last line at the bottom of the field represented by point 1 in Fig. 19, the beam is ready to return to the upper edge of the field. As in the case of horizontal scanning, a sync pulse is required to return the beam to the top at the proper instant. All the information associated with the end of the field, required to return the beam to the top of the field in preparation for the one to follow, is contained in the interval designated as the "vertical blanking period." Essentially the following three functions are performed during the vertical blanking period: (1) A field synchronizing pulse is provided (the exact nature of this pulse is described later) so that the beam will be returned to the start of the frame at the proper instant. (2) The entire signal is blacked out so that the field retrace and lines scanned during this interval will not be apparent to the observer. (Actually, of course, the line-scanning circuits continue to function, but the beam does not exist because of the negative voltage on the control grid of the picture tube during this interval.) (3) The line synchronizing pulses are maintained during the vertical blanking period, which lasts for about 15 lines, so that the horizontal deflecting circuit in the receiver will not slip out of synchronism during this period. In addition to the vertical and horizontal sync pulses, two groups of so-called "equalizing pulses" are transmitted during the vertical blanking period; these are required for reasons which will be explained later.

### RMA Standard Television Signal

It is desirable at this point to show the complete signal which has been recommended by the RMA to be used as the standard for this country. To illustrate the makeup of this signal, Fig. 20 shows the signal for two successive fields in the neighborhood of the vertical blanking pulse. Accordingly the left-hand portion of A shows the last four lines of any one field. This is followed by the vertical blanking period which contains equalizing pulses both preceding and following the vertical sync-pulse interval. After the last equalizing pulse the horizontal sync pulses are resumed; by this time the beam has been returned to the upper portion of the screen so that shortly thereafter the normal video signal is resumed. To summarize, the first line, A, shows the complete signal as it exists for any one field both before and after the transmission of the vertical blanking period.

Part B of this figure describes the signal as it exists 1/60 second later for the following field. Since the scanning is interlaced, note that the line-sync pulses in B appear *between* the line-sync pulses in A, thus providing the timing which is essential for interlacing. Again the last line in this field is followed by a vertical blanking period at the end of which the video signal is resumed. Note that for both parts of the figure, the reference point from which time is reckoned is the beginning of the vertical sync pulse, which is designated as taking place at any time represented by  $t = t_1$ . Using this time reference, it of course follows that the vertical sync pulse for the next field must begin 1/60 second later (since there are 60 fields per second); this is shown by part B of the figure so that the two vertical sync pulses are directly below each other but 1/60 second apart in time.

The description which follows shows in greater detail those parts of the complete video signal which have already been described. The specifications throughout are those of the RMA.

### Horizontal Blanking and Synchronization

As shown in Fig. 20, the horizontal sync signal is transmitted at the end of each line and consists of an essentially rectangular pulse erected on the horizontal blanking pedestal. The amount of time allowed for the blanking pedestal is specified as 15% of the total time from the beginning of one line to the beginning of the next line. Since the time for each line (including the retrace) is 75.6 microseconds (1/13230 second), the time devoted to horizontal blanking is about 11 microseconds. This interval of 11 microseconds has been found to be just large enough to allow for the retrace time, to allow the spot to assume normal scanning speed at the left edge of the picture and to maintain reliable synchronization.

The whole of the horizontal blanking interval is not utilized for the synchronizing pulse as can be seen by examining the enlarged view of the wave between C-C (Part A) shown in the detail view, Part C of the figure. Actually only about half the total blanking time is used, and the front or leading edge of the sync signal is placed as close as possible to the beginning of the blanking pulse. The small allowance which is made takes care of some variation in timing and insures that the sync pulse will not run into the video portion of the signal and thus upset the line timing.

### Vertical Blanking and Synchronization

The vertical blanking interval follows the last line of each field and consists of the following four parts which will be considered separately.

(1) *Equalizing-Pulse Interval*: Six equalizing pulses one-half line apart precede the sync pulse and accomplish (a) the maintenance of horizontal or line synchronization and (b) the "equalization" of the intervals preceding the vertical sync pulse so that *conditions preceding the vertical sync pulse are identical for alternate fields*. The need for these equalizing pulses arises because of the interlacing of alternate fields. As you can see from Fig. 20, the lines in the second field (B) are interlaced between those of the preceding field (A). If the equalizing pulses were eliminated and the vertical sync pulses were inserted in A at the end of the last line, then the vertical sync pulse would have to appear in the next field B at the middle of the line; the reason for this is that 1/60 second later the beam is in the middle of the line because of the interlacing. Thus *without the equalizing pulses*, the conditions preceding the vertical sync pulse would be different for each of the two fields. This would tend to produce a different type of vertical sync pulse for alternate fields, upset the synchronization and give rise to the distortion known as "pairing of the interlace." In a paired interlace, the even-scanned lines do not lie midway between the odd-scanned lines, because of the difference in timing on alternate fields.

In connection with the maintenance of line synchronization during the vertical blanking interval, note that the leading edges of the equalizing pulses function to maintain synchronization. Not all the pulses are used for each field, however. Thus note that because of the interlacing, the first, third and fifth equalizing pulses are used on the first field (A), and the second, fourth and sixth pulses are used on the succeeding field (B). This explains why six pulses are used, each spaced one-half line apart, rather than three pulses spaced one line apart. It would, of course, be possible to use three different pulses in each field, but if this were done the signal preceding the vertical sync pulse would be different for succeeding fields and there would be a resulting absence of equalization.

(2) *Vertical Sync Pulse*: The vertical sync pulse follows directly after the equalizing pulse interval and consists of six broad pulses in which the edges are serrated or cut at one-half line intervals. The function of the vertical sync pulse is to provide the control signal which tells the vertical oscillator that it is time to begin the retrace and thus to return the beam to the top for the beginning of the next field. The pulses in the vertical sync-pulse interval are considerably broader than the line pulses so that the sync separator circuit will be able to distinguish between the two types of pulses and thus be able to separate the vertical sync pulses from the horizontal sync pulses. At the same time the edges of the serrations

at half-line intervals provide the necessary control for maintenance of horizontal synchronization. The serrations are required at half-line intervals because of the interlacing; the reasoning used in connection with the equalizing pulses also applies here.

(3) *Lagging Equalizing Pulses*: It was explained previously that in order to provide identical conditions for the two successive fields preceding the vertical sync pulses, six equalizing pulses were inserted in front of the vertical sync pulse in each field. It is just as necessary to keep the conditions following the vertical sync-pulse interval the same for the two successive fields A and B; for this reason six lagging equalizing pulses appear in both A and B after the vertical sync pulse. If you examine the vertical sync-pulse interval in both A and B you will see that, although the lines in the two fields are displaced by one-half line because of the interlacing, nevertheless the conditions in the neighborhood of the vertical sync-pulse interval are the same for both fields. Note that the lagging equalizing pulses are also one-half line apart so that line synchronization is maintained for both the "odd" and "even" fields.

(4) *Normal Horizontal Sync Pulses*: The lagging equalizing pulse interval is terminated before the end of the vertical blanking period so as to prepare the line oscillator for the normal horizontal sync pulses which are to follow. In practice, the video signal is blanked out for a period of from 7 to 12 lines following the last equalizing pulse so that the line oscillator (which may have been operating at double line frequency during the preceding period) has a chance to settle down to being under control of the normal type of sync signal. At the end of the vertical blanking interval, the blanking is of course removed and the video portion of the signal again controls the intensity of the beam in the picture tube.

### Range of Frequencies in Video Signal

Unlike audio signals which contain frequency components ranging from a low value of about 20 cycles per second to a high value of about 12,000 cycles per second, video signals include a range from practically zero frequency (produced over areas where there is little variation in light intensity) to as high as 4 or more megacycles (produced over areas where there is a very rapid variation in light intensity).

It is interesting to examine the manner in which the maximum frequency required in the video signal is related to the amount of detail which is reproduced. This can be arrived at from the following considerations: Let us assume that we wish to transmit a picture in which the same resolution or detail is desired in the horizontal direction as in the vertical direction.

Now in the vertical direction we have a total of 441 lines or 441 elements. Since a horizontal line is  $4/3$  times as long as a vertical line (the picture is  $4/3$  times as wide as it is long), it follows that there are  $4/3$  as many elements in a horizontal line as there are in a vertical line. This makes a total of  $441 \times 441 \times 4/3$  or 260,000 elements in the complete picture.

Since we wish to calculate the maximum frequency which is required to reproduce the light and dark variations over each one of these 260,000 elements, let us assume that alternate elements in the picture are black and white so that the image resembles a checkerboard pattern. This type of scene requires the highest possible frequency for faithful reproduction because of the rapid variation in light intensity as the beam goes from one element to the next. The exact opposite of this type of scene would be one which was uniform over its entire area, for in this case it would be necessary for the system to transmit only very low frequen-

cies. For the checkerboard pattern under discussion, the variation from black to white in scanning two adjacent elements requires a certain amount of time. This amount of time represents the duration of one complete cycle and 1 divided by this number represents the highest frequency which must be transmitted.

Let us calculate this time interval required for the beam to scan two adjacent black and white elements. Since there are 260,000 elements in a complete picture and it requires  $1/30$  second to transmit this picture, the time allotted to the transmission of information on two elements (1 cycle) is equal to

$$\frac{2}{260,000} \times \frac{1 \text{ second}}{30 \text{ cycle}} = \frac{1}{3,900,000} \text{ second cycle.}$$

The frequency generated when the scanning beam passes over these two elements is thus equal to 3,900,000 cycles per second, or 3.9 megacycles.

441 LINES, 30 FRAMES PER SEC., 60 FIELDS PER SEC., INTERLACED

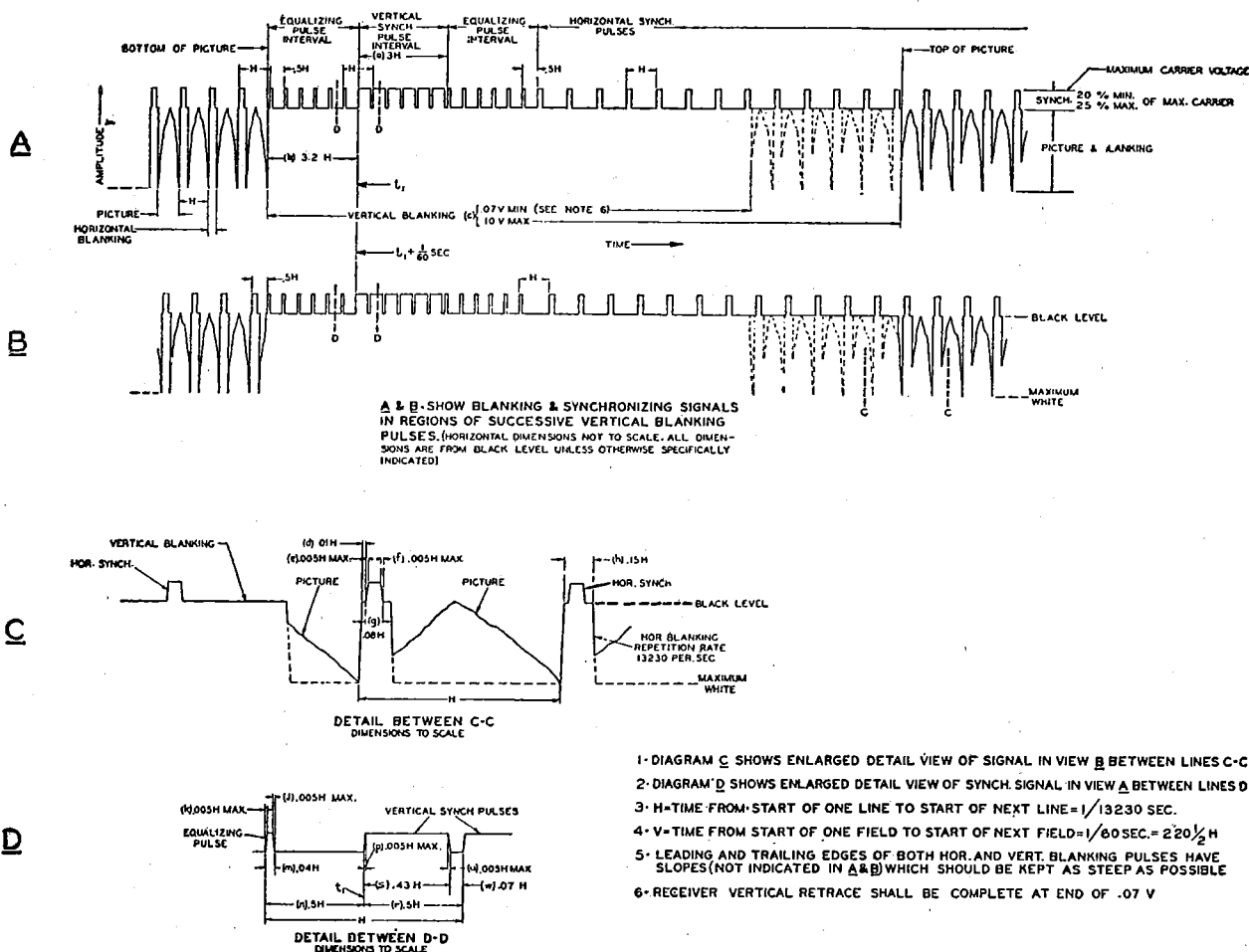


FIG. 20.—The standard RMA television signal. Diagram A shows the signal at the bottom of any one field; diagram B shows the signal at the bottom of the next field,  $1/60$  second later. Note the interlacing of the lines in the two successive fields shown by A and B.

As we have previously seen, the maximum frequency which is present in the video signal is related directly to the amount of detail required in the image. It has been found that for the smaller picture tubes satisfactory detail is obtained when frequency variations up to 2.5 megacycles are transmitted and that little is gained by transmitting the high frequency components produced in the scanning at the camera tube. However, where a comparatively large picture tube is used, additional detail and a finer image can be produced by transmitting frequency components ranging up to about 4 megacycles.

### The Modulated Wave

In previous sections we have described the video wave produced when a scene is scanned and the modifications which are made in this wave in order to provide for both line and field synchronization. We now need to consider the make-up of the modulated wave which is produced when this video wave is arranged to modulate a high-frequency carrier.

First let us review the result of modulating a carrier with a conventional audio signal. As Fig. 21a shows, if we modulate a 1000-kc carrier with an audio signal which contains frequency components ranging up to 5 kc, then the resulting modulated wave contains, in addition to the carrier frequency, new frequencies which extend to the limits of 5 kc below the carrier frequency and 5 kc above it. In other words, the process of modulating the carrier results in the introduction of two sets of *sidebands* which extend outward from the carrier to a value equal to the highest frequency in the modulating wave. The sideband which


contains frequencies lower than the carrier frequency is called the "lower sideband," and that which contains the frequencies higher than the carrier is called the "upper sideband."

It would be impossible to use a broadcast-band carrier for television work. This can be seen from the fact that unlike sound, the video modulating frequencies would themselves be higher than the carrier frequency. In order to make the modulation process work, it is necessary that the carrier frequency be at least several times the highest frequency of modulation. For this reason the carrier frequency in television must be several times as high as the maximum video frequency, or several times 4 mc. Actually the carrier frequencies which have been chosen for television are at least ten times the highest video frequency since the lowest carrier frequency which is being used for 441-line television is 44 mc.

Some of you may recall that a few years ago, carrier frequencies only a little higher than the broadcast-band were assigned to experimental television. This merely illustrates our point, however, since those early low-definition pictures contained comparatively few elements and consequently had maximum video frequencies far below those found in present-day high-definition work (for example, 100-line picture has a top video frequency only 1/16 as high as that of a 400-line picture).

Returning to the comparison between a broadcast-band carrier modulated by a sound wave and a modulated television carrier, we show in Fig. 21b the wave which results when a 44-mc carrier is modulated with a video signal. As in the case of the 1000-kc carrier, the process of modulation introduces two sets of sidebands, and for the example shown the two sidebands extend to 4 mc below and 4 mc above the 44-mc carrier.

It is interesting to compare the bandwidth required for the transmission of a scene by television with the bandwidth required in sound broadcasting. As Fig. 21 shows, a sound broadcast requires only a 10-kc channel whereas the television channel (arranged for double-sideband modulation) requires 8000 kc or 800 times as much space as the sound channel. Although it is possible to locate approximately 100 sound channels in the broadcast band it would require more than 8 times the space provided by the entire broadcast band for the transmission of a single television channel with double-sideband modulation. The large amount of the radio spectrum required for television is one of the reasons for the choice of the ultra-high frequency range for television.

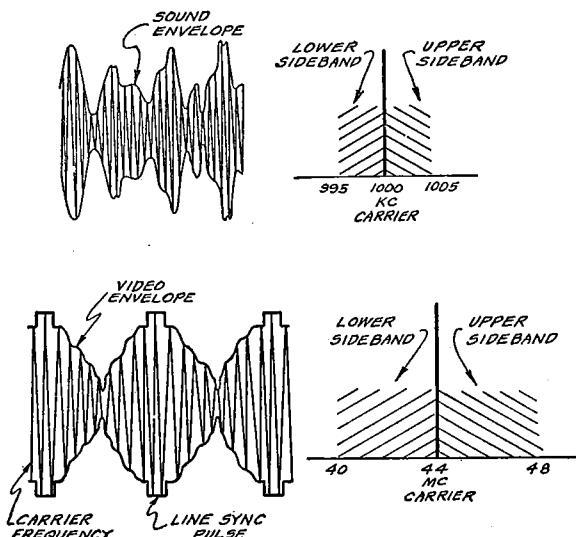

FIGS. 21a, 21b.—The sidebands in a sound signal occupy a bandwidth of only about 10 kc whereas the sidebands in a television signal require a bandwidth of about 8 mc or 8000 kc.

### Positive and Negative Modulation

In discussing video signals we pointed out that the video signal is said to have a positive or negative picture polarity depending upon whether the changes from the black level take place in a positive or a negative direction, respectively. In modulation we run into somewhat similar terms—positive and negative modulation—which are related not to the polarity of the video signal but to the modulated wave itself. A television carrier is said to have positive modulation when an increase in carrier amplitude corresponds to a brighter area in the scene being scanned. Thus for a wave with *positive* modulation, the *lowest* carrier amplitude corresponds to *black* while the maximum carrier amplitude corresponds to the brightest part of the image. On the other hand, for negative modulation, a decrease in carrier amplitude corresponds to an increase in the brightness of the image. Thus for a wave with *negative* modulation, the lowest carrier amplitude corresponds to maximum white in the image and the *highest* carrier amplitude corresponds to *black*.

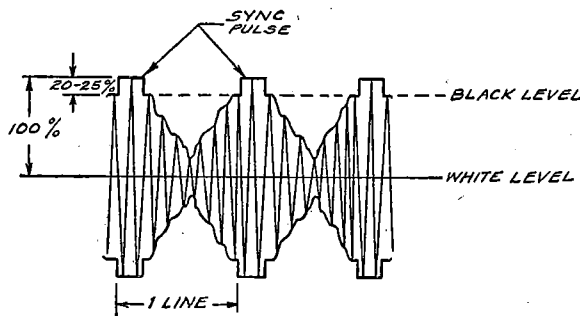


FIG. 22.—A modulated video wave. The sync pulses are located in the blacker-than-black region and occupy from 20 to 25% of the maximum carrier amplitude.

Because negative modulation offers certain advantages in improved performance and simplified receiver design, it has been recommended by the RMA as standard for this country. All television transmissions in this country therefore use negative modulation, although in England positive modulation is being used. As shown in Fig. 22, the maximum amplitude of the carrier is used for the synchronizing pulses and lies in the blacker-than-black region. The term "blacker-than-black" merely means that the sync signals have higher amplitude than black picture signals. It has been found that reliable synchronization can be secured so long as the amplitude of the synchronizing pulses is from 20 to 25 percent of the maximum carrier amplitude; this recommendation is also part of the RMA standards. Actually, then, not more than 80% of the total carrier amplitude is available for

transmitting information on the light values in the scene, the rest of the wave being used for synchronization.

### Channel Make-up

The standard RMA television channel is laid out so that the complete video signal and its accompanying sound signal can be transmitted as close together as possible, thus making for a compact channel which takes up a minimum amount of space in the radio spectrum. As shown in Fig. 23, the complete channel is 6 mc wide and the video carrier is placed 1.25 mc from the low-frequency end of the channel. The sound is transmitted on a separate carrier which is located 4.5 mc higher than the video carrier or 0.25 mc from the upper end of the band.

In order to use the minimum possible channel width, the major part of the lower sideband is *suppressed* and only the portion shown is transmitted. In this type of transmission, which is known as "vestigial sideband transmission," the transmission is essentially double-sideband for the *low* modulating frequencies (up to approximately 1.25 mc) and then becomes single-sideband for the higher modulating frequencies (above approximately 1.25 mc). This tends of course to overemphasize the *lower* frequencies (since they receive contributions from both the partially suppressed lower sideband and the upper sideband). Such overemphasis is avoided by designing the selectivity of the receiver to attenuate the carrier and the lower (double-sideband) frequencies. The difference between the transmitter selectivity curve and the receiver selectivity curve is shown by the dotted line in Fig. 23.

The advantage of this type of transmission is that it reduces the channel width required for a given maximum amount of detail in the image. We might mention here that earlier RMA proposed standards called for a double-sideband transmission which—although using the same 6-mc channel—made it possible to transmit video frequencies up to only 2.5 mc because both sidebands (occupying a 5-mc total bandwidth) were transmitted.

It is interesting to note the relatively small part of

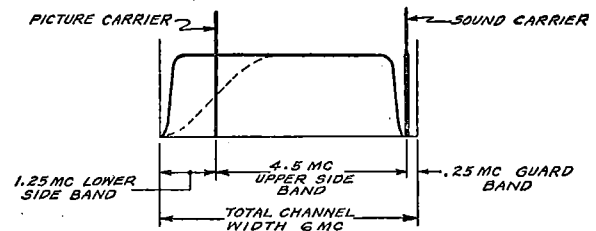


FIG. 23.—Make-up of the standard RMA television channel, showing the position of the picture and sound channels. The dotted line shows the receiver selectivity characteristic.

the total channel width occupied by the sound carrier. Even assuming that radio frequencies up to a maximum of 10 kilocycles are transmitted, this would make the total bandwidth (including both upper and lower sidebands) equal to 20 kc or 0.02 mc. It is thus apparent that the guard band of 0.25 mc is more than enough to prevent the sound modulation from spreading into the next channel. In practice, to take care of oscillator drift, the sound-carrier bandwidth is often about 100 kc.

### Frequencies Assigned to Television

The Federal Communications Commission has assigned a total of nineteen channels for television transmissions, each of these channels being 6 mc wide in accordance with the description in the preceding sections. The distribution of these channels is noted in

FIG. 24 <i>Channels Assigned to Television</i>		
44-50 MC	156-162 MC	234-240 MC
50-56	162-168	240-246
66-72	180-186	258-264
78-84	186-192	264-270
84-90	204-210	282-288
96-102	210-216	288-294
102-108		

Fig. 24; seven of the channels are located between 44 mc and 108 mc; the remaining 12 lie between 156 and 294 mc. At present, only the lower-frequency channels are in use, but it is expected that the higher-

frequency channels will be employed as television services expand.

For a number of reasons the ultra-high frequency bands are the most logical choice for television. In the first place, a relatively high-frequency carrier is required to accommodate the wide sidebands. Even if this requirement did not prevent the use of lower frequencies it would still not be feasible to use the lower radio frequencies because these are practically all in use already for other services. The ultra-short waves used for television have the advantage that the waves are not usually reflected by the ionosphere so that multiple signals and fading from this source are eliminated. This is desirable because the time difference in the reception of the direct image and each of the multiple reflected images causes a displaced "ghost" pattern to appear on the screen of the picture tube. The absence of *natural* static is another important feature in making the frequencies above 40 megacycles suitable for television work.

The fact that ultra-short waves travel essentially in straight lines and so do not follow the curvature of the earth limits the effective radius of a television station to a "horizon" which depends upon the height of the transmitting and receiving antennas. In the case of the transmitter atop the Empire State Building in New York City (about 1250 feet above street level) the expected range for reliable reception is about 40-45 miles. Although this is a disadvantage in that the coverage of any one station is limited, there is the slight compensating advantage that the same frequencies can be reassigned in various sections of the country which have a reasonable geographical separation.

## RECEIVER CIRCUITS: GENERAL

Having examined the fundamental principles of television, let us now investigate the operation of receiver circuits. These circuits are especially important because primarily the work of servicemen in the field deals with the installation and maintenance of receivers. In order to show the interrelationship between the many components that make up a receiver, we shall first break down the receiver into its major sections and later consider the functioning of these in more detail.

Fig. 25 shows a block diagram of a typical television receiver, this being arranged to show the general character of the signal and the function performed by each section. For convenience we shall assume that the receiver is tuned to the 44-50 mc channel. In accordance with the preceding description, this means

that the frequency of the video carrier is 45.25 mc (1.25 mc above the low-frequency end of the channel) whereas the frequency of the audio carrier is 49.75 mc (0.25 mc below the high-frequency end of the channel).

Both these signals, together with their sidebands, are picked up by the antenna and fed through a transmission line to the input of the r-f amplifier. Essentially the function of the r-f amplifier is the same as that of the r-f amplifier in any superheterodyne receiver—to amplify the signal and to reject unwanted signals in adjacent and other channels. In this case, the r-f amplifier is broadly tuned so that both the video and sound carriers, which are separated by 4.5 mc, are amplified equally.

After being amplified in the r-f amplifier, both sig-



nals are fed to the *first detector* circuit where the conversion of the signals to the intermediate frequencies takes place. Since there are two radio frequencies, it of course follows that two separate intermediate frequencies are produced.

In accordance with a proposed RMA standard, and general present practice, the oscillator operates at a frequency *12.75 mc above the video carrier frequency*. For the channel being received, the frequency of the oscillator in the receiver is thus equal to  $45.25 \text{ mc} + 12.75 \text{ mc}$ , or  $58 \text{ mc}$ . Since the oscillator frequency is  $12.75 \text{ mc}$  above the video carrier frequency, it follows at once that the video intermediate frequency produced is equal to  $12.75 \text{ mc}$ . In the same way, the intermediate frequency of the sound signal is equal to the difference between the oscillator frequency and the sound carrier frequency,  $58 \text{ mc} - 49.75 \text{ mc}$ , or  $8.25 \text{ mc}$ .

Following the first detector, the sound channel is entirely independent of the rest of the receiver and in practically every detail is similar to a conventional broadcast receiver. Thus the  $8.25\text{-mc}$  sound i-f signal passes through the sound i-f amplifier (the selectivity of which is broader than usual to minimize the effects of oscillator drift, as mentioned above) and is demodulated at the sound second detector. The avc voltage is supplied in the usual manner to control the gain of the stages in the sound i-f amplifier. The design of the audio amplifier and the reproducer is also conventional so that no further comment is required.

Returning to the video signal, we have seen that a  $12.75\text{-mc}$  i-f signal is produced by the first detector and that this signal carries the video modulation. As the diagram shows, this signal is amplified in the *video i-f amplifier*, which usually consists of several stages, and finally reaches the *video second detector* where

the signal is demodulated. The video signal recovered at this point is essentially the same as the output of the camera tube so that it contains all the information required to reproduce the picture, and in addition, includes the blanking and sync pulses. The video second detector is followed by the *video amplifier* which in terms of a sound receiver, corresponds to the audio amplifier. The function of the video amplifier is to amplify the video signal so that its amplitude will be great enough to "swing" the modulation grid of the picture tube. For the average picture tube this requires approximately 25 volts, peak-to-peak.

Note in the diagram that the polarity of the video signal is reversed 180 degrees for a single stage of video amplification and that the receiver is arranged so that the signal which reaches the control grid of the picture tube has a positive polarity. As a result the synchronizing impulses appear in the blacker-than-black (highly negative grid-bias) part of the picture-tube characteristic so that the beam is blocked during the retrace part of the line and field sweeps.

In addition to supplying the video signal and the signal which actuates the avc system, the second detector supplies the video signal to the *synchronizing separator*. The purpose of this separator is to remove the picture component from the complete video signal, and then to separate the horizontal sync pulses from the vertical sync pulses. As is shown, the horizontal sync pulses are arranged to control the timing of the horizontal deflection circuit, while the vertical sync pulses are arranged to control the timing of the vertical deflection circuit.

The power supply is not shown in the block diagram. As a general rule, a single low-voltage power supply is used to take care of all voltage requirements throughout the receiver with the exception of the high-

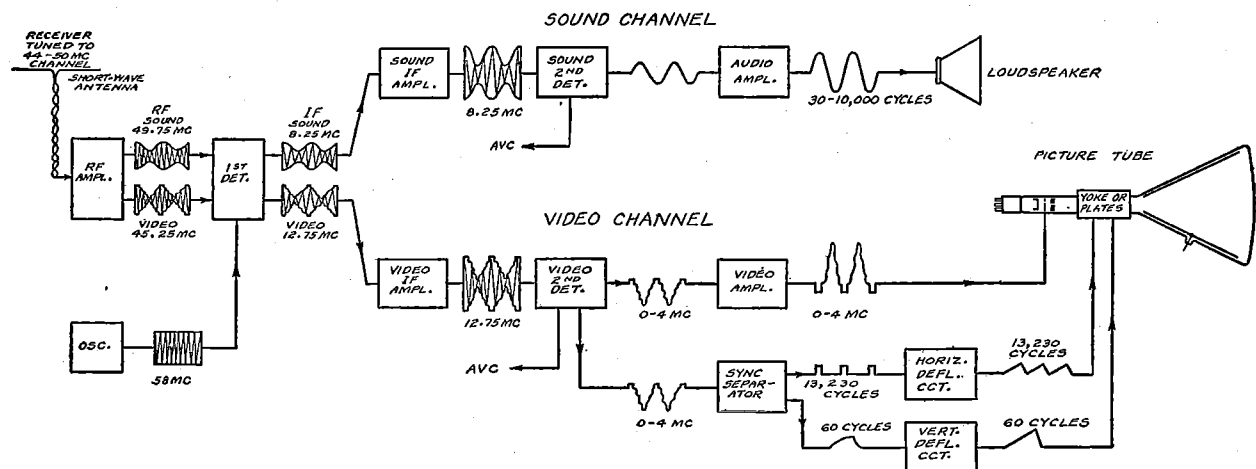


FIG. 25.—A block diagram of a typical television receiver showing the principal sections of which it is composed. Note the changes in the signal as it passes through the receiver.

voltage requirements for the picture tube. The latter, which may include voltages as high as 9000 volts, is

supplied by a separate high-voltage power supply which has its own transformer, rectifier and filter.

## RECEIVER CIRCUITS: DETAILS

The serviceman who examines a television receiver schematic for the first time is likely to be discouraged. Considering the size of the schematic, the large number of components, and the newness of many of the circuits, this is not at all surprising. Even the man who understands the basic ideas associated with television may find himself unable to understand immediately the operation of some of the circuits. Fortunately, however, the circuits are not actually as complicated as they appear on first sight. What is really required is an explanation of how the basic principles of radio have been applied in television receivers. With this explanation as a guide and with the aid of experience, the serviceman will find that the apparently complex television receiver schematic will begin to look more like an old friend.

We can best explain the circuits being used in television receivers by breaking down the complete receiver circuit into separate sections and considering the function and operation of each section separately. By this means we can for the time being eliminate the complications introduced by the related parts of the circuits and also eliminate unessential detail which tends to obscure the operation of the circuit. Since without exception all television receivers in this country are of the superheterodyne type, the divisions which will be followed are those characteristic of superheterodyne receivers.

### R-F Circuits

The action in a receiver circuit can well be considered as beginning at the antenna, for it is at this point that the signal enters the receiver. Since we shall consider antennas in more detail under the head of "Antennas and Installation," for the present it is sufficient to note that the function of the antenna is to provide the maximum signal pickup with a minimum of noise. To do this, the antenna must be located as high and as far away from sources of man-made noise as possible and placed for maximum pickup. The signal is fed from the antenna to the receiver input by means of a transmission line.

Since the complete television signal consists of a band of frequencies extending over a 6-mc channel, it is clear that the antenna and transmission line must be broad enough to pass the 6-mc band. A sharply tuned antenna system is undesirable because it discriminates against the different frequencies present in the signal and as a result produces distortion.

The characteristics of the r-f circuits in television receivers are the same as for ordinary broadcast receivers. As in any superheterodyne receiver, the function of the r-f circuits is to select and amplify the wanted signals and to reject all other signals. As a general rule, most television receivers do not use an r-f stage but rely on the selectivity of the tuned circuit which feeds the signal from the transmission line to the mixer input to provide the required selectivity and image rejection. In some receivers, however, an r-f stage is provided so that additional gain, selectivity and a higher signal-to-noise ratio are obtained.

In most cases you will observe that the r-f tuned circuits as well as tuned circuits in the i-f amplifier are shunted by resistors of comparatively low value. The function of these resistors is to damp the circuits so that sideband cutting will not take place and so that the complete television signal will be passed. Although these resistors lower the gain, this reduction in gain must be tolerated in order to broaden the circuits sufficiently.

Without exception all commercial receivers use push-button or switch-controlled tuning rather than conventional continuous tuning with a large variable condenser. This is feasible because the short-wave channels which have been assigned for television are limited in number and do not require continuous coverage as is the case, for instance, in the broadcast band. At the present time the lower channels are most in use and will probably be the only ones in use for some time.

As a general rule, a small vernier condenser is provided to permit a fine adjustment of the tuning. This condenser is placed across the oscillator tuned circuit and compensates for drift in the trimmers and other effects which tend to change the oscillator frequency. No external tuning adjustments are required for the r-f circuits since these are not critical of adjustment.

### Oscillator Circuits

As has been previously pointed out, the oscillator in a television receiver beats with both the sound and video carriers of the signal to form two separate intermediate-frequency signals: the video i.f. and the sound i.f. According to present standards, the oscillator frequency for any given channel is 14 mc above the low-frequency end of the channel, which in turn makes it 12.75 mc above the video carrier and 8.25 mc above the audio carrier. As a result, the frequency of the

signals produced by heterodyning with the oscillator signal is 12.75 mc for the video i.f. and 8.25 mc for the sound i.f.

Combination oscillator and mixer tubes are not satisfactory for the comparatively high frequencies at which the oscillator must operate, because of low conversion gain and because these tubes do not oscillate readily at the high frequencies required. For these reasons a separate tube is generally used for the oscillator circuit. The type 6J5 tube is more widely used than any other tube because of its high mutual conductance, low capacitance, and because it oscillates readily at frequencies up to 120 megacycles.

In the design of oscillator circuits much attention is given to the problem of minimizing frequency drift. Because of the high frequencies at which the oscillator operates, a comparatively small percentage change in the oscillator frequency, such as might be caused by drift, has the effect of spoiling the picture and causing the sound i.f. to drift out of the range of the sound i-f channel. Although the effect of oscillator drift is minimized because of the comparatively high intermediate frequencies, the problem of oscillator stability and freedom from drift is an important one. In commercial receivers, drift is minimized through proper circuit design and by the use of coils and condensers which are independent of changes in temperature and humidity.

### Mixer

As has previously been pointed out, combination oscillator-mixer tubes such as are satisfactory at lower frequencies are not satisfactory at frequencies above 40 mc. It is general practice to use one of the new high mutual conductance tubes in the mixer circuit, such as the type 1852. The 1852 is especially adapted for frequency conversion and provides high conversion efficiency. For proper mixer operation, it is essential that the output of the separate heterodyning oscillator be coupled to the mixer tube and that the mixer receive approximately the same value of voltage from the oscillator on all bands.

### Typical R-F, Oscillator, and Mixer Circuits

#### Belmont Model X-466

The circuit shown in Fig. 26 is that of the high-frequency section of the Belmont Model X-466 receiver. This receiver does not use an r-f stage but the signal is coupled directly to the grid of the 1851 mixer tube through a double-tuned closely coupled band-pass circuit. This bandpass circuit provides the required selectivity without sacrifice in gain. Five of the assigned television channels are covered, beginning

with the 44-50 mc channel, the highest channel being the 84-90 mc channel. The three highest-frequency channels are shunted by resistors having a value between 1000 and 2000 ohms in order to obtain the required pass band. These resistors do not have the loading effect that might be expected offhand, since the loading of the input resistance of the tube is itself of the order of 1000 ohms. In addition to improving the gain and selectivity of the input circuits, the tuned primary windings of the input transformers aid in proper matching of the transmission line and in eliminating reflections. These reflections are undesirable because they tend to produce more than one image on the screen of the picture tube.

The oscillator circuit, which uses a 6J5 tube, is conventional in design, with the tank circuit located in the grid circuit. Note the comparatively small value of grid condenser—25 mmf. The major portion of the total capacitance in the tank circuit of the oscillator is selected by means of the 5-position switch which is of course ganged with the r-f selector switch. A small vernier tuning condenser across the grid coil provides an adjustment which compensates for small variations due to oscillator drift. This control appears on the panel and is designated as the tuning control.

A type 1851 tube is used as the mixer tube. This is a pentode having a high mutual conductance, and is similar to the 1852 but has the grid cap on the top. It is used in preference to a 6J7 because it provides higher gain and a higher signal-to-noise ratio.

There is no direct coupling connection between the oscillator circuit and the mixer; the required coupling is provided inductively by placing the oscillator coil close to the mixer input coil.

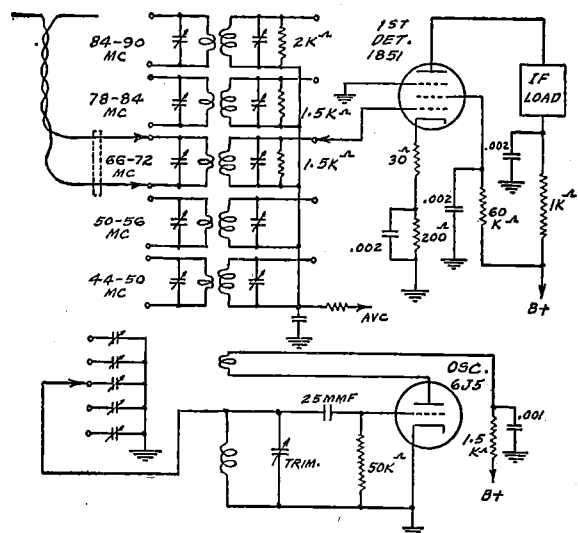


FIG. 26.—The high-frequency section of the Belmont Model X-466 receiver. The signal from the oscillator coil is inductively coupled to the mixer input coil.

### DuMont Models 180-183

The DuMont Models 180-183 use a tuned r-f stage preceding the mixer stage, as shown in Fig. 27. In this receiver the transmission line feeds directly into an untuned primary winding which is the same for all four channels. The secondary winding is tuned by one of the four trimmers, depending upon the channel selected. The secondary winding is loaded on all bands by the 3000-ohm shunt resistor which is required to obtain the necessary 6-mc pass band; on one of the bands, an additional shunt resistor of 10,000 ohms is provided.

The signal voltage developed across the secondary tuned circuit is fed to the grid of the 1853 tube used as the r-f tube. Note the small values of capacity—600 mmf—used for the cathode and screen bypasses. These condensers although they seem small in capacitance provide the same relative bypassing action at 50 mc as would be provided by a .06-mf condenser at 500 kc. The tuned circuit used in the grid of the mixer tube is similar to that used in the input circuit of the r-f tube. The r-f tube receives its plate voltage through the 3000-ohm resistor. This resistor, as far as r.f. is concerned, is effectively shunted across the coil in the mixer tube grid circuit, and thus provides the damping necessary to broaden the selectivity. Note that this type of circuit is not used at lower frequencies, such as the broadcast band, because the values of tuned-circuit impedance are much larger at the lower frequencies, and to attempt to use a high value of resistance would introduce a large voltage drop. For this reason, transformers are generally used at the lower radio frequencies rather than the resistive-tuned circuit coupling arrangement shown in Fig. 27.

The oscillator circuit used here is a conventional Hartley oscillator with the feedback obtained by re-

turning the cathode to a tap on the coil. Vernier tuning for each one of the four channels is provided by the small condenser C which appears on the panel as the tuning control. The oscillator coil and the mixer input coil are close to each other so that the oscillator voltage is coupled to the mixer magnetically.

### I-F Circuits

As a result of the action in the mixer circuit, we have seen that two intermediate frequencies are produced and that one of these—the video i.f.—carries the picture signal, while the other one—the sound i.f.—carries the sound signal. As in the conventional superheterodyne receiver, it is necessary to amplify both of these i-f signals before they are finally demodulated in the second detectors. These functions are performed by the video i-f and the sound i-f amplifiers. In this section we shall discuss the design of i-f circuits for television receivers and illustrate the principles with circuits taken from typical receivers on the market at the present time.

### Signal Output of Mixer

The frequencies which must be handled by the two i-f amplifiers are illustrated in Fig. 28. Let us assume that a signal in the 44-50 mc channel is being received. In this channel, the video carrier is at 45.25 mc and the sound carrier is at 49.75 mc; the local oscillator frequency, which is 14 mc above the low-frequency end of the channel, is therefore at 58 mc ( $44 + 14$ ). As a result of beating with the oscillator, the video i-f signal at 12.75 mc ( $58 - 45.25$ ) and the sound i-f signal at 8.25 mc ( $58 - 49.75$ ) are produced. It is important to note, as the figure shows, that whereas the video r-f carrier is lower in frequency than the sound r-f carrier,

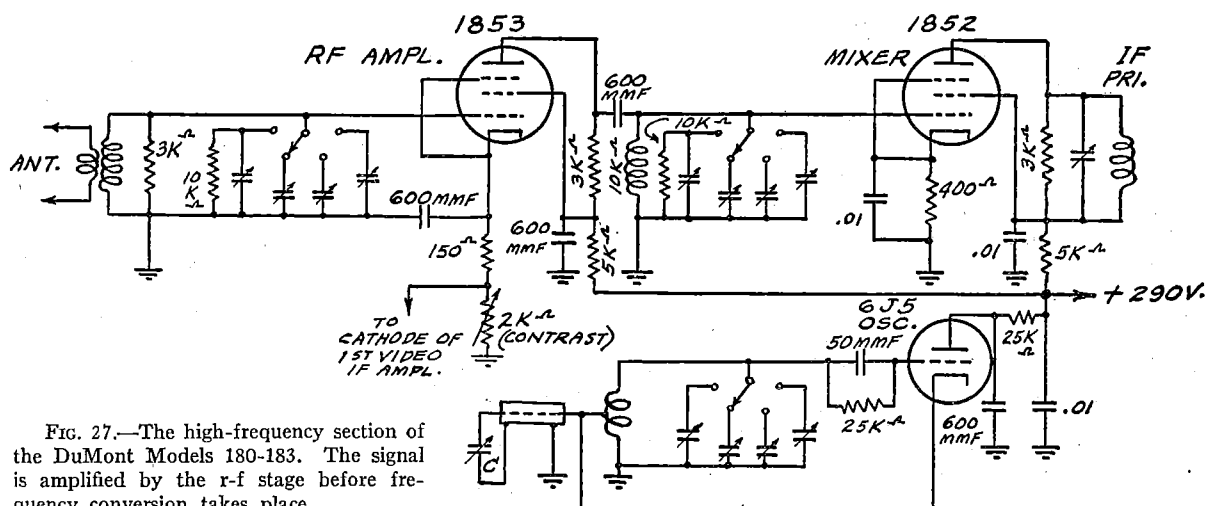


FIG. 27.—The high-frequency section of the DuMont Models 180-183. The signal is amplified by the r-f stage before frequency conversion takes place.

the video i.f. is higher in frequency than the sound i.f. However, the relative placement of the various components of the complete signal is the same in the i-f signal as in the r-f signal. Thus the frequency separation between the two carriers is constant at 4.5 mc in both cases as is also the separation from the two ends of the channel.

The intermediate frequencies used in television receivers have a number of desirable qualities which are the result of careful planning by television engineers.

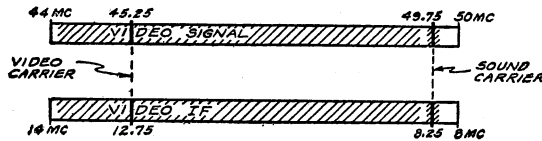


FIG. 28.—The upper part of this figure shows the make-up of a video signal in the 44-50 mc band. The lower part shows that the same frequency separation of the components of the signal is maintained in the i-f signal as in the r-f signal.

Thus the frequencies are high enough to give good image rejection; this is especially important because many receivers do not use an r-f stage. At the same time, the video i.f. is high enough so that there is sufficient space for the sidebands and the sound i.f. is high enough so that the sound selectivity is not too sharp. The effect of too sharp selectivity in the sound i-f amplifier is to make tuning critical, to exaggerate the effect of the slightest drift in the oscillator frequency and to prevent adjustment for the best picture detail without losing the sound signal.

Like any other superheterodyne, television receivers are subject to interference due to pickup by the antenna of frequencies within the range of the i-f amplifier. In the case of broadcast receivers, such interference shows itself in the form of squeals, code signals, and general distortion. Similarly, in the case of television receivers such pickup may distort either the picture, the sound, or both, depending upon the frequency of the interference. The range of intermediate frequencies between 8 and 14 mc has been especially chosen to minimize i-f interference; the fact that the amateur bands lie outside of this range is of considerable assistance in this respect.

### Sound I-F Channel

It is the function of the sound i-f amplifier to separate the sound component of the i-f signal from the video component and to amplify this signal before it is demodulated at the sound second detector. Because of the comparatively high frequencies involved, however, the design of a television sound i-f amplifier is somewhat more difficult than that of the conventional i-f amplifier in a radio receiver. Thus there is a

greater tendency toward regeneration and more attention must be paid to stray wiring and tube capacitance.

The bandwidth which must be passed is comparatively small and does not present the same problem as does the video i-f amplifier. Actually, of course, a bandwidth of from 10 to 20 kc is sufficient to transmit all the frequencies present in the audio signal. However, in practice, the bandwidth of the sound i-f amplifier is made approximately 100 kc. Primarily this larger bandwidth is necessary to allow for normal drift in the frequency of the oscillator. The significance of this is that if the bandwidth of the sound i-f amplifier were held to 10 kc, then a change of 10 kc in the oscillator frequency would cause the sound signal to drift completely out of the range of the sound i-f amplifier. However, a change of 10 kc, in an oscillator operating at a frequency of the order of 60,000 kc and up, represents a frequency drift in the oscillator of only one part in 6000, whereas in practice it is not possible to design receiver oscillators which will have a reliable frequency stability of better than one part in 1000. Therefore, instead of resorting to voltage regulation and expensive design to prevent oscillator drift, the bandwidth of the sound i-f amplifier is intentionally made about ten times as great as that required for the sound modulation, thus allowing for reasonable drift in the oscillator. Assuming that the receiver is initially tuned to the center of the sound i-f amplifier, a drift in the oscillator frequency as high as 25 kc will not cause any appreciable change in the quality of the audio signal. This is illustrated in Fig. 29, which shows that the effect of a change in the frequency of the oscillator is merely to shift the location of the sound signal within the band passed by the sound i-f amplifier.

Although the bandwidth of approximately 100 kc is sufficiently great to compensate for normal oscillator drift, this bandwidth is still small enough so that the receiver can be tuned by listening to the sound accompanying the picture. At the same time there is enough latitude so that the tuning can be varied slightly in

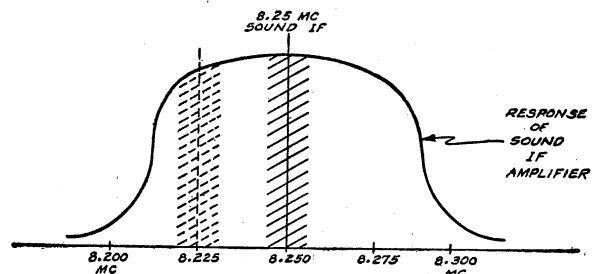


FIG. 29.—The frequency response of a typical sound i-f amplifier. The dotted signal shows that the sound signal can be detuned appreciably without falling outside the pass band of the amplifier.



amplifier is designed to have a sloping characteristic in the neighborhood of the video i-f carrier at 12.75 mc. This is illustrated in Fig. 31 which shows a typical *overall* selectivity curve for a video i-f amplifier.

The amplification which the i-f carrier receives is only 50% of the maximum amplification received by the upper sidebands and the lower sidebands, which are only partially transmitted, also do not receive the full amplification. In this way overemphasis of the lower video frequencies is avoided by shaping the overall selectivity so that the contribution of the lower sideband plus the contribution of the upper sideband is equal to the gain for the higher video frequencies. Since the upper video frequencies receive contributions only from the one sideband, the selectivity, as Fig. 31 shows, is such that the full gain is received by these frequencies.

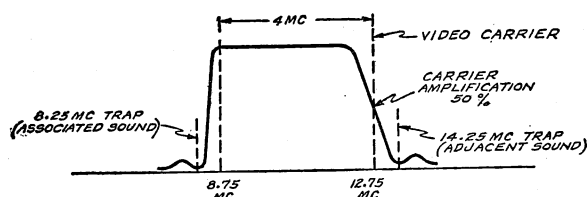


FIG. 31.—The overall frequency response of a typical video i-f amplifier. Note that the carrier receives only 50% of the maximum amplification.

If video frequencies up to a maximum of 4 megacycles are to be received, which is usual for the higher-priced sets using large picture tubes, then the i-f amplifier should cut off at about 8.75 mc ( $12.75 - 4.0$ ). Since the sound i-f carrier is located close by, at 8.25 mc, it is necessary that this cutoff be sharp in order to prevent the sound carrier and its sidebands from causing interference with the video signal. In practice this rejection of the sound carrier is secured by the use of rejection or trap circuits which generally are part of the video i-f coupling transformers.

In addition to rejecting the sound i-f carrier of the *associated* channel at 8.25 mc, it is desirable that the i-f amplifier have a sharp cutoff at the high-frequency end of the band. This is required in order to prevent the sound signal on the *lower adjacent* television channel from getting through the video amplifier. Because of the reversal of high and low frequencies which takes place in the mixer, the sound carrier of the lower adjacent channel will beat with the oscillator and cause an interfering signal which is located 0.25 mc above the edge of the channel, at 14.25 mc. These frequency relationships just described are shown in Fig. 32. A trap of the same general type as that used to reject the 8.25 mc carrier is used to reject possible interference from the adjacent sound carrier at 14.25 mc.

The maximum gain which can be obtained in a video i-f stage is considerably lower than that in an ordinary broadcast i-f stage because of the wide band of frequencies which must be passed and because of the high carrier frequency. This is true even where high mutual conductance tubes of the 1851 series are used, so that it is not unusual for as many as five separate stages to be used in the video i-f amplifier.

The transformer design is especially complicated in video i-f amplifiers because of the wide pass band of from 2.5 to 4.0 mc which must be obtained. To obtain close coupling so as to increase the pass band, direct coupling of the primary and secondary windings by means of a common inductance is often used. Loading of the tuned circuits with resistors so as to broaden the circuits is very common and will be found in practically all the circuits. Video i-f transformers are further complicated because the rejector circuits for the associated and adjacent sound channels are often an integral part of the interstage coupling transformers. Because of the comparatively high frequencies, the only capacitance used to tune the circuits is often that of the wiring and tube capacitance so that no condenser as such appears on the schematic. Nevertheless this capacitance forms a resonant circuit with the related windings of the transformer and should be taken into consideration. Since the wiring capacitance is an important part of the total circuit capacitance, it is important that no changes be made in the wiring when servicing is required.

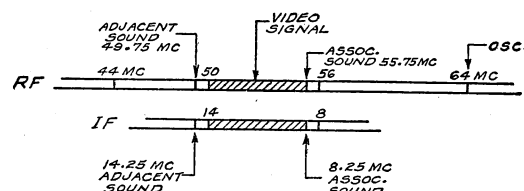


FIG. 32.—The sound signal of the associated channel at 8.25 mc and the sound signal of the adjacent channel at 14.25 mc are both close to the edges of the video band. Traps are provided to prevent interference from these signals.

AVC is often used in video i-f amplifiers, but as will be explained later under "AVC Circuits," the manner in which the AVC voltage is produced differs from that in radio receivers and in the sound i-f amplifier.

#### Video I-F in Andrea Model 1F5

In the Andrea Model 1F5 receiver, shown in Fig. 33, the video i-f amplifier employs two stages of amplification both of which use type 1852 tubes. In order to separate the sound i-f part of the signal from the video part, a separate secondary circuit L2-C2 is tuned to 8.25 mc so that the sound i-f signal appears across this circuit. The sound i-f signal is fed directly to

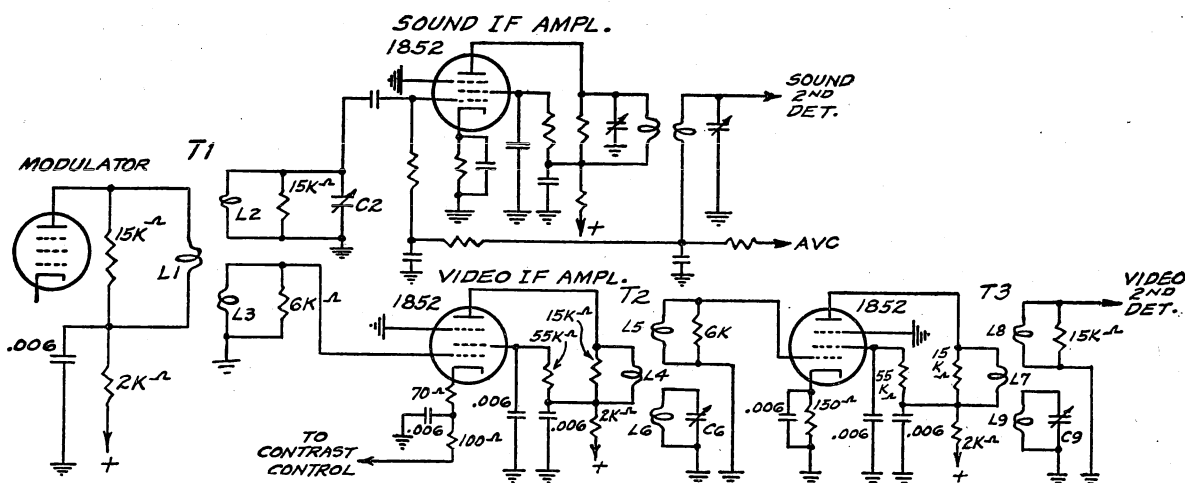


FIG. 33.—The video and sound i-f amplifiers in the Andrea Model 1F5 receiver.

the sound i-f channel which is conventional and requires no further comment.

The video component of the i-f signal is developed across L3. No trimmer condenser is used on this winding and the circuit is heavily loaded by the 6000-ohm resistor in order to pass the required band of frequencies. The video signal is applied directly to the grid of the type 1852 tube used in the first i-f stage. To obtain negative feedback and the increased stability which it makes possible, an unbypassed 70-ohm resistor is placed in the cathode circuit. The other end of this resistor is connected to a variable resistor—the “contrast control”—by means of which the gain of the i-f stage is controlled. Since no AVC is used, the control grid is returned directly to ground. The band of frequencies passed by this amplifier is approximately 2.5 mc; this pass band is generally considered to provide sufficient detail for the small picture tube used with this receiver.

The signal is coupled to the grid of the second i-f tube by means of the transformer T2. The windings L4 and L5 of this transformer function as the primary and secondary windings of the interstage transformer and are loaded by means of the 15,000-ohm resistor across the primary and the 6000-ohm resistor across the secondary. The only capacitance used to tune these windings is the tube and circuit capacitance.

The third winding L6 is tuned to 14.25 mc by means of the trimmer C6 and eliminates possible interference from the sound carrier of the lower adjacent television channel, as was previously shown in Fig. 32. This circuit acts as a trap by absorbing all the energy in the neighborhood of 14.25 mc so that it is not passed on to the grid of the following tube.

The second i-f stage feeds directly into the video i-f

second detector through the transformer T3 which is similar to T2. The circuit L9-C9 is likewise tuned to 14.25 mc so that it acts as a trap circuit for this frequency.

No AVC is used in the video i-f amplifier in this receiver and accordingly the grids of the two i-f tubes are returned directly to ground. The gain is controlled by means of the “contrast control” which varies the bias of both the first i-f stage and the first detector stage.

#### Video I-F Amplifier in the RCA Model TRK-12

The partial schematic in Fig. 34 shows the video i-f amplifier used in the RCA Model TRK-12 receiver, which is also used in the Westinghouse Model WRT-703. In contrast to the video i-f amplifier described above, this amplifier is designed so as to obtain a pass band of approximately 4 mc. As a result of the higher modulating frequencies which are passed, the detail in the image is increased correspondingly. A large 12-inch picture tube is used with this receiver; this permits finer detail, so that it utilizes the additional detail which the wide response of this more elaborate amplifier provides.

Unfortunately it is not possible to increase the pass band of the i-f amplifier without decreasing the gain obtained in each stage. As a consequence of this it is necessary to use a larger number of stages in the i-f amplifier; five stages are used in the receiver being described. In addition to the large number of stages required, the complexity of the coupling transformers is increased both as a consequence of the larger bandwidth and the fact that the trap circuits must be more effective. Thus the frequencies accepted by the i-f



amplifier are very close to the sound carrier so that the rejection must be more nearly perfect than in the case of a video i-f amplifier which passes a smaller band.

The transformers used in this receiver can be broken down into three basic elements which are shown in Fig. 35: the primary winding L1, the coupling winding L3 and the secondary winding L2. Inductive coupling between the primary and secondary is not used, but instead the primary and secondary are coupled directly by means of the inductance L3 which is common to both circuits. The primary circuit is resonated by C1 near one end of the pass band, whereas the secondary circuit is resonated by C2 near the opposite end of the band. R1 and R2 are loading resistors used to broaden the response.

Although the i-f transformers in the RCA TRK-12 use the relatively simple basic design shown above, the circuits are further complicated because of the blocking condenser required to keep the plate voltage off the grid and because of the presence of the trap circuit. The condensers C1 and C2 do not appear as such in the schematic because they are represented by the plate-to-ground and grid-to-ground capacitances, which include the stray wiring capacitances in addition to the tube capacitances.

Referring again to Fig. 34, let us consider the several transformers separately. The first-detector transformer assembly is more complicated than the others because the sound i-f signal is present at this point, and must be separated from the video i-f signal. This separation is accomplished by means of the circuit L18-C19 which is resonated to 8.25 mc, the sound i-f. The sound i-f signal is coupled to this circuit by means of the 12-mmf condenser C24; the resistor R10 is used to broaden the selectivity of the sound i-f channel.

With respect to the video section of this transformer, L17 and L20 are the primary and secondary windings which are tuned by the plate and grid capacitances as explained in connection with Fig. 35. These circuits are coupled to each other by the common coupling

condenser C23. A trap circuit is made an integral part of the transformer assembly. This circuit is tuned by L19 to 14.25 mc and prevents frequencies close to this value from getting into the video i-f amplifier. There are thus four adjustments required for proper operation of this transformer which can be

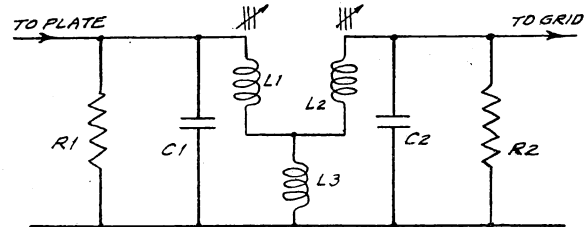


FIG. 35.—A simplified diagram of the video i-f transformers used in RCA television receivers. Direct coupling is provided by the inductance L3 which is common to both primary and secondary circuits.

summarized as follows: L17 and L20 control the primary and secondary tuning and are resonated at opposite ends of the pass band of 4 mc; L18 tunes the sound pickup circuit and is resonated at 8.25 mc; L19 tunes the trap circuit so as to reject interference in the neighborhood of 14.25 mc.

The first and second i-f transformer assemblies are practically identical, and are somewhat similar to the first detector unit. In the first i-f assembly, L21 and L25 are the primary and secondary inductances which are again resonated at opposite ends of the pass band. L24 provides the direct coupling between the primary and secondary as shown in the simplified drawing of Fig. 35. L23 is part of a trap circuit which is tuned to 8.25 mc, so that, in all, two sharply tuned trap circuits are provided at this frequency. These are required because the wide pass band necessitates passing video frequencies which are close to the sound carrier frequency; at the same time this sound carrier and its sidebands must be rejected and this is effected by means of the tuned circuits associated with L23 and L28.

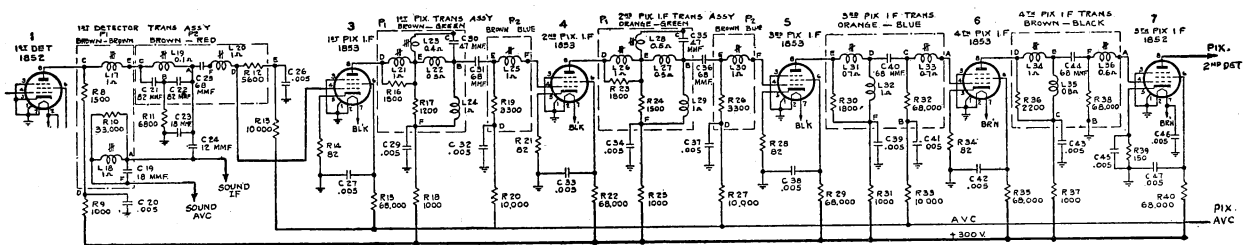


FIG. 34.—The video i-f amplifier in the RCA Model TRK-12. Five i-f stages are used to obtain a pass band of 4 mc. Traps are provided at 8.25 mc and 14.25 mc to prevent interference from the associated and adjacent sound channels.

The third and fourth transformer assemblies do not incorporate any trap circuits and are similar to the transformer shown in Fig. 35. The condensers C40 and C44 are blocking condensers which prevent the plate voltage from being applied to the control grid of the following tube. The plate of the fifth i-f tube feeds through a special coupling transformer to the video second detector; this transformer is not shown in the figure but will be discussed later in connection with video second detector circuits.

As the schematic of Fig. 34 shows, the first, second, third and fourth video i-f tubes are controlled by the video AVC circuit; the grids of these tubes are each returned to the common AVC bus through a filter combination consisting of a 10,000-ohm resistor and a .005-mf condenser. In addition, the gain of the first detector tube is controlled by the same AVC voltage, so that effectively there are five stages under control. This makes for a very effective AVC action which keeps the signal applied to the video second detector and sync separating circuits essentially constant.

### Video Second Detector Circuits

In a radio receiver the second detector rectifies the i-f signal and as a result the audio signal corresponding to the variations in the carrier is recovered. In the same way, the video second detector in a television receiver rectifies the video i-f signal and as a result the video signal corresponding to the variations in the amplitude of the carrier is recovered. This video signal is of course that produced by the camera tube and contains in addition the pulses required for synchronization; it is similar to the standard RMA signal shown in Fig. 20.

Generally speaking, video second detectors are similar to the second detectors of the diode rectifier type used in radio receivers. However, because modulating frequencies as high as 4 mc (in the larger receivers) must be passed, a lower value of load resistance is used in order to prevent the attenuation of the higher video frequencies. The value of load resistance generally used is of the order of 2500 ohms; on the other hand, the values used in radio receivers are of the order of 250,000, or approximately 100 times as

great. Because of the low value of diode load resistance, receivers are generally designed so that the signal level at the second detector is approximately 5 volts or more. This minimizes distortion due to the curvature of the diode characteristic, which is more pronounced when low values of diode load resistance are used.

### Video Second Detector in DuMont Models 180-183

The video second detector circuit used in the DuMont Models 180-183 receivers is shown in Fig. 36. A full-wave rectifier circuit is used so that both halves of the signal are rectified. Since the cathodes are connected to the ends of the centertapped secondary, each diode will draw current when its cathode is negative with respect to ground (the diode plates both return to ground through the 3000-ohm load resistor). As a result the current flow through the load resistor will be in the direction shown. Thus when a video signal is applied to the primary of the transformer, the plate end of the load resistor will become negative in proportion to the amplitude of the carrier. When the carrier amplitude is greatest, as it is for the sync pulses, the greatest negative voltage will be produced at A. The various shades of white and gray in the signal will produce lesser values of voltage at A, zero voltage of course corresponding to whitest white. In accordance with the definition of signal polarity previously given, the video signal produced at A is said to have *positive polarity*.

It is worth while noting that if the diode plates, instead of the cathodes, had been connected to the ends of the coil, then the polarity of the video signal would have been reversed. As we shall see in the discussion of video amplifiers, whether or not the diodes are connected to give a signal of positive or negative polarity depends upon the number of stages in the video amplifier. The controlling factor is that the amplified signal which is finally applied to the grid of the picture tube must of course have a positive polarity since a more positive voltage on the grid produces a brighter spot on the screen of the tube.

### Video Second Detector in RCA Model TRK-12

The video second detector in the RCA Model TRK-12 (also used in the Westinghouse Model WRT-703) is shown in Fig. 37. The signal is coupled through an autotransformer arrangement from the plate of the last video i-f tube into the full-wave diode rectifier circuit. Thus the signal voltage between A and the centertap C is stepped up so that the voltages across each half of the coil L38 are equal. The sec-

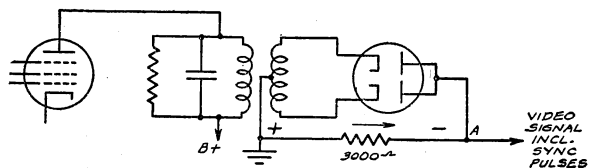


FIG. 36.—The video second detector circuit in the DuMont Models 180-183. A full-wave rectifier circuit is used.

ondary winding is loaded to broaden the frequency response. By means of the bypassing action of the .005-mf condenser C48, the centertap of L38 is maintained at ground i-f potential; in other words, there is no signal voltage at point C.

Unlike the previous circuit, the video signal produced across the 4000-ohm load resistor R45 has a negative polarity. This can be seen from the fact that a large carrier amplitude, which corresponds to black in the picture, produces a more positive voltage at B. R45 is a potentiometer and serves to regulate the magnitude of the video signal fed into the video amplifier. Since it controls the maximum voltage swing of the video signal on the grid of the picture tube between black and white, it is called the "contrast control."

An important advantage which results from the use of a full-wave rectifier circuit in video second detectors is that the filtering of the i-f components from the video signal is more easily accomplished. Because of the balanced nature of the circuit, the lowest frequency which is present across the output load R45 is the second harmonic of the video i.f. and this is more readily prevented from getting into the video amplifier. On the other hand, in the case of a single-ended circuit using only one diode, the fundamental video i.f. is present across R45 and is more difficult to filter out.

### Video AVC Circuits

Although the ultra-high frequencies used for television are not subject to fading of the same type as that found in the high and medium radio frequencies, the signal strength may still vary because of swinging of the antenna or the presence of automobiles and other moving objects. Since these variations will cause a change in the contrast of the picture being received, they are undesirable and can be avoided if the receiver is equipped with AVC. The use of AVC also simplifies the design of both the video gain control circuit and the sync separating circuits because it assures the maintenance of a constant signal voltage at the video second detector.

In the conventional AVC circuits used in radio receivers, the control voltage is produced by rectifying the carrier and as a result the control voltage is proportional to the *average* value of the carrier. Because the average value of the carrier in ordinary broadcasting does not change during modulation, it is a measure of the signal strength and hence can be used to control the gain of the receiver.

In television this same system cannot be used because the average value of the video carrier is dependent upon the average illumination of the scene being televised. Thus if the average background of the

scene is white, then the average carrier amplitude will be small; on the other hand, if the average background is dark, then the average carrier amplitude will be large. (The above conditions are of course only true for negative modulation which is standard for this country.) Obviously, then, we cannot use the average amplitude of a video signal to obtain the necessary d-c control voltage, because such a control action would vary the gain of the amplifier in accordance with the average background illumination and as a result produce distortion.

However, although the average value of a video signal does not remain constant, the *peak* value always has the same fixed value regardless of the percentage of modulation or the average illumination of the scene. For this reason the peak value of the carrier serves as a convenient reference to establish the strength of the carrier and is the basis of operation of video AVC circuits. As we have seen, this peak value is transmitted at the end of each line, that is, 13,230 times in every second, and thus it is available at regular intervals which are frequent enough to make possible the production of an automatic control voltage.

It is of interest to note here that one of the important reasons for the use of negative rather than positive modulation is that only in negative modulation is this regular succession of peak pulses available for AVC purposes. The design of AVC circuits where positive modulation is used, is considerably more complicated; for positive modulation the peak values of the signal are not fixed but depend upon the brilliance of the scene being televised.

Satisfactory operation in the smaller and less expensive receivers is often secured without the use of a separate AVC system in the video channel. In these receivers, relatively few video i-f stages are used so that the problem of manual gain control is not so difficult. In addition, the first detector is often controlled by the AVC voltage produced in the sound channel, so that some degree of automatic control is provided. Since the video and sound carriers are close to each other, they undergo approximately the same varia-

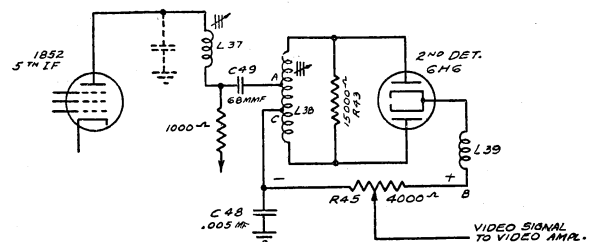


FIG. 37.—The video second detector circuit in the RCA Model TRK-12.

tions in transmission from the transmitting antenna to the receiving antenna, but in general these variations are not sufficiently alike to permit the use of sound AVC voltages on all the video stages.

### Video AVC Circuit in the RCA Model TRK-12

The video second detector and AVC circuit used in the RCA Model TRK-12 is shown in Fig. 38. Although the second detector has been described previously, it is shown here because the action of the AVC circuit is connected with the detector. When a signal is being received, full-wave rectification takes place in the 6H6 and as a result the demodulated video signal is produced across the 4000-ohm load R45 in series with the peaking coil L39. The polarity of this signal is indicated by the insert wave which shows that point B of the load is positive with respect to point A; B can be considered as being at a fixed reference voltage since it is tied down to  $-33$  volts through the filter resistor R47.

The circuit used to obtain the AVC voltage from the signal across AB is essentially a peak voltmeter using one section of the 6F8-G tube as a diode. As the circuit shows, the grid is used as the diode plate and is connected directly to B; the cathode is bypassed to ground by a 1-mf condenser C54 and is returned to A through a 470,000-ohm resistor, R46.

During the sync intervals, the grid of the diode is highly positive with respect to its cathode so that a current flow takes place through R46 and a positive charge is stored in C54. Because the sync pulses are repeated rapidly, 13,230 times per second, this charge

is continually replenished and C54 remains charged to the peak value of the video signal. If, for example, we assume a 10-volt peak signal, then C would charge up to a potential 10 volts greater than that at A or  $-23$  volts ( $-33 + 10$ ).

Since the voltage produced in this way is proportional to the peak value of the carrier, it is a suitable measure of the signal level at the second detector. However, its polarity must be reversed in order that an increase in signal input will produce a more *negative* rather than a more positive control voltage. This reversal of polarity is effected by means of the second section of the 6F8-G which is used as a d-c amplifier.

This tube receives its plate voltage through a 680,000-ohm load resistor R50 which is 2 volts negative with respect to ground. Since the cathode is returned to  $-23$  volts on the bleeder, the net plate voltage with no input signal is equal to 21 volts ( $-2 + 23$ ). The grid bias is equal to the voltage at the grid minus that at the cathode or  $-10$  volts ( $-33 + 23$ ). When no signal is present this value of bias is so great that the cathode current is completely cut off and as a result the voltage at D is equal to  $-2$  volts. This is the minimum bias with no signal and in combination with the drop of 0.7 volt across the 82-ohm cathode resistor of each of the controlled tubes, provides a net bias of 2.7 volts for each of the video i-f tubes.

On the other hand, when a signal is being received, C54 charges up positively to the peak value of the signal and this positive voltage is applied to the grid of the AVC triode amplifier. If the signal is strong enough, the plate current will increase, the voltage drop across R50 will increase, and D will become more

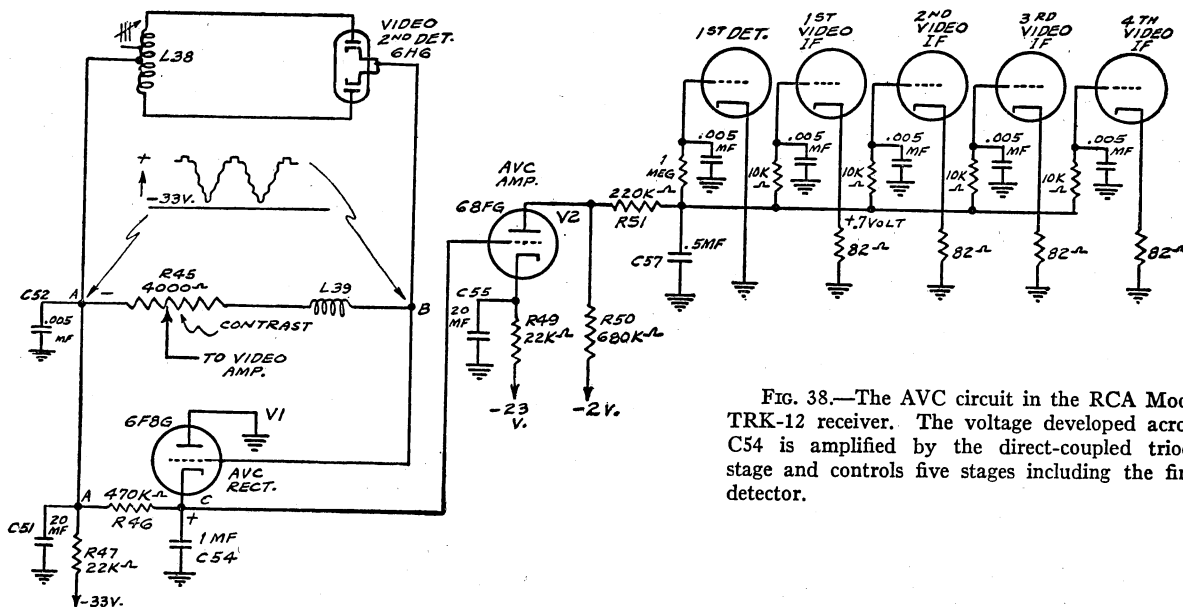


FIG. 38.—The AVC circuit in the RCA Model TRK-12 receiver. The voltage developed across C54 is amplified by the direct-coupled triode stage and controls five stages including the first detector.

negative than  $-2$  volts. The amount of negative voltage produced at D is proportional to the strength of the signal and hence the voltage is available for AVC.

A delayed AVC action is secured because the negative bias of 10 volts, which exists with no signal, drives the grid of the AVC amplifier tube considerably beyond cutoff. Thus the signal level must reach a certain minimum value before the plate current will flow and the AVC voltage be produced.

In addition to the delay action, the fact that five stages are controlled results in a very effective AVC action which maintains the signal level at the second detector essentially constant.

### Video Amplifiers

In the same way that the audio signal in a radio receiver requires amplification before it has sufficient power to drive the speaker, so the video signal in a television receiver requires additional amplification following the video second detector before it has sufficient amplitude to swing the grid of the picture tube. This amplification is supplied by the video amplifier which works between the video second detector and the grid of the picture tube.


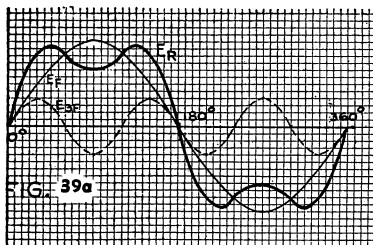


FIG. 39a, on the left, shows the resultant wave ( $E_R$ ) when a 1000-cycle sine wave ( $E_F$ ) and a 3000-cycle sine wave ( $E_{SF}$ ) are added in phase.

FIG. 39b, on the right, shows how the resultant wave ( $E_R$ ) is distorted when the 3000-cycle sine wave ( $E_{SF}$ ) is retarded half a cycle.

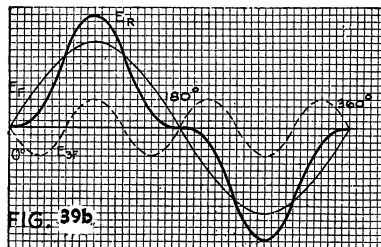

The problems associated with the video amplifier, like most television problems, are considerably more difficult than the corresponding problems for a radio receiver. Thus the video amplifier must amplify uniformly frequencies ranging from a few cycles to frequencies as high as 2 to 4 mc. Whereas phase shift is not important in an audio amplifier, in a video amplifier all the frequencies in the signal must take the same time to pass through the amplifier from input to output. This is important because distortion of the waveform, and hence of the picture, is produced when

the different video frequencies do not all take the same time to pass through the amplifier. This type of distortion is illustrated in Fig. 39 which shows the difference in waveform produced when a 3000-cycle wave is retarded half a cycle in passing through the amplifier. That the uniformity of time delay plays an important part can be seen from the fact that it takes only approximately seven one-millionths of a second for the cathode-ray beam to move one inch across the screen of the picture tube. Thus even a small non-uniformity in time delay can cause serious distortion of the image.

The video amplifiers being used in television receivers now on the market have successfully met the problems outlined above. By using low values of load resistance, the shunting effect of tube and circuit capacitances has been minimized and the upper frequency limit extended. Fig. 40 shows how the use of a low value of plate load resistance, although it lowers the maximum amplification obtainable, makes possible a more uniform gain over a wide range of frequencies. The sacrifice in gain accompanying the use of low values of load resistance has been partially compensated for by the use of the new high mutual conductance tubes which provide approximately three times as much amplification for a given value of load resistance, as was previously possible with the older tubes.

The most common method for obtaining uniform gain is to use so-called "peaking coils" in series with the plate load resistor. These are small inductances of the order of 100 microhenries, which are resonated with the tube and wiring capacitance near the high-frequency limit of the video amplifier. Peaking coils permit higher values of plate load resistor for a given uniformity of amplification, and consequently make possible reasonably high gains per stage.

In most video amplifiers, filter resistors and condensers are used in the plate and screen leads to provide low-frequency compensation for both gain and time-delay. These filter resistors and condensers are

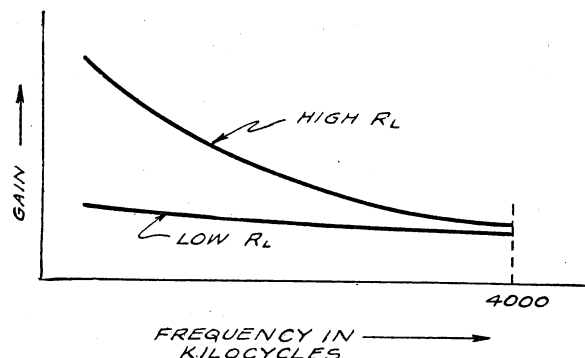


FIG. 40.—The use of a small value of load resistance provides a more uniform gain over a wide range of frequencies, although the maximum gain is decreased.

more critical in value than they are in a radio receiver where the primary purpose is to reduce hum and prevent circuit interaction through the common power supply. For this reason, whenever replacement becomes necessary, the resistors and condensers should be replaced with the correct value. Although a larger plate filter condenser, for example, will cause no harm and may even do some good in reducing hum in a radio receiver, the same procedure followed in a video amplifier may cause serious distortion of the picture.

### Average Brightness and D-C Restorer Circuits

In our previous discussion of the video signal, we looked upon this signal as containing a series of voltage values each of which corresponded to a particular value of light intensity in the televised image. We considered that in the same way that light values can be reckoned from black as a reference level, so a particular voltage value can be assigned to black and then each light value represented electrically by assigning a higher (or lower) voltage to the signal, depending upon the brightness of the light value at the scanned area. This method of looking upon a video signal is shown in Fig. 41 (a), in which it is clear that all light values are with reference to the black level—which is taken as the zero-voltage axis.


Insofar as video amplifier operation is concerned, the important thing about Fig. 41 (a) is that it shows that a video signal is inherently a pulsating d-c voltage. In other words (as in the case of a rectified a-c voltage which is also a pulsating voltage) all the light values are represented by electrical values on one side of the zero-voltage axis. The video signal must therefore contain both a d-c and an a-c component in the same way that a rectified a-c voltage representing the output of a power supply contains a d-c component—the d-c voltage of the power supply, and an a-c component—the hum ripple of the power supply.

Physically what does it mean to say that a video signal contains a d-c as well as an a-c component? Actually it is only another way of looking at the sig-

nal, as Fig. 41 (b) clearly shows. In this figure we describe the signal by saying that the light values are represented by fluctuations in both directions from an average level which we can call the "average brightness," or the "picture background." Thus instead of describing the light value at any point in the scene by stating how much brighter it is than black, as in (a), in (b) we accomplish exactly the same thing by stating how much brighter or blacker is the particular light value than the *average brightness*. In (a) we use the black level as the reference level whereas in (b) we use the average brightness as the reference level.

Electrically speaking, the average brightness level represents the average value of the video signal or in other words the d-c component of the signal. On the other hand, the fluctuations in the signal on either side of the average brightness level, which is electrically the a-c axis of the signal, represent the a-c component of the signal. An important characteristic of the average brightness or a-c axis is that the area between the positive part of the cycle and the a-c axis is equal to the area included between the negative part of the cycle and the same a-c axis. This is shown in Fig. 41 (b), where it can be seen that area 1 is equal to area 2 + area 3.

From the preceding it will be clear to you that proper operation of the picture tube requires that both the d-c and a-c components of the video signal be passed by the video amplifier. For if only the a-c component reaches the grid of the picture tube, then the picture tube will have information only on the fluctuations in light values *with reference to the average brightness level* but it will have no information whatsoever on the value of this average brightness level. Thus the picture cannot be reproduced accurately since the same variations (represented by the a-c component) might be superimposed on say either a dark or light background of any shade. The average brightness, or the d-c component of the video signal, must be present before the picture can be reproduced.

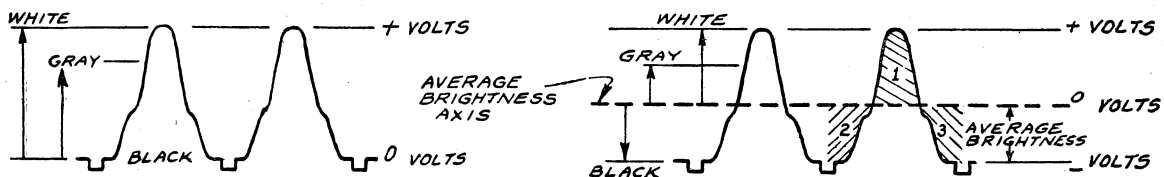

FIGS. 41a, 41b.—The light values in a video signal can be reckoned in two ways: In (a) the various light values are described with reference to the black level, whereas in (b) the same light values are described with reference to the average brightness of the signal.

### D-C Restorer Circuits

Unfortunately it is not possible to transmit the d-c component of any signal without using a direct-coupled amplifier. However, the use of direct-coupled amplifiers is not practical in television receivers because of their comparative instability and high cost. For this reason, television engineers have developed circuits which make possible the use of conventional a-c amplifiers with condenser coupling and at the same time provide for the restoration or *recreation* of the d-c component after the a-c component has been amplified by itself.

It will be helpful at this time to consider several video signals which have different values of average brightness and to describe the action which takes place when these signals pass through an amplifier which employs a blocking condenser as a coupling element between stages. It is because of the presence of the blocking condenser that only the a-c component is passed and that the d-c component is lost.

In Fig. 42, the picture being scanned is a white triangle on a black background, with the vertex of the triangle near the top. Part (a) shows two lines scanned near the top of the picture; part (b), near the middle of the picture; and part (c), near the bottom. Thus (a), (b) and (c) represent three sections of the picture where the average brightness is

low, medium, and high respectively. Fig. 42 can be said to represent the signal as it is at the output of the camera tube or as it is recovered at the video second detector. Of special importance is the fact that all the blacks are lined up so that the d-c component of the signal is represented in all cases. Note that the d-c component, like the average brightness which it represents, is successively larger in (a), (b), and (c).

Now what happens to this signal when it is passed through an a-c amplifier which contains coupling condensers and therefore will not pass the d-c component? This is clearly illustrated in Fig. 43 which shows that the blacks are no longer lined up, but instead the separate average-brightness or a-c axes are all lined up. In other words, when the d-c component is lost, only the fluctuations on either side of the average brightness are transmitted and this axis must of necessity be the zero voltage axis in all instances because no d-c component can get through the amplifier.

Having investigated the video signal both with and without the d-c component, let us now examine the manner in which the picture tube is affected by the presence or absence of the d-c component. In Fig. 42, we see that black in every case corresponds to the same definite voltage value and that is also true for white and every intermediate shade between black and white. Thus when the voltage of Fig. 42 is applied to

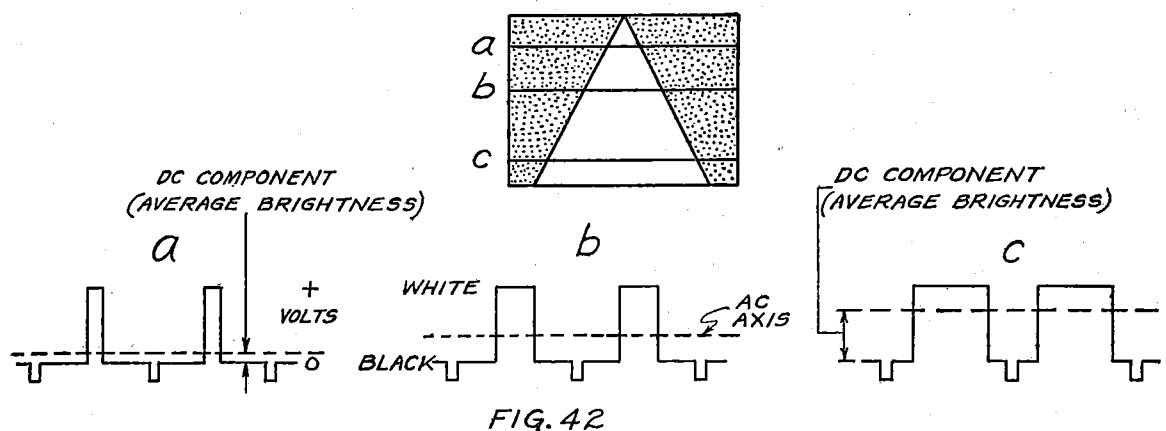


FIG. 42

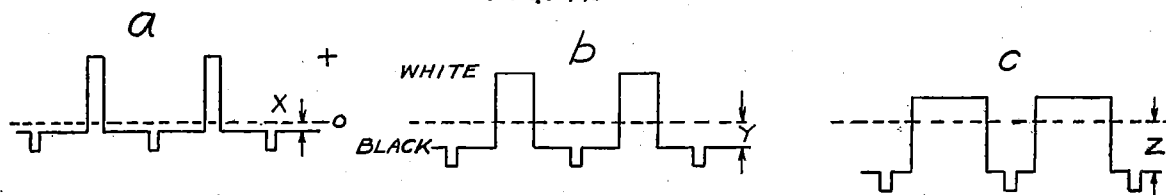


FIG. 43

FIGS. 42, 43.—FIG. 42 shows the video wave produced when two lines are scanned at a, b, and c of the white triangle on a black background. Since the black level is the same for all three cases, this signal contains the d-c component. FIG. 43 shows the same signal after it has passed through an a-c amplifier; note that the d-c component has been lost so that black in the signal no longer corresponds to a fixed voltage level as it does in FIG. 42.

the grid of the picture tube, the picture will be reproduced without any distortion.

This, however, is not true of the signal in Fig. 43, from which the d-c component has been removed. Black no longer corresponds to the same value in all instances, but instead the signal voltage associated with black takes on a value which is entirely dependent upon the average brightness of the strip being scanned. In the same way, this figure shows that white, and in fact every intermediate shade as well, has a different voltage value which is also dependent upon the average brightness of the strip being scanned. A little reflection will show you that this gives rise to serious distortion because the same light value in different parts of the picture does not correspond to the same voltage value in the signal. Thus, for example, the grid of the picture tube receives a *different voltage* for the *same shade* of gray in (a), (b) and (c) of Fig. 43 and as a result this shade is reproduced differently in the three instances.

In order to remove this source of distortion, it is apparent that the average brightness or the d-c component must be restored. At first glance this seems impossible, for how can the d-c component be restored after it has once been lost in the video amplifier? As a matter of fact, it is generally not possible to restore the d-c component of a pulsating wave after the d-c component has been lost in transmission, because no information relative to the d-c component is contained in the a-c component; the two are entirely independent of each other. Fortunately, however, the sync pulse is transmitted at the end of each line, *and the pedestal on which the sync pulse stands corresponds to a definite black reference level*. These facts make it possible to restore the lost d-c component. Thus to restore the d-c component to the signal of Fig. 43 it is only necessary to modify the signal so that all the synchronizing pulses are lined up. When this is done, the signal in Fig. 43 is exactly the same as that in Fig. 42 and the d-c component has been completely restored.

The solution of the problem depends upon finding this varying d-c voltage and adding it to the signal. This is accomplished in a very simple manner by using a diode to rectify the "black" half of the a-c video signal (which contains the sync signal) and in this way the required voltage is produced. Thus in Fig. 43, at (a) this rectification produces the voltage x; at (b) it produces the voltage y; and at (c) it produces the voltage z. In general, the addition of this varying d-c voltage lines up all the pedestals to produce the original signal (Fig. 42) with the d-c component restored.

### Basic D-C Restorer Circuit

In Fig 44 we show a straightforward circuit which is used to restore the d-c component in the video signal before the signal is applied to the control grid of the picture tube. The video signal is developed across the 3000-ohm plate resistor R1 and fed to the control grid through a 0.1-mf coupling condenser C1. As the sketch shows, the signal has the required positive polarity both at the plate of the video amplifier and the grid of the picture tube. However, the d-c component is not present at the plate side of C1, whereas the diode circuit shown in heavy outline has restored the d-c component on the grid side.

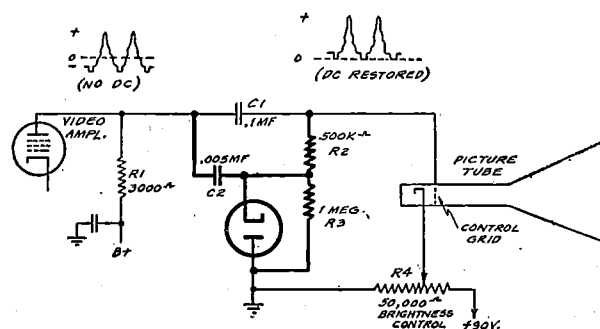


FIG. 44.—The heavy outline shows a typical d-c restorer circuit arranged to restore the d-c component to the video signal before it is applied to the control grid of the picture tube.

Let us see just how the diode circuit restores the d-c component. Considering the series circuit composed of the video voltage across R1, the .005-mf condenser C2, and the diode in shunt with a 1-meg resistor,—we can see that the following takes place: On the positive half of the cycle the cathode of the diode is swung positive with respect to its plate so that no current flows in the diode circuit. On the negative half of the cycle, however, the cathode is swung negative with respect to the diode plate, and current flows in the diode circuit through R3. It is this current flow which charges C2 and makes the cathode end of R3 positive, and as a result provides the d-c restoring bias.

Note that the d-c voltage across R3 satisfies all the conditions required to line up the sync pulses so as to restore the d-c component. Essentially the action in the diode circuit is such that the *negative* part of the video wave is rectified and that the diode current charges C2 positively to a value equal to the amount by which the sync pulses in (a) are depressed below the a-c axis. Since the grid of the picture tube is returned to this d-c voltage through the 50,000-ohm resistor R2, the d-c voltage is added to the video signal at (a) and "raises" the pedestal so that it lies along the zero-voltage axis, as shown at (b).



Now suppose, as in Fig. 43 (c), that the average brightness is higher than that shown at (a) in Fig. 44. This results in the pedestal being more negative with respect to the a-c axis, so that the diode produces a more positive voltage which again raises the pedestal to the same zero-voltage axis as at (b) in Fig. 44. Thus the action is entirely automatic so that all the pedestals are lined up at the grid of the picture tube, *regardless of the value of the average brightness.*

It is important to understand that the voltage produced at the cathode varies constantly throughout the scanning and that its value at any time depends upon the average brightness of the *portion* of the picture being scanned at that particular time. The time constant (RC) of the diode circuit is designed so that C2 will not discharge appreciably during the interval between successive sync impulses. At the same time, the time constant is sufficiently small so that when the average brightness changes, the condenser is able to change its charge rapidly enough to respond to the new conditions.

Insofar as the grid of the picture tube is concerned, it receives the a-c component of the video signal through C1, and *only* the d-c component through R2. Although the a-c component is also present at the cathode of the diode, R2 acts as a filter resistor to prevent that portion of the video signal present at the cathode from reaching the picture-tube grid through R2.

### Brightness Control

We have just seen how the d-c restorer circuit automatically lines up all the sync pulses so they are at the same voltage level. For correct operation of the

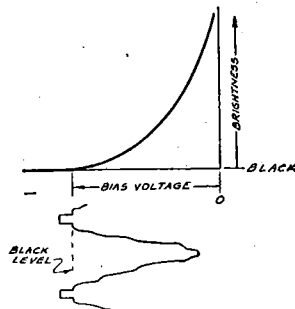


FIG. 45.—The effect of bias voltage on the brightness of the image. The brightness control (see FIG. 44) should be adjusted so that the black level on the signal occurs approximately at the cutoff of the picture tube characteristic.

picture tube, the bias on the picture tube must be so adjusted that these aligned pedestals occur at the cut-off or black level. The sync pulses will then lie in the blacker-than-black region and the various shades of gray and white will be reproduced correctly.

Fig. 45 shows the illumination characteristic of a picture tube and the manner in which the brightness of the scanning spot depends upon the bias voltage on the control grid. Referring again to Fig. 44, it will

be observed that the cathode of the picture tube is returned to a potentiometer which makes it possible to vary the bias voltage from 0 to 90 volts.

When the bias is highly negative, the tube is cut off and the spot intensity is zero. As the bias becomes more positive, the intensity of the spot increases. For correct operation, the brightness control should be adjusted manually so that the pedestals occur at the black or cutoff points. Once the brightness control has been set, the d-c restorer circuit automatically keeps the pedestals in alignment so that no further adjustment is required.

### Grid Leak—Condenser Restorer

Another type of d-c restorer circuit which is very widely used is shown in Fig. 46. In this circuit the

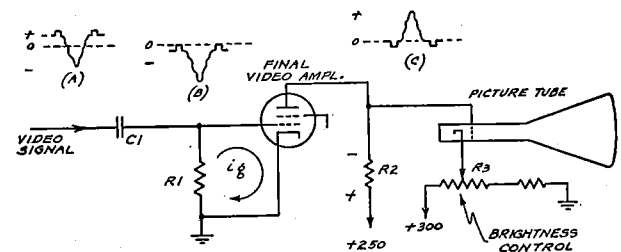


FIG. 46.—A widely used type of d-c restorer circuit in which the video amplifier output tube is operated at zero bias so that the grid-cathode elements function as a diode to reinsert the d-c component.

output video amplifier tube is operated at zero bias and the grid-cathode elements are used as a diode to insert the missing d-c component. To prevent the loss of the newly restored d-c component which would occur if condenser coupling were used in coupling the plate to the picture tube, the plate is coupled *directly* to the picture tube grid.

From the explanation already given of the process of d-c restoration, it is easy to understand how circuits of this type operate. The waveform of the video signal on the left side of C1 is shown at (a); at this point the signal has a negative polarity and of course the d-c component is missing. When this a-c signal is impressed on the grid of the output tube through C1, the positive parts of the video cycle (including the sync pulses) place the grid positive with respect to its cathode so that grid current flows through R1. The direction of this grid-current flow is such that the grid becomes negative with respect to ground.

When the average brightness of the signal is small, the a-c axis of the signal will be near the black level, the positive peaks will be small in amplitude, only a small value of grid current will flow, and consequently the grid will be displaced only slightly negative. On the other hand, when the average brightness is great,

the a-c axis is away from the black side, the positive peaks will be large in amplitude, a relatively large flow of grid current will take place, and the grid will be made highly negative. *In each instance, the grid will be made more negative by an amount equal to the height of the sync pulses above the a-c axis of the wave.* As a result of this action all of the pedestals in the signal are depressed by an amount sufficient to align them to the same zero-voltage level at the grid. This is shown by the signal waveform at (b). Essentially the action here is the same as that previously described for the circuit using a separate diode. The condenser C1 performs the same function of storing the grid charge as in the previous method.

At the plate of the output tube, the polarity of the video signal is reversed and as (c) shows, the signal at this point has the required positive polarity. Since no blocking condensers are interposed between the plate and the grid of the picture tube, the sync pulses remain in alignment.

As in the previous circuit, provision must be made for initial adjustment of the bias of the picture tube so that the pedestals of the signal will occur at cutoff (black level) on the picture-tube characteristic. To accomplish this, the cathode of the picture tube is returned to a bleeder-potentiometer which makes it possible to place up to a maximum of +300 volts in the cathode. Since the grid can at most have a potential of +250 volts, this makes a bias of -50 volts available on the grid of the picture tube. Under actual operating conditions, the voltage drop across R2 makes the grid more negative; this is compensated for by making the cathode of the picture tube less positive by adjusting the brightness control R3.

When the receiver is first turned on, there is no voltage drop across the plate-load resistor R2 until the output video tube warms up and draws plate current. The final adjustment of the brightness control therefore should not be attempted until the receiver has been turned on for a few minutes. In particular the brightness control should be all the way to the left (with the rotor at +300) until the receiver has warmed up; this is done to avoid possible damage to the picture tube because of excessive beam current.

### The Contrast Control

The "contrast control" is the gain control which determines the magnitude of the video signal applied to the grid of the picture tube. Its counterpart in a sound receiver is the volume control, and in the same way that the sound volume control determines the range of intensities between the loudest sound and the softest sound, so the video contrast control determines the range of light intensities between the highlights

and the shadows of the picture. Referring to Fig. 45, the setting of the contrast control determines how much of the picture tube characteristic is used and how bright will be the brightest element of the scene. When the contrast control is not advanced far enough, the picture lacks brilliance and the highlights are comparatively dark; when the contrast control is advanced too far, the picture becomes blurred, there is a loss of detail in the highlights, and in general the intermediate shades are lost.

### Synchronizing Circuits

The circuits devoted to synchronization in a television receiver are those which remove the sync information contained in the complete video signal and utilize it to control the timing of the horizontal and vertical deflection oscillators. To perform these functions, the sync part of the signal must first be separated from the picture part of the signal. In addition the vertical sync pulses must be separated from the horizontal sync pulses so that each can be applied to the respective deflection oscillator which it controls.

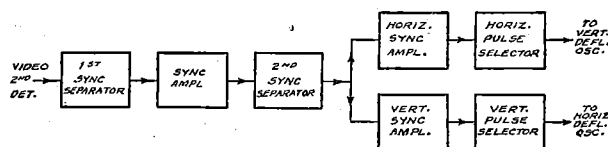


FIG. 47.—Block diagram of the sync circuits used in the RCA Model TRK-12 receiver.

The circuits used to separate the synchronizing pulses from the picture portion of the signal are called "sync separators" or "clippers." These circuits are designed so that they are responsive only to the sync pulses which lie above the pedestals; thus they reject the picture portion of the signal. The clipper or sync separator is generally followed by additional amplification and finally the sync signal is fed to a frequency-selecting circuit which separates the horizontal sync pulses from the vertical sync pulses. This separation is accomplished by circuits which depend for their action upon the difference in the time duration of the two types of pulses.

To illustrate the principles involved in sync circuits, we shall describe the circuits used in the RCA Model TRK-12 receiver. As the block diagram in Fig. 47 shows, the video signal is taken directly from the second detector and passes through the *first sync separator* which removes most of the video signal from the sync signal. The sync signal is then amplified in a *sync amplifier* stage and fed to a *second sync amplifier* stage which completes the separation of the sync signal. The output of the second clipper is fed to two

separate stages, the horizontal sync amplifier and the vertical sync amplifier. The output of the horizontal sync amplifier feeds the sync pulses to a circuit—the *horizontal pulse selector*—which selects the vertical sync pulses; the output of the vertical sync amplifier also feeds the sync pulses to the *vertical pulse selector* which selects the vertical pulses.

On the whole, the block diagram presents quite an imposing array of circuits considering that it represents but a small part of all the circuits in the complete receiver. However, synchronization is so important in the operation of the television system that great care must be taken to make the synchronization positive in action.

### Sync Separator Circuit

Referring to the partial schematic in Fig. 48, the video signal is fed from the second detector directly into the grid of the first sync separating tube. This stage uses one section of the 6N7 dual triode. The distinguishing features of this stage are that the tube is operated at the very low plate voltage of 15 volts and at zero bias (when no signal is present). When a signal is being received the grid leak-condenser combination R75-C77 provides a bias voltage as a result of the rectified grid current. As the waveform shows, the polarity of the video signal applied to the grid is negative so that the grid bias is supplied by the sync pulse part of the signal. As previously explained in connection with d-c restorer circuits, the bias at the grid varies in accordance with the average brightness and the result is that all the sync pulses are lined up with the zero-voltage axis at the grid of the first sync separator. This is illustrated in Fig. 49 which shows the plate current-grid voltage characteristic of the first sync separator stage.

Because of the low plate voltage of only 15 volts, plate-current cutoff is reached at a low value of nega-

tive grid voltage. Consequently the picture part of the signal lies beyond cutoff, and only the sync pulses are effective in causing the plate current to change. Thus the picture part of the signal is removed and so does not appear in the plate circuit of the first sync amplifier tube. An important part of the action in this circuit is the operation with grid leak bias so that all the sync pulses are lined up. As in the d-c restoring circuits, the time constant of the input circuit is sufficiently large so that the bias is maintained during the interval between sync pulses.


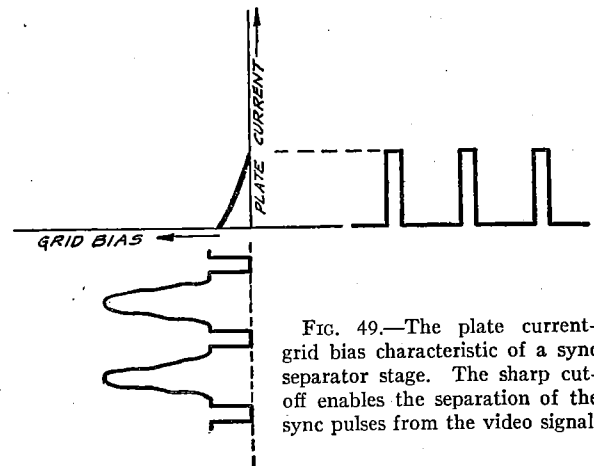


FIG. 49.—The plate current-grid bias characteristic of a sync separator stage. The sharp cutoff enables the separation of the sync pulses from the video signal.

The signal produced in the plate circuit of the first sync separator no longer contains the picture part of the signal but instead the latter has been removed because of the sharp cutoff of this stage. A term often used to describe the action of a circuit similar to the first sync separator is the term "clipper." This term is appropriate because the stage can be thought of as clipping the video portion of the signal and leaving only the sync pulses.

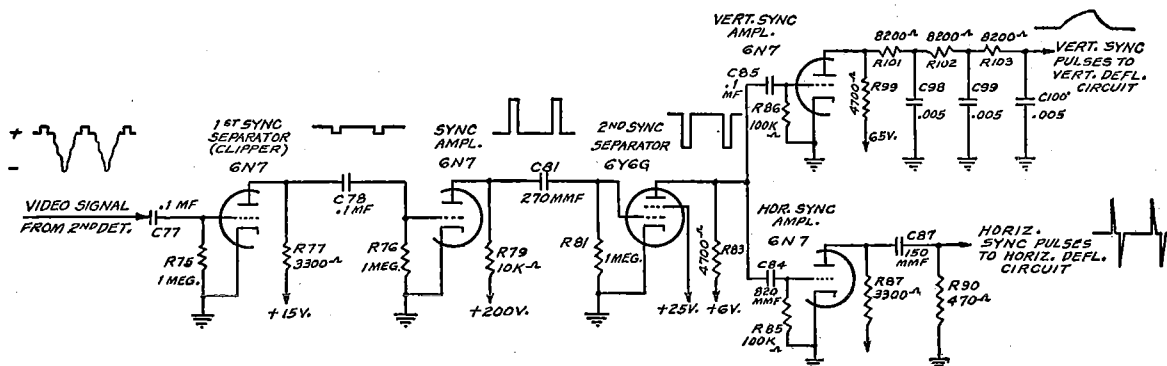The clipped sync signal is next fed to the grid of the second triode of the 6N7 which is arranged to func-



tion as an amplifier. For this reason a high value of plate voltage, 200 volts, is used. Note that the sync pulses have been reversed in polarity so that the grid of the amplifier tube goes negative on the peaks of the sync pulses. However, the operating characteristics of the amplifier stage are such that the sync pulse waveform in the plate circuit of the sync amplifier is simply an amplified version of the signal in the grid circuit. The polarity of the signal is of course reversed 180 degrees so that the sync signal in the grid circuit of the following clipper tube is negative in polarity.

The action in the second sync separator is similar to that in the first sync separator. A screen grid tube is used with the screen placed at a higher voltage than the plate and with both these voltages comparatively low. Thus the screen voltage is only 25 volts and the plate voltage about 6 volts. Under these conditions the stage has a very effective clipping action on both the positive and negative peaks of the sync pulse. In this way, if any video signal still remains it is clipped sharply by the plate-current cutoff; at the same time, the positive peaks of the sync pulses are again clipped as in the previous sync separator. As a result of this second clipping of the sync pulses, the waveform is made flat and any noise components that may have been added to the signal are removed. Thus noise is prevented from interfering with the synchronization.

The output of the second sync separator feeds the

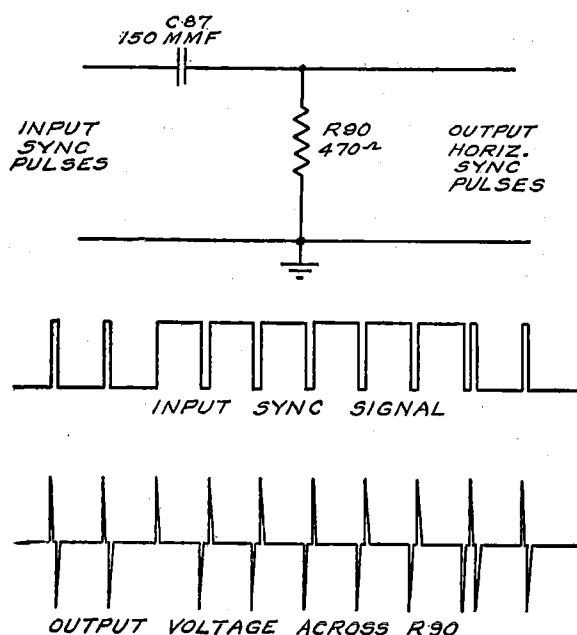


FIG. 50.—Circuit used for separating the horizontal sync pulses from the complete sync signal. The waveform of the sync signal at the input of the circuit and the corresponding waveform at the output are shown below the circuit.

sync pulses to two separate amplifier stages, a vertical sync amplifier and a horizontal sync amplifier. These individual stages provide further amplification of the sync pulses and at the same time act as buffer stages to isolate the vertical sync circuits from the horizontal sync circuits. The circuits used in the output of these stages are frequency-selecting circuits which differentiate between the two types of sync pulses by making use of the fact that the duration of the vertical sync pulses is greater than that of the horizontal sync pulses.

### Horizontal Sync Selector

The signal is coupled to the horizontal sync amplifier through the 820-mmf condenser C84. The amplified signal appears across R87 and is fed to the *selector circuit* consisting of C87 (150-mmf) and R90 (470 ohms). This circuit separates the horizontal sync pulses, which appear across R90.

The manner in which this selector circuit operates requires some explanation. Essentially the current which passes through R90 is limited by C87 because of the small value of capacitance and the low value of resistance. As a result the current through R90 is proportional to the rate of change of the sync pulse voltage and in this way sharp voltage pulses are produced across R90. This is clearly illustrated in Fig. 50 which shows the input sync signal during the interval between successive fields. Note that at each edge of the sync signal where the waveform changes abruptly, this rapid change results in a pulse of current through C87 and R90, which produces the voltage drop across R90 shown in the figure. As explained later, only the positive pulses across R90 are effective in synchronizing the deflection circuit; those below the axis have no effect. As Fig. 50 shows, horizontal sync pulses are also produced during the vertical blanking period because the leading edge of each vertical sync pulse represents a rapid change of voltage and therefore produces a pulse through R90.

### Vertical Sync Selector

The complete sync signal is also fed from the second sync separator into the grid of the vertical sync amplifier. The amplified sync signal appears across R99 and is fed to the selector circuit consisting of R101 and C98. Two additional sets of resistor-condenser combinations are used in series in order to increase the effectiveness of the vertical pulse selection.

The action of R101 and C98 in differentiating between the vertical and horizontal sync pulses is a direct result of the longer duration of the vertical pulses. Thus Fig. 51 shows that each one of the sync

impulses, including the horizontal impulses, contributes a small amount of charge which is stored in the condenser. The greater the duration of the pulse, the greater the voltage across the condenser. During the

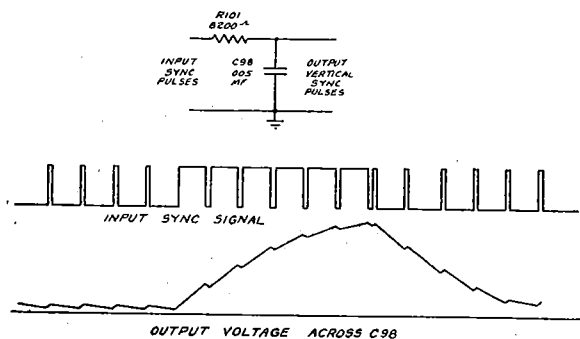


FIG. 51.—Circuit used for obtaining the vertical sync pulses required for field synchronization. The corresponding waveforms at the input and output are shown below the circuit.

transmission of the long vertical sync pulses, the accumulation of charge on the condenser is greater than during the transmission of the short line sync pulses. As a result, the voltage across the condenser C98

builds up to a peak once during each field or 60 times in each second. As the figure shows, the vertical pulse builds up to a maximum at the end of the last vertical sync pulse and then steadies down to an average value of voltage which remains constant until the beginning of the next field pulse.

To increase the circuit effectiveness, two more similar resistor-condenser combinations are used in series as shown in Fig. 48. These circuits accomplish a further selection of the two pulses so that a sharper pulse is produced once during each field. The peak of this pulse is used to synchronize the vertical deflection oscillator.

For exact interlacing it is important that the vertical pulses produced at the output of the vertical selector circuit be the same on alternate fields. The equalizing pulses, previously described, accomplish this by making the conditions exactly the same before and after the transmission of the actual broad vertical sync pulses. As a result, the condenser charges up to the same value of peak voltage on both the odd and even fields so that the vertical oscillator is maintained in perfect timing.

## DEFLECTION CIRCUITS

In describing the picture tube we explained how the electron beam can be deflected by sawtooth waves applied to the deflecting elements of the picture tube. The previous sections have explained the necessity for synchronizing these waves and how the sync signals are selected at the receiver. The next problem is to generate the sawtooth waves, control them by the sync signals and to apply them to the deflecting system of the picture tube.

The block diagram of Fig. 52 shows the essential parts of a common type of deflection circuit for television. From the sync separator described in the previous section, horizontal sync pulses are applied to the horizontal deflection circuits and vertical sync pulses to the vertical deflection circuits. Both sets of deflection circuits contain the same type of elements, the principal difference being the operating frequencies.

The sawtooth waves shown in Fig. 15 are formed in the *discharge circuit*. This circuit includes a condenser which is slowly charged from the B supply and then rapidly discharged through a vacuum tube. The voltage across this condenser varies in such a way as to form a sawtooth voltage wave similar to that shown in Fig. 15. The exact moment at which the discharge tube operates is determined by the *blocking oscillator* which provides pulses to the grid of the discharge tube of sufficient amplitude to "trip" it. The frequency of

the blocking action is itself synchronized with the incoming signal by pulses from the *sync separator*. The sawtooth voltage wave formed in the discharge circuit

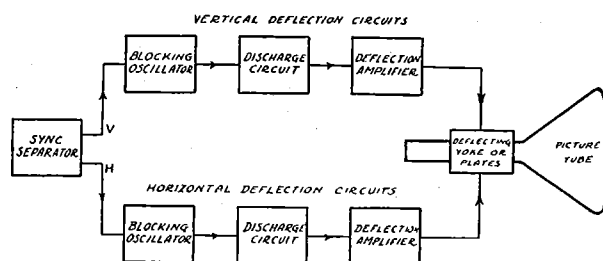


FIG. 52.—Block diagram of the essential parts of a widely-used type of deflection circuit.

is amplified in the *deflection amplifier* and then applied to the deflecting yoke or plates which cause the scanning action of the beam in the *picture tube*.

### Circuits for Electromagnetic Deflection

The schematic, Fig. 53, shows the deflection circuits used in the RCA Model TRK-12 and Westinghouse Model WRT-703 receivers. These are examples representative of circuits for use with a picture tube deflected by the electromagnetic method.

To describe the formation of the sawtooth wave, let us assume that the grids of the 6N7 tube (in the horizontal circuit) are biased to cutoff so that the tube

is non-conducting. The plate voltage starts to charge the .001-mf condenser C90 through resistors R93, R94 and R95 in series. The voltage across C90 (from D to ground) rises as shown by the line designated "trace" in Fig. 15a. About 65 microseconds later, a positive pulse of voltage is applied to the grids of the 6N7 and the tube "trips" or starts conducting. The triode section, whose plate is connected to D, then acts as a short to ground and discharges C90 in about 11 microseconds. The voltage across C90 falls as shown by the line designated "retrace" in Fig. 15a. The discharge is stopped after 11 microseconds by a sudden blocking of the grids, and the charging cycle starts again. The relatively short time allowed for the charge and discharge of condensers C90 (horizontal) and C103 (vertical) assures that the sawtooth wave will be essentially linear.

### Blocking Oscillator

The periodic blocking and tripping of the 6N7, which has just been mentioned, is accomplished by the blocking oscillator. In connection with the latter, the question naturally arises as to why the sync pulses could not be used directly to trip the discharge tube. Actually, the sync pulses could be used directly, but it has been found more satisfactory to use the blocking oscillator circuit being described. The blocking

oscillator provides a steep pulse of high amplitude which is more readily adapted to the control of the discharge tube than is the sync pulse itself. The necessary timing of the blocking oscillator is of course obtained from the sync pulses.

As the name implies, the blocking oscillator is a regenerative oscillator in which the feedback is so large that the oscillator is blocked on the first cycle of oscillation. Thus when oscillation starts, the amplitude is so great that the negative charge which accumulates on the grid condenser drives the tube to cutoff. Before the oscillations can start up again, the charge on the grid condenser must leak off. The rate at which this charge leaks off determines the rate at which the steep pulses are produced by the blocking oscillator. Because the circuit constants are such that the natural frequency at which the oscillator attempts to work is higher than the frequency of blocking, the pulse produced when oscillations start has a very steep waveform which is advantageous in controlling the discharge tube.

The rate of blocking, and hence also the rate at which the pulses for the discharge tube are produced, is controlled by R91 and R92. The lower the value of this grid resistance, the more rapidly the charge leaks off so that the oscillations can begin again and produce another pulse. The "free-running" frequency of

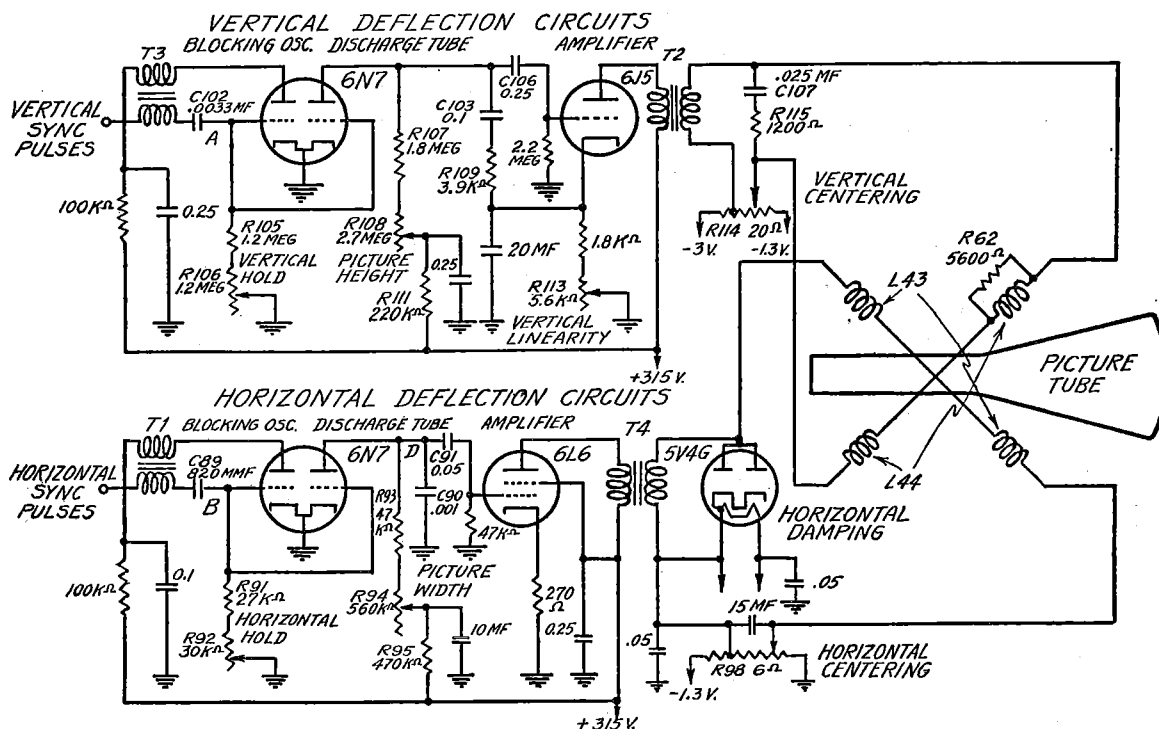


FIG. 53.—Deflection circuits used in the RCA Model TRK-12 receiver. Compare with the block diagram shown in Fig. 52.

the blocking oscillator is thus controlled by the value of C89, which determines the amount of charge stored in the grid circuit, and R91 and R92 which determine the rate at which this charge leaks off.

In practice, the free-running frequency is adjusted by means of the *horizontal hold control* R92 so that it is lower than the line frequency of 13,230 cycles. The application of the horizontal sync pulse to the grid circuit, as shown, will then introduce a positive pulse into the grid circuit and cause the blocking oscillator to start operating slightly before the instant when it would normally resume operation. In this way the sync pulse keeps the blocking oscillator exactly in synchronism with the frequency of the scanning at the camera tube.

The circuit for the vertical deflection operates in the same manner. In this case R106, the *vertical hold control*, is adjusted so that the free-running frequency of the vertical oscillator is slightly less than 60 cycles. The introduction of the vertical sync pulse trips the oscillator just before it would otherwise resume oscillation so that the frequency is kept in synchronism with the vertical sync pulses.

#### Width and Height Controls

The peak value of the sawtooth voltage which is developed across C90 depends on the setting of R94. Since the peak value of the voltage across C90 determines the magnitude of the horizontal scan and therefore the picture width, R94 is called the *picture*

*width control*. Similarly R108 controls the vertical sawtooth amplitude and therefore is called the *picture height control*.

The *vertical linearity control* R113, which is in series with the vertical wave-forming condenser C103, corrects the waveshape so that a sawtooth wave of current will be obtained through the deflecting coils.

#### Centering

As a result of the circuits described, accurately timed sawtooth voltages are available at points C and D. These waves are amplified and coupled to the deflecting coils L44 and L43 by transformers T2 and T4 respectively. The picture is centered on the picture-tube screen by sending a small direct current through the deflecting coils. Potentiometers are provided for making the vertical and horizontal centering adjustments.

#### Damping Tube

The 5V4G diode shunted across the secondary of T4 is provided so as to prevent transient voltages being set up when the scanning current changes abruptly. This diode acts as an automatic switch so that the transformer is loaded only during the trace period, and the load removed during the retrace period. It is not possible to use a permanently-connected resistor in place of the diode switch because this continuous loading would tend to prolong the retrace period by an excessive amount.

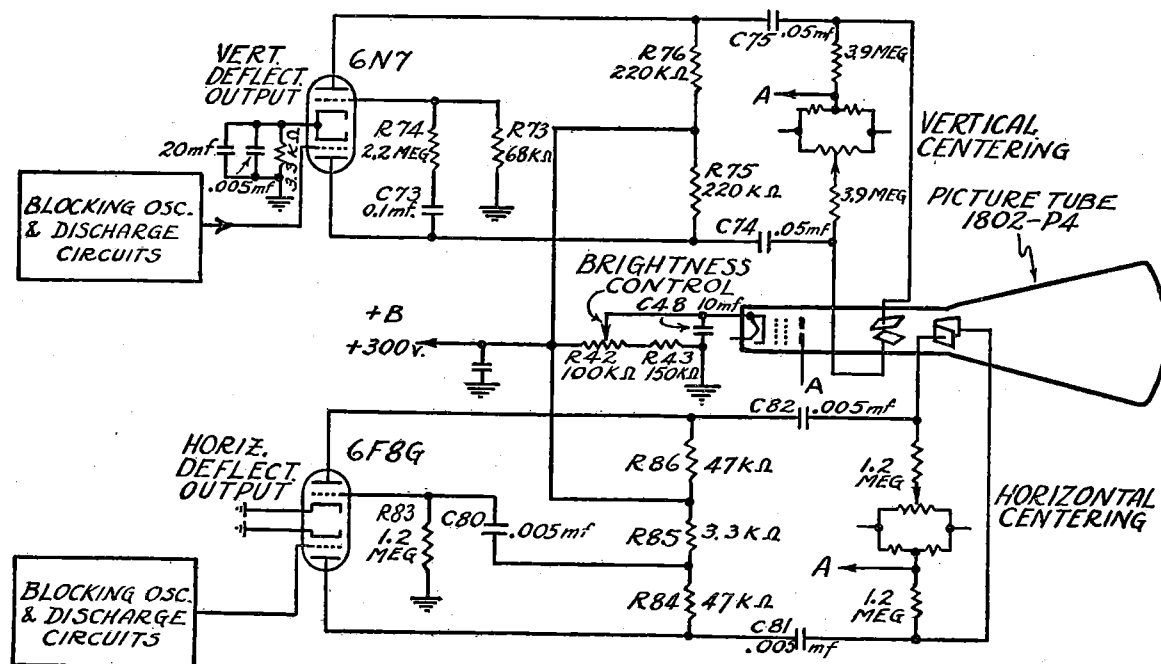


FIG. 54.—Circuits used for electrostatic deflection in the RCA TRK-5 receiver. Note the push-pull output in both the horizontal and vertical channels.

### Electrostatic Deflection

In electrostatic deflection systems for television, it is usual to use the same type of sawtooth-wave generator as is used for electromagnetic deflection. The output systems, however, are quite different. To avoid distortion of the raster and defocusing of the spot, the sawtooth waves on each plate of any pair must be alike but 180 degrees out of phase. A balanced amplifier using a phase inverter is used to furnish these deflecting voltages. The force acting on the electron beam is thus due to the difference between the potentials of the two plates, since at any one instant the positive voltage on the one plate attracts the electron beam at the same time that the corresponding negative voltage on the other plate repels the electron beam. Thus, if at any instant the deflecting voltage on one plate is +50 volts, then the voltage on the other plate is -50 volts and the effective deflecting voltage is the sum or 100 volts.

### Electrostatic Deflection Circuits

Fig. 54 shows the output circuits of the electrostatic deflection circuits used in the RCA TRK-5 and Westinghouse WRT-701 receivers. The blocking oscillator and discharge circuits are shown in block form because they are similar to those shown in Fig. 53. In the vertical circuit the signal across R75 is fed to one of the vertical deflecting plates through con-

denser C74. This same signal is also fed to the grid of the phase inverter section of the 6N7 tube through condenser C73 and a voltage divider consisting of R74 and R73. The signal across the phase inverter load R76, which is 180 degrees out of phase with the signal across R75, is fed through condenser C75 to the other vertical deflecting plate. The voltage divider R74, R73 is used to compensate for the gain of the phase inverter section of the 6N7 so that the signal amplitude applied to each deflecting plate is the same except for the phase reversal. In the case of the horizontal deflecting circuit, the action is similar; here the voltage divider consists of R84 and R85.

### Centering Control

Fig. 54 also shows the type of centering circuit used with electrostatic deflection. One plate of each pair is returned to the second anode through a high resistance. The second plate is returned through a high resistance to the potentiometer which permits a d-c voltage, either zero, plus or minus with respect to the first plate, to be applied to the second plate in order to center the raster on the screen of the picture tube. These potentiometers, called *centering controls*, are usually adjusted during installation and seldom need readjustment. The details of this type of circuit are shown in Fig. 55 in the following section on power supplies.

## POWER SUPPLIES

As a general rule, two separate rectifiers are used to supply the d-c voltages for television receivers. A low-voltage supply provides approximately 300 volts for the tubes associated with the amplifier, deflection, and sync circuits of the receiver. A separate high-voltage power supply provides the high voltages—from approximately 2000 to 10000 volts—required for the picture tube.

Since the low-voltage power supplies are very similar to those used in radio receivers, a separate low-voltage schematic is not shown here. The regulation in a television low-voltage power supply is generally better than that in a radio receiver because of the importance of preventing variations in the numerous circuits from interfering with each other and with the picture. The hum level is also kept down to a lower value because of the large number of circuits and stages, and because hum which would be inaudible in a sound receiver may cause appreciable distortion of the picture.

Unlike the low-voltage power supply, a half-wave rectifier is invariably used in the high-voltage supply.

The advantages of the half-wave rectifier are that the transformer does not have to be as large and that the peak voltage is reduced to about one-half the value required for full-wave rectification. Ordinarily the half-wave rectifier is not used in radio receiver power supplies because its output is harder to filter and because it cannot supply as much current to the load as the full-wave rectifier. However, these characteristics are not disadvantages in television receivers because only a very small current is drawn and a resistor-condenser filter can be used.

### High-Voltage Power Supply in RCA TRK-5, Westinghouse WRT-701

The high-voltage power supply used in the RCA Model TRK-5 and Westinghouse WRT-701 receivers is shown in Fig. 55. A type 879 high-voltage half-wave rectifier is used, the complete path of the rectified current being from the low-voltage end of the secondary, through the secondary winding, the 879 rectifier tube, the first filter resistor R91, the second filter resistor R92, and the bleeder resistors from R93



to R98, inclusive, and back to the low-voltage side of the secondary.

R91 acts as a filter resistor and also limits the voltage and current through the first filter condenser C86. Good filtering is secured by using a high value of filter resistance; R92 is 470,000 ohms, and in combination with the two .05-mf condensers provides adequate filtering. Note that large values of filter resistance rather than large values of capacitance are used to obtain the required filtering. The advantage of this is the reduced cost and size of the condensers; in addition, the smaller the size of the filter condenser, the less is the danger of fatal shock if one accidentally comes in contact with a charged or partly-discharged condenser. Nevertheless, the high-voltage filter condensers should always be discharged before any measurements are made so as to guard against the possibility of an open bleeder circuit.

In the circuit being described the cathode of the picture tube is near ground potential while the second anode is 2000 volts positive with respect to the cathode. The focusing anode is returned to the focusing control which places approximately 500 volts on this electrode. Centering of the beam horizontally and vertically is accomplished by returning one plate of each of the pairs to point M which is at a voltage slightly lower than the maximum output of the power supply. The remaining plates are then returned to

the sliding taps on the horizontal and vertical centering potentiometers so that the voltages can be varied either positively or negatively with respect to the other plates. These circuits should not be tested while the power is on since the maximum high voltage is present on all the deflection plates and centering adjustments. The deflecting plates are capacitively coupled to the horizontal and vertical deflection output tubes through .05-mf and .005-mf condensers as shown in Fig. 54; these condensers are of course rated to withstand the full high-voltage output.

The high-voltage supply is not entirely independent of the low-voltage power supply in the sense that the entire high-voltage power supply is returned to ground through the brightness control in the low-voltage power supply. If the connection to the brightness control at R42 were broken, then the entire high-voltage power supply would "float." In actual operation, the potential at the cathode is approximately 200 volts above ground potential, depending upon the setting of the brightness control; as a result the low end of the high-voltage rectifier circuit, including the cathode of the picture tube, is above ground potential by this same amount. The control grid of the picture tube, which is tied to the plate of the 6V6 video output tube, is approximately 175 volts above ground potential so that the proper average brightness can be secured by means of the setting of R42.

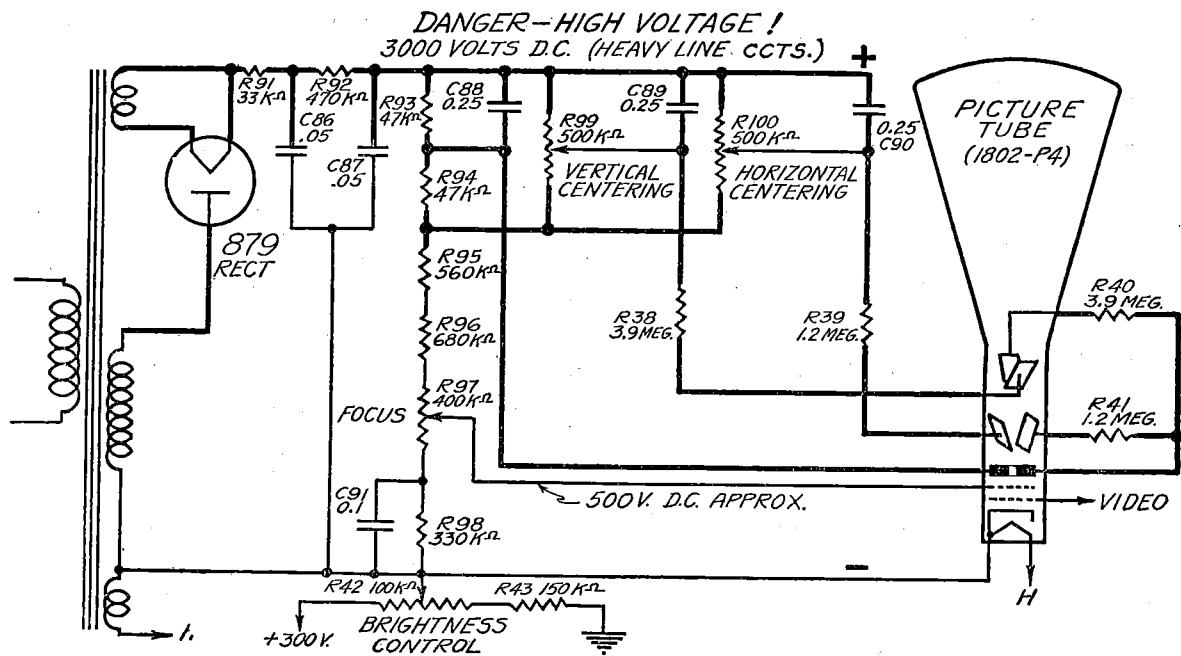


FIG. 55.—High-voltage power supply used in the RCA Model TRK-5 receiver. The heavy black lines represent the high-voltage circuits. Extreme caution should be observed to avoid coming in contact with high-voltage points.

### Grounding of High-Voltage Power Supply

The high voltage difference required between the cathode and second anode of the picture tube can be obtained with either the positive or negative side of the high-voltage power supply near ground potential. In receivers using the electromagnetic method of deflection, it is usual for the negative side of the power supply to be grounded since this enables coupling the video output tube to the modulation grid without the use of a high-voltage condenser. This same system is also used in some receivers which use electrostatic deflection, as for example in the RCA Model TRK-5 receiver. Where electrostatic deflection is used, however, high-voltage blocking condensers are required in the circuits which couple the deflection output tubes to the horizontal and vertical deflection plates.

To avoid the use of high-voltage blocking condensers in the deflection plate circuits and at the same time maintain the deflection plates at the same potential as the second anode (which is necessary to avoid distortion in the picture tube), the positive side of the high-voltage power supply is sometimes grounded and the cathode is then several thousand volts negative with respect to ground. The DuMont Models 180-183 are examples of receivers using this type of circuit. Although high-voltage condensers are not required in the deflection circuits, a high-voltage blocking condenser must be used between the plate of the video output tube and the modulation grid.

Regardless of whether the positive or negative side of the power supply is grounded, the usual precautions against electrical shock must be observed.

## ANTENNAS AND INSTALLATION

The proper operation of a television receiver depends to a very great extent upon the care with which the installation is made. No matter how well designed the receiver may be, its performance will be poor unless proper attention is given to the type of antenna, its location, and the installation of the receiver itself.

The receiver should be placed where no direct light will fall on the cathode-ray tube viewing screen. Although television pictures can be seen satisfactorily without total darkness, the vicinity of the receiver should be capable of being darkened readily. The location chosen should permit adequate ventilation and be close enough to a power outlet to avoid the use of extensions to the power cord. A good ground connection is also important. If the receiver is of the type intended to be used with a broadcast receiver, it should be placed in such a way that the sound appears to come from the picture, and the connections between the receivers should be as short as possible. The relation between the receiver location and the length of the antenna lead-in should also be considered, since the antenna location itself is usually determined by external conditions which cannot readily be changed.

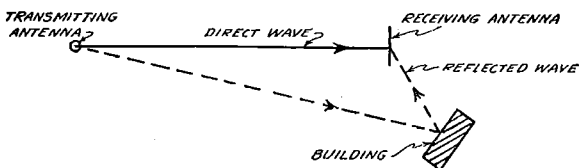


FIG. 56.—The same signal may reach the receiving antenna by two different paths. The dotted line shows the signal being reflected from a building. The example in the text is for a case in which the reflected (dotted) signal travels two miles farther than the direct signal.

The most important problem is the choice and installation of the antenna. The various manufacturers offer different types of antennas, some types being recommended for suburban areas, others for city use. All are of special design suitable for the ultra-short waves used in television, an ordinary broadcast antenna not being suitable for television use.

The necessity for special antennas for television is more apparent when we consider some of the differences between the short waves used in television and the comparatively long waves used in ordinary broadcasting. The shorter the wavelength of a radio wave, the more it behaves like light. For example, we know that light travels in straight lines through space. For this reason we cannot see objects far enough away to be "below the horizon." Clearly a taller object can be seen from a greater distance than one closer to the surface of the earth since it projects above the horizon. In the same way, the "coverage" of a television transmitter depends upon the height of both the transmitting antenna and the receiving antenna. In addition to increasing the range of reception, placing the receiving antenna as high as possible has the important advantage of increasing the signal pickup and decreasing the noise pickup. It is interesting to note that the television transmitter of the National Broadcasting Company in New York, which is located atop the Empire State Building (1250 feet high), covers a radius of about 40 miles or an area of about 5000 square miles.

In ultra-short wave transmissions as in light, buildings, mountains and other opaque objects cast "shadows" which result in no signal or very weak signal

within the shadow area. In addition such objects can cause reflections which may result in distorted pictures because of the small but appreciable difference in the time of arrival of the direct wave and reflected wave. Fig. 56 shows how this reflection may occur. The transmitter sends out waves in all directions, one of which may be considered as going directly to the receiver. Another wave reaches the receiver indirectly by going first to a building or other reflector and then to the receiver. The important point here is the difference in the total length of the path which the reflected wave has to travel as compared with the path of the direct wave. Here the difference is 2 miles. Since both waves travel at the same velocity of 186,000 miles per second, the reflected wave will arrive

$\frac{2}{186,000}$  second, or approximately  $\frac{1}{100,000}$  second later than the direct wave. The time required for the electron beam to travel 1 inch horizontally across the picture tube is also about  $\frac{1}{100,000}$  second. Therefore the

reflected wave will cause a second image which is displaced about 1 inch horizontally to the right of the image due to the direct wave. Smaller time differences may produce only lack of sharpness in the picture, but in any case, when installing the antenna the serviceman should try to avoid multiple images due to reflections. This effect can often be reduced or eliminated by slight changes in the position of the antenna, or by the use of a special antenna.

In general, since American television transmitting antennas will be mounted horizontally, the receiving antenna should also be approximately horizontal, and placed broadside to the direction of the transmitter. During installation, however, the best procedure is to watch an actual picture on the receiver, comparing different locations and positions of the antenna on the basis of the results obtained at the receiver. An intercommunication set between the man working on the antenna and another observing the received picture is obviously a useful accessory for antenna installation.

Automobile ignition systems and diathermy apparatus emit short-wave signals covering at least part of the television spectrum. Antennas should therefore be erected as far as possible away from these sources of interference.

The antenna should be erected at as high a point as conditions permit, since, other things being equal, the signal strength increases when the elevation of the antenna is increased. A high antenna is also likely to reduce local interference. Both these effects of course, tend to improve the signal-to-noise ratio.

Most television antennas consist of two rods or tubes of conducting material placed in a straight line end to end, but with some separation between them. Each section is about  $\frac{1}{4}$  wavelength (roughly 5 feet) long, making the total length about  $\frac{1}{2}$  wavelength. Such an antenna, shown in Fig. 57, is called a simple *half-wave dipole*.

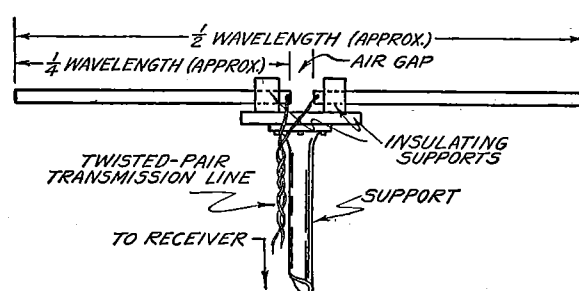


FIG. 57.—A half-wave dipole antenna—a type very widely used for television reception.

The lead-in or transmission line is usually a twisted pair of wires specially insulated against weathering; one wire of the pair is connected to each rod near the air gap. Some manufacturers have different kinds of transmission line for special purposes. The simple dipole is generally satisfactory, but improved performance can often be obtained from two such dipoles connected in parallel. Such double dipoles are mounted one above the other like the cross arms on a telephone pole.

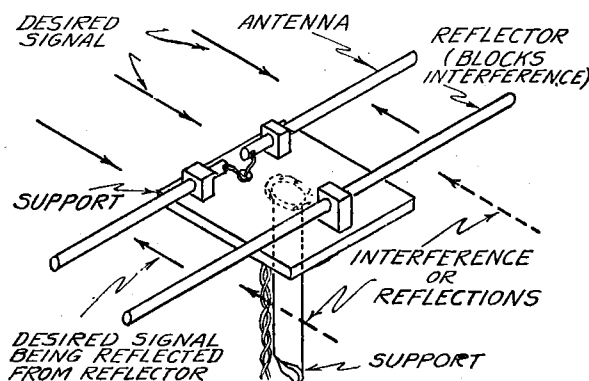


FIG. 58.—A half-wave dipole antenna with a reflector for increasing the signal pickup and reducing interference from reflections.

Where trouble is encountered from reflections or low signal strength, or both, a reflector element may be added to the antenna system. As shown in Fig. 58, the reflector is a continuous rod somewhat longer than the antenna and placed *behind* it; that is, the reflector is at the same elevation as the antenna and is parallel to it, but placed on the side of the antenna *away from* the transmitting station whose signal it is desired to receive. The reflector serves two desirable purposes:

it blocks interference or reflections coming from "behind" the dipole, and it strengthens the desired signal by reflecting it back to the dipole. The spacing between antenna and reflector is determined from the manufacturer's instructions or by experiment. The double dipole described previously may be provided with a double reflector.

No dipole of fixed dimensions can be equally efficient for all the television channels. The reason for this is that maximum efficiency requires that the length of the dipole (and also the reflector, if used) should have a fairly definite relation to the wavelength of the desired signal. We have mentioned, for example, that it should be about  $\frac{1}{2}$  wavelength long

overall. For the first two television channels (44 to 56 mc) the middle frequency is 50 mc and the corresponding wavelength is 6 meters, or almost 20 feet. A 10-foot half-wave dipole is therefore quite efficient for these two channels. It is not so efficient, however, for the 66-72 mc and 78-90 mc channels, since the mid-channel wavelengths for these are respectively about 14.3 and 11.7 feet. If all these channels are to be received on one antenna, they will not be received with equal efficiency. Depending upon the local conditions, it is possible to choose the antenna length suitable for either (1) the mid-point of the whole band, (2) the mid-point of the most popular station or stations, or (3) to provide an antenna of adjustable length.

## FREQUENCY MODULATION

Up to the present time all broadcast stations have used amplitude modulation for program transmission. In this method of transmitter operation the frequency of the carrier is maintained constant, usually by crystal control, while the amplitude of the carrier is varied by the audio modulation impressed upon it. A new system of broadcast transmission by frequency modulation is now being introduced by a few stations in the East. This system was devised by Major E. H. Armstrong and differs from amplitude modulation in that the carrier *frequency* is varied by the impressed audio modulation, while the carrier amplitude is held constant.

### Advantages of Frequency Modulation

The principal advantages of frequency modulation over amplitude modulation are an improved signal-to-noise ratio, particularly in poor reception areas where the signal strength of the transmitter is weak, and a reduction in interference when two frequency modulated transmitters are geographically separated but operating on the same frequency. In receiving, better fidelity is usually more easily obtained from frequency-modulated transmissions.

Since the carrier frequency in frequency-modulated broadcasting is varied over a wide band, wide channels are necessary for transmission. Present channels are 200-kc wide and have been allocated in ultra-high frequency bands to avoid interference with other services which would result if channels of such width were assigned within the standard broadcast band. The actual carrier frequency variation is limited to one-half the channel width, as with amplitude modulation, since the frequency of the carrier varies above and below the nominal assigned value when audio modulation is applied. In present frequency-modulated

broadcast transmissions, the maximum frequency deviation is held to approximately plus or minus 75 kc during audio modulation.

### How Noise is Reduced

The manner in which frequency modulation reduces noise may be understood by remembering that most electrical noises change the amplitude of the signal but not its frequency. Now, in the amplitude modulation method of broadcasting, both noise and audio modulation act to vary the carrier signal voltage so that the two are combined in the signal detected by the receiver. In frequency modulation, however, the audio modulation varies only the frequency of the carrier signal and not its amplitude. Noise, on the other hand, will cause no change in the carrier frequency, though it will affect its amplitude. If, then, the receiver is designed to detect only variations in signal frequency and not variations in amplitude, noise resulting from amplitude modulation is eliminated. Frequency modulation is not perfect, but a very great reduction in noise is secured by this method.

### Special Receivers Necessary

Conventional broadcast receivers are designed only for the reception of amplitude-modulated transmissions and therefore are not suitable for receiving frequency-modulated broadcast signals. The principal differences in the latter are in the design of the detector and in the limiter stage which precedes the detector.

A typical stage-by-stage lineup for a frequency modulation receiver is shown in Fig. 1. This shows an r-f amplifier, converter, 3-stage i-f amplifier, limiter, detector and a-f amplifier.

Since the transmitted frequency varies about 75 kc

above and below the point to which the receiver is tuned and flat amplification is necessary for high-quality reproduction, the carrier-amplifying stages and the converter must be designed to pass a 150-kc band without frequency discrimination. Ordinary tuned circuits are usually far too sharp for this purpose, particularly in i-f circuits, so we find in the frequency modulation receiver that low-Q circuits are necessarily employed to achieve broad tuning.

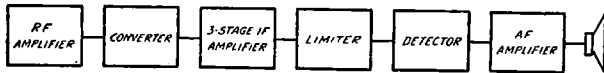


FIG. 1.—Block diagram of a receiver designed for the reception of frequency-modulated signals. With the exception of the limiter stage, the lineup is similar to that of a conventional superheterodyne receiver.

In the i-f stages, broad-band reception is secured by using a high intermediate frequency, usually of the order of 3 megacycles, and by broadening the i-f transformer response by resistance shunted across one or more windings.

#### What the Limiter Does

The limiter stage requires detailed consideration. Its purpose is to smooth out any variations in carrier amplitude so that it may pass on to the detector circuit a signal which is constant in voltage but varies in frequency. This is done by designing the circuit and operating the tube so that it overloads even when a weak signal is being received. Then any increase in signal voltage will not cause an increase in the carrier signal voltage which appears across the tuned circuit forming the limiter stage plate load. The high gain in the r-f, converter and i-f stages provides sufficient amplification for even weak signals so that the actual signal voltage at the limiter grid during reception will always be several volts. Any applied signal voltage greater than the overload point causes rectification in the grid circuit. A resistor in series with the grid return of the limiter input circuit is installed so that the grid current resulting from rectification in this circuit causes a voltage drop across the resistor which can be utilized to provide AVC action. This AVC voltage is applied, through appropriate filters, to preceding i-f, converter and r-f stages.

#### Special Detector Used

Since, in frequency modulation, the a-f modulation causes a variation in carrier frequency, we need a type of detector which will convert these frequency variations into the a-f signal voltages which originally produced these carrier frequency variations, and in this way restore the original modulation. Ordinary

detector circuits are not suitable, since they give an output voltage which is proportional to the amplitude of the carrier modulation and not to the carrier frequency. Since the voltage output of the discriminator circuits employed in AFC designs varies with the frequency shift of the applied carrier signal, it serves as an ideal device for the detection of frequency-modulated signals.

A typical AFC discriminator circuit is shown in Fig. 2. The primary coil,  $L_1$ , of the discriminator transformer is connected in the plate circuit of the limiter tube and is closely coupled to the center-tapped secondary  $L_2$ ,  $L_3$ . When the transformer secondary circuit is tuned to resonance with the alignment frequency of the i-f system, the voltages  $E_2$  and  $E_3$  are equal but opposite in phase. Since the d-c voltage across the discriminator load resistors,  $R_1$  and  $R_2$ , occurs as the result of rectification of  $E_2 + E_1$  and  $E_3 + E_1$ , then, at resonance, the d-c voltage from point B to ground is equal to that from point A, as both  $R_1$  and  $R_2$  are similar resistors. However, because of the manner in which the diodes are connected, the resulting d-c voltages will be opposite in polarity. Therefore, the voltage across  $R_1$  will cancel that across  $R_2$  and a measurement from point A to ground will show zero voltage between these two points when the circuit is tuned to resonance with the alignment frequency. This is the normal condition for perfect alignment of an AFC circuit.

When the signal voltage applied to the discriminator transformer is higher or lower in frequency than that to which it is tuned, the voltages  $E_2$  and  $E_3$  will remain equal but their phase relationship with respect to  $E_1$  will change. As a result,  $E_2$  plus  $E_1$  will no longer equal  $E_3$  plus  $E_1$ . Since this becomes the case, the resulting d-c voltages across  $R_1$  and  $R_2$  will no longer be equal and opposite in polarity and a voltage with respect to ground will accordingly appear at Point A. As the frequency of the carrier signal becomes higher or lower than that to which the discriminator is tuned, the voltages developed across  $R_1$

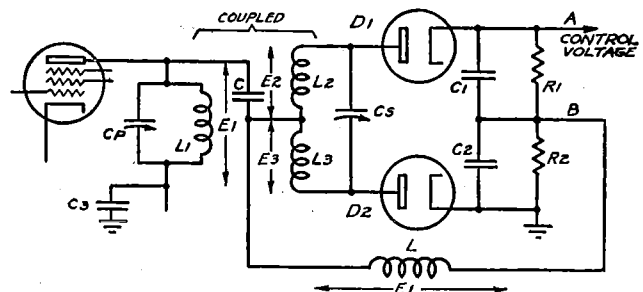


FIG. 2.—The second detector of a receiver for frequency-modulated signals is similar to the discriminator circuit shown.

and R2 add or subtract. Since point A is at zero voltage at resonance, this signal frequency variation causes point A to assume a potential with respect to ground which varies in a positive or negative direction in accordance with these frequency variations. The change in voltage of point A with respect to ground as a result of this shifting frequency is represented in the diagram, Fig. 3.

### How the Discriminator Detects

Now let us see how this characteristic of the AFC circuit serves to supply an audio signal to actuate the a-f amplifier of the receiver. We have seen, in frequency-modulated transmissions, that the carrier frequency changes at a rate which is in accordance with the audio modulation impressed upon the carrier. Let us assume that a 400-cycle audio note is being broadcast and the nominal frequency of the transmitter is 42 mc. On the positive half of the 400-cycle modulation, the carrier frequency may be increased while on the negative half it may decrease. If the modulating voltage is sufficient, this may cause a maximum increase of carrier frequency of 75 kc so that the maximum frequency at the peak of the positive half of the wave becomes  $42 \text{ mc} + 75 \text{ kc}$  and, at the peak of the negative half of the cycle, to  $42 \text{ mc} - 75 \text{ kc}$ . Now, referring again to Fig. 3, we see that a carrier frequency shift in a negative direction will cause the output voltage of the discriminator to become positive whereas an increase in carrier frequency will cause this output voltage to become negative. Since a 400-cycle note is being broadcast, the carrier frequency increases and decreases and the output voltage of the discriminator becomes positive and negative at the

same rate, 400 cycles per second, as that of the original broadcast note. Now, if we apply this rapidly-varying voltage to the grid of an amplifying tube, the voltage across its output load will vary at the same rate. Since this is precisely what occurs when an a-c signal is applied to a grid, we see that in this manner detection of frequency-modulated signals is effected.

Once the frequency-modulated signal is converted into audio frequencies, any type of conventional audio amplifier is suitable. Since the fidelity of reproduction in a carefully-designed receiver is exceptional, high-grade a-f amplifiers and speakers are usually employed.

### The G-E Model GM125 Receiver

The schematic (see page 10-35) shows the circuit of the G-E model GM125 receiver, which is designed for frequency-modulation reception. This is a 12-tube, single-band receiver which covers a frequency range of from 37 to 44 megacycles. A single r-f stage feeds the 6K8 converter; four i-f stages are employed, the fourth stage acting as the "limiter." The detector is similar to the AFC discriminator previously described. The triode section of a 6Q7G is employed as the first a-f amplifier and feeds a 6J5G phase inverter which drives the push-pull 6L6G output tubes.

The r-f and converter stages are similar to those which could be employed in conventional designs for the same frequency band, except that no effort has been made to acquire selectivity in the tuned stages since this would be undesirable in a receiver which is required to pass a wide frequency band without frequency discrimination.

The i-f stages are designed to give a band width of 300 kc. This is done by using a high intermediate frequency (3000 kc) and by shunting each i-f transformer primary winding with a 15,000-ohm resistor.

The last i-f stage operates as a limiter. The limiting effect is secured by using a 6SJ7 tube in this stage and operating it with zero control grid bias and only 65 volts on the plate and screen. Under these operating conditions, the tube overloads with a relatively small applied signal. The high overall gain of the stages preceding the limiter tube provides sufficient amplification so that even a weak signal in the antenna circuit is built up to a voltage sufficient to overload the limiter.

When the signal strength is sufficient to overload the limiter stage, grid current flows through the 330,000-ohm resistor, R15, in the grid return circuit of the 6SJ7. The resulting voltage drop across R15 is used to provide AVC action and thus prevent overloading of preceding stages. By incorporating AVC in this stage, there can be no AVC action until the

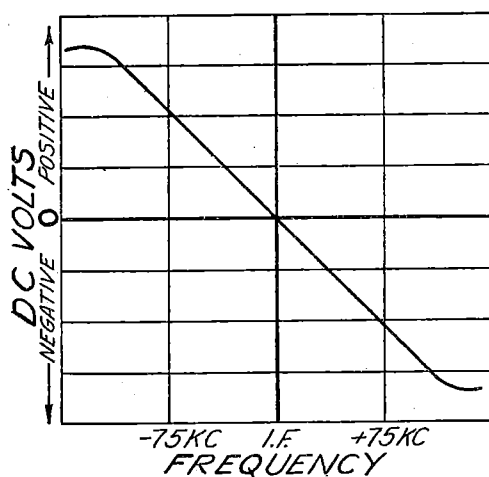


FIG. 3.—The output voltage of the frequency demodulator or second detector varies in accordance with the amount by which the signal frequency differs from the intermediate frequency.

limiter is overloaded, which is its required operating condition. When such is the case, an increase in signal voltage applied to the limiter grid will cause no increase in the output signal voltage across its plate load but the grid current will increase, thereby assuring an increasing AVC voltage.

The discriminator-type detector is similar in action to that reproduced in Fig. 2. It converts the frequency variations of the i-f signal output to a voltage which varies in amplitude at the audio frequency rate. The essential difference between this type of discriminator and one used solely for AFC purposes is that the audio component is not filtered out. This must be done when such circuits are used for AFC applications to avoid modulating the oscillator at the audio frequency. The discriminator load by-pass condensers, C18, C19, are accordingly only 22 mmfd each in this circuit, so there is no by-passing of the higher audio frequencies.

The output of the frequency-demodulator is coupled to a tone control network composed of R11, R20, R40 and the shunt and series condensers C39 and C17. Operation of R40 provides attenuation of either high or low frequencies, as desired. The output of this network connects to the volume control, R21, which returns to ground through an inverse-feedback network composed of R37 shunted by C16 in series with R22. The balance of the audio system is conventional.

#### Alignment Procedure

To align the i-f amplifier, connect an electronic voltmeter (or any other d-c voltmeter which has a

high input resistance) across R15. Feed a 3-mc signal to the grid of the third i-f tube. Temporarily shunt the secondary winding of T7 with a 10,000 or 15,000-ohm resistor and adjust C48 until the voltmeter reading is a maximum. Then remove the secondary shunting resistor and adjust C49 for maximum reading on the voltmeter. Then connect the shunting resistor across T6 secondary, feed the 3-mc signal to the second i-f grid and peak the trimmers of T6 in the same manner. Repeat this process for each of the i-f transformers in turn until all are aligned.

The frequency demodulator circuit may also be aligned with the voltmeter and signal generator. Feed a 3-mc signal to the input of the i-f amplifier and connect the voltmeter from the cathode connection of R18 to ground. A small voltage reading usually will be indicated if the circuit is slightly out of adjustment. If not, adjust C51 until a reading is secured. Then adjust C50 until the voltage reading is a maximum. After this is done, adjust C51 until the voltmeter reads zero. The discriminator alignment is then complete.

The r-f and oscillator stages are aligned by feeding a 42.8 mc signal to the antenna terminals and, with the receiver tuned to this point on the dial scale, adjusting the oscillator trimmer C4 for maximum reading on the voltmeter, which should be connected across R15. Then peak the antenna and r-f trimmers (C2 and C3) in the same manner.

The receiver may also be aligned with a frequency-modulated signal generator as described in the service notes given in Volume X of Rider's Manual.

## WIRELESS RECORD PLAYERS

A number of different wireless record players are described in Volume X. These were first announced about the middle of 1938, although phonograph oscillators were available commercially as far back as 1935. Contributing to the present popularity of these record players is that fact that no direct connection is required between the record player and the receiver, as well as the element of mystery which is introduced because of the absence of any wire connection to the radio. Although specific service data are shown in Volume X for the models listed in the index, there are certain general considerations which apply to all wireless record players.

Essentially a wireless record player is a low-powered transmitter which provides a signal much in the same way as an ordinary broadcast transmitter. However, instead of the modulation being obtained from a

studio microphone, the phonograph pickup converts the vibrations on the record into an audio signal and this voltage is used to modulate the oscillator contained in the wireless record player. The modulated signal is radiated to the receiver which is tuned to the signal and as a result the record is reproduced by the receiver in the conventional manner. Note that the entire receiver is used rather than just the audio section. Unlike the phonograph oscillators which preceded wireless record players, there is no direct connection to the receiver and hence the name "wireless" record player.

In general, the design of the radiating system in these record players is such that the effective range of pickup is approximately fifty feet. Since excessive radiation will cause interference in other radio receivers, the Federal Communications Commission has

limited the amount of radiation to a value which is high enough to permit satisfactory operation of the record player in a typical installation, and which at the same time is not so high as to cause interference in neighboring receivers. In general a long antenna should not be attached to the record player to supplement the built-in antenna, but where the signal input to the receiver is too small the coupling between the record player and the receiver should be increased. This can be accomplished by running the antenna of the record player closer to the antenna lead-in of the receiver.

Most wireless record players use two tubes, one tube as a combination oscillator and modulator, and the other tube as the rectifier tube. The 6A7 and the 25Z5 (or their newer equivalents) are commonly used to perform these functions. In some cases a single combination tube, such as the 12A7, is used both as an oscillator-modulator and as a rectifier.

The power supply design for the most part follows conventional practice and is not unlike the power supplies used in midget receivers. In some cases a small power transformer is used, but in general the d-c voltage for the oscillator-modulator tube is obtained by means of half-wave rectification of the line voltage. In the latter case, the voltage for the heaters and the pilot bulb are obtained through a line cord or ballast tube, although in some instances the heaters are in series with the motor windings so that no ballast resistor is required.

Where the 6A7 tube is used as the oscillator-modulator, the first two grids are not used to form the oscillating circuit, as is the case in the pentagrid converter. Instead, the tuned circuit of the oscillator is connected to the signal grid (the #4 grid) and the feedback circuit is through the plate of the tube, which carries the feedback or tickler winding. Essentially, then, as far as the action of the tube as an oscillator is concerned, the tube may be considered as an ordinary regenerative triode oscillator, in which the signal grid acts as the control grid and in which the feedback is supplied through the plate.

The unmodulated signal produced by this oscillator is modulated by means of the audio signal from the phonograph pickup. The action which takes place here is similar to that which takes place in the pentagrid converter. In the pentagrid converter, the local oscillator signal is produced by the first two grids of the tube, and the incoming signal (applied to #4 grid) is modulated by means of this local oscillator signal so as to produce the intermediate frequency. In wireless record players, however, the signal to be modulated is the oscillator signal (produced as explained above by connecting a tuned circuit to the #4 grid) and the

modulation is accomplished by feeding the audio signal to the #1 grid. Both grids #2 and the screen grid (#3 and #5) are connected to B+.

As a general rule a crystal pickup is used in wireless record players and, where the type 6A7 tube is used, the pickup is connected to the #1 grid. The output of these pickups is of the order of 1 volt or more, so that with average circuit conditions the percentage of modulation is fairly low. In order to prevent distortion as a result of non-linearity of the modulation, some designs do not apply the full value of the pickup output to the grid, but use a high value of series resistance to form a voltage divider. Where a volume control is used in the record player, this control appears in the input circuit so that it is possible to control the level of the audio signal which is fed to the modulator grid.

### General Service Notes

The servicing of wireless record players is similar to that of radio receivers so that no special instructions are required. However, the following notes will be found helpful in dealing with the specific conditions which are enumerated below and which are peculiar to these record players.

1. *High Noise Level:* A condition wherein the noise level is excessively high can generally be eliminated by coupling the record player more closely to the receiver. As a result of the closer coupling, the signal input from the record player to the receiver is increased, so that the noise level is correspondingly decreased. It is preferable, in coupling more closely to the receiver, to bring the antenna wire of the record player in close proximity to the lead-in of the receiver, rather than to extend the antenna of the record player in a random direction. In places where the noise level is especially high and it is difficult to find a clear channel, it will be found helpful to wind several turns of the antenna wire around the lead-in of the receiver. In no case should a direct connection be made to the antenna post of the receiver.

An alternative method of increasing the signal input to the receiver is to couple a wire to the tuned circuit of the record player through a 20-mmf condenser and to wrap several turns of this wire around the antenna lead in.

In some cases it will be helpful to tune the receiver over the range of the record player as it may turn out that a more quiet channel is clear which can be used advantageously. The record player should be off while this check is made. If a more quiet channel is found, then the record player should be tuned to this frequency.



**Hum:** Reversing the line cord plug has been found of help in reducing hum and in some instances a further reduction of hum can be effected by using the same receptacle for both the record player and the receiver. Aside from the usual causes of hum such as defective filtering in the power supply, excessive hum may be caused by proximity of the pickup leads (or the leads in the tuned circuit) to the line cord or rectifier leads.

**Distortion:** Where distorted operation is encountered, a check should be made to determine whether the distortion is being introduced by the record player or by the receiver. It should be remembered that in the last analysis the quality of reproduction can, at best, be equal to that of the receiver when it is operating on ordinary broadcast signals. This follows inasmuch as the entire receiver, and not just the audio section, is used to reproduce the signal.

If the operation of the receiver is good on broadcast signals but the output is distorted when the record player is used, then the distortion is most likely in the record player. A probable cause of distortion is a defective oscillator-modulator tube and this should be replaced to see whether another tube makes any dif-

ference. Other possible causes of distortion are a worn needle, defective crystal cartridge, or improper operating conditions. The actual cause of the distortion can be localized by following usual service procedure. It should be noted that in some cases placing the record player too close to the radio may cause microphonic action to take place with resulting distortion. On records which are deeply cut, distortion may sometimes be encountered as a result of amplitude distortion. This can be eliminated by changing to a softer needle or by reducing the setting of the volume control in order to feed a weaker signal to the modulating grid of the record player. The resulting decrease in volume which results can be compensated for by advancing the volume control setting in the radio receiver and, if necessary, by increasing the coupling between the wireless record player and the receiver in the manner previously described. In general, the volume control in the receiver should be adjusted for the highest volume that will be required and the volume control in the record player should only be used for further control of volume. The quality of reproduction will generally be better when the volume control in the record player is not fully advanced.

## FACSIMILE RECEIVERS

On Crosley pages 10-41 to 10-44 of Rider's Manual Volume X there are included service notes on the Crosley Models 118, 119 facsimile receivers. Although these service notes are complete in themselves, they assume that the reader understands the theory and operation of the vasic system. For this reason the following description of facsimile as used in the Crosley-Finch system will be of interest.

As the name implies, facsimile transmission is the transmission of an exact copy of original material which may be composed of black and white characters of various shades of gray. This, of course, includes all printed material, line drawings, sketches, or photographs.

It is, therefore, necessary to prepare the copy which you desire to send by facsimile transmission. In the Crosley-Finch system, this represents the printing of copy on a sheet of plain white paper of the same size as is used in the Reado printer. Sketches or drawings are also made directly on this piece of paper, or may be pasted on as half-tone photographs usually are handled. It is essential that all characters of this copy be sharply defined, if best results are to be obtained.

This copy is then fed through the scanning mechanism by means of a paper feed system practically identical to the one used in the Reado Receiver. As the

paper is fed through the machine at the rate of 1/100 of an inch per second, it is scanned from left to right by a small, intensely bright point of light 1/100 of an inch in diameter. This light strikes either the characters which are black or some shade of gray, or the white spaces between the characters, and reflects back off the copy on the plate of a photoelectric cell. Optical lenses are used to obtain the small point of light from the 50 candle power 6 volt automobile headlamp, and a lens is also used to gather the reflected light from the copy and focus it on the plate of the photoelectric cell. The photoelectric cell emits electrons when light falls upon its plate, and these electrons form a small current which, as it flows through a very high value resistor, produces a voltage which regulates the amount of signal from a 2000-cycle oscillator that will pass through the 1851 modulator tube. When the tiny point of light falls on black characters, most of the light is absorbed and very little is reflected; but when the light falls on white paper, most of the light is reflected, and in this way the photoelectric cell may differentiate between black and white. Shades of gray reflect light according to their degree of whiteness, and so they are also detected by the photoelectric cell. We, therefore, have obtained from the black and white characters on the paper small pulses of electrical waves

(2000 cycles) which are proportional in intensity to the blackness of the characters and proportional in time duration to the length of the particular black character scanned by the small spot of light on its journey from left to right on its narrow path of  $1/100''$  across the paper.

### Synchronizing

Since even such small type as 6 or 8 point is from .040 to .060" in height, it is readily apparent that the small light spot from the scanner will have to make from four to six journeys from left to right to complete one line of type. In a like manner in the Reado printer the small stylus which travels from left to right across the recording paper is only  $1/100''$  in diameter, and therefore must make the same number of journeys from left to right to print the same line of type. It is apparent, therefore, that both the spot of light and the recording stylus must move across the paper in perfect synchronism, if the characters are to be built up as they appear in the original copy.

Various systems of synchronism have been used in facsimile. One of the simplest systems makes use of the fact that two synchronous motors running on the same power line will run exactly at the same speed, and therefore if both are started at the same instant, will remain together. However, if the scanner and printer are on separate power lines, serious distortion occurs since one or the other may be going faster or slower. In the Reado system, the printer is geared to run 2% faster than the scanner. It will, therefore, complete one journey from left to right and back from right to left in a shorter time than will the scanner. The stylus arm is then held over at the left side of the copy by slipping a clutch between the motor and the stylus arm. This clutch is released by a small pulse of 500 cycles which is set up by the scanner just before

it starts on the journey from left to right across the copy, thereby insuring that both the small spot of light and the stylus needle start on their journey in perfect synchronism. It is perfectly true since the recording stylus travels 2% faster than the small spot of light, it will arrive at the right side of the copy sooner than the spot of light, but this difference in speed is constant and so slight that no distortion is noticed.

This, of course, means that the Reado printer will receive perfect transmission regardless of its power source and makes possible the transmission of facsimile from a phonograph record, as the records have not only the small electrical impulses represented by the black and white characters but also the small pulse of 500 cycles which releases the clutch in the receiver impressed upon them.

The simplicity of the Crosley Reado printer is due primarily to the ability of the Reado paper to turn black or some shade of gray as the small current emanating from the stylus point passes through this paper. This does away with expensive types of ink, chemically treated paper which must be used in a slightly moist condition, or carbon paper pressure recording systems. This white-coated electro-sensitive paper is a development of the Crosley laboratories. It is capable of reproducing some five or six shades of half-tone as well as sharp definite characters which, of course, is necessary in handling small type size.

The paper feeds through the machine at the rate of  $1/100$  inch per second, which means that three feet of copy should be received during an hour broadcast from stations using the Finch system of facsimile.

Two small coils are mounted on the left side of the printer which actuate the small pawl to release the clutch, which makes possible the synchronization of the printer and scanner at the beginning of each stroke.

## SERVICING BY SIGNAL TRACING

This business of radio servicing has been in existence now for a good many years and the one subject that is of primary importance to every man actively connected with it is how a defective receiver should be tested or inspected in order that the fault may be found accurately, quickly, and easily, because unless the test be conducted so that these conditions are met, the chances are good that the serviceman will not show a reasonable profit on any one particular job.

Ream after ream of paper has been covered describing all manner of test procedures—some good—some fair—and others decidedly not so good. There have been advocates of one system or another and they

apparently find one suited to their needs for they have built up a successful business. Yet when each and every one of these systems of testing be analyzed—taken apart to see upon what it is based, it will be found that there are almost as many bases as there are systems. Now to our way of thinking—and we feel sure that you will agree with our premise—there is just one way to test any machine or system—no matter what its variations may be—and that is to decide what is the essential factor that is responsible for the functioning of the system; then when that has been determined, to investigate its behavior as it progresses through the system and performs useful

work. All too often this thought of the power itself is sidetracked and because of some reason, a multitude of minor procedures come into practice that check the *parts* of the system but not the fundamental or driving force itself.

For example, when a steam generating plant is tested, upon what are the observations made? The live steam itself—the moving force that performs work. If you were to look in at such a test, you would find the engineers reading gauges and thermometers, watching flow meters—inspecting the condition of the steam as it progresses through the system . . . watching the force itself, as it were. True, you would find men taking the temperature of the fire with a pyrometer—checks being made on the gases going up the flue with a CO<sub>2</sub> analyzer—records made of the amounts of the coal and water being consumed—but these are only to calculate the overall efficiency of the installation—it is the steam itself that is the important factor.

Now apply this same line of reasoning to the testing of a radio receiver—*any* receiver, mind you—old or new or yet to be designed—a-c or d-c operated—trf or superhet. . . . Just what is the one essential factor upon which the functioning of every radio receiver ever built or ever to be built, is based? What is this common denominator of all receiving systems—the fundamental—the elemental? It is the signal itself.

What is it that is superimposed upon the carrier wave? The signal. What is it that every condenser, resistor, transformer, tube or any other part in a receiver works on? The signal. When you are called into a customer's home, you are wanted because the receiver is not functioning as it should and the *signal* has been affected in some way or other. Perhaps it has become distorted—perhaps hum is superimposed upon it—maybe there is a reduction in the sensitivity or a loss of control or maybe no signal at all. . . . Any way you approach it, the signal, and the signal alone, is the all-important factor. And this is what you as a serviceman must restore to its normal state. . . . No matter *how* you do it, it is your job to fix the trouble as easily and as quickly as you can.

### Diagnosis All-Important

But before the signal can be brought back to normality, the condition or conditions causing the trouble—and they may be external as well as in the set itself, although the chances are that they will be the latter—must be discovered. And that brings us back to our starting point: the testing of the receiver—the diagnosis of the condition that is affecting the signal. You know as well as we do that it is the

ability of a serviceman to diagnose trouble that makes him valuable to his business. . . . The locating of the fault is 90% of the whole job of bringing back the signal and if the time to do this great percentage can be reduced, even a few minutes, then that will automatically make for increased profits.

And that is what we have been striving to do and it is our belief that we have found a way that you can localize the faulty condition in a receiver more quickly and more efficiently than it has been possible to do heretofore.

First of all, if one method of finding out what is causing the signal's abnormality could be equally well applied to *any* type of receiver, matters would be simplified enormously. Furthermore, if this method could be applied to any *new* receiver as well as those now on the market, then it would be unnecessary to clutter up your mind with a thousand and one details. Now taking the premise that in every radio receiver essentially the identical things happen to the signal, a good start towards universality has been made.

In general terms the signal in every receiver is detected, amplified at audio frequencies, and then the electrical energy is delivered to the actuating mechanism of a loud speaker. If the signal be amplified at radio frequencies before detection that still does not spoil the picture . . . it is just an additional step—just as the introduction of avc or afc would be. . . . Also if a locally generated current be mixed with the signal before it is detected that is just one more step that does not detract from the main idea. Think in generalities and you will find nothing complicated. If you will look into the future a bit, you will see that unless the whole system of broadcasting be entirely changed—and there is little chance of that coming to pass—receivers of the future will have exactly the same features as those of today . . . perhaps a few refinements and embellishments, but nothing to affect the main idea. It is just like the automobile industry: new models are introduced annually with knee action, improved brakes, balloon tires and what have you, but still the same old fundamentals are there—you have a motor in which the expanding gases push a piston down and that mechanical energy makes the rear wheels revolve.

### Signal Tracing

Granting that all receivers are alike fundamentally in their action on the signal, some way had to be found whereby the signal could be inspected from the instant it enters the receiver at the antenna until it arrives at the output. Moreover if some practical way of doing this existed, it would make possible the locating of the point at which the signal departed from

normal . . . where it became distorted . . . where it weakened or where something else happened to it. Yet no matter how desirable such a procedure might prove to be, with the equipment available to the serviceman such a method was out of the question. Therefore, in order to employ this signal-checking procedure, which we consider to be universally practical, it was first necessary to develop some apparatus that would give the information required under actual operating conditions and without influencing the signal in its passage through the receiver. Moreover, theoretical analysis of the problem showed that if such apparatus could be developed, it would not only localize the fault in some particular circuit, but it would also go a long way in tracking down the part that caused the signal to depart from its normal condition.

#### Accessibility of Parts

We then turned our attention to the physical side of the receivers themselves. Granting the signal-tracing system of testing to be the best, would it be possible to get at the different points in the sets where connections would have to be made and what effect would such connections have not only on the readings but on the operation of the receiver? Schematics of all kinds were examined as well as the chassis of a large number of existing receivers. . . . Design engineers were consulted concerning the electrical and physical trends in the sets to come; what would be the result if the ideas of today were incorporated in the sets of tomorrow? All our findings were encouraging; the further we went, the firmer were our convictions that we were on the right track. As far as we were able to discover the parts in the new receivers were to be as accessible as possible in order to assure simple and economical maintenance. And it goes without saying that if the parts are easily reached, then the paths along which the signal flows will also be accessible. Furthermore, as our method offered no interference with the receiver's operation, the complex interlocked circuits would not offer any problem in respect to its application.

The problem was also considered from the point of view of the servicemen's technical capabilities in relation to the new design of receivers. It was clear that a new attack—a new method of approach was in order so that the trouble in a receiver could be diagnosed systematically, efficiently, and quickly. As our readers will admit, although receiver design has advanced with gigantic strides in the last few years, the serviceman's methods of trouble localization might well be described as belonging to the Stone Age. It has been conceded that some new method must be devised if the service industry is going to survive by mastering the

problems presented by the new receivers. We wish that you would think back over the last few months' work and remember the number of conditions that you were unable to check in late receivers or the number of things you had to assume—mainly because it was impossible for one reason or another to check them.

#### Three Essentials

With all these facts marshalled before us, we arrived at the conclusion that this signal-tracing method of testing required three major items in order to be effective; it must have universal application, positive identification, and speedy operation. In no one of the methods in use up to the present time are these three factors incorporated and you can readily see that they are necessary for rapid and accurate work. Although the signal is really the basis of the system, yet its tracing through the receiver is the primary, but not the only test. It is supplemented by a voltage test which although secondary, plays an important part. The primary test locates the trouble in some certain portion of the receiver—sometimes the exact defective part. The supplementary test identifies the defective part in many cases—but in every case furnishes the required information.

Now what must we be able to do in finding the portion of the receiver that is not functioning correctly and locating the faulty component? First we must be able to trace the passage of a signal entering the receiver through the antenna post throughout the various signal-current-carrying circuits, no matter if it be at radio frequency, intermediate frequency or audio frequency. Then the signal must be traced throughout the receiver without altering the constants of the circuits and as a consequence, impairing the operation of the receiver and so nullifying the observations. Simultaneously, the operation of the receiver oscillator also is checked. The voltage tests must be of such a kind that they will take care of the operating voltages and also the control voltages that are developed by the signal. These voltage measurements can be made simultaneously with the observation of the signal and at points common to both the signal and the voltage. The measurement of the d-c voltages must be made with reasonable accuracy with respect to the true voltage present at the point under test without changing the constants of the circuit.

It is our belief that you will agree that the different points outlined above would go far towards helping servicemen over many difficult spots, if it were possible to perform the signal-tracing tests and make the various voltage measurements. And all this is possible.

## AUTHOR'S FOREWORD

Volume X is a continuation of the "Perpetual Trouble Shooter's Manual" series. In addition to this Volumes I, II, III, IV, V, VI, VII, VIII and IX have been published.

Inasmuch as owners of preceding volumes are familiar with the Manual and with the nature of its contents, an elaborate description is not required. However, it might be well to state that the information presented in Volume X is condensed as much as possible in accordance with the requests of owners of previous volumes of this publication. You will find that in many cases facts associated with a number of the receivers contained under any one manufacturer's heading have been grouped upon a single page, and references are made to this page in the description of the various models which employ a component, utilize the adjustment, and in general make use of the facts given upon this company's reference page. By arranging the contents in this manner we avoid duplication and make space available for the inclusion of a greater number of schematics. Examples of the foregoing are push-button tuning adjustments, dial cable adjustments, etc.

In a number of instances references are made to "conventional alignment." This term is used in conjunction with simple receivers which do not require elaborate alignment instructions. Such conventional alignment was described in the "How It Works" section of Volume VIII, and we feel that so many men are familiar with simple alignment that it would be a waste of space to include such alignment in conjunction with each of the receivers contained in the Manual.

We feel that reference to a given source of such information makes available additional space so badly needed for the inclusion of the large number of receiver models being manufactured. An example of the successful application of such space conservation is the fact that Volume X contains approximately 2600 models in its 1650 pages; whereas the number of models which hitherto have been incorporated in a Manual with an equivalent number of pages was roughly 1900.

We take this opportunity to request comments and criticism concerning the contents and make-up of Volume X.

JOHN F. RIDER.

## HOW TO USE THIS INDEX

This index covers all Rider's Manuals issued thus far. The three columns of pages are used to identify the pages employed in the various series of manuals published up to the present time. The column headed "Revised Pages" covers the ten individual Volumes I, II, III, IV, V, VI, VII, VIII, IX, and X which were arranged with a new type of folio. With respect to earlier editions of Rider's Manuals, the revised folios appear only in Volumes I and II.

Hence any material which appears in Volumes I or II is shown in the columns marked "Revised" and also "Early," establishing the correct page in either of these issues of manuals. Thus if you own the early editions of Volumes I and II and the regular editions of Volumes III, IV, V, VI, VII, VIII, IX, and X you will refer to the "Early" column for material in Volumes I and II and to the "Revised" column for material in subsequent volumes. This work is simplified by the fact that the "Early" column has its equivalent in the "Revised" column only for the material which has been shown in Volumes I and II.

Referring to the folios listed in the "Revised" column and covering all manuals, the number 1, before the page number, establishes the data as being in Volume I. The numeral 2 before the page number establishes the material as being in Volume II. The numeral 3 before the page number establishes the material as being in Volume III and the numeral 4 before the page number establishes the material as being in Volume IV, etc.

Concerning the pages listed in the "Early" column, all page numbers preceded by an asterisk (\*) are in Volume I. All numbers which do not have an asterisk are in Volume II. The word "Front" shown in the "Early" column establishes that the material was shown in the front end of Volume II.

An example of the use of this index is as follows:

Electrical Research Laboratories, Inc.

Model	Revised Pages	Early Pages	Radiotron Complete Pages
75, 77 (231)	2-6	252-I	870
81, 82 (245)	1-5	*252-C	871
81-P, 82-P, 30 (248)	3-2		872

The receiver model 75, 77 (231) is on page Erla 2-6 in the revised Volume II; on page 252-I of the early Volume II and on page 870 of the Radiotron Complete Manual. The receiver model 81, 82 (245) is on page Erla 1-5 in the revised Volume I; on page 252-C in the early Volume I and on page 871 in the Complete Manual. The model 81-P, 82-P, 30 (248) is on page Erla 3-2 in Volume III and on page 872 of the Complete Manual.

Volumes III, IV, V, VI, VII, VIII, IX, and X pages require no comment, since their identity is established by the numerals 3, 4, 5, 6, 7, 8, 9, or 10 which precede the page number.

When seeking any page, remember that the manufacturers' names are arranged alphabetically and that the trade names are shown in connection with the folios. Sometimes more than one model using the same chassis is listed upon the same line. Where a chassis is used in more than one model, the extra model numbers appear in their numerical order, referring back to the lowest model number. Chassis numbers are also listed numerically and cross indexed to the lowest model number.

# INDEX

MODEL	ABC RADIO LABORATORIES	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON PAGE
100	Schematic ..... Misc. 7-1			
<b>THE A-C DAYTON CO.</b>				
Navigator	Schematic, socket, voltage..... 1-8	*7		8
XL-5	Schematic ..... 1-1	*1		1
XL-10	Schematic ..... 1-3	*2-A		3
XL-20	Schematic ..... 1-1	*1		1
XL-25	Schematic ..... 1-1	*1		1
XL-30	Schematic ..... 1-4	*3		4
XL-40	Schematic, socket ..... 1-2	*2		2
XL-50	Schematic ..... 1-2	*3		3
XL-60	Schematic, socket ..... 1-4	*3		4
XL-61 Battery	Schematic, socket, voltage..... 1-5	*4		5
AC-83	Schematic, socket, voltage..... 1-6	*5		6
AC-85	Schematic, socket, voltage..... 1-7	*6		7
AC-86	Schematic ..... 1-3	*2-A		3
XL-70				
<b>ACME</b>				
See RADIO CIRCULAR CO.				
<b>ACME APPARATUS CO.</b>				
"B" Eliminator	Schematic ..... 1-1	*727		9
5-tube Reflex	Schematic ..... 1-1	*8		9
<b>ACME ELECTRIC &amp; MFG. CO.</b>				
Moto Midjet	Schematic ..... 4-1			
AC-7	Schematic, socket ..... 1-1	*9		13
E-60 (Power Pack)	Schematic, wiring diagram ..... 3-1			15
SG-88	Schematic, socket ..... 1-1	*9		13
AC-98	Schematic, values, voltage..... 3-2			14
<b>ACRATEST PRODUCTS CO., INC.</b>				
Also see FEDERATED PURCHASER				
37	Schematic, impedance ..... 6-1			
38	Schematic, impedances ..... 6-2			
47	Schematic, notes ..... 7-3			
55	Schematic, layout ..... 7-3			
108	Schematic, notes ..... 5-1			
120	Schematic ..... 6-4			
126	Schematic, voltage, alignment ..... 7-1			
194	Schematic, impedance ..... 6-1			
196, 197	Schematic, impedance ..... 6-1			
198, 199	Schematic, impedance ..... 6-2			
200	Schematic, notes ..... 7-2			
202	Schematic, notes ..... 7-2			
247	Schematic, notes ..... 5-4			
418	Schematic, socket ..... 6-3			
738	Schematic ..... 5-4			
759	Schematic ..... 5-4			
770	Schematic ..... 6-4			
1416	Schematic, voltage ..... 8-1			
1800	Schematic, voltage ..... 8-1			
1820	Schematic, voltage ..... 8-2			
1850	Schematic, voltage ..... 8-2			
1900	Schematic ..... 7-4			
<b>ACRATONE</b>				
See FEDERATED PURCHASER				
<b>ADMIRAL</b>				
See CONTINENTAL RADIO & TELEVISION CO.				
61	Schematic ..... Misc. 5-1			
<b>ADVANCE ELECTRIC CO.</b>				
Falck Superhet "B"	Schematic ..... 2-1			10-A
Falck 77, 88, 89	Schematic ..... 2-1			10-A
	Schematic ..... 2-2			10-B
<b>AERO PRODUCTS, INC.</b>				
See CHARLES HOODWIN				
<b>AEVNA</b>				
Also see WALGREEN				
252	Schematic, socket, voltage Misc. 6-1			
<b>AIR-CASTLE</b>				
Also see RADIO PRODUCTS CORP.				
Also see SPIEGEL, INC.				
A31	Schematic ..... Misc. 5-2			
<b>AIR CHIEF</b>				
See FIRESTONE TIRE & RUBBER CO.				
<b>AIR KING PRODUCTS CORP.</b>				
Armor	See model 211			
Atlas 5-Tube Universal	Schematic ..... 5-3			
All-Wave				
Autocrat	See model 221			
Castlet	See model 76			
Comet	See model 4-tube Comet			
Council	See model 221			
Dynamic 2-Range	Schematic ..... 7-4			
Elli	See model 76			
King	See model 213			
King	Schematic, notes ..... 7-1			
Knave	See model 211			
Magnetic	See model 18			
Palace	See model 227			
Pirate	See model 227			
Premier	See model 227			
Prince	See model 209			
Queen	See model 76			
Regent	See model 221			
Royalty	Schematic, notes ..... 7-2			
Star	See model 211			
5-Tube Comet	Schematic ..... 5-1			
5-Tube Atlas Universal	Schematic ..... 5-2			
All-Wave				
6-Tube TRF L-W.	Schematic ..... 5-3			
7-Tube BC Super	Schematic ..... 5-1			
7-Tube TRF L-W.	Schematic, data ..... 5-4			
9E	Schematic ..... 9-1			
10F	Schematic ..... 9-3			
11F	Schematic, alignment ..... 7-4			
21, 22, 41, 42 Magnetic	Schematic, alignment ..... 8-1			
21, 22, 522, 81 Series	Schematic, layout, data ..... 8-2			

**AIR KING**  
**ALL-AMERICAN**

AIR KING PRODUCTS CORP.—(Cont.)			REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
MODEL				
27, 28A	Schematic		7-8	
37, 39	Schematic		Misc. 4-1	
40	Schematic		6-1	
41, 42	See model 10		7-8	
47, 48, 57, 58	Schematic		6-1	
50	Schematic		4-1	
52-54	See model 47		6-2	
57, 58	Schematic		6-2	
70	Schematic		8-3	
72, 73	Schematic, alignment		9-2	
76, 501 Queen, 503 Earl, 505 Castle				
81	See model 21		7-6	
209, Prince	Schematic, notes		7-7	
211, 224, 225	Schematic, notes		7-7	
Lancer, Spear, Armor				
213, King	Schematic, notes		7-3	
214	Schematic, socket		8-8	
221, 222, 223	Schematic, notes		7-9	
Regent, Autocrat, Council				
222	Schematic, socket		9-4	
224, 225	See model 211			
227, 228, 229	Schematic		7-5	
Piermer, Palace, Pirate				
250	Schematic		8-4	
250-B	Schematic		9-4	
252	Schematic, socket		9-3	
257	Schematic, voltage, socket, trimmers, alignment		10-1	
260	Schematic		10-2	
261	Schematic, alignment		8-4	
501, 503, 505	See model 76		8-5	
592	See model 21			
600	Schematic		7-10	
688, 886	Schematic		9-5	
699	Schematic		9-5	
700	Schematic, socket		8-6	
700 LW	Schematic		9-6	
701, 702, 703	Schematic		9-7	
704	Schematic		9-6	
705	Schematic, socket		8-6	
710, 715	Schematic, socket		8-7	
720, 721, 770, 771, 870, 871	Schematic, alignment		9-3	
795	Schematic		9-7	
730, 731, 850 (Early)	Schematic, alignment		8-5	
777	Schematic		9-9	
X-780B	Schematic		9-10	
801	Schematic		9-10	
810	Schematic, alignment		9-11	
815	Schematic		9-12	
825	Schematic, alignment		9-13	
828, 833	Schematic, alignment		9-13	
835, 834	Schematic, alignment		9-13	
X-825	Schematic, alignment		9-8	
X-826, 838	Schematic, alignment		9-11	
X-837S	Schematic, alignment		9-15, 16	
850 (Late)	Schematic, alignment		9-15, 16	
870, 871	Schematic		9-14	
886	See model 720			
908	See model 688			
909	Schematic, socket		9-17	
910 Early	Schematic, socket		9-17	
911	Schematic		9-9	
912	Schematic, socket, notes		9-14	
	Schematic, socket, trimmers, alignment, tuner data		10-1	
1000, 2000	Schematic, socket		8-7	
1001, 2001, Early, Late	Schematic, socket		8-3	
1001B, 2001B	Schematic, socket		9-12	
3905	Schematic, socket		9-12	
	Schematic, voltage, alignment socket		10-2	
3910	Schematic, socket		10-3	
X-8312	Schematic, alignment		9-18	
				AIRLINE
				See MONTGOMERY WARD

**AIRLINE**  
**See MONTGOMERY WARD**



ALL AMERICAN MOHAWK CORP.—(Cont.)			ALLIED RADIO CORP.—(Cont.)		
MODEL	REVISION	PAGE	MODEL	REVISION	PAGE
Mohawk 226, 7-contact SPU	Schematic, cable connections.....	3-4	G-9551	Schematic, voltage, alignment, notes.....	6-3
Mohawk 226, 12-contact SPU	Schematic, color code.....	3-6	G-9553	Schematic, voltage.....	6-7
606 Battery	Schematic, socket, data.....	3-18	F-9555	Schematic, voltage, alignment, notes.....	6-8
			G-9557	Schematic, voltage.....	6-7
			G-9561	Schematic, voltage.....	6-8
			G-9563	Schematic, voltage.....	6-8
			G-9565	Schematic, voltage.....	6-8
			G-9955	Schematic, voltage.....	6-8

ALLIED RADIO CORP.

5-tube Dual Wave AC	Schematic.....	4-1
5-tube Dual Wave Batt.	Schematic.....	4-1
6-tube Auto Set	Schematic, parts list.....	3-18
6-tube Dual Wave	Schematic.....	3-10
7-tube Superhet '32	Chassis, voltage, parts.....	3-11
	Schematic, voltage.....	3-15
	Alignment data, notes, color code.....	3-16
8-tube All-Wave Battery '32-'33 (12-tube Super, Class B)	Schematic.....	3-17
	Schematic.....	3-14
A1 Chassis	See model A9857	
B1 Chassis	See model A9775	
B2 Chassis	See model A9851	
Z3 Chassis	See model A9870	
AM4 Chassis	See model A9891	
M5 Chassis	See model A9861	
5X Chassis	See model A10505	
5Z Chassis	See model A10500	
Z5 Chassis	See model A9776	
AC-5 Chassis	Schematic, socket.....	3-2
AC-5 Chassis	Schematic, socket.....	3-3
A-5-30 SG, Roamer Auto Set	See model A9780	
P6 Chassis	See model A10508	
GP Chassis	See model A9800	
U6 Chassis	See model A9806	
6V Chassis	See model A10502	
R-5-30 Battery	Schematic, socket.....	3-3
W7 Chassis	See model A9788	
W7 Chassis	See model A10522	
M Chassis	See model A9784	
B3 Chassis	See model A10510	
8K Chassis	See model A10515	
8T Chassis	See model A9785	
AM8 Chassis	Schematic.....	3-4
SG-8	Chassis, wiring, voltage.....	3-5
	Schematic, socket.....	3-1
	Schematic.....	3-6
	Schematic.....	3-7
8-9 AC	See model A9752	
SG-9, 1930 (AC 9-30)	See model A9880	
46A Chassis	See model A9760	
47AE Chassis	See model A9833	
60B Chassis	See model A9848	
66B, 66BE Chassis	See model A9848	
68 Chassis	See model A9768	
68E, 68BE Chassis	See model A9740	
69U Chassis	See model A9741	
72A Chassis	See model A9757	
76A Chassis	Schematic.....	7-1
80 AC	See model A9820	
B102 Chassis	Schematic, socket.....	3-8
118 AVC Super	Chassis, voltage, alignment data.....	3-9
266, 268 Chassis	See model A9848	
F-9501	Schematic, alignment.....	5-1
G-9503	Schematic, alignment.....	5-2
F-9505	Schematic, alignment.....	5-2
G-9505	Schematic, alignment.....	5-2
F-9511	Schematic, alignment.....	5-2
G-9511-13	Schematic, alignment.....	5-3
F-9515	Schematic, alignment.....	5-3
G-9515	Schematic, alignment.....	5-3
F-9517, G-9582	Schematic, alignment.....	5-3
G-9521	Schematic, alignment.....	5-4
F-9525, F-9527	Schematic, alignment.....	5-4
G-9527	Schematic, alignment.....	5-5
F-9531, F-9591	Schematic, alignment.....	5-5
G-9533	Schematic, alignment.....	5-5
F-9541	Schematic, alignment.....	5-6
G-9545, G-9547, G-9549	Schematic, voltage.....	5-6
F-9551	Schematic.....	5-7

# ALLIED ANDREA

MODEL	ALLIED RADIO CORP.-(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIO TRON
A9788, A9789, A9852, A9854 Chassis AM7	Schematic, socket, trimmers.....9-19		*697	108
A9802	Alignment, parts .....9-20		*697	108
A9805	Schematic .....8-8			
A9807	Schematic .....8-4			
A9809	Schematic .....10-4			
A9811	Schematic .....10-4			
A9813	See model A9724			
A9820, Chassis B102	Schematic .....10-5			
A9825	See model A9740			
A9826, A9828	See model A9760			
A9830, A9831 Chassis 47AE	Schematic, voltage trimmers .....9-21, 22			
E-9830 (8-tube Super)	Alignment, parts .....9-25			
F-9831 (10-tube Super)	Schematic .....3-12			
A9833, A9834, A9835, A9836, A9837, A9838 Chassis 66B, 66BE	Schematic, trimmers, voltage, coils .....9-23, 24			
A9848, A9849, Chassis 68	Socket, trimmers, layout .....9-27			
A9848, A9849 Chassis 266	Alignment, parts .....9-28			
A9848, A9849 Chassis 268	Schematic .....9-29			
A9848, A9849, Chassis 266, 268	Socket, voltage, trimmers .....9-31			
A9851, Chassis B2	Alignment .....9-32			
A9852, A9854	Schematic, socket, trimmers, alignment .....10-6			
A9855, A9856	See model A9788			
A9857, A9857E, Chassis A1	Schematic, socket, trimmers, alignment .....10-7			
A9860	See model A9775			
A9861, A9862, A9863, A9864, A9865, A9866, Chassis M5	Schematic, socket, trimmers, alignment .....10-8			
A9870, Chassis Z3	Schematic, socket, trimmers, alignment .....8-9			
A9880, Chassis U6	Schematic, socket, trimmers, alignment .....8-10			
G-9881	See model G-9516			
G-9882	See model G-9517			
A9891, Chassis AM4	Schematic, socket, trimmers, alignment .....10-9			
A10500, A10501 Chassis 5Z	Schematic, socket, trimmers, alignment .....10-10			
A10502, A10503, Chassis 6Y	Schematic, socket, trimmers, alignment .....8-11			
A10505, Chassis 5X	Schematic, socket, trimmers, alignment .....8-12			
A10506, Chassis 6W	Schematic, socket, trimmers, alignment .....8-12			
A10507, Chassis 7M	Schematic, socket, trimmers, alignment .....8-13			
A10508, Chassis 6P	Schematic, socket, trimmers, alignment .....8-14			
A10510, A10511, A10512, A10513, Chassis 8K	Schematic .....10-11			
A10515, A10516, A10517, A10518, Chassis 8T	Alignment, socket, trimmers, tuner .....10-12			
	Schematic .....10-11			
	Alignment, socket, trimmers, tuner .....10-12			

## AMERICAN FOUNDATION FOR BLIND

U	Schematic .....7-1
X	Chassis wiring .....7-2
	Schematic .....7-1
80	Chassis wiring .....7-2
	Schematic .....7-1
	Chassis wiring .....7-2

## AMRAD CORPORATION

Also see CROSLEY

Inductrol	Schematic .....1-4	*54	108
AC-5 and Power Pack	Schematic .....1-4	*58	108
AC-6, AC-6C	Schematic, socket .....1-6	*60	110
DC-6, DC-6C	Schematic, socket .....1-6	*58	110
AC-7, AC-7C	Schematic, socket .....1-8	*59	107
DC-7, DC-7C	Schematic, socket, voltage .....1-8	*61	112
70	Schematic, socket, voltage .....1-8	*60	108
80, 82, 83	Schematic, socket, data, voltage 3-1		113
81 Bel-Canto	Condenser data .....3-2		114
84	Schematic, socket .....1-5		109
171 ABC Power Pack	Schematic .....1-2	*56	106
F-516	Schematic, parts .....7-1		
	Socket, trimmers, voltage, alignment .....7-2		
S-522	Schematic .....1-1	*55	105
F-546	Schematic, parts .....7-3		
	Socket, trimmers, voltage, alignment .....7-4		
F-616	Schematic, parts .....7-5		
	Socket, trimmers, voltage, alignment .....7-6		
F-626	Schematic, parts .....7-7		
	Socket, trimmers, voltage, alignment .....7-8		
S-738	Schematic, socket .....1-5	*54	109
3500-1, Tuner #3475, Amplifier #2634	Schematic .....1-1	*55	105
3500-2, Tuner #5780, Amplifier #2634	Schematic .....1-1		
3590	Schematic .....1-5	*54	109
7100	Schematic .....1-7	*57	111
7191	Schematic .....1-7		

## ANDREA RADIO CORP.

MI Chassis	See model OA5
PUE-1 Chassis	See model 1531
PUE-3 Chassis	See model 1530
1A5, 3A5, Chassis A5L	Schematic, coils .....8-1
1A7, 3A7, Chassis A7L	Schematic, coils .....8-2
1B6, 3B6, Chassis B6L	Schematic, trimmers, coils, alignment .....8-3, 8-4
1B8, 2B8, Chassis B8L, B8S	Schematic, trimmers, alignment, parts .....9-3
1C5, 2C5; 510, 511 (AO Models) Chassis C5L, C5S, UC6L, UC6S	Schematic, coils, parts .....9-1
1D7, 3D7, 5D7, 7D7, Chassis D7L	Alignment, trimmers, notes .....9-2
1D8, 3D8, 5D8, 7D8, Chassis D8L, 2D8, 4D8, 6D8, 8D8, Chassis D8S	Schematic, trimmers, coils, alignment .....8-5
1D10, 3D10, 5D10, 7D10, 9D10, Chassis D10L	Notes, alignment .....8-6
1E6, 2E6, Chassis PE6L	Schematic, trimmers, alignment, coils, parts .....9-4
1E6, 2E6, Chassis PE6S	Schematic, trimmers, coils, parts .....9-5
1E8, 3E8, 5E8, 7E8, 9E8, Chassis PE8L, 2E8, 4E8, 6E8, 8E8, 10E8, Chassis PE8S	Alignment, tuner .....9-6
1F5 Television	Schematic, coils, parts .....10-1, 2

MODEL	ANDREA RADIO CORP.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE	MODEL	ANDREA RADIO CORP.—(Cont.)	REVISED PAGE
22B8	Service chart	10-3		6E11	See model 3E11	
22B9	Socket, alignment, video block diagram	10-3		6E11	See model 3E11	
22B10	Schematic, coils	10-4		6E11	See model 3E11	
22B11	Schematic, trimmers, coils, alignment	8-3, 8-4		6E11	See model 3E11	
22B12	See model 1B8			6E11	See model 3E11	
22B13	See model 1C5			6E11	See model 3E11	
22B14	Schematic, coils, trimmers, alignment, parts	9-13		6E11	See model 3E11	
22B15	Alignment data	9-16		6E11	See model 3E11	
22B16	Schematic, coils, parts	9-14		6E11	See model 3E11	
22B17	Alignment, trimmers	9-16		6E11	See model 3E11	
22B18	Schematic, trimmers, coils, alignment	8-5		6E11	See model 3E11	
22B19	Notes, alignment	8-6		6E11	See model 3E11	
22B20	See model 1D8			6E11	See model 3E11	
22B21	Schematic, coils, data, trimmers	8-8		6E11	See model 3E11	
22B22	Alignment	8-9		6E11	See model 3E11	
22B23	See model 1E6			6E11	See model 3E11	
22B24	See model 1B8			6E11	See model 3E11	
22B25	See model 1A7			6E11	See model 3E11	
22B26	See model 1B6			6E11	See model 3E11	
22B27	See model 2D5			6E11	See model 3E11	
22B28	See model 1D7			6E11	See model 3E11	
22B29	See model 1B8			6E11	See model 3E11	
22B30	See model 1D8			6E11	See model 3E11	
22B31	See model 1D10			6E11	See model 3E11	
22B32	Schematic, coils, trimmers, alignment, tuner, parts	9-11, 12		6E11	See model 3E11	
22B33	See model 400			6E11	See model 3E11	
22B34	See model 2B6			6E11	See model 3E11	
22B35	See model 2D5			6E11	See model 3E11	
22B36	See model 2D8			6E11	See model 3E11	
22B37	See model 2D9			6E11	See model 3E11	
22B38	See model 2D10			6E11	See model 3E11	
22B39	See model 1E3			6E11	See model 3E11	
22B40	See model 3E11			6E11	See model 3E11	
22B41	See model 410			6E11	See model 3E11	
22B42	See model 411			6E11	See model 3E11	
22B43	See model 1A5			6E11	See model 3E11	
22B44	See model 2A5			6E11	See model 3E11	
22B45	Schematic	8-10		6E11	See model 3E11	
22B46	See model 1C5			6E11	See model 3E11	
22B47	See model 2D5			6E11	See model 3E11	
22B48	See model 1D7			6E11	See model 3E11	
22B49	See model 1D8			6E11	See model 3E11	
22B50	See model 1D10			6E11	See model 3E11	
22B51	Schematic, Phonograph notes	9-8		6E11	See model 3E11	
22B52	See model 1E8			6E11	See model 3E11	
22B53	See model 3E11			6E11	See model 3E11	
22B54	See model 6D5			6E11	See model 3E11	
22B55	See model 62PX			6E11	See model 3E11	
22B56	See model 500			6E11	See model 3E11	
22B57	See model 1C5			6E11	See model 3E11	
22B58	See model 1C5			6E11	See model 3E11	
22B59	See model 511			6E11	See model 3E11	
22B60	See model 510			6E11	See model 3E11	
22B61	See model 521			6E11	See model 3E11	
22B62	See model 520			6E11	See model 3E11	
22B63	See model 62X			6E11	See model 3E11	
22B64	See model 2A5			6E11	See model 3E11	
22B65	See model 1B6			6E11	See model 3	

<b>RADIOTRON</b>	<b>125</b>
<b>COMPLETE</b>	<b>127</b>
<b>PAGE</b>	<b>125</b>
	<b>126</b>
	<b>127</b>

ANDREA RADIO CORP.—(Cont.)				RADIO-TRON	
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
630, 631	Chassis PUE6S Schematic, coils, alignment, parts ..... 9-32 Alignment data ..... 9-7				
634, Chassis, PUE6S	Schematic, phonograph data ..... 9-33				
636, Chassis, PUE6L	Schematic, trimmers, coils, alignment ..... 8-12				
1401, 1403, 1405, 1407, 1409, Chassis UD14L	Schematic, coils, alignment, parts ..... 9-34				
1402, 1404, 1406, 1408, 1410 Chassis UD14S	Schematic, coils, trimmers, data, parts ..... 9-35, 36				
1530, 1534, 1536, 1538, Chassis PUE-S 153L, 1533, 1535, 1537, Chassis PUE-L	Alignment, notes ..... 9-37 Tuner and phonograph data.....9-38				
ANSLEY RADIO LABORATORIES					
DO Electric Set	Schematic ..... 2-1				
B-1, Early, Late	Schematic ..... 7-1				
D-1, Dynaphone, Type 2	Schematic ..... 7-2				
D-1, Dynaphone, Type 2	Schematic ..... 6-1				
D-1, DIA, D16, D20, D26	Schematic ..... 8-1				
MD-1, AC-DC	Schematic, socket, chassis.....2-2				
U-1, AC-DC	Schematic ..... 2-3				
U-2, AC-DC	Schematic ..... 2-4				
D-3, D-4, D-6	Schematic ..... 5-1				
U-3	Schematic ..... 5-2				
U-3	Schematic ..... 5-3				
D-9, D10, D17, D18, U10, U11	Schematic ..... 3-2				
U-10	Schematic, socket ..... 6-2				
U-10, Revised	Schematic, socket ..... 7-4				
D-12, Dynaphone	Schematic ..... 7-2				
D12	Schematic ..... 8-3				
D-16 (Early)	Schematic ..... 7-3				
D20	See Model D1				
D21, D22	Schematic ..... Misc. 9-1				
D24, D25, Chassis 7152	Schematic, trimmers, alignment ..... 8-4				
D26	See Model D1				
7152 Chassis	See model D24				
APEX					
See U. S. RADIO & TELEVISION					
APPEL-HENDERSON					
Silver-King DC Combination	Schematic, notes ..... 2-1				
Silver-King AC Combination	Schematic ..... 2-2				
4-tube AC	Schematic ..... 2-3				
4-tube Portable	Schematic ..... 2-4				
5-tube Battery	Schematic ..... 2-4				
5-tube AO	Schematic ..... 2-3				
ARBORPHONE					
45	Schematic ..... Misc. 3-1				
ARCADIA					
See WELLS-GARDNER					
ARGUS RADIO CORP.					
B-125	Schematic ..... 1-1				
B-195	Schematic ..... 1-1				
	Chassis ..... 1-2				
ARIEL RADIO, INC.					
101	Schematic ..... Misc. 6-2 Chassis Wiring ..... Misc. 7-2				
ARKAY					
See R-K. RADIO LABORATORIES					
ARVIN					
See NOBLITT-SPARKS					
ATOHISON RADIO MFG. CO.					
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
5-AO	Schematic ..... 1-1 Chassis layout ..... 1-3				
5-DO	Schematic ..... 1-1 Schematic, SPU chassis ..... 1-2 Chassis layout ..... 1-3				
6-AO	Schematic ..... 1-1 Chassis layout ..... 1-3				
ATWATER KENT MFG. CO.					
Summers:	D = DC F = 25 cycles Q = Battery operated Z = 32 volts DC E = European long wave range P = Phonograph conn. I = Installation data ..... 7-66 Model specifications ..... 5-34 Model specifications ..... 5-46 Data ..... 5-16 7-6				
Prefixes:	32-Volt DO Sets 1934 Sets 1935 Sets Double Antenna General Notes General Parts List Phonograph pickup Test Circuit Tubular Resistors Tun-O-Matic Chassis D-1, D-2, F, L-1, L-2, P, Q Chassis H-1, H-2 10-B 12 19, #4880 20, #4640 20 #7570 20 #7960 21 #7780 30, 35, 48 30, Early, late 32 33, 49 35 (2 volt aircell) 36, Early, Late, Power Pack 36 Power Pack, Model Y, Serial #260,000 36 Power Pack, Above serial #260,000 36 Early, Below serial #2,610,000 36 Late, Above serial #2,610,000 37 Early, Below serial #1,385,000 37 Late, Above serial #1,385,000 37, 37-F, 37-O 38 40, 42, 52, 56, 57 40, 42, 52 Power Pack 40, 42, 44, 52, Power Pack 40, 42, 52 40, 45 Power Pack (2nd type) 41 DO 41 Power Pack, 3 types 41, 51 42 43 44 Power Pack				
115	(1) 88-A				
116	(1) 88-B				
117	(1) 88-C				
118	(1) 88-D				
119	(1) 89-A				
120	(1) 89				
121	(1) 89-B				
122	(1) 89-C				
123	(1) 89-D				
124	(1) 89-E				
2745					
89					
90					
123					
123					
124					
101					
149					
150					
151					
152					

ATWATER KENT MFG. CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	EARLY COMPLETE	MODEL	REVISION	EARLY COMPLETE
	PAGE	PAGE		PAGE	PAGE
44, 45	3-19	157	80	3-66 & 3-68	212 & 214
44, 45 Power Unit, (2nd type)	3-19	157	80-F	3-68	214
46, 47, 53	104-A	154	81, 81-B, 81-C, Auto Set	3-69	215
46, 58	2-2	155	81, 1st type	3-70	216
47	3-17	155	81, 2nd type	3-66	213
48	3-18	156	81-B, 81-C	3-83	229
49	3-18	156	82, 82-F	3-85	221
50	3-20	158	82	3-76	222
51	3-20	158	82-D	3-66	213
52	3-20	158	82-D, 1st type	3-71	217
53	3-20	158	82-D, 2nd type, Above serial #5,760,801	3-72	218
55, 55-C, Early	3-28	166	82-D, 2nd type, Above serial #2,550,940	3-73	219
55, 55-C, Late	3-28	166	82-Q, 1st type, Below serial #2,550,940	3-74	220
55-F, 55-FC, Early	3-28	166	82-Q, 2nd type, Above serial #2,550,940	3-83	229
55-F, 55-FC, Late	3-28	166	83, 83-F	3-77	223
56, 57	3-27	165	84	3-66	212
56, 60-C	3-27	165	84, 84-F, Early	3-84	230
60, 60-C, Early	3-29	167	84, 84-F, Late	3-85	231
60, 60-C, Late	3-30	168	84, 84-F, Early, late	3-86	232
60, 60-C, 3rd type	3-31	169	84-D	3-81	227
60, 60-C, three types	3-32	170	84-Q, Early, late	3-82	228
61, 61-C, DC, Early	3-33	171	85	3-66	212
61, 61-C, Early	3-33	171	85, 85-F	3-66	212
61, 61-C, Late	3-33	171	85-Q, 1st type, Below serial #163,767	3-88	234
66	3-34	172	85-Q, 2nd type, Above serial #163,767	3-88	234
66, 67-C	3-35	173	86, 1st type	3-94	240
67, 67-C, Battery	3-35	173	86, 86-F, 1st type, Below serial #5,876,861	3-94	240
67, 67-C, Early	3-36	174	86, 86-F, 2nd type	3-96	242
70, 74, 76, Chassis D-1	3-37	175	86, 86-F, 2nd type	3-96	242
70, 74, 76, Chassis D-2	3-38	176	87, 1st type	3-97	243
70, 74, 76, Chassis F	3-39	177	87, 1st type, Below serial #2,525,871	3-98	244
70 Series	3-40	178	87, 1st type, Below serial #2,525,871	3-99	245
70, 74, 76, Chassis L-1	3-41	179	87, 3rd type	3-100	246
70, 74, 76, Chassis L-2	3-42	180	87, 3rd type, Above serial #2,525,871	3-100	246
70, 74, 76, Chassis L-2, P	3-43	181	87-D, DC Superhet	3-101	247
70, 74, 76, Chassis L-2, P	3-44	182	89, 89-F, 89-P, 1st type	3-102	248
70, 74, 76, Chassis L-2, P	3-45	183	89, Below serial #6,755,181	3-103	249
70, 74, 76, Chassis L-2, P	3-46	184	89-F, Below serial #1,585,395	3-104	250
70, 74, 76, Chassis L-2, P	3-47	185	89-P, Below serial #1,935,904	3-105	251
70, 74, 76, Chassis L-2, P	3-48	186	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-49	187	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-50	188	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-51	189	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-52	190	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-53	191	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-54	192	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-55	193	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-56	194	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-57	195	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-58	196	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-59	197	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-60	198	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-61	199	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-62	200	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-63	201	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-64	202	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-65	203	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-66	204	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-67	205	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-68	206	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-69	207	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-70	208	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-71	209	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-72	210	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-73	211	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-74	212	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-75	213	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-76	214	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-77	215	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-78	216	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-79	217	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-80	218	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-81	219	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-82	220	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-83	221	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-84	222	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-85	223	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-86	224	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-87	225	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-88	226	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-89	227	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-90	228	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-91	229	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-92	230	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-93	231	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-94	232	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-95	233	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-96	234	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-97	235	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-98	236	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-99	237	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-100	238	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-101	239	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-102	240	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-103	241	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-104	242	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-105	243	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-106	244	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-107	245	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-108	246	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-109	247	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-110	248	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-111	249	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-112	250	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-113	251	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-114	252	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-115	253	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-116	254	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-117	255	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-118	256	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-119	257	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-120	258	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-121	259	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-122	260	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-123	261	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-124	262	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-125	263	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-126	264	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-127	265	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-128	266	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-129	267	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-130	268	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-131	269	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-132	270	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-133	271	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-134	272	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-135	273	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-136	274	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-137	275	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-138	276	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-139	277	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-140	278	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-141	279	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-142	280	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-143	281	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-144	282	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-145	283	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-146	284	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-147	285	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-148	286	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-149	287	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-150	288	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-151	289	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-152	290	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-153	291	89, Below serial #6,755,181	3-106	252
70, 74, 76, Chassis L-2, P	3-154	292	89-F, Below serial #1,585,395	3-106	252
70, 74, 76, Chassis L-2, P	3-155	293	89-P, Below serial #1,935,904	3-106	252
70, 74, 76, Chassis L-2, P	3-156	294	89, 89-F, 89-P, 1st type	3-106	252
70, 74, 76, Chassis L-2, P	3-157	295			

# ATWATER

ATWATER KENT MFG. CO.—(Cont.)				RADIOTRON	
MODEL	ATWATER KENT MFG. CO.—(Cont.)	REVISI	EARLY COMPLETE	PAGE	PAGE
89, 3rd type	Voltage	3-83 & 3-126	229 & 272	253	
89, 89-F, 89-P, 3rd type	Schematic	3-107	253		
	Chassis layouts, condenser	3-107	253		
	data	3-108	254		
90, 90-F	Voltage	3-83 & 3-126	229 & 272		
90, 90-F, Early, late	Voltage	3-83 & 3-126	255		
	Schematic	3-109	255		
	Chassis layouts, condenser	3-110	256		
	data	3-110	256		
90 Late	Schematic changes	3-111	257		
91, 91-B, 91-C	Schematic, speaker connec-	3-111	258		
	tions	3-111	258		
	Chassis layouts	3-112	259		
	Voltage	3-126	272		
92, Early, late	Schematic	3-113	259		
	Chassis layouts	3-114	260		
92-F	Schematic	3-115	261		
92, 92-F	Chassis layouts	3-116	262		
	Voltage	3-83 & 3-126	229 & 272		
92, 92-F, Late	Bypass condenser data	3-117	263		
93, SW Converter	Schematic	3-118	264		
	Chassis layouts	3-119	265		
94	Voltage	3-83 & 3-126	229 & 272		
94, 94-F	Schematic	3-120	266		
	Chassis layout	3-120	268		
94 Late	Schematic changes	3-121	267		
96, 1st type, Below serial #7,289,885	Schematic	3-122	268		
	Chassis layouts, condenser	3-122	269		
	data	3-122	269		
96, 2nd type, serial num-	Voltage	3-83, 3-126	270		
bers #7,289,885 to #7,291,674	Schematic	3-123	270		
	Chassis layout	3-124	271		
96, 3rd type, Above serial #7,291,674	Schematic	3-125	272		
	Voltage	3-83 & 3-126	229 & 272		
96, 96-F	Schematic	3-127	274		
96-F	Chassis layouts, condenser	3-128	275		
	data	3-128	276		
99, 1st type, Below serial #4,882,380	Schematic	3-129	276		
2nd type, from serial #4,882,380 to #4,884,901	Chassis layout, condenser	3-130	276		
99, 1st type	data	3-130	276		
99, 99-F, 99-P	Schematic	3-131	277		
	Voltage	3-83 & 3-126	229 & 272		
99, 2nd and 3rd types	Chassis layouts	3-131	278		
99, 3rd type	Schematic	3-132	279		
99-F, 99-P	Condenser data	3-133	279		
99-F	Filter circuit schematic	3-133	279		
99-P	Phonograph switching circuit	3-133	279		
112	Alignment	3-133	279		
	Schematic, voltage, notes 6-1, 6-2	3-133	279		
	Trimmer notes	3-133	279		
	Alignment, trimmers, socket	3-133	279		
	Chassis wiring	3-133	279		
	Parts list	3-133	279		
	Schematic	3-133	279		
	Socket, trimmers, chassis, align-	3-133	279		
	ment, parts	3-133	279		
	Installation data	3-133	279		
	Schematic, voltage	3-133	279		
	Trimmers, socket, alignment	3-133	279		
	Chassis layouts	3-133	279		
	Parts list	3-133	279		
	Schematic, socket, trimmers	3-133	279		
	Chassis	3-133	279		
	Parts list	3-133	279		
	Schematic, voltage	3-133	279		
	Socket, trimmer, chassis	3-133	279		
	Alignment	3-133	279		
	Parts list	3-133	279		
126, 136, 416, 446					
136Z, 215Z					
137					
145, 325, Early and late					

ATWATER KENT MFG. CO.—(Cont.)				RADIOTRON	
MODEL	ATWATER KENT MFG. CO.—(Cont.)	REVISI	EARLY COMPLETE	PAGE	PAGE
145, 325, Early and late	Chassis (late), changes	Changes 7-13	229 & 272	253	
E-145, E-145X	Socket, trimmers, chassis, align-	ment	254		
	Schematic	7-10	254		
	Changes	7-11	254		
	Parts list	7-9	254		
155 (1st type) Below serial #7,086,900	Schematic, socket, voltage	3-179	255		
155 (2nd type) Above serial #7,086,900	Schematic, socket, voltage	3-180	256		
155 (3rd type) Above serial #7,088,700	Schematic, socket	4-1	257		
	Parts list	4-3	258		
	Changes	7-2	259		
	Schematic, socket	4-2	260		
	Parts list	4-3	261		
165 (2nd type), 185, 525	Schematic, socket, voltage	5-9	262		
	Socket, trimmer, parts	5-10	263		
165-Q, 525-Q	Schematic, voltage	4-23	263		
	Socket, trimmers, parts	5-1	264		
168	Schematic	7-13	264		
	Parts list	7-9	265		
	Socket, trimmers, chassis	7-14	266		
184, 184-X	Schematic	7-15	267		
	Socket, trimmers, chassis	7-8	268		
185-A	Parts list	7-12	269		
	Schematic, voltage	5-11	270		
	Socket, trimmers, parts	5-12	271		
188, 188-F, (1st type)	Schematic	3-185	272		
	Chassis layout, socket	3-186	273		
188 (2nd type), Above serial #8,074,387	Voltage	3-126 & 3-134	274		
188-F, 2nd type, Above serial #5,693,025	Schematic	3-137	275		
188, 188-F, (2nd types)	Chassis layout, socket	3-138	276		
185-F	Voltage	3-126 & 3-134	277		
200	Schematic	3-137	278		
200, 317, 337	Chassis layout, socket	3-138	279		
206, 376 (1st type)	Voltage	3-126	280		
	Same circuit as Model 317 except that Model 200 has terminals for phono. connection.		281		
206, 376, 559, 825, 944	Parts list	7-12	282		
206D, 376D, Early	Schematic, voltage	5-13	283		
	Socket, trimmers, parts	5-14	284		
	Alignment, trimmers	5-29	285		
	Parts Lists	5-15	286		
	Schematic	7-17	287		
	Socket, trimmers, chassis	7-16	288		
	Parts list	7-12	289		
	Schematic	7-13	290		
	Parts list	7-12	291		
	Parts list	7-12	292		
	See model 135Z		293		
	Parts list	7-12	294		
206D, 376D, Late	Socket, trimmers, chassis, align-	ment	295		
E206, E206X	Schematic	7-22	296		
E208, E248	Schematic, voltage	4-4	297		
E208X, E248X	Socket, trimmers, parts	5-3	298		
P215-Z, P216X, P336, P366X	Changes	7-20	299		
P216, P336	Schematic, voltage	4-5	300		
	Socket, trimmers, parts	5-4	301		
217, 427, 667	Socket, Model 435		302		
	Schematic	3-139	303		
217-D, 427-D, 667-D	Chassis layouts	3-140	304		
225	Schematic	3-141	305		
228, Early, late	Chassis layout, socket	3-142	306		
228-F	Socket, bypass condenser data	3-142	307		
228, 228-F	Schematic	3-143	308		
228-D	Chassis layouts, data	3-144	309		
228-Q	Schematic	3-145	310		
	Chassis layouts, condenser	3-146	311		
236	Schematic	7-23	312		
	Socket, trimmers, chassis	7-24	313		
	Parts list	7-32	314		

ATWATER KENT MFG. CO.—(Cont.)			RADIOTRON		
MODEL	ATWATER KENT MFG. CO.—(Cont.)	REVISED	EARLY COMPLETE	PAGE	
287-Q, 407-Q, Early	Schematic, voltage ..... 6-12	6-12			
	Trimmers, alignment ..... 6-46	6-46			
	Installation notes, dry cell data, speaker adjustments ..... 7-27	7-27			
	Parts list ..... 7-28	7-28			
246	Schematic, voltages across resistors ..... 3-147	3-147			
	Chassis layouts, voltage, con-denser schematic ..... 3-148	3-148			
246, 266 (2nd type)	Schematic, voltage ..... 4-6	4-6			
E248	See Model E208				
255	Schematic ..... 7-25	7-25			
	Parts list ..... 7-32	7-32			
257	Same as model 137 but with a 2A5 instead of a 47				
260, 260-F (1st type), Below serial #8,422,101	Schematic ..... 3-149	3-149			
260, 260-F (2nd type), Above serial #8,422,101	Chassis and socket layouts ..... 3-150	3-150			
	Schematic ..... 3-151	3-151			
	Chassis layout, bypass con-denser data ..... 3-152	3-152			
260, 260-F, (3rd type), Above serial #6,188,242	Schematic ..... 3-153	3-153			
260	Chassis layout, socket ..... 3-154	3-154			
260-F	Voltage ..... 3-126 & 3-134	3-126 & 3-134			
266 (2nd type)	See model 246 2nd type				
273D	Schematic ..... 7-26	7-26			
275 (1st type)	Schematic, voltage parts ..... 4-7	4-7			
275	Socket, trimmers, parts ..... 5-5	5-5			
285-Q, 415-Q	Schematic, voltage ..... 6-13	6-13			
	Trimmers, chassis, alignment ..... 6-14	6-14			
	Parts list ..... 7-23	7-23			
286, 856	Schematic, voltage ..... 6-15	6-15			
	Trimmers, chassis, alignment ..... 6-22	6-22			
	Parts list ..... 6-8	6-8			
305-Z, 565-Z	Trimmers, socket, alignment ..... 6-8	6-8			
	Schematic, voltage, SPU layout ..... 6-9	6-9			
	Chassis layouts ..... 6-10	6-10			
	Parts list ..... 6-11	6-11			
E808	Same as model 318 but with a long wave range instead of police range, and long wave oscillator tracking condenser is 50 MMF.				
310, 510	Schematic, voltage ..... 4-8	4-8			
312, E912	Socket, trimmers, parts ..... 5-6	5-6			
	Schematic ..... 7-29	7-29			
317, 337, Early	Parts list ..... 7-32	7-32			
	Schematic, voltage ..... 6-17	6-17			
	Trimmers, alignment ..... 6-46	6-46			
	Socket, trimmers, chassis ..... 7-31	7-31			
	Parts list ..... 7-12	7-12			
	Changes ..... Changes 7-11				
318	Similar to 447				
325	See model 145				
328, Early	Schematic, voltage ..... 6-18	6-18			
	Trimmers, alignment ..... 6-47	6-47			
	Chassis layout ..... 7-34	7-34			
	Parts list ..... 7-30	7-30			
328 (110v.), 328X (230v.), 2nd Type, above serial #6438750	Schematic ..... 7-33	7-33			
P336, P336X	Chassis layout ..... 7-34	7-34			
337	Parts list				
349	See model P316, P316X				
356	Same as model 649				
376	See model 286				
376D	See model 206				
385-Q, 625-Q	See model 206D				
	Schematic, voltage ..... 6-19	6-19			
	Trimmers, socket, chassis, alignment ..... 6-20	6-20			
	Parts list ..... 6-22	6-22			
387, 427-Q	Schematic, voltage ..... 4-9	4-9			
387, above serial #7,873,966	Schematic, voltage ..... 5-17	5-17			
	Socket, trimmers, parts ..... 5-18	5-18			
ATWATER KENT MFG. CO.—(Cont.)			RADIOTRON		
MODEL	ATWATER KENT MFG. CO.—(Cont.)	REVISED	EARLY COMPLETE	PAGE	
P412, E412, P412X, E412X	Schematic, voltage ..... 7-35	7-35			
	Socket, trimmers, chassis ..... 7-31	7-31			
	Coil data ..... 7-1	7-1			
	Parts list ..... 7-30	7-30			
415-Q	See model 285Q				
416	See model 126				
424, 584	Socket, chassis, parts list ..... 4-10	4-10			
	Schematic, voltage ..... 4-11	4-11			
425, 665	Changes ..... 7-36	7-36			
	Schematic, voltage ..... 4-24	4-24			
427	Socket, trimmers, parts ..... 5-2	5-2			
427-D	See model 217				
427-Q, above serial #1,948,501	See model 217D				
	Schematic, voltage ..... 4-9	4-9			
435, Early	Schematic, voltage ..... 5-17	5-17			
	Socket, trimmers, parts ..... 5-18	5-18			
	Schematic, voltage ..... 6-21	6-21			
	Parts list ..... 7-32	7-32			
435, 2nd Type	Schematic, voltage ..... 7-37	7-37			
	Socket, trimmers, chassis layout ..... 7-38	7-38			
	Parts list ..... 7-32	7-32			
446	See model 126				
447	Alignment, trimmers ..... 5-29	5-29			
	Schematic, voltage ..... 7-39	7-39			
	Chassis layout ..... 7-40	7-40			
448	Parts list ..... 7-30	7-30			
	Schematic, voltage, socket ..... 4-12	4-12			
456	Parts list, chassis ..... 4-13	4-13			
465Q, 655Q	Similar to model 856				
	Schematic, voltage ..... 6-23	6-23			
	Trimmers, socket, chassis ..... 6-24	6-24			
	Speaker data, alignment ..... 6-25	6-25			
	Parts list ..... 6-26	6-26			
467Q	See model 237Q				
469	Voltage ..... 3-126 & 3-134	3-126 & 3-134			
469, 469-F (1st type)	Schematic ..... 3-155	3-155			
	Chassis layout, socket ..... 3-156	3-156			
469, (2nd type), Above serial #8,493,122	Schematic ..... 3-157	3-157			
469-F, (2nd type)	Chassis layout, socket ..... 3-158	3-158			
469, 469-F, (2nd types)	Schematic ..... 3-163	3-163			
469-D, 558-D	Chassis layout, socket ..... 3-164	3-164			
	Voltage ..... 3-134	3-134			
469-D, 469-Q	Voltage ..... 3-126	3-126			
469-F	Schematic ..... 3-165	3-165			
469-Q, 558-Q	Chassis layout, socket ..... 3-166	3-166			
475, 735	Schematic, voltage ..... 6-27	6-27			
	Parts list ..... 6-22	6-22			
	Trimmers, socket, chassis, alignment ..... 6-28	6-28			
480	Schematic ..... 3-159	3-159			
	Chassis layout, socket ..... 3-160	3-160			
	Frequency-range-switch circuit, early ..... 3-161	3-161			
	Frequency-range-switch circuit, simplified schematic ..... 3-162	3-162			
485Q, 515Q	Voltage ..... 3-134	3-134			
	Schematic, voltage ..... 7-41	7-41			
	Socket, trimmers, chassis, alignment ..... 7-42	7-42			
	Parts list ..... 7-28	7-28			
487	Schematic ..... 7-43, 7-44	7-43, 7-44			
	Chassis layout ..... 7-40	7-40			
	Parts list ..... 7-54	7-54			
509	Schematic, socket, trimmers ..... 7-45, 7-46	7-45, 7-46			
	Chassis wiring ..... 7-47	7-47			
510	Parts list				
511, Tun-O-Matic	See model 310				
	Schematic, data ..... 5-19	5-19			
	Data ..... 5-20	5-20			
	Data ..... 5-21	5-21			
511	Schematic, voltage ..... 6-29, 6-30	6-29, 6-30			
	Parts list ..... 6-6	6-6			
	Tune-O-Matic data, socket, chassis ..... 6-31	6-31			

MODEL	ATWATER KENT MFG. CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
5555	Chassis wiring	6-32		
5555	Changes	7-48		
5555	Schematic	6-33		
5555	Trimmers, socket, alignment	6-84		
5555	See model 485Q			
5555	See model 165 2nd type			
5555	See model 165Q			
5555	See model 424			
5555	Schematic, voltage	5-23		
5555	Socket, speaker, trimmers,			
5555	parts	5-24		
5555	Same as model 435 but the short			
5555	wave range goes to 18 MC			
5555	Parts list	7-54		
5555	Schematic, voltage	6-35		
5555	Trimmers, socket, chassis,			
5555	alignment	6-36		
5555	Schematic, voltage, chassis,			
5555	socket	4-14		
5555	Schematic, voltage	4-15		
5555	Schematic, voltage	7-49		
5555	Socket, trimmers, chassis, align-			
5555	ment, parts	7-4		
5555	Installation data	7-5		
5555	Schematic	3-169		
5555	Chassis layout, socket	3-170		
5555	See model 469D			
5555	Voltage	3-134		
5555	See model 469-Q			
5555	Schematic, voltage	5-25		
5555	Chassis wiring	5-26		
5555	Socket, trimmers, alignment			
5555	notes (1), balancing gadget	5-27		
5555	Alignment	5-28		
5555	Parts list—See model 206			
5555	See model 305Z			
5555	Schematic	3-167		
5555	Chassis layout, socket, bypass			
5555	condenser data	3-168		
5555	Circuit changes in late type	3-168		
5555	Schematic, voltage	7-51		
5555	Socket, trimmers, alignment	7-52		
5555	Parts list	7-54		
5555	Schematic	3-171		
5555	Chassis layout, socket	3-172		
5555	Voltage	3-134		
5555	Change, general phono. con-			
5555	nections	7-50		
5555	See model 385Q			
5555	Schematic	3-173		
5555	Chassis layout, socket	3-174		
5555	Voltage	3-134		
5555	Schematic, socket, voltage	3-181		
5555	Trimmers, chassis	3-182		
5555	Parts list	4-16		
5555	Same as model 317			
5555	Similar to 649 but with glass tubes			
5555	Parts list	7-54		
5555	See model E608			
5555	Schematic, voltage	6-37		
5555	Trimmers, alignment	6-47		
5555	Chassis, parts	7-53		
5555	Changes	7-2		
5555	See model 465Q			
5555	Schematic, voltage	7-55		
5555	Socket, trimmers, chassis, align-			
5555	ment	7-56		
5555	Parts list	7-28		
5555	See model 425			
5555	Schematic, voltage	5-31		
5555	Socket, trimmers, parts layout	5-32		
5555	Parts list	5-33		
5555	See model 217D			
5555	See model 856			
5555	Schematic, voltage	4-17		
5555	Chassis wiring	6-32		
5555	Changes	7-48		
5555	Schematic	6-33		
5555	Trimmers, socket, alignment	6-84		
5555	See model 485Q			
5555	See model 165 2nd type			
5555	See model 165Q			
5555	See model 424			
5555	Schematic, voltage	5-23		
5555	Socket, speaker, trimmers,			
5555	parts	5-24		
5555	Same as model 435 but the short			
5555	wave range goes to 18 MC			



[illegible]

# BALKHEIT BELMONT

MODEL	REVISION	EARLY COMPLETE PAGE	RADIOTRON
<b>BALKHEIT RADIO CO.</b>			
C	Schematic, socket, voltage, parts list.....1-3		368
	Chassis, two views.....3-3	*128	369
E	Schematic.....3-4		370
F	Schematic, socket, voltage, parts list.....1-4		
KP	Chassis, two views.....3-1	*127	366
M	Schematic.....3-5		367
A-3, A-5, A-7	Schematic.....4-2		371
D-5	Schematic, voltage, chassis.....1-2		
SG-6	Schematic, socket.....4-3	*125	364
A-7	Schematic.....4-1		
B-7, B-9	See Model A-3		
L-7	Schematic, chassis, data.....1-1		365
L-8	Schematic, socket.....3-6	*126	372
GT-10A	Schematic.....4-9		
G-18A, G-19B	Schematic.....6-1		
GT-20, GT-200X	Schematic.....6-2		
GT-33	Schematic.....6-3		
38	Schematic.....6-4		
41-A	Schematic.....5-1		
42-E, 42-G	Schematic.....6-1		
45	Schematic.....4-5		
48	Schematic.....5-2		
52-1	Schematic.....5-2		
55	Schematic.....4-6		
59	Schematic, socket.....5-3		
60, 70	Schematic, parts.....5-4		
69	Schematic.....5-3		
Windsor 70	Schematic.....4-4		
100	Schematic.....4-8		
GT-156BA	Schematic, socket, trimmers.....6-5		
GT-200X	Alignment, data.....6-6		
	See Model GT-20		
<b>BALKHEIT PRODUCTS CO.</b>			
Specifications	Voltages, charging rates, etc.....1-1	*728	353
B Form D	Schematic.....1-10	*737	362
B-H	Schematic.....1-10	*737	362
B-W Form D	Schematic.....1-9	*736	361
B-W Form D	Schematic.....1-10	*737	362
B-X	Schematic, wiring.....1-8	*735	360
BY	Schematic, wiring.....1-7	*734	359
H, J, K, N Chargers	Schematic.....1-2	*729	354
KX	Schematic, wiring.....1-11	*733	363
A-6	Schematic.....1-8	*735	360
AB-6 Form B	Schematic, wiring.....1-6	*733	358
AB-6-135 Form A	Schematic, wiring.....1-5	*732	357
AB-6-180 Form A	Schematic, wiring.....1-4	*731	356
B-135 Form A	Schematic, wiring.....1-3	*730	361
B-180 Form A	Schematic, wiring.....1-3	*730	355
B-180, Form B	Schematic, wiring.....1-4	*731	356
<b>BARKER BROS.</b>			
L	Schematic, voltage, alignment.....6-1		
M	Schematic, voltage, alignment.....6-1		
P, 2 types	Schematic, voltage.....6-2		
	Alignment.....6-1		
<b>BELMONT RADIO CORP.</b>			
Series 40, Models 45, 46	Schematic, speaker cable code.....3-1		373
Series 40, 41, 42, AC	Schematic, voltage.....3-7	879	
Series 40-A, 41-A, 42-A, AC	Schematic, voltage.....3-7	879	
45, 46	See Series 40		
Series 50	Schematic, voltage, speaker cable code.....3-2		374
	Schematic.....3-3		375
Series 50-A, 110-220-volt, 25 and 60 cycles	Schematic.....3-4		
Series 50-B	Schematic.....3-8		376
Series 50-C	Schematic.....5-1		380
50-F	Schematic.....3-5		
Series 60	Schematic, voltage, data.....3-6		377
Series 70	Schematic, socket, alignment.....5-2		378
70-A	Schematic.....5-1		
71-C	Schematic, socket, alignment.....5-1		
100	Schematic.....5-1		
<b>BELMONT RADIO CORP.—(Cont.)</b>			
MODEL	REVISION	EARLY COMPLETE PAGE	RADIOTRON
Series 110	Schematic.....3-9		381
401	Schematic, voltage.....6-1		
	Socket, trimmers, alignment, notes.....6-2		
401, Series B	Schematic, socket, voltage, alignment, parts list.....7-1		
403, Series A	Schematic, voltage, trimmers, socket.....10-1		
	Alignment.....10-2		
404, Above serial #5D115200A	Schematic, voltage, socket, trimmers.....6-3		
408, Series A	Alignment, parts, battery data.....6-4		
415, Series A	Schematic, voltage, socket, trimmers, alignment parts.....9-1		
415, Series B	Schematic, voltage, parts, socket trimmers, alignment.....8-1		
418, Series A	Schematic, trimmers, alignment.....8-2		
	Schematic, socket, trimmers.....10-3		
	Alignment, voltage, tuner data.....10-2		
420	Schematic, socket.....5-3		
425	Alignment.....5-4		
430	Schematic, socket.....4-1		
	Alignment, socket.....5-3		
435 Export Chassis	See model 524, Ser. A.....5-4		
440	Schematic, socket.....5-5		
444	Alignment.....5-6		
	Schematic, voltage, socket, chassis.....6-5		
X466 Television	Alignment, notes.....6-6		
489, Series A, Above Serial 71852800	Schematic.....10-39, 40		
489, Series B, Above Serial 80136800	Voltage, Notes.....10-41		
	Schematic, socket, trimmers, voltage, parts.....9-3		
501, Series A	Trimmers, alignment.....9-4		
	Schematic, socket, trimmers, voltage, alignment, parts.....9-2		
504, Series A	Schematic, socket, trimmers, voltage, alignment, parts.....9-5		
505, Series A, Above Serial 7381300	Schematic, voltage, socket, trimmers, parts.....9-6		
517, Series A	Alignment, trimmers.....9-4		
	Schematic, voltage, socket, trimmers, alignment, parts, tuner.....9-7		
519	Schematic voltage, alignment.....10-4		
	Socket, trimmers, tuner.....10-5		
520, Series A	Schematic, socket, trimmers, voltage.....10-6		
	Alignment.....10-5		
521, Series A	Schematic.....10-7		
	Socket, trimmers, voltage, alignment, tuner.....10-8		
522	Schematic, voltage, socket, trimmers, alignment, parts.....7-2		
523	Schematic, socket, trimmers, voltage, alignment, parts.....9-8		
523B	Schematic, socket, trimmers, voltage, alignment, parts.....9-9		
524, Series A; Export Chassis 435	Schematic, socket, trimmers, voltage, alignment, parts.....9-10		
525 AC-DO	Schematic, socket, servicing data.....3-8		
526	Schematic, socket, trimmers, voltage, tuner, alignment, parts.....9-11		
527, Series A	Schematic.....10-9		
	Socket, trimmers, voltage, alignment, tuner data.....10-10		
529	Schematic.....10-11		
	Socket, trimmers, alignment, tuner data.....10-12		
530	Schematic, socket, parts list.....4-2		
531 Series B, Above Serial 187500	Schematic, voltage, socket, trimmers, alignment, parts.....9-12		
540	Schematic, socket, alignment, parts.....5-7		

BELMONT RADIO CORP.—(Cont.)			RADIOTRON		
MODEL	REVISI	PAGE	MODEL	REVISI	PAGE
541	Schematic, voltage, socket, trimmers	6-7	683, Series A	Schematic, socket, trimmers, voltage	10-19
544, 545	Alignment, parts, notes	6-8	684, Series A	Alignment, tuner, parts	10-20
550	Schematic, voltage, socket, trimmers, parts	6-9		Schematic, socket, trimmers	10-21
551, Series A	Alignment, notes	6-10	640	Tuner, phono data, parts	10-22
553, Series A	Schematic, voltage, socket, trimmers	6-11	650	Schematic, socket, trimmers	5-9
555	Trimmers, alignment, notes	6-12		Alignment	5-10
556 (Export)	Schematic, socket, trimmers	7-3	660	Schematic, voltage, socket, parts list	5-11
566	Alignment, parts	7-4		Schematic, socket, parts list	5-12
575	Schematic, socket, trimmers, parts	7-5	661	Schematic, voltage, socket, trimmers, parts	4-6
577 Series A	Alignment, notes	7-6		Schematic, voltage, socket, trimmers, parts	8-7
	Schematic, voltage, socket, trimmers, tuner, alignment	7-8	665, Series A, 765	Alignment, assembly, wiring diagram	8-8
5770 Above Serial 203070	Schematic, voltage, socket, trimmers, parts	9-13		Schematic, voltage, trimmers, parts	9-21
578, 2 types, Serial 5G138670A to 5K179250A and Above	Schematic, voltage, notes	10-17	666	Alignment, tuner, trimmers, notes	9-22
578, Series A	Alignment, socket, trimmers, tuner data	10-18		Data	Changes 10-3
580	Schematic, voltage, parts	6-16	667	Schematic, socket, trimmers, parts	7-13
580, Revised, Above serial 11501	Installation details, parts	6-17		Schematic, voltage, socket, trimmers, parts	9-23
582, Series A, Above Serial 7L894500	Schematic, voltage, socket, trimmers, parts	9-15	670	Alignment, wiring data, notes	9-24
582, Series B, Above Serial 8B106200	Schematic, voltage, socket, trimmers, parts	9-16	670-A	Schematic, socket, trimmers	5-13
583 Export	Alignment, notes	9-18		Alignment, service notes	5-14
585, Series A, B, C	Schematic, voltage, socket, trimmers, parts	9-23		Schematic, voltage, parts	6-22
585, Series D	Schematic, voltage, socket, trimmers, parts	9-24	677	Schematic, voltage, socket, trimmers, parts	9-25
586, Series A, above serial 6E248475	Schematic, voltage, socket, alignment, parts	7-9	677, Issue C, Above Serial 50672	Installation, alignment, tuner	9-26
587, Series A	Schematic, socket, trimmers, parts	7-11		Schematic, socket, trimmers, voltage	10-23
588, Series A	Alignment, voltage, socket, trimmers, parts	8-3		Alignment, tuner data, notes	10-24
589	Alignment, trimmers	8-4	678, Issue A	Tuner data	10-18
589 Series A Above Ser. No. 8E-189200	Schematic, socket, trimmers, alignment	8-5		Installation	9-26
601, Series A & B	Changes	9-1	680	Schematic, voltage, socket, trimmers	10-25
602	Schematic, socket, parts, alignment, notes	7-10		Alignment, notes, tuner	10-26
602B, 602C	Schematic, socket, voltage, trimmers, alignment, parts	8-6		Tuner data, notes	10-27
611 Series A	Schematic, voltage, socket, trimmers, alignment, parts	9-29	685, Series A	Schematic, voltage, socket, trimmers	6-25
	Voltage, alignment, tuner, notes	9-17	686, Series A & B	Alignment, parts	6-26
625	Schematic, socket, parts list	4-5		Schematic, socket, trimmers	7-15
632 Series A	Schematic, voltage, parts	9-19	689 Series A	Alignment, notes	7-16
	Schematic, voltage, alignment, notes	9-20		Schematic, voltage, socket, trimmers, parts	9-27
			740	Alignment	9-28
				Schematic, voltage, socket, trimmers, parts	8-9
			746, Series A	Alignment, trimmers	8-10
				Schematic, socket, trimmers, voltage	7-17
			750	Alignment, parts	7-18
				Schematic	4-7
			751, Series A	Alignment, socket	5-19
				Schematic, voltage	10-29
				Tuner data	10-28
			755	Alignment, socket, trimmers, notes	10-30
				Schematic, socket, parts, layout	6-27
			761 Series A	Trimmers, alignment	6-28
				Schematic, voltage, socket, trimmers, parts	9-30
			767, Series A	Alignment, tuner	9-36
				Schematic, socket, trimmers	10-31
			770, Series A	Alignment, trimmers, voltage	10-32
			775	Notes	7-20
				Schematic, socket, trimmers, parts	5-17

**RADIOTRON<sup>®</sup>  
COMPLETE  
PAGE**

MODEL	BELMONT RADIO CORP.—(Cont.)	REVISED PAGE
1075, Series A, B	Socket, trimmers, voltage, phono, notes .....10-37	
1170, 1172	Tuner data, notes, parts .....10-38	
	Schematic, voltage, socket, trimmers, parts .....8-29	
1170B	Alignment .....8-30	
	Schematic, voltage, socket, trimmers, parts .....8-31	
1170C Above Serial 7C561750	Alignment .....8-32	
1171 Series A	Schematic, socket, trimmers, parts .....9-43	
	Alignment, trimmers .....9-44	
	Schematic, voltage, socket, trimmers, parts .....9-45	
1174	Alignment, notes .....9-46	
	Schematic, voltage, socket, trimmers, parts .....8-33	
1175 Series A	Alignment .....8-34	
	Schematic, voltage, parts .....9-47	
	Alignment .....9-40	
	Trimmers, tuner .....9-48	
6-U	BLACHAWK ..... Misc. 5-3	
	Schematic ..... Misc. 5-3	
	DAVID BOGEN CO., INC.	
	Master-tone Amplifier .....8-1	
	Supreme Amplifier .....8-1	
	2-5-10 Meter Superhet .....8-2	
	2SC Communicator .....8-3	
	2W Communo-Phone .....8-5	
	3A Communo-Phone .....8-6	
	5SC Communo-Phone .....8-3	
	B-20 Amplifier .....8-7	
	SX50 Amplifier .....8-8	
	BOSCH	
	See UNITED AMERICAN BOSCH	
	BRANDES PRODUCTS CORP.	
	Also see KOLSTER RADIO, INC.	
A-1	Schematic .....3-2	
B-10	Schematic .....1-1	
B-11, B-12	Voltage, socket, data .....1-2	
B-15, B-16	Schematic .....3-1	
	Schematic .....1-3	
	Voltage, socket, data .....1-4	
	BREMNER-TULLY MFG. CO.	
ABC Power Pack	Schematic .....3-4	
B-T 6	Schematic .....2-1	
6-40 Power Converter	Schematic .....1-5	
6-40, 6-41	Schematic, socket, voltage .....1-6	
7-70	Schematic, chassis wiring .....3-1	
7-70 Power Converter	Schematic, socket, voltage .....3-2	
8 Counterphase	Schematic .....1-3	
8-12 Counterphase	Schematic, socket .....2-1	
8-20, 8-21	Schematic, socket, voltage .....1-3	
80	Schematic, socket .....2-2	
81-A	Schematic, socket .....1-5	
81, 82	Schematic, socket, voltage .....1-6	
	Resistor, condenser, transformer connections .....3-4	
81, 82 Power Unit	Chassis wiring .....3-3	
S-81, S-82	Schematic, socket .....3-3	
S-81, S-82 RF	Chassis wiring .....1-7	
S-81, S-82 A-F, 60 cycles	Chassis wiring .....3-5	
S-81, S-82 A-F & SPU, 25 cycles	Schematic, choke and condenser connections .....3-6	
83-A	Schematic .....2-2	
	BRENARD MFG. CO.	
Heraldyne	Schematic ..... Misc. 6-4	

A-1	Schematic	3-2	383
B-10	Schematic	1-1	383
	Voltage, socket, data	1-2	384
B-11, B-12	Schematic	3-1	385
B-15, B-16	Schematic	1-3	386
	Voltage, socket, data	1-4	387
<b>BREMER-TULLY MFG. CO.</b>			
ABC Power Pack	Schematic	3-4	396
B-T 6	Schematic	2-1	389
6-40 Power Converter	Schematic	1-5	395
6-40, 6-41	Schematic, socket, voltage	1-4	390
7-70	Schematic, chassis wiring	3-1	391
7-70 Power Converter	Schematic, socket, voltage	3-2	392
8 Counterphase	Schematic	1-3	393
8-12 Counterphase	Schematic, socket	2-1	380
80	Schematic, socket, voltage	1-3	393
81	Schematic, socket	2-2	394
81-A	Schematic, socket	1-5	395
81, 82	Schematic, socket, voltage	1-6	396
	Resistor, condenser, transformer	3-3	398
	connections	3-4	397
81, 82 Power Unit	Chassis wiring	3-3	399
S-81, S-82	Schematic, socket	1-7	400
S-81, S-82 RF	Chassis wiring	2-3	401
S-81, S-82 A-F, 60 cycles	Chassis wiring	3-5	401
S-81, S-82 A-F & SPU,	Schematic, choke and condenser	3-6	402
25 cycles	connections	3-3	394
88-A	Schematic	2-2	132-A

[illegible]

# BULOVA CAPEHART

MODEL	THE CAPEHART, INC.	REVISED PAGE	EARLY PAGE	RADIOTRON COMPLETE PAGE
E-1	Tuner schematic, voltage alignment Amplifier schematic, voltage alignment Trimmers, chassis Schematic Chassis, service notes, Part 1 Service notes, part 2 Service notes, part 3 Service notes, part 4 Adjustments, Part 1	10-1 10-2 10-3 10-3 10-3 2-1 2-3 2-3 2-4 10-25	192-D 192-D-1 192-D-2 192-D-3	525 526 527 528
10, 12-C	Standard Amplifier			
16-E Deluxe Record changer				
21	Adjustments, Part 2 Adjustments, Part 3 Notes Complete assembly Chassis views Chassis views Chassis view, parts Chassis views Cabinet wiring Complete wiring Schematic Wiring diagram Trimmers, chassis, alignment Amplifier schematic Wiring diagram See model 100 Wiring diagram Wiring diagram Wiring diagram Wiring diagram	10-26 10-27 10-28 10-29 10-30 10-31 10-32 10-33 10-34 3-1 3-2 5-1 3-3 10-5 10-4 10-4 3-4 3-5 3-6 3-7 3-8		517 518
100, 100 1/4, 101, 101 1/4, 130, 130 1/4	Chassis Z 103, 104, Cosmopolitan, Chassis Z 110-Amperton 110-G, Paramuse			
111-Amperton				
130, 130 1/4				
150, 151-Amperton				
170-Amperton				
180, 180 1/4, 182, 182 1/4				
200-F Tuner				
202				
203				
400, 401, 402				
400 Series, PZ Amplifier				
400 Series, RF				
400, 401, 402				
400-A Series Tuner				
400-B Tuner				
400-B Amplifier				
400-B, 402-B, 404-B Tuner				
400-B, 402-B, 404-B				
400-B, 402-B, 404-B Amplifier				
400-D				
400-E, 500-E Series				
400-F Tuner				
400-G, 500-G Series				
400-G				

MODEL	BULOVA WATCH CO.—(Cont.)	REVISED PAGE	EARLY PAGE	RADIOTRON COMPLETE PAGE
M-501	Chassis layout, assembly wiring, voltage	2-2	187-B	504
600, 601, 605, 610	Schematic, voltage, socket	5-1		
M-701, G-781	Alignment, trimmers	5-2		
Q-751	Test data	2-3	187-D	505
	Schematic, socket	2-4	187-E	506
	Voltage, service data	2-5	187-F	507
		2-6		508
10	BUSH & LANE PIANO CO.			
	Schematic	1-1	*189	509
	Voltage, socket, tests	3-1		510
12	Chassis layout	8-2		511
	Schematic, socket, voltage	1-2	*188	512
24-27	C. R. O.			
24-45	Schematic	4-1		
24-47	Schematic	4-1		
58-47	Schematic	4-2		
	Schematic	4-3		
6X	CADILLAC DIV.—GENERAL MOTORS			
	Schematic, voltage, socket, trimmers	8-1		
6W	Alignment, notes	8-2		
	Notes on mounting	5-1		
	Notes on mounting, Part 2	5-2		
	Schematic, socket, alignment	5-3		
	Parts list	5-4		
6KB	Schematic, voltage, socket, trimmers	8-3		
	Alignment, notes	8-2		
6-Q	Schematic	7-1		
	Voltage, resistances, socket, trimmers, transformer data	7-2		
6R	Circuit data, parts, alignment	7-3		
	Schematic	8-5		
6S	Alignment, voltage, socket, trimmers, data	8-6		
	Schematic, parts	8-7		
6T	Alignment, voltage, socket, trimmers, changes, notes	8-8		
	Schematic, notes	8-9		
6U2	Alignment, voltage, trimmers, socket, data	8-10		
C-8	Schematic	8-4		
	Schematic, voltage, sensitivity	10-1		
56V1	Socket, trimmers, chassis	10-2		
2029, 2029A, 2080	Tuner, alignment notes	10-3		
2721 (072)	Tuner, alignment data	10-4		
	Schematic	5-12		
	See Delco Radio 3026			
2722 (072A)	Schematic	5-5		
	Voltage, socket, assembly	5-6		
	Chassis wiring	5-11		
	Parts, trimmer data	5-8		
	Power pack data	5-7		
	Trimmer data	5-8		
	Chassis wiring	5-11		
	Power pack data	5-7		
	Trimmer data	5-8		
	Voltage, parts list, special notes	5-10		
1425470, 1425471	Schematic	9-1		
	Socket, trimmers, layout, voltage, alignment	9-2		
7232502	Schematic	9-3		
	Socket, trimmers, layout, voltage, alignment	9-4		
A-50-A	CALVEET MOTORS ASSOCIATES			
A-51-A, A-52-A	Schematic, voltage	6-1		
	Schematic, voltage, parts	6-2		

518  
514  
515  
516

\*192-A  
\*192-C  
\*192-B  
\*192-D

10-7, 8  
10-11  
8-2  
8-3  
8-3  
10-18  
10-19  
10-17  
10-20  
10-21  
10-13  
10-12  
10-14  
10-22  
10-16

Tuner schematic, voltage alignment  
Amplifier schematic, voltage alignment  
Trimmers, chassis  
Schematic  
Chassis, service notes, Part 1  
Service notes, part 2  
Service notes, part 3  
Service notes, part 4  
Adjustments, Part 1  
Adjustments, Part 2  
Adjustments, Part 3  
Notes  
Complete assembly  
Chassis views  
Chassis views  
Chassis view, parts  
Chassis views  
Cabinet wiring  
Complete wiring  
Schematic  
Wiring diagram  
Trimmers, chassis, alignment  
Amplifier schematic  
Wiring diagram  
See model 100  
Wiring diagram  
Wiring diagram  
Wiring diagram  
Wiring diagram  
Schematic—See 110G  
Schematic, voltage  
Amplifier and power pack  
Schematic  
Tuner schematic, voltage  
Schematic  
Chassis wiring  
Chassis wiring  
Complete wiring diagram  
Schematic  
Schematic  
Schematic  
Schematic  
Schematic  
Tuner schematic, voltage  
Base Amplifier schematic, voltage  
Treble amplifier schematic, voltage  
Schematic, voltage  
Trimmers, layout  
Schematic  
Schematic  
Schematic  
Remote control installation  
Mixing panel chassis, notes  
Mixing panel notes  
Trimmers, chassis  
Extended control wiring  
Extended control, wiring assembly  
Tuner schematic, voltage  
Assembly wiring  
Base amplifier schematic, voltage  
Volume control schematic, data, parts list  
Tuning meter adjustments, chassis, assembly

600  
601  
1437  
5237  
6138P  
6238P  
7373, 7383

Schematic ..... 7-8  
Schematic ..... 7-9  
Schematic ..... 9-4  
Coil data ..... Misc. 10-2  
Schematic ..... 9-5  
Schematic ..... 9-5  
Schematic ..... 9-6  
Coil data ..... 9-2

CHEVROLET DIV.—GENERAL MOTORS

See also UNITED MOTORS SERVICE

See United Motors 4037

600153

Schematic, voltage ..... 10-1

601525

Socket, trimmers, chassis, changes, alignment ..... 10-2

601586

Schematic, voltage, changes ..... 10-3

985200

Socket, trimmers, chassis, alignment, parts ..... 10-4

985254

Schematic, voltage ..... 10-5

985283

Socket, trimmers, chassis, alignment, parts ..... 10-6

985400

Socket, trimmers, chassis, alignment, parts ..... 10-7

985424

Socket, trimmers, chassis, alignment, parts ..... 10-8

985425

Tuning unit notes, Part 1 ..... 10-9

985426

Tuning unit notes, Part 2 ..... 10-10

Socket, trimmers, alignment, chassis ..... 10-11

Socket, trimmers, chassis, views ..... 10-12

Tuning unit wiring, condenser assembly, voltage ..... 10-13

Alignment ..... 10-14

Schematic ..... 10-15

Socket, trimmers, voltage, chassis, alignment, tuner ..... 10-16

Schematic, alignment ..... 10-17

Voltage, socket, trimmers, alignment, chassis ..... 10-18

CHRYSLER

See PHILCO RADIO & TELEVISION CORP.

OLAGO RADIO CORP.

Radiochron "B" ..... Misc. 4-9  
581 "Heritage" ..... Misc. 9-3

CLARION

See TRANSFORMER CORP. OF AMERICA

CLEARSTONE RADIO CORP.

60 Goldcrest ..... 1-1  
70 Clearodine ..... 1-1  
80 (Improved) ..... 1-2  
100 Series ..... 1-2  
110 ..... 1-3  
112 ..... 1-3

CLIMAX RADIO & TELEVISION CO., INC.

Diamond ..... 8-1  
Duke ..... 8-5  
Lee ..... 8-5  
Opal ..... 8-1  
AA ..... 7-3  
AA ..... 7-3  
AB, ABX, Early ..... 7-4  
ABX, Late ..... 7-4  
AD ..... 7-5  
AH, AHE ..... 8-2  
AJ ..... 8-3  
AK ..... 8-4  
AKE ..... 8-5  
AL ..... 9-1  
Schematic, socket, alignment ..... 9-1  
Schematic, socket, alignment ..... 9-2

400-G  
Remote control, cable notes ..... 10-24  
Treble amplifier, schematic, alignment, voltage ..... 10-15  
Play control, assembly, adjustments ..... 10-23

CARTER GENEMOTOR CORP.

Notes ..... 4-2  
Schematic ..... 4-1  
113A, 1180A, 1680A, 1685A, 4680A, 4685A

CASE ELECTRIC CORP.

Also see U. S. RADIO & TELEVISION CO.

Planetary Drive Assembly Notes ..... 7-16

601, Chassis 16 SM ..... 7-2

Alignment, trimmers ..... 7-1

Voltage, parts, chassis ..... 7-3

Schematic ..... 7-4

Alignment, trimmers ..... 7-5

Voltage, parts, chassis ..... 7-6

Voltage, chassis, parts ..... 10-1

Schematic, trimmers, alignment ..... 10-2

Schematic ..... 7-8

Alignment, trimmers ..... 7-7

Voltage, parts, chassis ..... 7-9

Schematic ..... 7-11

Trimmers, alignment ..... 7-10

Voltage, parts, chassis ..... 7-12

Schematic ..... 7-13

Trimmers, alignment ..... 7-14

Voltage, parts, chassis ..... 7-15

CAVALCADE RADIO CO.

Schematic, data ..... 6-1

Schematic, installation data ..... 6-2

Schematic, socket, trimmers ..... 6-3

Alignment data ..... 6-4

CENTURY RADIO PRODUCTS CO.

Schematic ..... 8-6

Schematic ..... 8-7

Schematic ..... 8-1

Schematic ..... 3-2

Schematic ..... 3-3

Schematic ..... 3-4

Schematic ..... 3-5

CHAMPION RADIO

Auto Radio Power Sup. Schematic, data ..... 8-8

ply Data ..... 7-10

Coil Connections ..... 7-1

4-Tube, AC-DC ..... 7-1

5-Tube, 3-Band ..... 7-2

6-Tube, 3-Band ..... 9-1

30 ..... 8-1

Schematic, notes ..... 7-5

40-R, 40-DW, 40-RM, 40-DWN ..... 8-2

40UM ..... 7-3

42 ..... 8-3

50A2M ..... 8-4

50UD ..... 8-4

50UP ..... 7-4

52 (47 output) ..... 7-5

52 (42 output) ..... 7-4

52-DWG ..... 9-2

54, 55 ..... 9-1

307, 317 ..... 9-3

400 ..... 7-6

500 ..... 7-7

501 ..... 8-5

521UD ..... 8-6

526DW ..... 8-7

531D ..... 8-2

558 ..... 7-1

CLIMAX  
COLONIAL

MODEL	REVISED PAGE	MODEL	REVISED PAGE	MODEL	REVISED PAGE
ASE	Schematic, socket, alignment.....9-1	32 DC Issue A	Schematic, socket, voltage.....1-12	32 DC Issue A	Schematic, socket, voltage.....1-12
ATE	Schematic, socket, alignment.....9-1	32 AC, Issue J	Chassis wiring.....1-13	32 AC, Issue J	Chassis wiring.....1-13
B	Schematic, parts.....8-6		Schematic, socket, voltage.....1-14		Schematic, socket, voltage.....1-14
C, D	Schematic, parts.....8-6		Schematic, socket, voltage.....1-15		Schematic, socket, voltage.....1-15
E	Schematic, parts.....8-7		Chassis layout.....1-15		Chassis layout.....1-15
F	Schematic, parts.....8-7		Remote Control Notes.....2-1		Remote Control Notes.....2-1
FBT	Schematic, parts.....Misc. 10-3		Parts list.....2-3		Parts list.....2-3
G	Schematic, parts.....8-8		Schematic, wiring, cable.....1-17		Schematic, wiring, cable.....1-17
H	Schematic, parts.....8-9		Schematic, socket.....2-4		Schematic, socket.....2-4
IE	Schematic, parts.....8-9		Schematic.....1-19		Schematic.....1-19
JEBT	Schematic, parts.....8-10		Chassis wiring, parts list.....2-6		Chassis wiring, parts list.....2-6
JL	Schematic, parts.....8-10		Data on parts.....2-5		Data on parts.....2-5
M	Schematic, parts.....7-9		Schematic.....1-19		Schematic.....1-19
M, ME Revised	Schematic, parts.....8-11		Schematic, socket.....2-7		Schematic, socket.....2-7
MBT	Schematic, parts.....8-8		Chassis wiring.....2-8		Chassis wiring.....2-8
R	Schematic, parts.....8-9		Parts coding, voltage.....2-10		Parts coding, voltage.....2-10
RBT	Schematic, parts.....8-9		Schematic.....2-11		Schematic.....2-11
SBT	Schematic, parts.....8-12		Chassis wiring.....2-11		Chassis wiring.....2-11
T	Schematic, parts.....8-12		Schematic.....2-12		Schematic.....2-12
U, UE	Schematic, socket, alignment.....9-2		Chassis wiring.....2-13		Chassis wiring.....2-13
U-2	Schematic, socket, alignment.....7-6		Voltage, parts coding.....2-12		Voltage, parts coding.....2-12
A-4	Schematic.....7-7		Schematic, socket, data.....2-15		Schematic, socket, data.....2-15
KSW-4	Schematic.....7-6		Chassis wiring.....2-14		Chassis wiring.....2-14
M-4 (Early)	Schematic.....7-7		Schematic.....1-18		Schematic.....1-18
M-4 (Late)	Schematic.....7-6		Parts coding.....2-19		Parts coding.....2-19
4Tube ACDO	Schematic.....7-2		Chassis wiring, voltage.....2-17		Chassis wiring, voltage.....2-17
4Tube Batt	Schematic.....7-2		Schematic.....2-16		Schematic.....2-16
5Tube ACDO	Schematic.....7-2		Chassis wiring.....2-18		Chassis wiring.....2-18
SW-5 (Lee)	Schematic.....7-1		Schematic, voltage, data.....2-21		Schematic, voltage, data.....2-21
6Tube Batt.	Schematic.....7-1		Parts coding.....2-22		Parts coding.....2-22
AD6	Schematic, socket, alignment.....9-2		Schematic.....Misc. 10-4		Schematic.....Misc. 10-4
7-B	Schematic.....7-9		Chassis wiring.....2-28		Chassis wiring.....2-28
10 to 19 inclusive	Schematic.....7-10		Chassis wiring, voltage.....2-29		Chassis wiring, voltage.....2-29
30, 31, 32, 33, 34	Schematic.....7-11		Schematic, socket, parts coding.....2-30		Schematic, socket, parts coding.....2-30
35	Schematic.....7-12		Chassis wiring.....2-31		Chassis wiring.....2-31
50 to 59 inclusive	Schematic.....7-13		Schematic, socket.....2-32		Schematic, socket.....2-32
Z-55	Schematic.....8-14		Voltage, parts coding.....2-33		Voltage, parts coding.....2-33
AC60, AC61, AC64, AC65	Schematic, parts.....8-15		Schematic, socket.....3-1		Schematic, socket.....3-1
U60, U61, U64, U64B, U65	Schematic, parts.....8-16		Voltage.....3-3		Voltage.....3-3
66	Schematic.....7-15		Parts coding.....3-4		Parts coding.....3-4
Q-69	Schematic.....7-14		Schematic.....3-3		Schematic.....3-3
90 to 99 inclusive	Schematic.....7-14		Parts coding.....3-5		Parts coding.....3-5
90B to 99B inclusive	Schematic.....7-15		Schematic, voltage.....3-6		Schematic, voltage.....3-6
424	Schematic.....7-15		Parts coding.....3-7		Parts coding.....3-7
457	Schematic.....Misc. 5-4		Schematic, voltage.....3-8		Schematic, voltage.....3-8
557	Schematic.....7-16		Parts coding.....3-9		Parts coding.....3-9
			Schematic, data.....3-10		Schematic, data.....3-10
			Voltage, socket.....3-11		Voltage, socket.....3-11
			Parts coding.....3-12		Parts coding.....3-12
			Coil connections.....3-13		Coil connections.....3-13
			Switch connections.....3-14		Switch connections.....3-14
			Schematic, coil connections.....3-15		Schematic, coil connections.....3-15
			Voltage, chassis layout.....3-16		Voltage, chassis layout.....3-16
			Schematic, I-F data.....3-17		Schematic, I-F data.....3-17
			Voltage, parts coding, socket.....3-18		Voltage, parts coding, socket.....3-18
			Schematic, transformer notes.....3-19		Schematic, transformer notes.....3-19
			Voltage, chassis layout.....3-20		Voltage, chassis layout.....3-20
			Parts coding.....3-21		Parts coding.....3-21
			Service notes.....3-22		Service notes.....3-22
			Simplified schematic.....3-23		Simplified schematic.....3-23
			Schematic, voltage.....3-24		Schematic, voltage.....3-24
			Parts coding.....3-25		Parts coding.....3-25
			Schematic, transformer data.....3-26		Schematic, transformer data.....3-26
			Schematic.....3-27		Schematic.....3-27
			Parts coding.....3-28		Parts coding.....3-28
			Voltage, alignment data.....4-1		Voltage, alignment data.....4-1
			Notes.....4-2		Notes.....4-2
			Notes, cable data, antenna.....4-3		Notes, cable data, antenna.....4-3
			Drive cable data.....4-4		Drive cable data.....4-4
			Cable data.....4-4		Cable data.....4-4

CLIPPER  
See RADIO PRODUCTS SALES CO.

## COAST TO COAST

A-14	Schematic.....Misc. 3-3
56, 3-46, 83	Schematic.....Misc. 3-4
56, 2-59, 2-81	Schematic.....Misc. 3-4
52B	Schematic.....4-1
D-3008	Schematic.....4-2
D-3031	Schematic.....4-3
4978	Schematic.....4-4

## COLONIAL RADIO CORP.

Suffix A:	16" spkr. used instead of 8"
General Notes	Alignment, image frequency data.....5-1
Intermediate Frequencies	I-F. Peaks.....Changes 7-4
16-5	Schematic.....1-2
16-6	Schematic.....1-1
17-5	Schematic.....1-2
20	Schematic.....1-3
21	Schematic.....1-3
25	Schematic, socket.....1-4
26	Schematic, socket.....1-5
28 AC, Serial #90,001	Schematic, socket.....1-6
28 DC, Serial #85,001	Schematic, socket.....1-7
31 AC	Schematic, socket.....1-10
31 AC, 31 DO	Voltage.....1-9
31 DO	Schematic, socket, voltage.....1-8
32 DO, Issue A	Chassis wiring, data.....1-9
	Chassis wiring.....1-11

*194	542
*193	541
*194	542
*195	543
*196	544
*197	545
*198	546
*199	547
*200	548
*201	549
*203	553

*202	552
*207	553
*206	554
*204	556
*208	557
*208-1	559
*208-2	560
*208-3	561
*208-4	562
*208-A	563
*208-B-1	564
*208-B-2	565
*208-A	566
*208-B-5	567
*208-B-6	568
*208-B-7	569
*208-B-8	570
*208-5	571
*208-B	574
*208-B-9	575
*208-B-10	576
*208-B-11	581
*208-B-12	582
*208-B	579
*208-B-15	577
*208-B-13	580
*208-B-14	578
*208-D	584
*208-C	583
*208-E	585
*208-B-18	587
*208-B-17	586
*208-G	589
*208-F	588
*208-I	591
*208-H	590
*208-B-20	593
*208-B-19	592
*208-K	594
*208-J	595
*208-L	596
*208-L	597
*208-L	599
*208-L	600
*208-L	598
*208-L	599
*208-L	601
*208-L	602
*208-L	603
*208-L	604
*208-L	605
*208-L	606
*208-L	607
*208-L	608
*208-L	609
*208-L	610
*208-L	611
*208-L	612
*208-L	613
*208-L	614
*208-L	615
*208-L	616
*208-L	617
*208-L	618
*208-L	619
*208-L	620
*208-L	621
*208-L	622
*208-L	623
*208-L	624






# COLONIAL CONTINENTAL

MODEL	CONTINENTAL RADIO CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON PAGE
700, 701, 702	Parts location .....4-59			
700 AC, 701 AC, 702 AC	Parts list, terminal board data.....4-60			
	Circuit notes, voltage .....4-61			
	Schematic .....4-62			
	Parts location, speaker terminal data .....4-63			
	Socket layout, parts list.....4-64			
	Voltage, service notes.....3-38			
	Parts coding .....3-39			
	Supplementary service notes (A) .....3-40			
	Schematic .....3-41			
	Spkr., notes, parts. See model T-345			
<b>COLUMBIA PHONOGRAPH CO.</b>				
C-1, C-3	Schematic, socket .....1-1			
C-2, C-4	Schematic, socket .....1-2			
C-5 (205)	Schematic, socket, voltage .....1-3			
C-5 (310)	Schematic, socket .....1-3			
C-6, C-7	Schematic, socket .....1-4			
CM-18-A, C-19-A	Dynamic speakers data .....3-6			
C-25-31, C-25-32, C-81, C-82 (Chassis C101)	Schematic, socket, voltage.....2-2			
32, 34 (Chassis C102)	Chassis, test data .....2-1			
C-80-A	Chassis layouts .....2-3			
C-80-B	Schematic .....3-2			
	Schematic .....3-3			
	Power transformer data .....3-5			
	Chassis, notes .....3-6			
C-80-A, C-80-B, C-800-A	Voltage .....3-5			
C-80-A, C-800-A	Power transformer data .....3-6			
C-90	Power transformer data .....3-5			
	Schematic .....3-7			
	Silent tuning notes .....3-8			
	Voltage, tuning notes .....3-9			
C-100	Schematic, voltage, socket .....3-10			
C-101 Chassis	See model C-25-31			
C-102 Chassis	See model 32, 34			
120-B	Schematic, alignment data, notes .....3-11			
C-800	Schematic .....3-12			
C-800-A	Schematic .....3-4			
	Voltage, pwr. data. See model C-80-A			
900, 901	Schematic, socket .....1-4			
902	Schematic, socket .....1-5			
920, 990	Schematic .....1-6			
930	Schematic, socket .....1-6			
930-300	Schematic, socket .....1-7			
931	Schematic, socket .....1-7			
940	Schematic, socket .....2-4			
950	Schematic, socket .....1-8			
961	Schematic, socket .....1-9			
980	Schematic, socket .....1-10			
990	See model 920			
<b>COLUMBIA RADIO CORP.</b>				
SG-5 1930	Schematic .....3-1			
SG-8	Chassis wiring, voltage .....1-1			
	Schematic .....1-2			
	Chassis .....3-2			
SG-9 1930	Schematic, socket .....3-3			
SG-10	Schematic .....3-4			
150	Schematic ..... Misc. 5-5			
<b>COMMONWEALTH RADIO MFG. CO.</b>				
8-In-Line	Schematic ..... Misc. 6-4			
<b>CONSUMABLE</b>				
Star Raider	See model R-20			
Slagle 9 with '71-A	Schematic, socket, voltage.....1-1			
Slagle 10, A and B with '71-A Power Pack	Schematic, socket .....1-2			
R-20, R-30, R-40, Star Raider	Schematic .....1-6			
<b>CONTINENTAL RADIO CORP.</b>				
Slagle 29-C with '71-A Power Pack	Schematic, socket .....1-3			
Slagle 29-A and 29-B with '50 Power Pack	Schematic, socket .....1-4			
Slagle 29-C and 29-D with '50 Power Pack	Schematic, socket .....1-5			
R-40	See model R-20			
<b>CONTINENTAL RADIO &amp; TELEVISION CORP.</b>				
Touch-O-Matic, Type T-21	Schematic, assembly .....8-21			
	Installation, notes, adjustments .....8-22			
M-1	Schematic, voltage, socket, trimmers .....7-9			
	Alignment, parts .....7-10			
L-2, ML156, ML266	Schematic .....6-2			
Z-2	Schematic, voltage, socket, trimmers .....7-13			
4A, 4B, Early, Late, 40	Alignment, parts .....7-14			
4D, Early, Late	Schematic, socket, trimmers .....10-1			
	Schematic .....10-2			
4D-PH	Alignment, socket, trimmers .....10-2			
4	Schematic .....10-3			
4H	Alignment, socket, trimmers .....10-2			
	Schematic .....10-3			
L-4, ML-4	Alignment, socket, trimmers .....10-2			
Z-4	Schematic, voltage .....6-1			
	Schematic, voltage, socket, trimmers .....7-15			
5A	Alignment, parts .....7-16			
	Schematic, socket, trimmers, alignment, tuner, parts .....9-1			
5AZ	Schematic, socket, trimmers, alignment .....9-2			
5B	Schematic .....10-5			
	Socket, trimmers, alignment, tuner, voltage, phono data .....10-6			
50	Schematic, socket, trimmers, alignment, parts .....9-3			
50U	Schematic .....10-5			
	Socket, trimmers, alignment .....10-6			
5D, 5DL	Schematic .....10-4			
	Alignment, socket, trimmers .....10-2			
5E	Schematic, socket, trimmers, alignment, parts .....9-4			
5EA	Schematic .....10-4			
	Alignment, socket, trimmers .....10-2			
5F	Schematic, socket, trimmers, alignment, parts .....9-5			
5G	Schematic, socket, trimmers, alignment .....9-6			
5J	Schematic .....10-1			
	Alignment, socket, trimmers .....10-2			
5L, 5LL	Schematics, voltage .....10-7			
L-5	Alignment, socket, trimmers .....10-2			
5LL Phono	Schematic, parts .....7-3			
5M Chassis	Schematic, voltage .....10-7			
5VU	alignment .....8-1			
	Schematic, socket, trimmers, alignment .....9-7			
5X Chassis	See model 160-5X			
5Z Chassis	See model 150-5Z			
6A	Schematic, socket, trimmers, alignment .....10-8			
6B	Schematic, socket, trimmers, alignment .....10-9			
6C	Tuner data .....10-10			
	Schematic, socket, trimmers, alignment .....10-11			
6D	Tuner data .....10-10			
	Schematic, socket, trimmers, alignment .....9-8			
6G	Schematic, socket, trimmers, alignment .....10-12			
	Tuner data .....10-10			
6H	Schematic, socket, trimmers, alignment .....9-9			

CONTINENTAL RADIO & TELEVISION CORP.—(Cont.)			RADIO-TRON		
MODEL	REVISION	PAGE	EARLY COMPLETE	REVIS	PAGE
6K	Schematic, socket, trimmers, voltage, alignment	10-13			
6L	Schematic, socket, trimmers, alignment	9-10			
L-6	Schematic, socket, trimmers	7-5			
6P Chassis	Alignment, parts	7-6			
6PU	Schematic, alignment	8-5			
6Q Chassis	Socket, trimmers, notes, parts	8-6			
	Schematic, socket, trimmers, alignment	9-11			
	Schematic, socket, trimmers, alignment, battery connections	8-4			
6W Chassis	See model 165-6W				
6Y Chassis	Schematic, socket, trimmers	9-12			
7A	Alignment	9-8			
7G	Schematic, socket, trimmers, alignment, tuner	9-13			
7J Chassis	Schematic, socket, trimmers, alignment, parts	8-9			
L-7	Schematic, socket, trimmers	7-7			
7M Chassis	Alignment, parts	7-8			
7MU Chassis	Schematic, socket, trimmers	8-10			
8A	Alignment	8-12			
8AU	Schematic, alignment	10-14			
	Trimmers, tuner, parts	10-15			
	Schematic, alignment	10-16			
	Socket, trimmers, tuner, parts	10-15			
	Alignment	10-14			
8K Chassis	Schematic, alignment	8-13			
	Socket, trimmers, dial adjustments	8-14			
8KU Chassis	Schematic, socket, trimmers	8-15			
8T	Alignment, dial adjustments	8-16			
8TU	Schematic, socket, trimmers, alignment, tuner	9-14			
X-8	Schematic, socket, trimmers, alignment, tuner	9-15			
	Schematic, voltage, socket, trimmers	7-11			
9G	Alignment, parts	7-12			
11A	Schematic, socket, trimmers, alignment, tuner	9-16			
	Schematic, socket, trimmers, alignment	10-17			
	Alignment	10-14			
	Tuner data, parts	10-18			
	Schematic, layout, notes	10-19			
AW11 Wireless record player					
11S Chassis	Schematic, socket, trimmers, parts	8-17			
	Alignment, notes	8-18			
16R	Electric tuner, data	8-19			
	Schematic	9-17, 18			
16S	Socket, trimmers, alignment, tuner	9-19, 20			
	R-F schematic	10-20			
	Tuner data, parts	10-18			
	Tuner, A.F. and S.P.U. schematic	10-21			
	Socket, trimmers, align, notes, parts	10-22			
T-21 Touch-O-Matic	See Touch-O-Matic, Type T-21				
A-31	Schematic	7-1			
55	Schematic, socket, trimmers, alignment	9-21			
66, 660	Schematic, socket, trimmers, alignment	9-22			
69	Schematic, socket, trimmers, alignment	9-23			
77, 78, 770, 780	Schematic, socket, trimmers, alignment	8-20			
78, 780	Data	Changes 9-1			
86, 880	Schematic, socket, trimmers, alignment	9-24			
137X, 150X, 171X	Schematic, alignment	6-3			
150-5Z, 155-5Z, 985-5Z	Schematic, socket, trimmers, alignment	8-3			
990-5Z, Chassis 5Z					
CONTINENTAL RADIO & TELEVISION CORP.			RADIO-TRON		
Voice of the Road			EARLY COMPLETE		
Schematic			REVIS		
Misc. 3-1			PAGE		
CORONA RADIO AND TELEVISION CORP.			RADIO-TRON		
Schematic, socket			EARLY COMPLETE		
Schematic, alignment			REVIS		
Schematic, socket			PAGE		
Alignment			7-2		
Schematic			9-2		
Schematic, parts			9-3		
Schematic, parts			9-4		
Schematic, parts			8-1		
Schematic			8-2		
CORONADO			RADIO-TRON		
See GAMBLE-SKOGMO, INC.			EARLY COMPLETE		
COURIER			REVIS		
See UNITED REPRODUCERS			PAGE		
CRANE			RADIO-TRON		
Schematic			EARLY COMPLETE		
Misc. 5-6			REVIS		
CROSLEY CORP.			RADIO-TRON		
Schematic			EARLY COMPLETE		
Schematic, socket, chassis wiring			REVIS		
See model 577			PAGE		
See model 601 or 602			1-1		
See models 401 or 401-A			2-7		
See models 5A3 or 5B3 or 527			*219		
See model 4B1			877		
See model 6B1			879		
See model 815					
See model 635					
Schematic, socket, voltage, data			*280		
See model 586			694		
See model 1014					
See model 567					
See model 915					
See model 1055					
See model 715					
See model 615					
See model 617					
See model 617					
See model 1327					
See model 515 or 517					
See model 517					
See model 517					
See model 517					
See model 517					
See model 609 or 610					
See models 709, 704A, 704B					

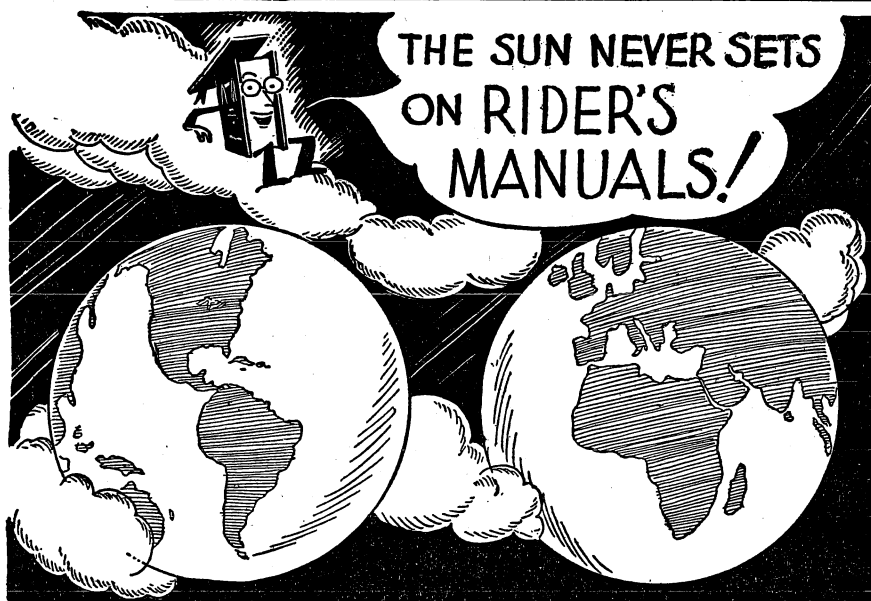

**EVERY MINUTE OF EVERY DAY**

**RIDER'S MANUALS**

**ARE BEING CONSULTED BY SERVICEMEN**  
**TO SOLVE THEIR PROBLEMS**

Over 19,000 pages of servicing information comprise the greatest aid ever made available to servicemen. ¶ In every country RIDER'S MANUALS are recognized as the ONLY source of reliable information. ¶ And this data can be easily and quickly found, for EVERYTHING ON EVERY PAGE of Rider's nine volumes is listed in the revised 200 page Index that is cross-referenced. ¶ The products of hundreds of manufacturers covered in Rider's Manuals make them absolutely essential to every serviceman.



CROSLEY CORP.—(Cont.)			CROSLEY CORP.—(Cont.)			CROSLEY CORP.—(Cont.)			CROSLEY CORP.—(Cont.)		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
Merrimac	See model 855		51, Chassis 502			51, Chassis 502			51, Chassis 502		
Olympia	See model 655		53, 54, 57			53, 54, 57			53, 54, 57		
Prestitone Eleven	See model 1137		55			55			55		
Quiktone Fiver	See model 517		56			56			56		
Roamio	See model A158, A267 or A358		58			58			58		
Roamio (Auto)	See models 90, 95 & 96		59 AO			59 AO			59 AO		
Sampler	See model 201		RFL 60, 75			RFL 60, 75			RFL 60, 75		
Sixer Roamio	See model A168		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Super Six	See model 637		Dual Sixty, Chassis 6V2,			Dual Sixty, Chassis 6V2,			Dual Sixty, Chassis 6V2,		
Super Eight	See model 817		Dual Sixty-LB			Dual Sixty-LB			Dual Sixty-LB		
Super Eleven	See model 1117		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Tridyn	See model 1117		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Tuning Condenser Alignment	Notes, part 1.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Notes, part 2.....	3-2	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Notes, part 3.....	3-3	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Two-step A-F Amplifier	Schematic.....	2-7	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Vanity	See model 418		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
Viking	See model 725		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
20L, Sampler	Schematic, voltage, socket, parts, data.....	6-1	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
3-B, 8-O	Schematic, chassis wiring.....	1-1	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
4-29	Schematic, socket.....	1-2	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
4A1	Schematic, parts list.....	5-17	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
4B1, Battery Forty	Alignment, voltage.....	5-18	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5-38	Schematic, socket, parts.....	6-2	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5A1	Schematic, socket, parts list.....	5-47	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5A3, Battery Fiver	Schematic.....	6-3	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5B3, Battery Fiver	Voltage, parts.....	6-4	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
502 Chassis	Additional data.....	7-15	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5H1 Chassis	Schematic, socket, parts.....	6-5	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5M3 Chassis, Fiver Jr.	See model 51		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5V1 Chassis, Deluxe Fiver, L-B Chassis	See model 50		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
5V2, Fiver Deluxe	Voltage, notes, alignment.....	5-19	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
6B1, Battery Six	Schematic, socket, parts list.....	5-20	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
6H2 Chassis	Voltage, data, parts list.....	5-21	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
6V2 Chassis	Schematic, alignment, socket.....	5-22	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
7-1	Schematic, socket, parts, voltage.....	6-6	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
7-2	Additional data.....	7-15	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
AC-7, AC-70	Schematic, parts, socket.....	6-7	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
AC-7 and 7H3 Chassis	Chassis, trimmers.....	6-8	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
8B1, Battery 8 AF	Voltage, alignment.....	6-9	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
8H1 Chassis	See model 61		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
10	Schematic, socket, parts.....	6-18	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
20, 21, 22	See model Dual Sixty		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
26	Schematic, socket.....	1-3	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
27, 28	Schematic, socket, data.....	2-1	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
30S, 31S, 33S, 34S	Schematic, socket, data.....	2-2	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
32 DC SIX	Voltage.....	2-2	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
38	Schematic, socket, data.....	1-18	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
40S, 41S, 42S, 83S	Schematic.....	1-5	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
41, 41-A, 42	See model 72		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
48	Data.....	7-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
50, 50 LB, Chassis 5H1	Schematic, parts.....	6-10	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
51	Schematic, parts.....	6-10	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
51, Chassis 502	Schematic, socket, voltage, data.....	4-1	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, parts list.....	1-19	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, data.....	2-3	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, data.....	2-4	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, data.....	1-20	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	See model 645		60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic.....	4-1	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, data.....	1-21	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket, voltage, data.....	1-22	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, voltage, socket, notes.....	3-4	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Voltage, data.....	5-23	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Alignment, notes.....	5-24	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, trimmers.....	5-25	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Parts list.....	5-26	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S, 63S, 69S		
	Schematic, socket.....	1-16	60S, 61S, 63S, 69S			60S, 61S, 63S, 69S			60S, 61S		

## CROSLEY

CROSLEY CORP.—(Cont.)			RADIOTRON		
MODEL	REVISI PAGE	EARLY COMPLETE PAGE	MODEL	REVISI PAGE	EARLY COMPLETE PAGE
126-1	2-14	732	A-177	8-5	682
127	2-15	733		8-6	682
127-1	2-16	734	178	5-7	
128	3-11	735	179	5-8	
129	3-12	736	180	5-9	
129-1	3-13	737	181	5-10	
130	3-14	738	182	5-11	
130-1	4-5		183	5-12	
131	4-6	739	184	5-13	
132-1	3-12	740	A258	5-14	
133	3-15	741	A-266	5-15	
134	3-16	742		5-16	
134-1	3-17		A267, Roamio		
135	3-18		A268		
136-1	3-19	743	A358, Roamio		
137	3-20	744	A-366		
141	3-21	745	401 Bandbox Jr.		
148	3-22	746	401-A Bandbox Jr.		
146	4-7		415		
146-1	3-23	747	416		
147	3-24	748	418, Vanity		
148	3-25	749			
150	3-26	750			
152	3-27	751			
154	3-28	752			
156	3-29	753			
A-156	7-1				
157	7-2	754			
A-157, Fiver Roamio	3-30				
158	3-31	755			
A158, A258 Roamio	3-31				
159	3-32	756			
160	3-33	757			
161	3-34				
163	3-35				
164	3-36				
166	3-37				
A-166	3-38				
167, Series 2	3-39				
A-167	3-40				
168	3-41				
A168, A268, Sixer Roamio	3-42				
169	3-43				
169, Revised	3-44				
170	3-45				
171	3-46				
172	3-47				
173, 173-5	3-48				
174	3-49				
175	3-50				
176	3-51				



# CROSLEY DAY FAN

CROSLEY RADIO CORP.—(Cont.)			RADIOTRON	
MODEL			EARLY COMPLETE PAGE	REVISI PAGE
716	Trimmers, chassis, alignment, parts	8-30		
718	Schematic, parts	8-46		
	Socket, trimmers, voltage, chassis, data	10-21		
725, Viking	Alignment, drive data	10-22		
	Schematic, voltage	7-45		
	Socket, trimmers, chassis, parts, alignment	7-46		
726	Schematic, voltage	8-31		
	Socket, trimmers, chassis, alignment, parts	8-32		
736	Schematic, voltage	8-33		
	Socket, trimmers, alignment, chassis, parts	8-34		
758	Schematic, socket, trimmers, chassis	10-23		
804	Schematic, socket, voltage, chassis	1-15		
814	Schematic, socket, parts	6-25		
815	Data	Changes 7-13		
815, Battery 8	Schematic	7-47		
	Socket, trimmers, chassis, parts, alignment, voltage	7-48		
816	Schematic, parts	7-49		
	Socket, trimmers, voltage, chassis, alignment	7-50		
817, Super Eight	Schematic, socket	9-43		
	Voltage, socket, trimmers, layout	9-44		
	Alignment, phonograph data, parts	9-45		
818	Schematic	10-25		
	Socket, trimmers, chassis, voltage, phono	10-24		
	Alignment, notes, parts	10-26		
828	Schematic, phono	10-27		
	Chassis, parts	10-28		
	Socket, trimmers, voltage, alignment, drive data	10-29		
855, Merrimac	Schematic, voltage, socket	7-51		
	Socket, trimmers, chassis, parts, alignment	7-52		
865	Schematic, voltage	7-53		
	Socket, trimmers, chassis, parts, alignment	7-54		
915, Clipper	Schematic, voltage	7-55		
	Socket, trimmers, chassis, phono	7-56		
916	Alignment, parts	7-57		
	Schematic, parts	7-59		
	Socket, trimmers, chassis, voltage, alignment	7-60		
926	Schematic, socket, voltage	8-35		
	Trimmers, alignment, parts	8-36		
955	Schematic, parts	7-61		
	Socket, trimmers, chassis, voltage, alignment	7-62		
1014, Centurion	Schematic, socket, parts	6-26		
	Chassis, trimmers, voltage, data	6-27		
1016	Alignment, data	6-28		
	Schematic, socket	7-63		
	Alignment, voltage, parts	7-65		
1018	Socket, trimmers, chassis, phono	7-64		
	Schematic, notes	7-64		
	Voltage, alignment, drive data, notes, tuner	10-31		
1026	Socket, trimmers, parts	10-30		
	Schematic, socket	10-32		
	Parts	8-37		
	Socket, trimmers, voltage, chassis, resonance curves, phono, pick-up	8-39		
1055, Constitution	Alignment, notes	8-40		
	Schematic	7-67		
	Socket, trimmers, chassis, voltage	7-66		
1117 (Early) Super Eleven	Alignment, parts	7-65		
	Schematic, socket	9-47		
	Trimmers, chassis, alignment, parts	9-48		
	Socket, trimmers, layout, voltage, phono, graph data, transformer	9-49		
1117 (Late) Super Eleven	Schematic, socket	9-48		
1117 Early and late	Alignment, changes, data	9-49		
1118, 1128	Socket, trimmers, layout, voltage, phono, graph data, transformer	9-50		
	Schematic	10-33		
	Parts list	10-34		
	Alignment, tuner, notes, drive data	10-35		
	Voltage, socket, trimmers, chassis, drive data	10-36		
1126	Schematic, socket, notes	8-41		
	Parts, notes	8-42		
	Socket, trimmers, voltage, resonance curves, phono, pick-up, data	8-43		
	Alignment, notes	8-44		
	Schematic, socket	9-51		
1127, Dynatrol Eleven	Socket, trimmers, voltage, layout	9-52		
	Motor assembly, transformer data, phonograph data	9-53		
	Alignment, data, parts	9-54		
1128	See model 1118			
1137, Prestotune Eleven	Schematic, socket	9-55		
	Socket, trimmers, voltage, layout	9-56		
	Motor assembly, tuner, phonograph data, transformer	9-57		
1155	Alignment, tuner, parts	9-58		
	Schematic	7-69		
1216	Socket, trimmers	7-70		
	Voltage, parts, alignment	7-71		
	Schematic, socket	8-45		
	Parts	8-46		
	Socket, trimmers, voltage, resonance curves, pick-up	8-47		
1217, 1227	Alignment, notes	8-48		
	Schematic	10-37		
	Tuner, parts list	10-38		
	Socket, trimmers, chassis, drive data, phono	10-39		
1316	Voltage, alignment, notes	10-40		
	Schematic	7-73		
	Voltage, trimmers, socket, chassis	7-72		
1386	Alignment, parts	7-74		
	Schematic, socket	8-49		
	Parts	8-50		
	Socket, trimmers, chassis, voltage, resonance curves, phono, pick-up, notes	8-51		
1516	Alignment, notes	8-52		
	Schematic, socket	8-53		
	Parts, notes	8-54		
	Socket, trimmers, chassis, voltage, resonance curves, phono, pick-up, notes	8-55		
5515	Alignment, notes	8-56		
5516	See model 515			
5517	See model 516			
5526	See model 517			
5536	See model 526			
5538	See model 536			
5548	See model 548			
5555	See model 555			
5628	See model 628			
5656	See model 656			
5666	See model 666			
6516	See model 516			
6615	Schematic, parts	7-75		
6695	Socket, chassis, trimmers, voltage, alignment	7-76		
	Schematic	7-77		
	Socket, chassis, trimmers, parts, alignment, voltage	7-78		

DAY FAN ELECTRIC CO.  
See GENERAL MOTORS RADIO CORP.



MODEL	DAYRAD	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON	DETROLA RADIO & TELEVISION CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
	See RADIO PRODUCTS CO.							
	DeFOREST RADIO CORP.							
F-5	Schematic	Misc. 1-3	*240	763	102M	Schematic	7-4	
CS-5	Schematic	Misc. 1-3	*240	763	48	Alignment	7-5	
D-10	Schematic	Misc. 1-3	*240	763	100	Schematic, socket	6-1	
D-17	Schematic	Misc. 1-3	*240	763	101	Schematic, socket	7-6	
					101-A	Schematic, socket	7-7	
					102	Schematic, socket	7-8	
					103	Schematic, socket	7-9	
					104	Schematic, socket	7-1	
					106	Schematic, socket	7-6	
RB-B, RA-B	Schematic	8-1	767		106-E	Schematic, socket	7-10	
	Voltage, color codes	8-2	768		108	Schematic, socket	7-10	
RB-1, RC-1	Schematic	8-3	770		109	Schematic, socket	7-11	
	Voltage, color codes	8-4	771		111	Schematic, socket	8-1	
RB-9, RA-8	Schematic, voltage, color code, notes	8-5	769		114	Schematic, socket	7-12	
		8-8			116	Schematic, socket	7-11	
					117B	Schematic, socket, alignment, parts	8-2	
					120	Schematic, socket	7-1	
					121	Schematic, socket	7-1	
					130	Schematic, notes	8-3	
3002	Schematic, socket, chassis wiring, voltage	1-1	*843	765	134A, 134AR, 134AZ	Schematic, socket	8-4	
	Chassis layout, control wiring, data	1-2	*843	766	134X	Schematic, socket	8-3	
3026	Schematic	1-3			135, 135E	Schematic, socket, trimmers, alignment	8-4	
	Socket layout, cable data	4-1			136, 149, 149E	Schematic, socket, trimmers, alignment	8-5	
	Terminal data	4-4			137	Schematic, socket, parts	8-6	
	Control drive data	4-5			139, 139E	Schematic, socket	8-7	
	Values, resistance, plug data	4-6			140	Schematic, socket, parts	8-8	
	Values, changes	4-7			141A	Schematic, socket	8-3	
3026 below serial #1400	Chassis layout	4-8			144B, 144C	Schematic, socket, alignment, trimmers, parts	8-9	
3026 above serial #1400	Chassis layout	4-3			145B, 145CR	Schematic, socket, trimmers, alignment, parts	8-10	
		4-8			146	Schematic, socket	8-11	
					147, 147E, 147EOR	Schematic, socket, trimmers, alignment, parts	8-12	
					147A, 147B, 147OR	Schematic, socket	8-7	
					148	Schematic, socket, parts	8-13	
					149, 149E	See model 136		
					150	Schematic, socket, notes	8-14	
					154E	Schematic, socket, trimmers, alignment, parts	8-15	
					155X	Schematic, parts	8-16	
					157A	Socket, trimmers, alignment	8-17	
					158A	Schematic, socket	8-3	
					159	Schematic, socket	8-11	
					162	Schematic, socket	8-11	
					162A	Schematic, socket	8-19	
					163	Schematic, parts	8-18	
					165	Socket, trimmers, alignment	8-17	
					166	Schematic, trimmers, parts	8-21	
					167	Alignment, socket, trimmers, alignment, parts	8-22	
					168	Schematic, socket, trimmers, alignment, parts	8-20	
					169	Schematic, socket	8-23	
					172	Schematic, socket, trimmers, alignment, parts	8-19	
					172 Series (T1, C1), 190, 192 Series (T2, T3), 195 Series (C4)	Schematic, socket, trimmers, alignment, parts	8-19	
					176	Schematic, socket	9-1	
					178	Schematic, socket	9-2	
					183	Schematic, socket, trimmers, alignment, parts	9-3	
					184 Series	Tuner data, alignment	9-5	
					190, 193	Schematic, socket, alignment	9-3	
					192 Series (C3)	See model 175		
					195 Series	Schematic, socket, trimmers, parts	9-6	
					197, Pee-wee	Tuner data, alignment	9-7	
					204	Schematic, socket	9-3	
					206	Schematic, socket, trimmers, tuner, parts	9-8	
						Alignment	9-2	
						Schematic, socket, trimmers	9-9	

DE SOTO  
See PHILCO RADIO & TELEVISION CORP.

DETROLA RADIO & TELEVISION CORP.

E = Tuning Eye (Other letters indicate cabinet styles)

Detrola Jr. Pee-wee	See model 216, 280
Pee-wee	See model 197, 218
Roadchief	Schematic
Roadmaster	Schematic
	I-F. peak
Super Pee-wee	Changes 7-8
Warwick	See model 219, 276U, 284
4-Tube TRF '92	Schematic, socket
5-Tube Super. Midget	Schematic
4C	Schematic
4D	Schematic, socket
4F	Schematic, socket
4H	Schematic, socket
4J	Schematic, socket
4W	Schematic, socket
4Y	Schematic, socket
5B	Schematic, voltage, socket, data
5D	Alignment, parts
5L	Schematic, voltage, socket, data
5W	Alignment, parts
5WG	Schematic, socket
5X	Schematic, voltage, parts
6A	Alignment
6M, 6E	Schematic, socket
6W	Schematic, voltage, alignment
6X	Installation data, voltage, parts, alignment
6ZM	Schematic, voltage, parts
7A	Alignment
7ZM	Schematic, voltage, parts

DETROLA RADIO & TELEVISION CORP.--(Cont.) REVISED  
PAGE

DEWALD RADIO

DEWALD RADIO—(Cont.)			RADIOTRON		
MODEL	REVISED PAGE	EARLY COMPLETE PAGE	MODEL	REVISED PAGE	EARLY COMPLETE PAGE
527	Schematic, socket, chassis, in-stallation, notes .....	8-5	811-A	Schematic .....	5-18
528, 528LW	Schematic, notes .....	8-6	1002, 1003	Socket layout. See model BAH-9	9-9
529, 529LW	Schematic, alignment .....	8-7	1004	Schematic, alignment, parts .....	9-8
530, 530LW	Schematic, alignment .....	9-2	1100, Early	Data .....	10-2
531, 531LW	Schematic .....	10-3	1100, Late	Schematic, data .....	7-11
532, 532LW	Schematic .....	10-3	1102-3	Schematic, socket, trimmers, alignment .....	7-12
533, 533LW	Schematic .....	10-3	1104, 1105	Schematic, socket, trimmers .....	10-6
534, 534LW	Schematic, alignment .....	9-2	1106	Alignment, parts .....	9-1
535, 535LW	Schematic, alignment .....	9-2	1200	Data .....	10-1
536, 536LW	Schematic, notes .....	10-4	1201	Schematic .....	8-6
537, 537LW	Schematic .....	10-4		Schematic, alignment .....	9-8
538LW, 538	Schematic .....	2-6			
539LW, 539	Schematic .....	2-7			
540LW, 540	Schematic .....	2-7			
541LW, 541	Schematic .....	2-7			
542LW, 542	Schematic .....	2-7			
543LW, 543	Schematic .....	2-7			
544LW, 544	Schematic .....	2-7			
545LW, 545	Schematic .....	2-7			
546LW, 546	Schematic .....	2-7			
547LW, 547	Schematic .....	2-7			
548LW, 548	Schematic .....	2-7			
549LW, 549	Schematic .....	2-7			
550LW, 550	Schematic .....	2-7			
551LW, 551	Schematic .....	2-7			
552LW, 552	Schematic .....	2-7			
553LW, 553	Schematic .....	2-7			
554LW, 554	Schematic .....	2-7			
555LW, 555	Schematic .....	2-7			
556LW, 556	Schematic .....	2-7			
557LW, 557	Schematic .....	2-7			
558LW, 558	Schematic .....	2-7			
559LW, 559	Schematic .....	2-7			
560LW, 560	Schematic .....	2-7			
561LW, 561	Schematic .....	2-7			
562LW, 562	Schematic .....	2-7			
563LW, 563	Schematic .....	2-7			
564LW, 564	Schematic .....	2-7			
565LW, 565	Schematic .....	2-7			
566LW, 566	Schematic .....	2-7			
567LW, 567	Schematic .....	2-7			
568LW, 568	Schematic .....	2-7			
569LW, 569	Schematic .....	2-7			
570LW, 570	Schematic .....	2-7			
571LW, 571	Schematic .....	2-7			
572LW, 572	Schematic .....	2-7			
573LW, 573	Schematic .....	2-7			
574LW, 574	Schematic .....	2-7			
575LW, 575	Schematic .....	2-7			
576LW, 576	Schematic .....	2-7			
577LW, 577	Schematic .....	2-7			
578LW, 578	Schematic .....	2-7			
579LW, 579	Schematic .....	2-7			
580LW, 580	Schematic .....	2-7			
581LW, 581	Schematic .....	2-7			
582LW, 582	Schematic .....	2-7			
583LW, 583	Schematic .....	2-7			
584LW, 584	Schematic .....	2-7			
585LW, 585	Schematic .....	2-7			
586LW, 586	Schematic .....	2-7			
587LW, 587	Schematic .....	2-7			
588LW, 588	Schematic .....	2-7			
589LW, 589	Schematic .....	2-7			
590LW, 590	Schematic .....	2-7			
591LW, 591	Schematic .....	2-7			
592LW, 592	Schematic .....	2-7			
593LW, 593	Schematic .....	2-7			
594LW, 594	Schematic .....	2-7			
595LW, 595	Schematic .....	2-7			



See model CA208  
See model CB243  
See model CD206  
See model CE259  
See model CF255  
See model CG211  
See model CH243  
See model CI246  
See model CLW134  
See model CM260  
See model CR261  
Schematic, socket, voltage.....8-4  
See model CT375  
See model D134  
See model D134LW  
See model E138  
See model E128

See P. R. MALLOY & CO.

**EL-REY RADIO MFG. CO.**

CR	Control	See model
CS	Chassis	See model
CT	Chassis	See model
D	Chassis	See model
DLW	Chassis	See model
E	Chassis	See model
E	Chassis	See model
F	Chassis	See model
G	Chassis	See model
H	Chassis	See model
I	Chassis	See model
J	Chassis	See model
K	Chassis	See model
L	Chassis	See model
M	Chassis	See model
N	Chassis	See model
O	Chassis	See model
P	Chassis	See model
Q	Chassis	See model
R	Chassis	See model
S	Chassis	See model
T	Chassis	See model
U	Chassis	See model
V	Chassis	See model
W	Chassis	See model
X	Chassis	See model
Y	Chassis	See model
Z	Chassis	See model
AA	Chassis	See model
AB	Chassis	See model
AC	Chassis	See model
AD	Chassis	See model
AE	Chassis	See model
AF	Chassis	See model
AG	Chassis	See model
AH	Chassis	See model
AI	Chassis	See model
AJ	Chassis	See model
AK	Chassis	See model
AL	Chassis	See model
AM	Chassis	See model
AN	Chassis	See model
AO	Chassis	See model
AP	Chassis	See model
AQ	Chassis	See model
AR	Chassis	See model
AS	Chassis	See model
AT	Chassis	See model
AU	Chassis	See model
AV	Chassis	See model
AW	Chassis	See model
AX	Chassis	See model
AY	Chassis	See model
AZ	Chassis	See model
BA	Chassis	See model
BB	Chassis	See model
BC	Chassis	See model
BD	Chassis	See model
BE	Chassis	See model
BF	Chassis	See model
BG	Chassis	See model
BH	Chassis	See model
BI	Chassis	See model
BJ	Chassis	See model
BK	Chassis	See model
BL	Chassis	See model
BM	Chassis	See model
BN	Chassis	See model
BO	Chassis	See model
BP	Chassis	See model
BQ	Chassis	See model
BR	Chassis	See model
BS	Chassis	See model
BT	Chassis	See model
BU	Chassis	See model
BV	Chassis	See model
BW	Chassis	See model
BX	Chassis	See model
BY	Chassis	See model
BZ	Chassis	See model
CA	Chassis	See model
CB	Chassis	See model
CC	Chassis	See model
CD	Chassis	See model
CE	Chassis	See model
CF	Chassis	See model
CG	Chassis	See model
CH	Chassis	See model
CI	Chassis	See model
CJ	Chassis	See model
CK	Chassis	See model
CL	Chassis	See model
CM	Chassis	See model
CN	Chassis	See model
CO	Chassis	See model
CP	Chassis	See model
CQ	Chassis	See model
CR	Chassis	See model
CS	Chassis	See model
CT	Chassis	See model
CU	Chassis	See model
CV	Chassis	See model
CW	Chassis	See model
CX	Chassis	See model
CY	Chassis	See model
CZ	Chassis	See model
DA	Chassis	See model
DB	Chassis	See model
DC	Chassis	See model
DD	Chassis	See model
DE	Chassis	See model
DF	Chassis	See model
DG	Chassis	See model
DH	Chassis	See model
DI	Chassis	See model
DJ	Chassis	See model
DK	Chassis	See model
DL	Chassis	See model
DM	Chassis	See model
DN	Chassis	See model
DO	Chassis	See model
DP	Chassis	See model
DQ	Chassis	See model
DR	Chassis	See model
DS	Chassis	See model
DT	Chassis	See model
DU	Chassis	See model
DV	Chassis	See model
DW	Chassis	See model
DX	Chassis	See model
DY	Chassis	See model
DZ	Chassis	See model
EA	Chassis	See model
EB	Chassis	See model
EC	Chassis	See model
ED	Chassis	See model
EE	Chassis	See model

**EMERSON RADIO & PHONOGRAPH CORP.**

See model F117	See model, socket.....8-8
See model G127	Schematic, voltage, socket.....8-3
See model G130	Schematic, socket, voltage.....8-3
See model J106	See model L143 or L117
Schematic, voltage, socket.....8-8	See model L171W
See model K116	See model M134
Schematic, socket, voltage.....8-3	See model P117
See model L143 or L117	See model Q157
See model L171W	See model R152 Early
See model M134	See K152 Late
See model P117	See model S147
See model Q157	Schematic, voltage, socket.....3-2
See model R152 Early	Schematic, voltage, socket.....3-2
See K152 Late	See model U154
See model S147	See model V195
Schematic, voltage, socket.....3-2	See model X116
Schematic, voltage, socket.....3-2	See model X175
See model U154	See model Z117
See model V195	
See model X116	
See model X175	
See model Z117	

A4 Chassis	See model 409	
4B Chassis	See model 23	
G4 Chassis	See model 20A	
L-A-C-4	Schematic, socket, voltage.....	3-1
L-DC-4	Schematic, voltage, socket.....	3-2
U4A Chassis	See model 109	
U4B Chassis	See model 118	
U4C Chassis	See model 409	
UV4	See model 19	
V4	See model 420	
5A	Schematic.....	6-1
B5 Chassis	Alignment, voltage.....	6-2
C5 Chassis	See model 86	
DS-5 Chassis	See model 117	
E5 Chassis	See model 89	
F5 Chassis	See model 107A-C	
G5 Chassis	See model 108	
Chassis H-5	See model 116	
Chassis H-5-L	See model 80	
K5 Chassis	Schematic.....	4-5
L5 Chassis	See model 28	
M5 Chassis	See model 117LW	
N5 Chassis	Schematic, voltage, socket.....	3-1
U5A Chassis	See model 108	
U5B Chassis	See model 108LW	
U5C Chassis	See model 32	
U5S Chassis	Schematic, voltage.....	6-1
6-A	Alignment.....	6-2
6BD Chassis	See model 45	
C6, D6 Chassis	See model 84C	
F6B Chassis	See model 280	
T6 Chassis	See model 85	
U6, U6D Chassis	See model 98	
U6A Chassis	See model 107	
U6A Chassis, Revised	See model 119	
U6B Chassis	See model 106	
U6C Chassis	See model 107LW	
U6D Chassis	See model U6	
U6F Chassis	See model 107	









EMERSON RADIO & PHONOGRAPH CORP.—(Cont.)	REVISÉD PAGE	EARLY COMPLETE PAGE	RADIO TRON
MODEL	REVISED PAGE	EARLY COMPLETE PAGE	
See model BN206	9-48		
See model OD206	9-48		
Schematic	9-48		
Voltage, alignment, parts	9-47		
Schematic, voltage, alignment	9-50		
See model AX311	9-50		
Schematic, voltage, parts	9-53		
Alignment, tuner, notes	9-54		
Schematic, voltage, changes	10-7		
Schematic, voltage, changes	10-8		
Schematic, voltage, changes	10-9		
Alignment, notes, parts	10-10		
Schematic, voltage, changes	10-11		
Tuner data	10-12		
Schematic, notes	10-13		
Alignment, voltage	10-12		
Record changer data	10-14		
Record changer adjustments	10-15		
Record changer, diagrams	10-16		
Schematic, voltage	9-55		
Alignment, tuner, parts	9-56		
See model BQ225			
See model BQ225			
See model BQ225			
Schematic	9-48		
Alignment, voltage, notes	9-49		
See model AX211			
See model AX238, AX237, AX235, AX234, AX233, AX2, AX1			
See model BN206	9-48		
See model OD206	9-48		
Schematic	9-48		
Voltage, alignment, parts	9-47		
Schematic, voltage, alignment	9-50		
See model AX311	9-50		
Schematic, voltage, parts	9-53		
Alignment, tuner, notes	9-54		
Schematic, voltage, changes	10-7		
Schematic, voltage, changes	10-8		
Schematic, voltage, changes	10-9		
Alignment, notes, parts	10-10		
Schematic, voltage, changes	10-11		
Tuner data	10-12		
Schematic, notes	10-13		
Alignment, voltage	10-12		
Record changer data	10-14		
Record changer adjustments	10-15		
Record changer, diagrams	10-16		
Schematic, voltage	9-55		
Alignment, tuner, parts	9-56		
See model BQ225			
See model BQ225			
See model BQ225			
Schematic	9-48		
Alignment, voltage, notes	9-49		
See model AX211			
See model AX238, AX237, AX235, AX234, AX233, AX2, AX1			
See model BN206	9-48		
See model OD206			

FADA RADIO & ELECTRIC CORP.				RADIO/IRON		FADA RADIO & ELECTRIC CORP.—(Cont.)		RADIO/IRON	
MODEL	REVISION	EARLY	REVISION	MODEL	REVISION	EARLY	REVISION	MODEL	REVISION
	PAGE	PAGE	PAGE		PAGE	PAGE	PAGE		PAGE
O Electric unit	.....1-7	905	.....5-1	35-B	.....1-17	82	.....2-3	35-B	.....1-17
S, 26-36	.....1-7	905	.....5-1	40	.....1-19	88	.....2-4	40	.....1-19
KA Chassis	.....1-7	905	.....5-1	41, 42, 44, 46, 47 (KA)	.....1-20	84	.....2-5	41, 42, 44, 46, 47 (KA)	.....1-20
KB Chassis	.....1-7	905	.....5-1	43, 52 (KF); 761, 762, 764, 766 (KG)	.....1-21	84-A	.....2-5	43, 52 (KF); 761, 762, 764, 766 (KG)	.....1-21
KE Chassis	.....1-7	905	.....5-1	45, 45Z (KU)	.....3-2		.....3-2	45, 45Z (KU)	.....3-2
KF Chassis	.....1-7	905	.....5-1	45, 48, 49	.....3-1		.....3-1	45, 48, 49	.....3-1
KG Chassis	.....1-7	905	.....5-1	SF 45-76	.....3-3		.....3-3	SF 45-76	.....3-3
KH Chassis	.....1-7	905	.....5-1	46, 47	.....3-3		.....3-3	46, 47	.....3-3
KI Chassis	.....1-7	905	.....5-1	S46	.....3-3		.....3-3	S46	.....3-3
KJ Chassis	.....1-7	905	.....5-1	48, 49 (KW)	.....3-3		.....3-3	48, 49 (KW)	.....3-3
KK Chassis	.....1-7	905	.....5-1	48, 49, 65 (KW)	.....3-3		.....3-3	48, 49, 65 (KW)	.....3-3
KL Chassis	.....1-7	905	.....5-1	B49, C49, T49	.....3-3		.....3-3	B49, C49, T49	.....3-3
KM Chassis	.....1-7	905	.....5-1	P49	.....3-3		.....3-3	P49	.....3-3
KN Chassis	.....1-7	905	.....5-1	50, 70, 71, 72	.....3-3		.....3-3	50, 70, 71, 72	.....3-3
KO Chassis	.....1-7	905	.....5-1	SF 50-80B	.....3-3		.....3-3	SF 50-80B	.....3-3
KP Chassis	.....1-7	905	.....5-1	E-180, E-180Z units for	.....3-3		.....3-3	E-180, E-180Z units for	.....3-3
KQ Chassis	.....1-7	905	.....5-1	50, 70, 71, 72	.....3-3		.....3-3	50, 70, 71, 72	.....3-3
KR Chassis	.....1-7	905	.....5-1	E-420, E-420Z units for	.....3-3		.....3-3	E-420, E-420Z units for	.....3-3
KS Chassis	.....1-7	905	.....5-1	50, 70, 71, 72	.....3-3		.....3-3	50, 70, 71, 72	.....3-3
KT Chassis	.....1-7	905	.....5-1	SF 50-80	.....3-3		.....3-3	SF 50-80	.....3-3
KU Chassis	.....1-7	905	.....5-1	51 (KO), 53, 57 (KOO)	.....3-3		.....3-3	51 (KO), 53, 57 (KOO)	.....3-3
KV Chassis	.....1-7	905	.....5-1	54	.....3-3		.....3-3	54	.....3-3
KW Chassis	.....1-7	905	.....5-1	F55	.....3-3		.....3-3	F55	.....3-3
KX Chassis	.....1-7	905	.....5-1	55 (RG)	.....3-3		.....3-3	55 (RG)	.....3-3
KY Chassis	.....1-7	905	.....5-1	59	.....3-3		.....3-3	59	.....3-3
NA Chassis	.....1-7	905	.....5-1	60	.....3-3		.....3-3	60	.....3-3
NE Chassis	.....1-7	905	.....5-1	R-60 Unit	.....3-3		.....3-3	R-60 Unit	.....3-3
NF Chassis	.....1-7	905	.....5-1	61, 66 (KX)	.....3-3		.....3-3	61, 66 (KX)	.....3-3
NK Chassis	.....1-7	905	.....5-1	62-R, 66-Q, ABO SPU	.....3-3		.....3-3	62-R, 66-Q, ABO SPU	.....3-3
NL Chassis	.....1-7	905	.....5-1	65	.....3-3		.....3-3	65	.....3-3
NO Chassis	.....1-7	905	.....5-1	66 (KY) Early	.....3-3		.....3-3	66 (KY) Early	.....3-3
NP Chassis	.....1-7	905	.....5-1	66 (KY) Late	.....3-3		.....3-3	66 (KY) Late	.....3-3
NQ Chassis	.....1-7	905	.....5-1	70, 70Z, 71	.....3-3		.....3-3	70, 70Z, 71	.....3-3
NR Chassis	.....1-7	905	.....5-1	73, 85 (RE)	.....3-3		.....3-3	73, 85 (RE)	.....3-3
NS Chassis	.....1-7	905	.....5-1	74, 76, 88, 89 (RA)	.....3-3		.....3-3	74, 76, 88, 89 (RA)	.....3-3
NT Chassis	.....1-7	905	.....5-1	75, 77	.....3-3		.....3-3	75, 77	.....3-3
NU Chassis	.....1-7	905	.....5-1	78, 79 (RO)	.....3-3		.....3-3	78, 79 (RO)	.....3-3
NV Chassis	.....1-7	905	.....5-1	78-10, 79-10	.....3-3		.....3-3	78-10, 79-10	.....3-3
NW Chassis	.....1-7	905	.....5-1	R-80A Unit, 480-A	.....3-3		.....3-3	R-80A Unit, 480-A	.....3-3
NX Chassis	.....1-7	905	.....5-1	SF 50-80 A, DC (KB)	.....3-3		.....3-3	SF 50-80 A, DC (KB)	.....3-3
NY Chassis	.....1-7	905	.....5-1	81, 82, 84, 86 DC (KB)	.....3-3		.....3-3	81, 82, 84, 86 DC (KB)	.....3-3
OA Chassis	.....1-7	905	.....5-1	82W, 86W ABO SPU	.....3-3		.....3-3	82W, 86W ABO SPU	.....3-3
OB Chassis	.....1-7	905	.....5-1	83, 88, 89	.....3-3		.....3-3	83, 88, 89	.....3-3
OC Chassis	.....1-7	905	.....5-1	85 (RE)	.....3-3		.....3-3	85 (RE)	.....3-3
OD Chassis	.....1-7	905	.....5-1	97-10	.....3-3		.....3-3	97-10	.....3-3
OE Chassis	.....1-7	905	.....5-1	101 (RK) Motocet	.....3-3		.....3-3	101 (RK) Motocet	.....3-3
OF Chassis	.....1-7	905	.....5-1	102 (RP)	.....3-3		.....3-3	102 (RP)	.....3-3
OG Chassis	.....1-7	905	.....5-1	103 (RL) Fadalette	.....3-3		.....3-3	103 (RL) Fadalette	.....3-3
OH Chassis	.....1-7	905	.....5-1	104-B (RV) Auto	.....3-3		.....3-3	104-B (RV) Auto	.....3-3
OI Chassis	.....1-7	905	.....5-1	105, 106, 107 (RN)	.....3-3		.....3-3	105, 106, 107 (RN)	.....3-3
OJ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OK Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OL Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OM Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
ON Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OO Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OP Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OQ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OR Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OS Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OT Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OU Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OV Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OW Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OX Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OY Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OA Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OB Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OC Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OD Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OE Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OF Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OG Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OH Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OI Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OJ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OK Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OL Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OM Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
ON Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OO Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OP Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OQ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OR Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OS Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OT Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OU Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OV Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OW Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OX Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OY Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OA Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OB Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OC Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OD Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OE Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OF Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OG Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OH Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OI Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OJ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OK Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OL Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OM Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
ON Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OO Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OP Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OQ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OR Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OS Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OT Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OU Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OV Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OW Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OX Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OY Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OA Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OB Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OC Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OD Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OE Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OF Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OG Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OH Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OI Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OJ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OK Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OL Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OM Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
ON Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OO Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OP Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OQ Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OR Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OS Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OT Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OU Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OV Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OW Chassis	.....1-7	905	.....5-1		.....3-3		.....3-3		.....3-3
OX Chassis	.....1-7	905	.....5-1						

FADA RADIO & ELECTRIC CORP.—(Cont.)			REVISED	RADIOTRON	
MODEL		PAGE	PAGE	EARLY COMPLETE	PAGE
105, 106, 107 (RN)	Voltage, point-to-point data	4-9			
108, 109, 125 (RY)	Socket layout	4-10			
110, 111 (RS)	Schematic	4-11			
112 (KE)	Socket layout	4-11			
122, 127, 128, Chassis NK	Schematic, socket	4-11			
131, 132 (RU)	Schematic	4-12			
133, 134, 135, 78-10, 79-10, 97-10 (RW)	Alignment notes	4-13			
141 (NA)	Schematic	4-14			
141A, 141Z (NA)	Alignment, trimmers, socket	5-8			
150, 2 types	Schematic, trimmers, voltage, socket	5-4			
151, 152 (NE)	Schematic	6-1			
155	Alignment, trimmers, socket, voltage	6-2			
156	Socket layout	6-3			
157	Schematic, socket, trimmers	6-3			
160 Series	Alignment, voltage	6-4			
160 Neutrodyne Reflex	Schematic	6-5			
166, Motostat	Schematic	6-6			
167	Socket, trimmers, alignment, voltage	6-7			
168	Schematic	6-8			
170	Schematic	6-9			
171, 173 (KOO) 110-volt DO	Alignment, socket, trimmers, data	6-10			
180	Schematic, changes, parts	7-1			
181	Schematic, parts list	7-2			
182	Schematic	6-11			
183	Socket, trimmers, alignment, voltage	6-12			
184	Schematic	6-19			
185	See model 50				
186	Schematic	6-13			
187	Socket, trimmers, alignment	6-14			
188	Schematic, parts	6-15			
189	Alignment, part 2, voltage	6-17			
190	Schematic				
191	Socket, trimmers, alignment, voltage	6-18			
192	Schematic, chassis wiring, data	1-28			
193A (193S, 192BS units)	Schematic, voltage, parts	7-3			
211	Alignment, changes, socket, trimmers	8-1			
211A, 220 volts	Schematic, parts	8-2			
211B, 220 volts	Schematic, voltage, parts	8-3			
212	Schematic, socket, trimmers	8-4			
216, Early, Late	Alignment, socket, trimmers	8-5			
216, 3rd Production	Alignment, socket, trimmers	8-8			
216, 220 volts, Early, Late	Schematic, parts	8-6			
222	Alignment, socket, trimmers	8-7			
224	Schematic, parts	8-8			
226	Alignment, socket, trimmers	8-9			
M-250, M-250Z Units	Schematic, parts	8-10			
250, 2 types, Early, up to Serial 50698, Late, from Serial 50699	Alignment, socket, trimmers	8-11			
	See model 25				
	Schematic, parts list	7-4			
254	Socket, trimmers, voltage, alignment	9-2			
255	Schematic, voltage, socket, trimmers, alignment	8-12			
260	Schematic, parts	8-13			
261	Alignment, voltage, socket, trimmers	7-5			
262	Schematic, parts	7-6			
263	Schematic, parts list	8-14			
264	Schematic, parts list	7-7			
265	Schematic, parts	8-15			
266	Schematic, parts	8-16			
267	Schematic, parts	8-17			
268	Schematic, parts	8-18			
269	Schematic, parts	8-19			
270	Schematic, parts	8-20			
271	Schematic, parts	8-21			
272	Schematic, parts	8-22			
273	Schematic, parts	8-23			
274	Schematic, parts	8-24			
275	Schematic, parts	8-25			
276	Schematic, parts	8-26			
277	Schematic, parts	8-27			
278	Schematic, parts	8-28			
279	Schematic, parts	8-29			
280	Schematic, parts	8-30			
281	Schematic, parts	8-31			
282	Schematic, parts	8-32			
283	Schematic, parts	8-33			</

# FADA FAIRBANKS

FADA RADIO & ELECTRIC CORP.—(Cont.)				RADIOTRON	
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
475-A, SF 45-75	Schematic, socket, data	1-2	900		
480-A	See model R-80A				
480-B, SF 50-80-B	Schematic, socket	1-4	902		
490	Schematic	10-18			
554	See model 6A54				
761, 762, 764, 766, 767 (KG)	See model 43				
1255	Schematic, socket, trimmers, alignment, parts	8-26			
1262	Schematic, socket, trimmers, alignment, parts	8-27			
1265	Schematic, socket, trimmers, alignment, parts	8-28			
1462, 2 types	Schematic	6-19			
	Socket, trimmers, alignment, voltage	6-20			
	Schematic, parts	7-19			
1462, Revised, above					
Serial 22102	Schematic, parts list	7-20			
1463	Schematic	6-21			
1556	Schematic	6-22			
1582	Schematic	6-16			
1583	Schematic				
FAIRBANKS MORSE & CO.					
4A, 4B	Schematic, notes	9-1			
	Socket, trimmers, alignment, voltage, resistance	9-2			
5A	Parts list	9-3			
	Schematic, socket, trimmers	9-3			
	Parts list	9-4			
	Alignment, voltage, resistance	9-4			
	Data	Changes 10-2			
5B	Schematic, socket, trimmers	9-7			
	Alignment, voltage, resistance	9-8			
	Parts list	9-9			
50, 6A	Schematic, socket, trimmers, color code	8-1			
	Alignment, voltage, resistance	8-2			
5D	Schematic, battery connections	8-3			
6A	Alignment, socket, trimmers	8-4			
60	See model 50				
	Schematic, socket, trimmers	8-5			
	Alignment, voltage, resistance	8-6			
	Data	Changes 10-2			
C-6 Auto	Schematic	6-2			
7A	Alignment	7-17			
	Schematic, socket, trimmers	10-1			
	Alignment, voltage, tuner, phono	10-2			
8A	Schematic, trimmers	8-7			
	Alignment, voltage, resistance	8-8			
9A	Socket, trimmers	8-8			
	Data	Changes 10-1			
	Schematic	8-9			
	Socket, trimmers, alignment, voltage, resistance	8-10			
	Automatic dial notes	8-13			
	Data	Changes 10-1			
	Schematic, socket, trimmers, tuner layout	10-3			
	Alignment, voltage, tuner, phono	10-4			
12A	Schematic	8-11			
	Socket, trimmers, voltage, resistance	8-12			
12B	Alignment, automatic dial notes	8-13			
	Schematic, socket, tuner, trimmers, voltage, phono	10-5, 6			
	Alignment	10-7			
	Tuner data, parts, Naturalizer notes	10-8			
1206, Chassis 120	Schematic	8-15			
	Socket, trimmers, voltage, resistance	8-14			
	Alignment	8-16			
	Schematic	6-1			
	Voltage, resistance	7-1			
	Socket, trimmers, alignment, chassis, transformer data	7-2			
FAIRBANKS MORSE & CO.—(Cont.)					
MODEL	FAIRBANKS MORSE & CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE		
41	Schematic	6-1			
	Socket, alignment, trimmers	7-3			
420IB, 42TOB, Chassis 42	Schematic, notes	8-17			
	Socket, trimmers, alignment, battery connections	8-18			
430IB, 43TIB, Chassis 43	Schematic, notes	8-19			
	Alignment, voltage, socket, trimmers, resistance	8-20			
51 Chassis	See model 5106				
52 Chassis	See model 5212				
53 Chassis	See model 5312				
54	Schematic	6-4			
	Socket, voltage, resistance	7-4			
	Alignment, notes, transformer data	7-5			
56	Schematic	6-2			
	Voltage, transformer data, parts list	7-6			
	Alignment, socket, chassis, trimmers	7-7			
57TO, Chassis 57	Schematic, voltage, resistance	8-21			
	Alignment, socket, trimmers, notes	8-22			
58TI, 58T2, Chassis 58	Schematic, voltage, resistance	8-23			
	Alignment, socket, trimmers, notes	8-24			
60 Chassis	See model 6010				
61	Schematic	5-6			
62 Chassis	See model 6210				
63	Schematic	6-3			
	Socket, chassis, trimmers, voltage, resistance	7-8			
	Alignment, AVO data, trans former data	7-9			
64 Battery	Schematic	6-4			
64, Auto	Schematic	6-3			
	Voltage	7-10			
	Alignment	7-17			
65 Export	Schematic	9-10			
66	Schematic, socket, trimmers, voltage, resistance	7-11			
	Alignment, notes, transformer data	7-5			
67	Schematic, voltage, resistance, socket, trimmers, chassis	7-12			
	Circuit data, alignment, notes	7-13			
68T6, Chassis 68	Schematic	8-25			
	Socket, trimmers, alignment	8-26			
69T7	Voltage, resistance	8-27			
	Schematic, socket, trimmers, alignment	8-28			
	Voltage, resistance	8-27			
70 Chassis	See model 7014				
71	Schematic	6-5			
	Voltage, socket, trimmers, chassis, resistance	7-14			
	Alignment, AVO data, trans former data	7-9			
72C2, 72C3, 72T3, Chassis 72	Schematic, voltage, resistance	8-29			
	Alignment, socket, trimmers, data	8-30			
73C3B, 73T3B, Chassis 73	Schematic, voltage, resistance	8-31			
	Socket, trimmers, alignment, data	8-32			
74 Auto	Schematic	6-5			
	Alignment	7-17			
81 Chassis	Schematic, voltage	7-10			
82	See model 8110				
	Schematic	6-6			
	Voltage, socket, trimmers, chassis, resistance	7-15			
	Alignment, oscillograph notes, Notes	7-16			
	Circuit and AVO data, tuning indicator and transformer notes	7-17			
90	Schematic	7-18			
	Voltage, socket, trimmers, chassis, resistance	6-7			
		7-19			

FAIRBANKS MORSE & CO.—(Cont.)

MODEL	REVISION	REVISOR	REVISION	REVISOR
90	7-18	Notes	7-18	Notes
91	7-17	Alignment, oscillograph notes	7-17	Alignment, oscillograph notes
91C4, 9105, 9174, Chassis	7-16	Schematic, voltage, resistance	7-16	Schematic, voltage, resistance
91	7-15	Socket, trimmers, alignment, data	7-15	Socket, trimmers, alignment, data
100	7-14	Schematic, voltage, resistance	7-14	Schematic, voltage, resistance
110 (Temporary)	7-13	Circuit, AVC, tuning indicator	7-13	Circuit, AVC, tuning indicator
110 (Revised)	7-12	Alignment, trap, transformer	7-12	Alignment, trap, transformer
Chassis 120	7-11	Schematic, voltage, resistance	7-11	Schematic, voltage, resistance
247, B-6	7-10	Schematic, voltage, resistance	7-10	Schematic, voltage, resistance
316, 840, 32-Volt	7-9	Schematic, voltage, resistance	7-9	Schematic, voltage, resistance
5106, 5107, 5108, 5109, 5111, 5112, 5141, 5143 (51)	7-8	Schematic, voltage, resistance	7-8	Schematic, voltage, resistance

FEDERAL RADIO CORP.—(Cont.)

MODEL	REVISION	REVISOR	REVISION	REVISOR
F, Code 79-080	7-13	Chassis wiring	7-13	Chassis wiring
F-10 DC, F-11 DC	7-12	Schematic, socket	7-12	Schematic, socket
F (25 cycles)	7-11	Schematic, socket, data	7-11	Schematic, socket, data
G (25 cycles)	7-10	Schematic, socket, data	7-10	Schematic, socket, data
H, Code 71-030	7-9	Schematic, socket, voltage	7-9	Schematic, socket, voltage
H Receiver	7-8	Chassis wiring	7-8	Chassis wiring
H Power Unit	7-7	Chassis wiring	7-7	Chassis wiring
K	7-6	Schematic, socket	7-6	Schematic, socket
M	7-5	Voltage data	7-5	Voltage data
	7-4	Schematic, socket, voltage	7-4	Schematic, socket, voltage

FEDERATED PURCHASER

Also see AORATEST				
Cathedral Tone	3-2	Schematic	3-2	Schematic
Acratone 2	2-1	Schematic	2-1	Schematic
Acratone 5	2-2	Schematic	2-2	Schematic
7-A, 12-A, 24-A	5-1	Schematic, voltage	5-1	Schematic, voltage
8-A, 9B, 11B	5-1	Schematic, voltage	5-1	Schematic, voltage
Royal 9-A	5-1	Schematic, voltage	5-1	Schematic, voltage
14-A	5-2	Schematic, voltage	5-2	Schematic, voltage
Acratone 17	5-2	Schematic, voltage	5-2	Schematic, voltage
24-A	5-2	Schematic, voltage	5-2	Schematic, voltage
29C, 30C, 31C	5-2	Schematic, voltage	5-2	Schematic, voltage
31-40	5-2	Schematic, voltage	5-2	Schematic, voltage
32-A, 36-A	5-2	Schematic, voltage	5-2	Schematic, voltage
32C, 33C	5-2	Schematic, voltage	5-2	Schematic, voltage
35, 40	5-2	Schematic, voltage	5-2	Schematic, voltage
38-A	5-2	Schematic, voltage	5-2	Schematic, voltage
39-A, 43-A, 44-A, 86, 87	5-2	Schematic, voltage	5-2	Schematic, voltage

FANSTEEL

See BALKITE PRODUCTS CO.				
7-Tab A0	7-10	Schematic	7-10	Schematic
7-Tab A0	7-9	Schematic	7-9	Schematic
7-Tab A0	7-8	Schematic	7-8	Schematic

FARRAND MFG. CO.

Chassis 59, 102	7-10	Schematic, socket	7-10	Schematic, socket
A-10	7-9	Chassis wiring	7-9	Chassis wiring
B	7-8	Schematic	7-8	Schematic
C	7-7	Chassis wiring	7-7	Chassis wiring
D, Code 68-070	7-6	Schematic, socket	7-6	Schematic, socket
D, Code 68-070	7-5	Schematic, socket	7-5	Schematic, socket
D, Code 68-070	7-4	Schematic, socket	7-4	Schematic, socket
D, Code 68-070	7-3	Schematic, socket	7-3	Schematic, socket
D, Code 68-070	7-2	Schematic, socket	7-2	Schematic, socket
D, Code 68-070	7-1	Schematic, socket	7-1	Schematic, socket
D, Code 68-070	7-0	Schematic, socket	7-0	Schematic, socket

FEDERAL RADIO CORP.

Chassis 59, 102	7-10	Schematic, socket	7-10	Schematic, socket
A-10	7-9	Chassis wiring	7-9	Chassis wiring
B	7-8	Schematic	7-8	Schematic
C	7-7	Chassis wiring	7-7	Chassis wiring
D, Code 68-070	7-6	Schematic, socket	7-6	Schematic, socket
D, Code 68-070	7-5	Schematic, socket	7-5	Schematic, socket
D, Code 68-070	7-4	Schematic, socket	7-4	Schematic, socket
D, Code 68-070	7-3	Schematic, socket	7-3	Schematic, socket
D, Code 68-070	7-2	Schematic, socket	7-2	Schematic, socket
D, Code 68-070	7-1	Schematic, socket	7-1	Schematic, socket
D, Code 68-070	7-0	Schematic, socket	7-0	Schematic, socket

FERRANTI, INC.

250, B-3	7-10	Schematic	7-10	Schematic
250-C	7-9	Schematic	7-9	Schematic

FIRESTONE TIRE & RUBBER CO.

R-1922, Chassis R-192	7-10	Schematic	7-10	Schematic
R-1932, Chassis R-193	7-9	Schematic	7-9	Schematic
R-1451	7-8	Schematic	7-8	Schematic

FENWAY

Superheterodyne, Early, late	7-10	Schematic	7-10	Schematic
------------------------------	------	-----------	------	-----------

FAIRBANKS  
FIRESTONE

Superheterodyne, Early, late	7-10	Schematic	7-10	Schematic
250, B-3	7-9	Schematic	7-9	Schematic
250-C	7-8	Schematic	7-8	Schematic
R-1922, Chassis R-192	7-10	Schematic	7-10	Schematic
R-1932, Chassis R-193	7-9	Schematic	7-9	Schematic
R-1451	7-8	Schematic	7-8	Schematic



FREED TELEVISION & RADIO CORP.—(Cont.)			RADIOFRESHMAN CO., INC.—(Cont.)			RADIOFRESHMAN CO., INC.—(Cont.)		
MODEL	EARLY COMPLETE PAGE	REVISED PAGE	MODEL	EARLY COMPLETE PAGE	REVISED PAGE	MODEL	EARLY COMPLETE PAGE	REVISED PAGE
NR-8, NR-8A	Schematic, socket	1-2	L	Schematic, socket	1-7	2N with 2N-60-S Power Unit	Schematic	1-1
A-9	Schematic	4-1	M	Schematic, socket, voltage	1-6	3-Q-15, 3-Q-16	Schematic, socket, voltage	1-10
MB-9 90	Schematic	3-5	N	Schematic, socket, voltage	1-7	Q-15, Q-16	Schematic, socket, voltage	1-9
NR-9, NR-9A	Schematic	1-3	Equaphase	Schematic	1-1	QD-16-S	Schematic, socket, voltage	1-11
NR-10	Schematic, socket	1-3	Masterpiece	Schematic	1-1			
NR-11	Schematic, socket	1-4	Unit	Schematic	1-1			
NR-11 Power Pack	Schematic	1-5	2N with 2N-60-S Power Unit	Schematic	1-1			
NR-12	Schematic	1-5						
FE-15	Schematic	1-4						
FE-16	Schematic	1-6						
FE-18	Schematic	1-6						
NR-20	Schematic	1-7						
FE-30 48N	Schematic	1-7						
40N, 48N	Schematic	1-7						
50 DO	Schematic	1-8						
51 DO	Schematic, socket	3-1						
NR-53	Schematic	1-22						
54, 56, 59	Schematic, socket	8-3						
NR-55 DO	Schematic, socket	8-3						
NR-55, NR-56 AO	Schematic, socket, voltage	1-10						
NR-57	Schematic, socket	1-11						
	Power Unit	1-11						
	Schematic, socket	1-11						
58 AO	Schematic, socket	3-1						
59	See model 54							
NR-60 DO	Schematic	1-12						
NR-60 AO	Schematic, socket	1-13						
FE-63 DO	Schematic	1-13						
NR-66, 66-A	Schematic, socket	1-14						
NR-70 AO	Schematic, socket	1-15						
72, 74, MB-7	Schematic, socket	3-4						
NR-77	Schematic, socket	1-16						
NR-78 DC, NR-79 DO	Schematic, socket, voltage	1-17						
NR-78 AC, NR-79 AO	Schematic, socket, voltage	1-18						
NR-80 DO	Schematic, socket, voltage	1-19						
NR-80 AO	Schematic, socket, voltage	1-20						
NR-85 AO	Schematic, socket, voltage	1-21						
90	See model MB-9							
NR-90-S	Schematic	1-22						
91 DO	Schematic, socket	3-6						
92 AO	Schematic, socket	3-7						
NR-95 AO	Schematic, socket, voltage	1-23						
FE-96 DO	Schematic, socket	3-9						
FE-98	Schematic, socket	3-10						
FE-99 DO	Schematic, socket	3-8						
346-4	Schematic, socket, parts list	4-2						
354	Schematic, socket	4-3						
355	Schematic, socket	4-4						
360, 360X	Schematic, socket	4-5						
365, 365X	Schematic, socket	4-5						
NR-457	Schematic, socket	4-6						
NR-460 AO Power Unit	Power Unit—See NR-57							
NR-470 AO	Schematic	1-13						
800	Schematic	1-15						
	Schematic	1-16						
5X, 6X, 7X	Schematic	5-1						
	Socket, voltage, parts list	5-2						

GALVIN MFG. CO.—(Cont.)			RADIOTRON		
MODEL		REVISI	EARLY COMPLETE	PAGE	
6A, Chassis 6-1		8-6	Schematic, voltage, parts	8-6	
E6T		8-4	Socket, trimmers, alignment	8-4	
6T, 6Y, Chassis 6-2		8-7	Schematic, sensitivity, parts	8-7	
			Voltage, socket, trimmers, alignment		
6T-12 PL		8-8	Schematic	8-8	
7T-38		8-3	Parts list	8-3	
		7-9	Schematic	7-9	
		3-4	Test data, socket	3-4	
		3-5	Parts list	3-5	
7T-38-A		7-9	Schematic	7-9	
7T-47-A		3-6	Schematic	3-6	
		3-7	Connection data	3-7	
		3-8	Voltage, continuity test	3-8	
		3-9	I.F. Peak	3-9	
		4-3	Parts list	4-3	
J-8		9-1	Schematic, parts	9-1	
8-30		9-5	Sensitivity and gain notes	9-5	
		9-6, 9-8	Tuner notes	9-6, 9-8	
		9-9	Voltage, sensitivity and gain measurements	9-9	
		9-10	Alignment	9-10	
8-40		9-11	Tuner adjustments	9-11	
		9-2	Schematic, parts	9-2	
8-50		9-3	Sensitivity and gain notes	9-3	
		9-4	Tuner notes	9-4	
		9-6, 9-8	Voltage, sensitivity and gain measurements	9-6, 9-8	
		9-9	Alignment	9-9	
8-60		9-10	Tuner adjustments	9-10	
		9-11	Schematic, sensitivity and gain notes	9-11	
		9-5	Parts, tuner notes	9-5	
		9-6, 9-8	Voltage, sensitivity and gain measurements	9-6, 9-8	
		9-9	Alignment	9-9	
8-70		9-10	Tuner adjustments	9-10	
		9-11	Schematic, parts	9-11	
		9-4	Sensitivity and gain notes	9-4	
		9-6, 9-8	Tuner notes	9-6, 9-8	
		9-9	Voltage, sensitivity and gain measurements	9-9	
		9-10	Alignment	9-10	
		9-11	Tuner adjustments	9-11	
8-80, Golden Voice (1938)		8-7	Schematic	8-7	
		8-8	Parts list	8-8	
		9-6, 9-8	Voltage, sensitivity and gain measurements	9-6, 9-8	
		9-9	Alignment	9-9	
9A, Chassis 9-3, 9R, Chassis 9-2, 9Y, Chassis 9-1		8-9	Schematic, notes, parts	8-9	
9-24		8-10	Socket, trimmers, voltage, alignment	8-10	
		10-3	Schematic	10-3	
9-24A		10-4	Alignment, socket, trimmers, voltage, sensitivity, gain, dial cord data	10-4	
		10-3	Schematic	10-3	
9-29		10-4	Alignment, socket, trimmers, voltage, sensitivity, gain, dial cord data	10-4	
		10-5	Schematic, socket, trimmers, alignment	10-5	
9-44		10-6	Voltage, sensitivity, gain	10-6	
		10-7	Schematic, voltage, gain, sensitivity	10-7	
		10-8	Socket, trimmers, drive, alignment	10-8	
GALVIN MFG. CO.—(Cont.)			RADIOTRON		
MODEL		REVISI	EARLY COMPLETE	PAGE	
9-49		10-9	Schematic, voltage	10-9	
		10-8	Alignment	10-8	
		10-6	Alignment, sensitivity, socket, trimmers, gain	10-6	
		10-2	Procedure, Part 2, schematic of tuner, assembly, parts list	10-2	
9-49 (E5T)		10-1	Elec. Automatic tuner, data, procedure, assembly	10-1	
9-69		10-10	Schematic	10-10	
		10-8	Sensitivity, gain, socket, trimmers, alignment, voltage	10-8	
		10-2	Procedure, Part 2, schematic of tuner, assembly, parts list	10-2	
9-69 (E5T)		10-1	Elec. automatic tuner, data, procedure, assembly	10-1	
8-10		4-4	Schematic	4-4	
10Y, Chassis 10-1		7-9	Parts list	7-9	
		8-11, 8-12	Schematic, parts, trimmers	8-11, 8-12	
		8-13	Socket trimmers, alignment, voltage, sensitivity	8-13	
10Y-1, Chassis 10-2		9-13	Schematic, parts	9-13	
		9-17	Dial data, trimmers, alignment	9-17	
		9-18	Tuner assembly	9-18	
		9-19	Tuner notes, Part 1	9-19	
		9-20	Tuner notes, Part 2	9-20	
		9-21	Tuner notes, Part 3	9-21	
12Y, 12Y-1, Chassis 12-1		9-15	Schematic, parts	9-15	
		9-16	Socket trimmers, voltage	9-16	
		9-17	Dial data, trimmers, alignment	9-17	
		9-18	Tuner assembly	9-18	
		9-19	Tuner notes, Part 1	9-19	
		9-20	Tuner notes, Part 2	9-20	
		9-21	Tuner notes, Part 3	9-21	
15F		10-11	Schematic	10-11	
		10-12	Sensitivity, gain, voltage, alignment, socket, trimmers	10-12	
		10-2	Procedure, Part 2, schematic of tuner, assembly, parts list	10-2	
15F (E6T)		10-1	Elec. automatic tuner, data, procedure, assembly	10-1	
16C		10-13	Schematic, socket, trimmers	10-13	
		10-14	Sensitivity, gain, voltage, alignment, drive data	10-14	
17-D		10-15	Schematic	10-15	
		10-16	Alignment, voltage, gain, sensitivity, drive data	10-16	
17-D-A		10-15	Schematic	10-15	
		10-16	Alignment, voltage, gain, sensitivity, drive data	10-16	
18-O		10-17	Schematic, socket, trimmers	10-17	
19-B		10-18	Voltage, sensitivity, gain, alignment, drive data	10-18	
		10-19	Schematic, socket, trimmers	10-19	
		10-20	Alignment, voltage, gain, sensitivity, drive data	10-20	
20P, 21L, 24K		10-21	Schematic	10-21	
		10-22	Alignment, socket, trimmers, gain, sensitivity	10-22	
		10-1	Elec. automatic tuner, data, procedure, assembly	10-1	
		10-2	Procedure, Part 2, schematic of tuner, assembly, parts list	10-2	
M-33		7-10	Parts list	7-10	
M-33A		7-10	Parts list	7-10	
84		5-8	Schematic	5-8	
85		7-10	Parts list	7-10	
		8-15	Schematic, voltage, sensitivity, alignment	8-15	
		9-12	Coil data	9-12	
		4-5	Schematic	4-5	
		4-6	Data	4-6	
		4-7	Voltage, resistance data, adjustment notes	4-7	
		4-8	Chassis views	4-8	
		7-10	Parts list	7-10	





MODEL	GAMBLE-SKOGMO, INC.—(Cont.)	REVISI PAGE	RADIOTRON	
			EARLY COMPLETE PAGE	PAGE
26-B-5	Schematic, socket, parts, power unit .....7-15			
	Alignment, voltage, resistance, parts .....7-16			
26-FM-552	R-F chassis schematic .....7-17			
	A.F. & power unit schematic .....7-18			
	Color coding, changes, chassis layout, phono, connections .....7-19			
	Chassis views, voltage, trimmers, switch data .....7-20			
	Circuit data, alignment, phono, data .....7-21			
26-R-1	Parts list .....7-22			
	Schematic, alignment .....7-23			
26S1	Voltage, socket, trimmers, color code, resistance, mounting .....7-24			
	Schematic .....6-3			
	Installation details .....6-4			
	Voltage, alignment, socket, trimmers, resistance data .....6-5			
27O1, 27O5	Schematic, voltage, socket, trimmers, parts .....6-7			
	Drive cord adjustment, align- ment, resistance data .....6-8			
30-A	Schematic .....7-91			
31-BT	Schematic, trimmers .....7-27			
34BT	Alignment, parts list .....7-28			
	Schematic, trimmers, voltage .....7-29			
36-L	Alignment, parts list .....7-30			
	Schematic, socket, trimmers, voltage .....7-31			
42DL670	Alignment, voltage, parts .....7-32			
	Schematic, sensitivity .....8-9			
	Socket, trimmers, coils, phono, data .....8-10			
46L	Alignment, voltage, notes .....8-11			
	Schematic, coils, data .....8-13			
46-L-1	Alignment, voltage, parts .....8-14			
	Schematic, socket, trimmers, coil data .....7-83			
471L	Alignment, circuit, voltage, mounting .....7-84			
	Schematic, socket, data .....8-15			
47P608	Alignment, trimmers, voltage, coils, phono, data .....8-16			
	Schematic, data .....8-17			
	Voltage, trimmers, socket, coils, data .....8-18			
47R, 47RL	Alignment, power supply notes .....8-19			
	Schematic .....8-21			
	Voltage, socket, trimmers, coils, sensitivity .....8-22			
51-O	Alignment, notes, parts .....8-23			
70	Schematic .....7-42			
	Voltage, alignment, data, parts .....8-12			
71O	Schematic, voltage, socket, alignment chassis .....9-3			
72, Chassis 8, 8X	Voltage, alignment, data, parts .....9-4			
77	Schematic, socket, trimmers, .....9-4			
77-A	Schematic, alignment, parts .....6-6			
85	Schematic, socket, parts .....7-14			
	Alignment, socket, trimmers, voltage .....7-85			
90	Voltage, socket, trimmers, .....8-20			
92D, 92M	Schematic, socket, notes .....8-20			
400-A, 410-B	Schematic, socket, voltage, data .....8-24			
401, 402	Schematic, socket, alignment, parts chassis, coil data .....7-87			
404	Schematic, socket, trimmers, parts .....9-5			
425	Schematic, socket, voltage, trimmers, alignment .....7-88			
430	Schematic .....7-40			
	Alignment, parts .....7-89			
457, Regal	Schematic .....7-40			
460	Schematic, socket, parts .....8-25			
	Schematic, socket, trimmers, voltage, parts .....10-5			
	Alignment, trimmers .....10-6			
501	Schematic, alignment .....7-41			
504	Schematic, voltage, alignment, socket, trimmers .....10-7			
510, 511	Schematic, socket, trimmers, alignment .....8-26			
516, Symphony	Schematic, socket .....7-41			
2516	Schematic, socket .....8-27			
521	Voltage, alignment, parts .....8-28			
	Schematic, socket, trimmers, voltage, parts .....9-6			
Z-521	Voltage, socket, parts .....7-43			
525	Schematic, socket, trimmers, alignment, parts .....7-44			
526	Schematic, socket, trimmers, alignment, parts .....7-42			
527A	Alignment, voltage, parts .....9-5			
	Schematic, voltage, alignment, socket, trimmers .....10-8			
527O	Tuner procedure .....10-20			
	Schematic, voltage, alignment, socket .....10-9			
Z-530	Socket, trimmers, tuner .....10-10			
	Schematic .....7-45			
	Voltage, socket, alignment, parts .....7-46			
540 (Early)	Schematic, socket, alignment, parts, voltage .....6-10			
541A	Schematic, alignment .....10-12			
550 AO	Schematic, voltage, alignment, parts .....8-29			
550	Schematic .....6-11			
552	Alignment, parts .....7-53			
566	Schematic, alignment .....10-12			
	Schematic, socket, trimmers, parts .....9-7			
575	Alignment, dial data .....9-8			
	Schematic, socket, voltage, alignment .....6-12			
578 (2 types) Serial	Schematic, voltage parts .....7-47			
5G133670A to				
5K173250A and above				
578, Series A	Socket, trimmers, alignment .....7-48			
580	Schematic, voltage, socket, trimmers, data .....7-51			
	Alignment, installation data .....7-52			
585, Series A, B, C	Schematic, voltage .....7-55			
	Alignment .....7-56			
	Socket, trimmers, parts, changes .....7-54			
586-A	Schematic, voltage, socket, trimmers .....7-57			
	Alignment, parts .....7-58			
587, Series A	Schematic, voltage, socket, trimmers .....10-11			
600	Alignment .....10-10			
	Schematic, voltage, trimmers, alignment, parts .....9-9			
602	Schematic, voltage, socket, trimmers, alignment .....10-13			
602B	Schematics, socket, trimmers, alignment, voltage .....10-14			
602C	Alignment .....10-13			
	Schematic, socket, trimmers, alignment, voltage .....10-14			
623	Alignment .....10-13			
	Schematic, socket, trimmers, voltage, parts, alignment .....9-10			
645	Schematic, socket, trimmers, voltage, alignment, parts .....9-11			
648	Schematic, socket, trimmers, voltage, tuner, parts .....9-12			
650 A-B-C	Alignment .....8-80			
660	Schematic, alignment .....8-80			
	Schematic, voltage, socket, trimmers, parts list .....7-63			
666	Schematic, voltage, socket, trimmers, parts, notes .....10-15			

GAMBLE-SKOGMO, INC.—(Cont.)		RADIOTRON	
MODEL	REVISED PAGE	EARLY COMPLETE PAGE	PAGE

666	Speaker data, alignment.....	10-16	
667	Schematic, voltage, socket, trimmers, alignment, parts.....	10-17	
670	Schematic, voltage, socket, trimmers.....	6-13	
670-A	Schematic, voltage, socket, trimmers.....	7-61	
675	Alignment, installation data .....	7-62	
	Schematic, voltage, socket, trimmers.....	6-15	
675A, 685B	Alignment.....	6-16	
677A	Schematic, alignment.....	10-18	
	Schematic, parts.....	10-19	
677B	Alignment, socket, trimmers, automatic tuner procedure.....	10-20	
	Schematic, parts.....	10-19	
680	Alignment, socket, trimmers, automatic tuner procedure.....	10-20	
	Schematic, voltage, socket, trimmers, alignment.....	7-64	
685B	See model 675A		
686, A & B	Schematic, voltage, socket, trimmers, parts list.....	7-65	
690B	Alignment, parts.....	7-66	
715B	Schematic, alignment.....	10-21	
735	Schematic, alignment.....	10-22	
	Schematic, alignment, parts.....	9-14	
740	Tuner, voltage.....	9-13	
	Schematic, socket, trimmers, voltage, parts.....	8-31	
750	Alignment, trimmers.....	8-32	
	Schematic, voltage.....	7-67	
761A	Alignment, socket.....	7-68	
	Schematic, voltage, socket, trimmers.....	10-23	
762	Alignment, tuner.....	10-6	
	Schematic, data.....	8-33	
	Socket, chassis, voltage, coils.....	8-34	
	Alignment, trimmers, data.....	8-35	
	Circuit data, notes, parts.....	8-36	
	Telephone dial adjustments, data.....	10-24	
770	Phantom light dial, assembly views, data, parts list.....	10-25	
	Telephone dial, parts.....	10-26	
	Schematic, voltage, socket, trimmers.....	7-69	
774	Alignment, parts list.....	7-70	
	Schematic.....	8-37	
	Alignment, trimmers.....	8-38	
	Voltage, socket, chassis, coils.....	8-39	
	Notes, parts.....	8-40	
	Telephone dial adjustments, data.....	10-24	
776	Phantom light dial, assembly views, data, parts, telephone dial data, parts.....	10-25	
	Schematic, phono., speaker data.....	10-27	
	Telephone dial, adjustments, data.....	10-24	
	Phantom light dial, assembly views, data, parts, telephone dial data, parts.....	10-25	
	Alignment, socket, trimmers, voltage, coils, notes.....	10-28	
777C, 777L, Series A & B	Schematic, voltage.....	7-71	
	Socket, trimmers, parts list.....	7-72	
778-A	Alignment.....	7-73	
	Schematic, voltage, socket, trimmers, parts list.....	7-75	
780, 780B	Alignment.....	7-76	
	Schematic.....	6-14	
787	Alignment, parts list.....	7-74	
	Schematic, voltage, socket, trimmers, parts.....	8-41	
802A	Alignment, notes.....	8-42	
	Schematics, parts.....	10-29	

GAMBLE-SKOGMO, INC.—(Cont.)		RADIOTRON	
MODEL	REVISED PAGE	EARLY COMPLETE PAGE	PAGE

803A	Schematic.....	10-30	
803B	Schematic, parts.....	10-30	
806A	Schematic, alignment.....	10-29	
807B	Schematic, voltage, socket, trimmers.....	8-48	
810	Schematic, voltage, socket, tuner, coils, sensitivity.....	10-31	
810(1938)	Alignment, trimmers.....	10-32	
813A	Schematic, parts.....	10-29	
813B	Schematic, parts.....	10-29	
822	Schematic, socket, trimmers, parts.....	8-43	
	Alignment, notes.....	8-44	
850B	Schematic, trimmers, alignment.....	8-52	
867A	Schematic, voltage, parts.....	10-33	
	Alignment, trimmers.....	10-34	
	Socket, trimmers, tuner data, notes.....	10-35	
1050	Schematic, voltage.....	7-77	
	Socket, alignment, notes.....	7-78	
1170	Schematic, voltage, socket, trimmers, parts.....	8-45	
	Alignment, notes.....	8-46	
	Parts.....	8-47	
2056AW	Schematic, socket, voltage, alignment.....	10-36	
2078-D	Schematic, socket.....	7-79	
	Alignment, chassis, parts.....	7-80	
	Voltage, data, resistance.....	7-81	
2090	Schematic, notes.....	7-82	
	Circuit data, alignment, part 1.....	7-83	
	Alignment, part 2, socket, voltage, speaker connections, notes, transformer data.....	7-84	
2092, 2094	Schematic.....	7-85	
	Voltage, alignment, notes, change.....	7-86	
3128	Schematic.....	7-90	
3132, 3134, 3140	Schematic, socket, alignment.....	9-15	
5953A	Voltage, resistance.....	9-16	
	Schematic, voltage, trimmers.....	8-49, 8-50	
6100	Alignment, parts.....	8-51	
	Schematic, parts, power pack.....	9-17	
	Voltage, notes, alignment, parts.....	9-18	
6958-A	Schematic, voltage, trimmers, notes, parts list.....	7-87, 7-88	
7735, 7742, 7755	Alignment.....	7-89	
	Schematic.....	7-91	
	Alignment, voltage, parts list.....	7-92	

GAROD RADIO CORP.

Intermediate Frequencies		I-F. Peaks	
Challenger I	Challenger II, Challenger III	EA	Garod EM
2B2, 2B2-1, 2B6, 2B6-1	2B2, 2B2-1, 2B6, 2B6-1	25	25
26	26	26	26
31, 31LW, M-33, M-35LW	31, 31LW, M-33, M-35LW	31	31
M-32, M-32LW	M-32, M-32LW	32	32
33	33	33	33
33-LW	33-LW	33-LW	33-LW
M-33, M-33LW	M-33, M-33LW	33	33
35SW	35SW	35SW	35SW
37B, 37D	37B, 37D	37B, 37D	37B, 37D
49, 49M	49, 49M	49, 49M	49, 49M
58	58	58	58

1069  
1070  
1070

# GAROD GENERAL ELECTRIC

GAROD RADIO CORP.—(Cont.)			RADIOTRON	
MODEL			EARLY COMPLETE PAGE	REVISID PAGE
60	Schematic, voltage, alignment	7-2		
66	Schematic	6-5		
78, 73LW	Schematic	7-13		
88	Schematic	6-6		
83-LW	Schematic	6-6		
100 Television	Chassis wiring, top	10-3, 4		
	Chassis wiring, bottom	10-5, 6		
	Chassis view, socket, controls	10-7		
	Circuit data, assembly, wiring	10-8		
	notes	10-9		
	S.P.U. chassis wiring, voltage	10-10		
	Alignment, operating, antenna	10-11		
104 Early & Late, 104M	Notes	10-11		
115	Schematic, voltage	7-9		
159	Alignment, socket, trimmers	7-10		
205C, 205L, 205-1, 206L, 206C, 206-1, 206P4	Schematic	8-1, 8-2		
237, 837	Schematic, socket, trimmers	10-2		
250	Schematic, voltage, alignment	9-3		
259, 269	Schematic	9-4		
307L, 307T, 307-1, 307, 307E	Schematic, voltage, alignment	9-5		
309L, 309T, 309E-1, 309-2, 309L, 309-3, 309E-2, 309E-3, 309P-5, 309P-7, 309E-P6, 309E-P7	Schematic, socket, trimmers	10-13		
	Alignment	10-14		
	Schematic, socket, trimmers	9-6		
	Socket, trimmers, voltage, alignment	9-7		
310	Schematic	8-1, 8-2		
311	Schematic	8-4		
337	See model	287		
369	Schematic	10-12		
370, 870C, 970D, 370K	Alignment	10-14		
371, 871C, 371D, 371K	Schematic	8-5		
379, 3790	Schematic	8-5		
380, 380D, 380K	Socket, trimmers, tuner data	10-16		
	Schematic	8-6		
	Alignment, voltage, socket, trimmers	8-7		
381, 381D, 381K	Schematic	8-6		
	Alignment, voltage, socket, trimmers	8-7		
511-A, 511-G, 511-P	Schematic, voltage	7-11		
514	Alignment, socket, trimmers	7-12		
	Schematic	7-15, 7-16		
514M	Alignment, voltage	7-14		
520	Schematic	7-17, 7-18		
	Schematic	7-19		
	Alignment, voltage, socket, trimmers	7-20		
602C, 602L, 602-1	Schematic, voltage, alignment	9-9		
620	Schematic	8-8		
629, 729	Schematic, alignment	10-17		
703EC, 703EL	Alignment	10-14		
731	Schematic	9-10		
739	Schematic, notes	8-9		
	Schematic, socket, trimmers	10-18		
762	Alignment	10-14		
	Schematic, voltage, alignment, tuner	9-13		
	Tuner data	9-12		
782, 782-1	Schematic, voltage, socket, trimmers	9-11		
	Alignment, tuner	9-12		
803L, 803T, 803-1	Schematic, socket, trimmers	10-19		
830, 830C, 830D, 830K	Schematic	8-10		
830A	Schematic	8-11		
831, 831C, 831D, 831K	Schematic	8-10		
831A	Schematic	8-11		
839	Schematic	10-20		
903L, 903T, 903E-T, 903E-1, 903-2, 903P-7, 903E-2, 903P-5, 903E-P7, 903E-P5, 903E-P7	Schematic	9-15		
	Socket, trimmers, voltage, alignment	9-16		
GAROD RADIO CORP.—(Cont.)			RADIOTRON	
MODEL			EARLY COMPLETE PAGE	REVISID PAGE
930, 930D, 930K	Schematic	8-12		
930, 930D, 930K	Alignment, socket, trimmers, voltage	8-13		
930A	Schematic, voltage, socket	8-14		
	Alignment, socket, trimmers	8-13		
931, 931D, 931K	Schematic	8-12		
	Alignment, socket, voltage, trimmers	8-13		
931A	Schematic, voltage, socket	8-14		
	Alignment, socket, trimmers	8-13		
1203L, 1203T, 1203-3, 1203-P6, 1203-P7, 1204ET, 1204EL, 1204-3, 1204E-P6, 1204E-P7	Schematic	9-17		
	Socket, trimmers, voltage, alignment	9-18		
1240, 1240E, 1240LO	Schematic, voltage	8-15		
1240A	Socket, trimmers, alignment	8-16		
	Schematic, socket, voltage	8-17		
1603, 1604-4	Alignment	8-16		
	Schematic, voltage	9-19		
1649	Socket, trimmers, alignment	9-20		
	Tuner data	9-14		
	Schematic, socket	10-21		
	Alignment, trimmers	10-22		
	Tuner data	10-26		
1650, 1650H, 1650LC	Schematic, voltage	8-18		
1650A	Socket, trimmers, alignment	8-19		
	Schematic, voltage, socket, notes	8-20		
3119	Alignment	8-19		
3012L, 3012T, 3012-3, 3012-P6, 3012-P7, 4012ET, 4012EL, 4012E-3, 4012E-P6, 4012E-P7	Schematic	9-21		
3016, 4016-4	Socket, voltage, trimmers, alignment	9-22		
	Schematic, socket, trimmers	9-23		
	Voltage, alignment	9-24		
3790	Tuner data	9-14		
4110, 4110E, 4110K	See Model 379			
4159	Schematic, voltage	9-25		
	Socket, trimmers, alignment	9-26		
	Schematic	10-25		
	Alignment, tuner	10-26		
5140	Socket, trimmers	10-16		
	Schematic, voltage	9-27		
5240	Socket, trimmers, alignment	9-28		
	Schematic, voltage	8-21, 8-22		
	Socket, trimmers	8-23		
7390	Alignment	8-24		
	Schematic	10-24		
	Alignment	10-14		
GATES RADIO & SUPPLY CO.			RADIOTRON	
MODEL			EARLY COMPLETE PAGE	REVISID PAGE
P-1 SPU	Schematic	Misc. 7-7		
40-B Amplifier	Schematic	Misc. 7-7		
40-C Amplifier	Schematic	Misc. 7-7		
B-100 Amplifier	Schematic	Misc. 7-7		
105-OR	Schematic	Misc. 6-1		
120-B Amplifier	Schematic	Misc. 7-7		
125-P SPU	Schematic	Misc. 7-7		
A-300	Schematic	Misc. 6-1		
500-A	Schematic	Misc. 6-2		
901-A	Schematic	Misc. 6-2		
GENERAL ELECTRIC CO.			RADIOTRON	
MODEL			EARLY COMPLETE PAGE	REVISID PAGE
BX	See RCA R-17-M			
V-Doublet Antenna	See G.E. model KV-100			
B-1	See RCA Radiola 21			
B-2	See RCA Radiola 22			
PS-5 Remote Station	Schematic, chassis	8-1		
	Circuit data, operation, notes	8-2		
	Voltage, parts	8-3		
	Schematic, operating notes	10-1		
GM11, Wireless Record Player				
T-12	See RCA R-5			
T-12-E	See RCA R-5-X			
T-12-DC	See RCA R-5 DO			
S-22, S-22-X	See RCA R-7			

GENERAL ELECTRIC CO.—(Cont.)			RADIO TRON		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
S-22-A	See RCA R-7-A		B-52	See RCA M-116	
S-22-D	See RCA R-7 DO		D-52	See RCA M-108	
C-30	See RCA 91-B		E-52	See model E-50	Changes 9-3
H-81	See RCA Radiola 80		FB-52, FB-53, FB-56, FB-57	Schematic, battery connections, power adaptor	8-17
H-82	See RCA R-50			Voltage, chassis	8-18
B-40	See RCA M-34			Alignment, trimmers	8-19
F-40	Data	Changes 9-3		Drive cord data, notes, parts	8-20
	Schematic, voltage	9-1	GD-52	Schematic, voltage, socket, alignment, trimmers	10-3
	Circuit data, socket, trimmers, alignment, voltage	9-2	K-52	See RCA 110	
K-40	See RCA R-27		L-52	See RCA 112	
K-40-A (Revised)	See RCA R-27 (Revised)		M-52	See RCA 119	
K-40-A	See RCA R-18-W		A-52	Schematic	6-4
M-40	See RCA 102			Chassis wiring	6-5
C-41	See RCA M-105			Circuit data, alignment	6-6
FM-41 Handy Phone	Schematic, chassis	8-1		Alignment part 2, voltage, socket	6-7
	Circuit data, operation, notes	8-2	F-52	Voltage, parts	6-8
	Voltage, parts	8-3		Schematic, resistance, voltage, transformer data	8-21
	Schematic, voltage, alignment, parts, specifications	9-6	FB-52	See model FB-52	
GD-41, GD-41U	See RCA R-17-M		G-52, G-56	Schematic, socket, trimmers, dial data, chassis wiring	9-9
K-41	See RCA 100, 101			Alignment, specifications	9-10
M-41	See RCA 103		K-52	Circuit data, voltage, pick-up, parts	9-11
M-42	See RCA 48		K-52-M	See RCA 111	
T-41	See RCA R-9		L-52	See RCA 115	
S-42	See RCA R-48		A-54	Schematic, voltage, transformer data	7-5
S-42-B	See RCA R-9 DO			Circuit data, alignment, parts	7-4
S-42-D	See RCA R-7 AO, Radiola 86			Chassis wiring, socket, trimmers	7-6
SZ-42-P	See RCA 100		K-54	See RCA RE-40	
K-43	See RCA 100		K-54-P	See RCA RE-40-P	
GD-44A, GD-44AU, GD-44B, GD-44BU	Schematic, voltage, alignment	10-2	A-55	See model A-52	
K-48	See RCA 800		G-55	See model G-50	
M-49	See RCA M-101		M-55	See RCA 210	
D-50	Schematic, socket, trimmers, voltage	9-5	M-55	See RCA 214	
E-50, E-52	Chassis wiring	8-4	FB-55, FB-57	See model U-51	
	Alignment, parts	8-6		See model FB-52	
G-50, G-55	Schematic, coils	9-3		See model G-53	
	Circuit data, voltage, tuner, specifications	9-4		See RCA 211	
	Socket, trimmers, chassis, alignment, parts	9-5		Data	Changes 10-1
K-50-P, K-51-P	See RCA R-26-P			See RCA 310	
K-50, K-51	See RCA R-28			See RCA M-32	
L-50, L-51	See RCA R-22			See RCA M-107	
M-50	See RCA 117			Schematic, socket, trimmers, resistance	8-23
U-50	Schematic, socket, trimmers, voltage	8-7		Chassis and speaker layouts	8-24
	Alignment, dial drive data	8-8		Voltage, installation	8-25
D-51	See RCA M-104			Alignment, installation, parts	8-26
D-51, D-52	Data	Changes 9-3		Schematic, voltage, socket, trimmers, alignment	10-3
E-51	Schematic, socket, voltage, trimmers	8-9		See RCA R-37	
	Chassis wiring, alignment, voltage, parts	8-10		See RCA R-37-P	
F-51	Circuit data, alignment, voltage, parts	8-11		Schematic	7-7
	Schematic, socket, trimmers, dial data, chassis wiring	9-7		Circuit data, coils, alignment, resistance	7-8
	Alignment, parts, voltage, specifications	9-8		See RCA M-123	
	Schematic, socket, voltage, alignment, trimmers	10-11		Schematic, data	7-9
GD-51	See RCA 82			Chassis wiring, circuit data, coil data	7-10
H-51	See RCA 118			Socket, trimmers, circuit data, part 2	7-11
H-51, H-51-B	See RCA 118 (Revised)			Voltage, alignment, parts list	7-12
K-51	Schematic	8-13		See model FA-60	
L-51	Notes, parts	8-14		Schematic	10-5, 6
M-51	Coils, resistance, vibrator, notes	8-14		Socket, trimmers, chassis, dial, phono, connections	10-7
M-51-A	Socket, trimmers, voltage, dial assembly	8-15		Voltage, alignment, coils, parts	10-8
U-51, U-55	Alignment, notes, drive cord data	8-16		Phono, connections, motor data, changer assembly	10-10
	Schematic, voltage, socket, trimmers	7-1			
A-52, A-55	Chassis wiring data	7-2			
	Circuit data, alignment, parts	7-3			

# GENERAL ELECTRIC

GENERAL ELECTRIC CO.—(Cont.)			RADIOTRON	
MODEL	REVISION	EARLY COMPLETE	PAGE	
G61, G66, G68, G69	Automatic record changer data	10-9		
M-61	See RCA 128			
M-61 (Revised)	See RCA 128 (Revised)			
C-62	See RCA 126-B			
E-62	See model E-61			
FD-62, FD-625	Schematic, coils, voltage, resistance	9-13		
	Socket, trimmers, alignment, parts	9-12		
GA62	Specifications, alignment notes, voltage, circuit data, chassis wiring	9-14		
GD62, GD67	Schematic, voltage, socket, alignment, trimmers	10-12		
K-62	See RCA R-11			
K-62 (Revised)	See RCA R-11 (Revised)			
M-62	See RCA 125			
KZ-62-P	See RCA RE-18, RE-18-A			
A-63, A-65	Schematic, data	6-9		
	Chassis wiring	6-10		
	Circuit data, alignment	6-11		
	Alignment, voltage	6-12		
	Voltage, parts	6-13		
	Additional data	Changes 7-1		
	Schematic, resistance, voltage	8-27		
	Socket, trimmers, chassis, alignment	8-28		
F-63, F-65, F-66	Schematic, socket, voltage, alignment, trimmers	10-14		
GD63	See RCA 120			
K-63	See RCA 124			
M-63	Schematic	6-14		
A-64, A-66, A-67	Chassis wiring	6-15		
	Circuit data, trimmers, alignment, socket	6-16		
	Alignment part 2, voltage, dial data	6-17		
	Parts	6-18		
	Additional data	Changes 7-12		
G64, G65	Schematic, chassis wiring, alignment, voltage, socket, trimmers, dial data, phono, connections, parts	10-15		
		10-16		
K-64	See RCA 121			
K-64-D	See RCA 127			
F-65	See model F-63			
K-65	See RCA R-38			
K-65-P	See RCA R-38-P			
M-65	See RCA 221			
A-66	See model A-64			
F-66	See model F-63			
G66, G68, G69	See Model G61			
K-66	See RCA 220			
M-66	See RCA 222			
A-67	See RCA 226			
C-67	See G.E. model A-64			
M-67	See RCA 223			
GD67	See RCA 224			
E-68	See model GD62			
M-68	See model E-61			
M-69	See RCA Duo 821			
A-70, A-75	See RCA 322			
	Schematic	6-19		
	Chassis wiring	6-20		
	Alignment, trimmers, socket, voltage	6-21		
	Circuit data, dial data	6-22		
	Voltage, parts	6-23		
	Changes	Changes 7-1, 7-16		
O-70, Q-75	See RCA 135-B, 235-B			
F-70, F-75	Schematic, resistance	8-29		
	Alignment, socket, trimmers	8-30		
	Chassis, voltage	8-31		
J-70	See RCA R-4			
U-75	Schematic	8-33		
	Socket, vibrator, dial assembly, data	8-32		
GENERAL ELECTRIC CO.—(Cont.)			RADIOTRON	
MODEL	REVISION	EARLY COMPLETE	PAGE	
U-70, U-75	Trimmers, voltage, resistance, coils	8-34		
	Alignment, drive data	8-35		
	Parts	8-36		
E-71, E-72, E-76	Schematic, data	7-13		
	Chassis wiring, transformer data	7-14		
	Circuit data, alignment, socket, trimmers, voltage	7-15		
	Parts list	7-16		
H-71, H-71-R	See RCA 86, 86-R			
D-72	See model E-71			
E-72	See model E-71			
FB-72, FB-73, FB-76, FB-77	Schematic, battery connections, switch assembly, adapter, socket, trimmers, alignment, notes	8-37		
	Chassis, voltage	8-38		
	Dial assembly, notes, parts	8-39		
	See RCA RAE-59	8-40		
J-72	See RCA R-70			
H-73, H-77, H-79	Schematic, socket, alignment, trimmers	10-43		
Preliminary	Schematic, resistance, voltage, transformer data	9-15		
F-74, F-77	Socket, trimmers, chassis wiring	9-16		
	Alignment, voltage, parts	9-17		
A-75	See G.E. model A-70			
C-75	See RCA 235-B			
F-75	See model F-70			
G-75	Schematic, chassis wiring	10-17		
	Alignment, voltage, socket, trimmers, dial and phono, data	10-18		
J-75	See RCA R-6			
U-75	See model U-70			
E-76	See model E-71			
FB-76, FB-77	See model FB-72			
G-76	Schematic, socket, trimmers, alignment	10-21		
H-77, H-79	See Model H-73			
G-78	Schematic, socket trimmers, chassis wiring, voltage	10-19		
	Alignment, dial and phono, data	10-20		
K-78	See RCA 330			
E-79	Schematic	8-41		
	Chassis wiring	8-42		
	Voltage, socket, trimmers	8-43		
	Circuit data, alignment, dial data	8-44		
	Phono, data	8-45		
	Parts	8-46		
K-79, F-85	See RCA 331			
	Alignment, voltage, parts	9-18		
	Schematic, socket, trimmers, transformer data, voltage, resistance	9-19		
	Specifications, circuit data, chassis wiring	9-20		
	Schematic, resistance	8-47		
	Socket trimmers, chassis, voltage	8-48		
FA-80	Circuit data, alignment, installation	8-49		
	Parts	8-50		
J-80	See RCA R-8			
K-80, K-80-X	See RCA 140 series			
A-81	See RCA P-31			
B-81	See RCA 142-B			
E-81, E-86	Schematic	7-17		
	Chassis wiring	7-18		
	Circuit data	7-19		
	Alignment, parts, voltage, dial data	7-20		
F-81, F-86	Schematic, resistance	8-51		
	Voltage, chassis	8-52		
	Alignment, trimmers, socket	8-53		
	Dial data, notes	8-54		
	Parts	8-55		

GENERAL ELECTRIC CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	PAGE	MODEL	REVISION	PAGE
See RCA 143		6-24	See RCA 143 (Revised)		6-24
See RCA 143		6-25	Schematic		6-25
Chassis wiring		6-26	Chassis wiring		6-26
Circuit data, alignment		6-27	Circuit data, alignment		6-27
Alignment part 2		6-28	Alignment part 2		6-28
Sentry Box data, dial data		6-29	Sentry Box data, dial data		6-29
Voltage, parts		6-30	Voltage, parts		6-30
See RCA R-71		7-21	See RCA R-71		7-21
Schematic data		7-22	Schematic data		7-22
Chassis wiring		7-23	Chassis wiring		7-23
Circuit data, alignment, coil locations		7-24	Circuit data, alignment, coil locations		7-24
Socket, trimmers, voltage, dial data, parts list		7-25	Socket, trimmers, voltage, dial data, parts list		7-25
See RCA R-73		7-26	See RCA R-73		7-26
See RCA R-73		7-27	See RCA R-73		7-27
See model A-83		7-28	See model A-83		7-28
See model F-80		7-29	See model F-80		7-29
Schematic, socket, trimmers		10-22	Schematic, socket, trimmers		10-22
Chassis wiring, coil data, dial mechanism		10-23	Chassis wiring, coil data, dial mechanism		10-23
Alignment, voltage, parts, phono, data		10-24	Alignment, voltage, parts, phono, data		10-24
See RCA R-12		10-25	See RCA R-12		10-25
See RCA 240, 140		10-26	See RCA 240, 140		10-26
See RCA 243		10-27	See RCA 243		10-27
See model A-82		10-28	See model A-82		10-28
See RCA 241-B		10-29	See RCA 241-B		10-29
See model E-81		10-30	See model E-81		10-30
See model F-81		10-31	See model F-81		10-31
Schematic, voltage, socket, trimmers		10-32	Schematic, voltage, socket, trimmers		10-32
Alignment, chassis wiring, dial and phono, data, "Beam-A"		10-33	Alignment, chassis wiring, dial and phono, data, "Beam-A"		10-33
Scope" data		10-34	Scope" data		10-34
See RCA R-72		10-35	See RCA R-72		10-35
See RCA 143		10-36	See RCA 143		10-36
See G.E. model A-82		10-37	See G.E. model A-82		10-37
See RCA R-75		10-38	See RCA R-75		10-38
See RCA R-75		10-39	See RCA R-75		10-39
Schematic, socket, trimmers, voltage, transformer data, resistance		10-40	Schematic, socket, trimmers, voltage, transformer data, resistance		10-40
Changes, voltage		10-41	Changes, voltage		10-41
Specifications, chassis wiring		10-42	Specifications, chassis wiring		10-42
Circuit data, alignment, phono-graph data		10-43	Circuit data, alignment, phono-graph data		10-43
Alignment, parts		10-44	Alignment, parts		10-44
See RCA R-71		10-45	See RCA R-71		10-45
See RCA 340		10-46	See RCA 340		10-46
See RCA 340-E		10-47	See RCA 340-E		10-47
See RCA 341		10-48	See RCA 341		10-48
See RCA M-30		10-49	See RCA M-30		10-49
Schematic		10-50	Schematic		10-50
Circuit data, voltage, alignment		10-51	Circuit data, voltage, alignment		10-51
Chassis wiring, coil data		10-52	Chassis wiring, coil data		10-52
Visual alignment, socket, trimmers, dial data, parts		10-53	Visual alignment, socket, trimmers, dial data, parts		10-53
Schematic		10-54	Schematic		10-54
SPU Chassis wiring		10-55	SPU Chassis wiring		10-55
Assembly wiring		10-56	Assembly wiring		10-56
Schematic		10-57	Schematic		10-57
Chassis wiring of receiver		10-58	Chassis wiring of receiver		10-58
Assembly wiring		10-59	Assembly wiring		10-59
SPU Chassis wiring		10-60	SPU Chassis wiring		10-60
Specifications		10-61	Specifications		10-61
Notes		10-62	Notes		10-62
Remote control notes, voltage data		10-63	Remote control notes, voltage data		10-63
Parts list		10-64	Parts list		10-64
Parts list continued		10-65	Parts list continued		10-65
Parts list concluded		10-66	Parts list concluded		10-66
See model E-91		10-67	See model E-91		10-67
Schematic, chassis wiring, voltage, socket, trimmers		10-27, 28	Schematic, chassis wiring, voltage, socket, trimmers		10-27, 28
Alignment, phono, parts		10-29	Alignment, phono, parts		10-29
J-85		10-35	J-85		10-35
K-85		10-36	K-85		10-36
M-85		10-37	M-85		10-37
A-89		10-38	A-89		10-38
B-89		10-39	B-89		10-39
E-86		10-40	E-86		10-40
F-86		10-41	F-86		10-41
G-86		10-42	G-86		10-42
J-86		10-43	J-86		10-43
M-86		10-44	M-86		10-44
A-87		10-45	A-87		10-45
J-87		10-46	J-87		10-46
J-87-A		10-47	J-87-A		10-47
F-88		10-48	F-88		10-48
J-88		10-49	J-88		10-49
K-88		10-50	K-88		10-50
K-88-X		10-51	K-88-X		10-51
M-89		10-52	M-89		10-52
A-90		10-53	A-90		10-53
E-91, E-95		10-54	E-91, E-95		10-54
H-91		10-55	H-91		10-55
H-91-R		10-56	H-91-R		10-56
H-91, H-91-R		10-57	H-91, H-91-R		10-57
E-95		10-58	E-95		10-58
G-95, Radioforte		10-59	G-95, Radioforte		10-59

**RADIOTRON  
COMPLETE  
PAGE**

MODEL	GENERAL ELECTRIC CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
GM125	Alignment, socket, trimmers.....	10-36		
J-125	See RCA R-78			
J-125-A	See RCA R-78			
M-125	Schematic, resistance .....	8-61, 8-62		
E-126	Chassis wiring .....	8-63, 8-64		
	Sentry Box wiring .....	8-65		
	Socket, trimmers, voltage .....	8-66		
	Dial mechanism, alignment .....	8-67		
	oscillograms .....	8-68		
	Alignment, dial notes .....	8-69		
	Circuit data .....	8-70		
	Parts .....			
	See RCA R-281			
	See RCA R-280			
	See RCA Duo 880			
	Schematic, resistance .....	8-71, 8-72		
	Chassis wiring .....	8-73, 8-74		
	Sentry Box wiring .....	8-75		
	Dial mechanism, alignment .....	8-76		
	oscillograms .....	8-77		
	Socket, trimmers, voltage .....	8-78		
	Alignment .....	8-79		
	Circuit data .....	8-80		
	Phonograph data .....	8-81		
	Parts .....			
	See RCA R-381			
	See RCA R-10			
	Schematic, resistance .....	9-49, 50		
	Socket, trimmers, alignment .....	9-51		
	Voltage, chassis wiring .....	9-52		
	Specifications, circuit data, .....	9-53		
	dial mechanism .....	9-54		
	Tuner data, Part 1 .....	9-55		
	Parts list .....	9-56		
	Schematic, resistance .....	8-83, 8-84		
	Circuit data .....	8-85, 8-86		
	Chassis wiring .....	8-87		
	Sentry Box wiring .....	8-88		
	Dial mechanism, alignment .....	8-89		
	oscillograms .....	8-90		
	Socket, trimmers, voltage .....	8-91		
	Alignment .....	8-92		
	Dial data .....			
	Parts .....			
	See Model A205E			
	Schematic .....	9-57, 58		
	Chassis wiring, coil data .....	9-59		
	Speaker and power unit wiring .....	9-60		
	"Sentry Box" wiring .....	9-65		
	Socket, trimmers, voltage .....	9-66		
	Parts list, pick-up data .....	9-72		
	Parts list, concluded .....	9-73		
	Specifications, circuit data, .....	9-69		
	alignment, Part 1 .....	9-70		
	Alignment, Part 2 .....	9-71		
	"Sentry Box" notes, dial and .....	9-74		
	phonograph data .....	9-75, 76		
	Specifications, "Colorama" .....	9-77		
	Schematic .....	9-78		
	Trimmers .....	9-79		
	Phonograph data, installation .....	9-80		
	notes .....	9-81		
	Parts list, concluded .....	9-82		
	Parts list .....	9-83		
	Automatic record changer .....	9-84		
	adjustments .....	9-85		
	Circuit data, alignment, .....	9-86		
	Part 1 .....	9-87		
	Alignment, Part 2 .....	9-88		
	"Sentry Box" notes, dial and .....	9-89		
	phonograph data .....	9-90		
	Pick-up data .....	9-91		
	Schematic .....	9-92		
	Chassis wiring, coil data .....	9-61, 62		
	Speaker and power unit wiring .....	9-63		
	Assembly wiring .....	9-64		
	Automatic record changer .....	9-67		
	adjustments .....	9-68		
	Parts list .....	9-69		
	Alignment, Part 2 .....	9-70		
	"Sentry Box" notes, dial and .....	9-71		
	phonograph data .....	9-72		
	Pick-up data .....	9-61, 62		
	Schematic .....	9-63		
	Chassis wiring, coil data .....	9-64		
	Speaker and power unit wiring .....	9-65		
	Assembly wiring .....	9-67		
	Automatic record changer .....	9-68		
	adjustments .....	9-69		
	Parts list .....	9-70		
	Alignment, Part 2 .....	9-71		
	"Sentry Box" notes, dial and .....	9-72		
	phonograph data .....	9-73		
	Pick-up data .....</			



GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)			RADIOTRON		
MODEL			EARLY COMPLETE PAGE	REVISI PAGE	EARLY COMPLETE PAGE
542, Chassis 5J			Schematic, voltage, socket, trimmers, parts, alignment, chassis	8-38	
550 (5B), Temporary			See model 501		
550 (5B), Temporary			Alignment, parts list	5-5	
551, 553, Chassis 5K			Schematic, trimmers	5-6	
555, 572, Chassis 5L			Schematic, alignment, voltage, parts	8-3	
560, Chassis 5E			Socket trimmers, chassis	8-4	
564, Chassis 5R			Schematic, voltage, alignment, parts	8-5	
566, Chassis 5S			Socket trimmers, chassis	8-6	
570, 571, Chassis 5D, 570X, 571X, Chassis 5DX, 570Z, 571Z, Chassis 5DZ			Schematic, voltage, socket, trimmers, parts, chassis layout	6-5	
572, Chassis 5Q			Alignment	6-6	
576, 578, Chassis 5T			Schematic, voltage, socket, trimmers, chassis, alignment, parts	8-9	
580, 581, Chassis 5G			Schematic, chassis, socket, trimmers, voltage, parts	8-10	
580, 581, Chassis 5G, Revised			Alignment	8-11	
583, 585, 586, 588, Chassis 5W			Schematic, voltage, socket, trimmers, parts	6-7	
587, 589, 599, Chassis 5P, 5U			Alignment	6-8	
590, Chassis 5M			See model 587		
592, 594, Chassis 5N			Schematic, voltage, alignment, parts	8-13	
614, 618 Auto			Socket, trimmers, parts list, notes	7-4	
620, 621, Chassis 6HB			Schematic, parts	9-2	
622, 624, Chassis 6B, 6Q			Schematic, parts	9-3	
623, 627, Chassis 6K			Schematic, voltage, alignment, parts	8-7	
625 Auto			See model 587		
631, 643, Chassis 6M			Schematic, socket, trimmers, chassis, voltage, parts	8-14	
632, Chassis 6H			Alignment, control unit	8-16	
640, 641, Chassis 6J, Temporary			Schematic, voltage	7-7	
640, 641, Chassis 6J, Revised			Socket, trimmers, chassis	7-6	
643			Alignment, parts	7-8	
650, 651 (6A), Temporary			Schematic, parts	9-5	
650, 651, Chassis 6A, Revised			Schematic, socket, trimmers, voltage, chassis, parts	8-15	
654, Chassis 6N			Alignment, control unit	8-16	
660, 661, 662 (6O), Temporary			Schematic, voltage, parts	8-17	
			Socket, trimmers, chassis, alignment	8-18	
			Schematic, chassis, voltage	8-19	
			Socket, trimmers, alignment	8-20	
			Alignment, parts	5-9	
			Schematic, trimmers	5-10	

# GENERAL HOUSEHOLD GENERAL MOTORS

GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
660, 661, 662, Chassis 6C, Revised	Schematic, voltage, resistance, notes Socket trimmers, chassis	7-13 7-14			
663, Chassis 6E	Schematic, parts	9-8			
670, 671 (6D), Temporary	Alignment	5-11			
670, 671, Revised, Chassis 6D; 690, 691, Chassis 6F	Schematic, voltage	5-12 6-13			
680, 681, Chassis 6G	Schematic, trimmers	6-15			
680, 681, Chassis 6G, Revised	Alignment, notes Schematic, voltage	6-16 7-15			
690, 691, Chassis 6F	Socket trimmers, chassis	7-16			
700 w/8A1 Spkr. (Chassis 7-A)	Alignment, parts list	6-14			
700, 701 (Chassis 7-A)	Schematic, condenser assembly	4-7			
700, 701, 801, 901, 902, Chassis 7A, 8A, 9A	Parts list	4-8			
701 w/10A2 Spkr. (Chassis 7-A)	Alignment of I.F.	4-13			
711, Chassis 7NB	Alignment	4-14, 4-15			
720, 721, Chassis 7DB	Socket layouts Schematic, condenser assembly	4-16 4-7			
723, 731, 733, 735, Chassis 7M	Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis, vibrator	8-25 8-26 8-27 8-28			
750, 751, 752, 753 (7B)	Alignment Schematic, notes Socket trimmers, chassis	7-17 7-18 7-19			
755, Chassis 7Q	Schematic, voltage, parts Alignment	8-21 8-22			
760, 761, Chassis 7C	Service notes, socket Schematic, voltage Trimmers, coil data Alignment, parts Schematic, voltage, alignment, parts	5-13 5-14 5-15 5-16 5-17			
801, (Chassis 8A)	Socket trimmers, chassis Schematic, voltage	8-29 8-30			
821, (Chassis 8B)	Socket trimmers, chassis switch & coil assembly Alignment	7-20 7-21 7-22			
823, 831, 833, 835, Chassis 8H	Alignment—See model 700 Schematic, data Parts list Schematic, trimmers, socket parts	4-9 4-10 4-11 4-12			
801, (Chassis 8D)	Alignment Schematic, voltage, parts	6-17 6-18			
871, Chassis 8E	Socket trimmers, chassis Alignment Switch and coil assembly Schematic, voltage Switch and coil assembly, trimmers, chassis layout	8-32 8-33 8-34 6-19 6-20			
901, 902 (Chassis 9A)	Circuit data, socket layout Alignment, parts	6-21 6-22			
901, 902 (9A) Revised 921, Chassis 9C 941, Chassis 9E	Schematic, voltage Socket trimmers, chassis Alignment, parts list Alignment—See model 700 Schematic, data Parts list Schematic Schematic, parts, alignment Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis Alignment, notes Schematic, parts	7-23 7-24 7-25 7-26 4-11 4-12 5-19 7-26 8-35 8-36 8-37 9-9, 10			
1067, Chassis 10D 1091, Chassis 10G	Alignment, parts Schematic, parts	9-11, 12			

## GENERAL MOTORS RADIO CORP.

B and O SPU	Schematic	1-9			
Little General	See model 110				
E-2 Chassis	See model 200				
R-1A Chassis	See model 281				
S-1A, S-1B Chassis	See model 216				
S-2A, S-2B Chassis	See model 251				
S-3A, S-3B Chassis	See model 252				
S-4A, S-4B	See model 292				
Day-Fan 5-AC	Schematic	1-3			
Day-Fan 6	SPU Schematic, data	1-3			
Day-Fan 6 Jr.	Schematic, socket	1-3			
Day-Fan 6-61 (5050)	Schematic, socket	1-4			
OEM-7 (4 tube)	Schematic, socket, data	1-4			
OEM-7 Super-Sel.	Schematic, socket	1-1			
S-9A, S-9-B Chassis	Schematic, socket	1-1			
S-10A, S-10B	See model 211				
OEM-11 (3 tube)	See model 220				
Day-Fan 25, 26, 27, 28, 43, 48	Schematic, socket	1-1			
Day-Fan 35	Schematic, socket, voltage	1-10			
110, 180, 190, Little General	Schematic, socket	1-10			
120, 130, 140 Below Serial #29100A-1700B	Divisor data, notes Schematic, socket, voltage	8-2 1-14			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
1101 (Chassis 9-B, 2-A)	Schematic, data Alignment Socket layout, alignment Parts list	4-17 4-18 4-19 4-20			
1101 (9B-2A) Revised 1151, 1152 (11A), Temporary	Parts list Schematic	4-21 5-20			
1151, 1152, Chassis 11A (Final)	Alignment Schematic, voltage	5-18 6-23			
1151, 1152, 1161, 1162, Chassis 11A (type 2), Chassis 11B	Switch and coil assembly trimmers, chassis layout Switch data, socket Alignment, parts Switch and coil assembly, notes	6-24 6-25 6-26 8-39			
1171, Chassis 11C	Socket trimmers, chassis Schematic, voltage, data	8-40 6-37			
1181, 1183, 1185 Chassis 11H	Parts list	6-38			
1191, 1191B, Chassis 11G	Schematic, voltage Socket trimmers, chassis, switch & coil assembly Mechanical alignment, parts details	7-27 7-28 7-29			
1241, Chassis 12A	Alignment, parts Schematic, parts	7-30 9-13, 14			
1291, 1297, Chassis 12B, 12W (Preliminary)	Schematic, voltage, parts Socket trimmers, chassis Alignment, notes Schematic, voltage Socket trimmers, chassis Alignment, notes Alignment, parts	8-41 8-42 8-43 7-31 7-32 7-33 7-35			
1291, 1297, Chassis 12B, Chassis 12W, Final	Socket trimmers, chassis Alignment	7-34 7-35			
1541, Chassis 15W	Schematic, parts, voltage Socket trimmers, chassis Alignment, Teledial parts Schematic Range & Fidelity switches, schematic, range switch & coil schematic speaker	8-45 8-44 8-46 7-37 7-38			
	Socket trimmers, parts details Chassis, alignment curves Alignment, Part 1 Alignment, Part 2	7-39 7-40 7-41 7-42			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
660, 661, 662, Chassis 6C, Revised	Schematic, voltage, resistance, notes Socket trimmers, chassis	7-13 7-14			
663, Chassis 6E	Schematic, parts	9-8			
670, 671 (6D), Temporary	Alignment	5-11			
670, 671, Revised, Chassis 6D; 690, 691, Chassis 6F	Schematic, voltage	5-12 6-13			
680, 681, Chassis 6G	Schematic, trimmers	6-15			
680, 681, Chassis 6G, Revised	Alignment, notes Schematic, voltage	6-16 7-15			
690, 691, Chassis 6F	Socket trimmers, chassis	7-16			
700 w/8A1 Spkr. (Chassis 7-A)	Alignment, parts list	6-14			
700, 701 (Chassis 7-A)	Schematic, condenser assembly	4-7			
700, 701, 801, 901, 902, Chassis 7A, 8A, 9A	Parts list	4-8			
701 w/10A2 Spkr. (Chassis 7-A)	Alignment of I.F.	4-13			
711, Chassis 7NB	Alignment	4-14, 4-15			
720, 721, Chassis 7DB	Socket layouts Schematic, condenser assembly	4-16 4-7			
723, 731, 733, 735, Chassis 7M	Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis, vibrator	8-25 8-26 8-27 8-28			
750, 751, 752, 753 (7B)	Alignment Schematic, notes Socket trimmers, chassis	7-17 7-18 7-19			
755, Chassis 7Q	Schematic, voltage, parts Alignment	8-21 8-22			
760, 761, Chassis 7C	Service notes, socket Schematic, voltage Trimmers, coil data Alignment, parts Schematic, voltage, alignment, parts	5-13 5-14 5-15 5-16 5-17			
801, (Chassis 8A)	Socket trimmers, chassis Schematic, voltage	8-29 8-30			
821, (Chassis 8B)	Socket trimmers, chassis switch & coil assembly Alignment	7-20 7-21 7-22			
823, 831, 833, 835, Chassis 8H	Alignment—See model 700 Schematic, data Parts list Schematic, trimmers, socket parts	4-9 4-10 4-11 4-12			
801, (Chassis 8D)	Alignment Schematic, voltage, parts	6-17 6-18			
871, Chassis 8E	Socket trimmers, chassis Alignment Switch and coil assembly Schematic, voltage Switch and coil assembly, trimmers, chassis layout	8-32 8-33 8-34 6-19 6-20			
901, 902 (Chassis 9A)	Circuit data, socket layout Alignment, parts	6-21 6-22			
901, 902 (9A) Revised 921, Chassis 9C 941, Chassis 9E	Schematic, voltage Socket trimmers, chassis Alignment, parts list Alignment—See model 700 Schematic, data Parts list Schematic Schematic, parts, alignment Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis Alignment, notes Schematic, parts	7-23 7-24 7-25 7-26 4-11 4-12 5-19 7-26 8-35 8-36 8-37 9-9, 10			
1067, Chassis 10D 1091, Chassis 10G	Alignment, parts Schematic, parts	9-11, 12			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
1101 (Chassis 9-B, 2-A)	Schematic, data Alignment Socket layout, alignment Parts list	4-17 4-18 4-19 4-20			
1101 (9B-2A) Revised 1151, 1152 (11A), Temporary	Parts list Schematic	4-21 5-20			
1151, 1152, Chassis 11A (Final)	Alignment Schematic, voltage	5-18 6-23			
1151, 1152, 1161, 1162, Chassis 11A (type 2), Chassis 11B	Switch and coil assembly trimmers, chassis layout Switch data, socket Alignment, parts Switch and coil assembly, notes	6-24 6-25 6-26 8-39			
1171, Chassis 11C	Socket trimmers, chassis Schematic, voltage, data	8-40 6-37			
1181, 1183, 1185 Chassis 11H	Parts list	6-38			
1191, 1191B, Chassis 11G	Schematic, voltage Socket trimmers, chassis, switch & coil assembly Mechanical alignment, parts details	7-27 7-28 7-29			
1241, Chassis 12A	Alignment, parts Schematic, parts	7-30 9-13, 14			
1291, 1297, Chassis 12B, 12W (Preliminary)	Schematic, voltage, parts Socket trimmers, chassis Alignment, notes Schematic, voltage Socket trimmers, chassis Alignment, notes Alignment, parts	8-41 8-42 8-43 7-31 7-32 7-33 7-35			
1291, 1297, Chassis 12B, Chassis 12W, Final	Socket trimmers, chassis Alignment	7-34 7-35			
1541, Chassis 15W	Schematic, parts, voltage Socket trimmers, chassis Alignment, Teledial parts Schematic Range & Fidelity switches, schematic, range switch & coil schematic speaker	8-45 8-44 8-46 7-37 7-38			
	Socket trimmers, parts details Chassis, alignment curves Alignment, Part 1 Alignment, Part 2	7-39 7-40 7-41 7-42			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
660, 661, 662, Chassis 6C, Revised	Schematic, voltage, resistance, notes Socket trimmers, chassis	7-13 7-14			
663, Chassis 6E	Schematic, parts	9-8			
670, 671 (6D), Temporary	Alignment	5-11			
670, 671, Revised, Chassis 6D; 690, 691, Chassis 6F	Schematic, voltage	5-12 6-13			
680, 681, Chassis 6G	Schematic, trimmers	6-15			
680, 681, Chassis 6G, Revised	Alignment, notes Schematic, voltage	6-16 7-15			
690, 691, Chassis 6F	Socket trimmers, chassis	7-16			
700 w/8A1 Spkr. (Chassis 7-A)	Alignment, parts list	6-14			
700, 701 (Chassis 7-A)	Schematic, condenser assembly	4-7			
700, 701, 801, 901, 902, Chassis 7A, 8A, 9A	Parts list	4-8			
701 w/10A2 Spkr. (Chassis 7-A)	Alignment of I.F.	4-13			
711, Chassis 7NB	Alignment	4-14, 4-15			
720, 721, Chassis 7DB	Socket layouts Schematic, condenser assembly	4-16 4-7			
723, 731, 733, 735, Chassis 7M	Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis, vibrator	8-25 8-26 8-27 8-28			
750, 751, 752, 753 (7B)	Alignment Schematic, notes Socket trimmers, chassis	7-17 7-18 7-19			
755, Chassis 7Q	Schematic, voltage, parts Alignment	8-21 8-22			
760, 761, Chassis 7C	Service notes, socket Schematic, voltage Trimmers, coil data Alignment, parts Schematic, voltage, alignment, parts	5-13 5-14 5-15 5-16 5-17			
801, (Chassis 8A)	Socket trimmers, chassis Schematic, voltage	8-29 8-30			
821, (Chassis 8B)	Socket trimmers, chassis switch & coil assembly Alignment	7-20 7-21 7-22			
823, 831, 833, 835, Chassis 8H	Alignment—See model 700 Schematic, data Parts list Schematic, trimmers, socket parts	4-9 4-10 4-11 4-12			
801, (Chassis 8D)	Alignment Schematic, voltage, parts	6-17 6-18			
871, Chassis 8E	Socket trimmers, chassis Alignment Switch and coil assembly Schematic, voltage Switch and coil assembly, trimmers, chassis layout	8-32 8-33 8-34 6-19 6-20			
901, 902 (Chassis 9A)	Circuit data, socket layout Alignment, parts	6-21 6-22			
901, 902 (9A) Revised 921, Chassis 9C 941, Chassis 9E	Schematic, voltage Socket trimmers, chassis Alignment, parts list Alignment—See model 700 Schematic, data Parts list Schematic Schematic, parts, alignment Schematic, voltage, parts Switch and coil assembly Socket trimmers, chassis Alignment, notes Schematic, parts	7-23 7-24 7-25 7-26 4-11 4-12 5-19 7-26 8-35 8-36 8-37 9-9, 10			
1067, Chassis 10D 1091, Chassis 10G	Alignment, parts Schematic, parts	9-11, 12			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
1101 (Chassis 9-B, 2-A)	Schematic, data Alignment Socket layout, alignment Parts list	4-17 4-18 4-19 4-20			
1101 (9B-2A) Revised 1151, 1152 (11A), Temporary	Parts list Schematic	4-21 5-20			
1151, 1152, Chassis 11A (Final)	Alignment Schematic, voltage	5-18 6-23			
1151, 1152, 1161, 1162, Chassis 11A (type 2), Chassis 11B	Switch and coil assembly trimmers, chassis layout Switch data, socket Alignment, parts Switch and coil assembly, notes	6-24 6-25 6-26 8-39			
1171, Chassis 11C	Socket trimmers, chassis Schematic, voltage, data	8-40 6-37			
1181, 1183, 1185 Chassis 11H	Parts list	6-38			
1191, 1191B, Chassis 11G	Schematic, voltage Socket trimmers, chassis, switch & coil assembly Mechanical alignment, parts details	7-27 7-28 7-29			
1241, Chassis 12A	Alignment, parts Schematic, parts	7-30 9-13, 14			
1291, 1297, Chassis 12B, 12W (Preliminary)	Schematic, voltage, parts Socket trimmers, chassis Alignment, notes Schematic, voltage Socket trimmers, chassis Alignment, notes Alignment, parts	8-41 8-42 8-43 7-31 7-32 7-33 7-35			
1291, 1297, Chassis 12B, Chassis 12W, Final	Socket trimmers, chassis Alignment	7-34 7-35			
1541, Chassis 15W	Schematic, parts, voltage Socket trimmers, chassis Alignment, Teledial parts Schematic Range & Fidelity switches, schematic, range switch & coil schematic speaker	8-45 8-44 8-46 7-37 7-38			
	Socket trimmers, parts details Chassis, alignment curves Alignment, Part 1 Alignment, Part 2	7-39 7-40 7-41 7-42			

## GENERAL HOUSEHOLD UTILITIES CO.—(Cont.)

MODEL	REVISION	REVISION	REVISION	REVISION	PAGE
560, 661, 662, Chassis 6C, Revised	Schematic, voltage, resistance, notes	7-13			7-14
663, Chassis 6E	Socket, trimmers, chassis	7-13			7-14
670, 671 (6D), Temporary	Schematic, parts	9-8			9-8
670, 671, Revised, Chassis 6D; 690, 691, Chassis 6F	Alignment data	5-11			5-11
680, 681, Chassis 6G	Schematic	5-12			5-12
680, 681, Chassis 6G Revised	Schematic, voltage	6-13			6-15
690, 691, Chassis 6F	Schematic, trimmers	6-15			6-16
700 w/8A1 Spkr. (Chassis 7-A)	Alignment, notes	6-16			7-15
700, 701 (Chassis 7-A)	Socket, trimmers, chassis, alignment, parts list	7-16			7-16
700, 701, 801, 901, 902, Chassis 7A, 8A, 9A	Alignment, parts	6-14			6-14
701 w/10A2 Spkr. (Chassis 7-A)	Schematic, condenser assembly	4-7			4-8
711, Chassis 7NB	Parts list	4-8			4-13
720, 721, Chassis 7DB	Alignment of I.F.	4-13			4-14, 4-15
723, 731, 733, 735, Chassis 7M	Socket layouts	4-16			4-16
750, 751, 752, 753 (7B)	Schematic, condenser assembly	4-7			8-25
755, Chassis 7Q	Schematic, voltage, parts	8-25			8-26
760, 761, Chassis 7C	Switch and coil assembly	8-26			8-27
801, (Chassis 8A)	Socket, trimmers, chassis, vibrator	8-27			8-28
821, (Chassis 8B)	Alignment	8-28			7-17
823, 831, 833, 835, Chassis 8H	Schematic, notes	7-17			7-18
836, (Chassis 8D)	Socket, trimmers, chassis	7-18			7-19
837, Chassis 8E	Alignment, parts	7-19			8-21
901, 902 (Chassis 9A)	Schematic, voltage, parts	8-21			8-22
901, 902 (9A) Revised	Socket, trimmers, chassis	8-22			8-23
921, Chassis 9C	Service notes, socket	5-13			5-13
944, Chassis 9E	Schematic, voltage	5-14			5-14
961, (Chassis 8D)	Trimmers, coil data	5-15			5-15
967, Chassis 10D	Alignment, parts	5-16			5-16
991, Chassis 10G	Schematic, voltage, align- ment, parts	8-29			8-30
	Socket, trimmers, chassis	8-30			7-21
	Schematic, voltage	7-21			7-20
	Socket, trimmers, chassis, switch & coil assembly	7-22			7-22
	Alignment & parts	7-22			7-20
	Alignment—See model 700	7-20			7-22
	Schematic, data	4-9			4-10
	Parts list	4-9			4-10
	Schematic, trimmers, socket parts	6-17			6-18
	Alignment	6-18			6-31
	Schematic, voltage, parts	6-31			6-32
	Socket, trimmers, chassis	6-32			6-33
	Alignment	6-33			6-34
	Switch and coil assembly	6-34			6-19
	Schematic, voltage	6-19			6-20
	Switch and coil assembly, trimmers, chassis layout	6-20			6-21
	Circuit data, socket layout	6-21			6-22
	Alignment, parts	6-22			7-23
	Schematic, voltage	7-23			7-24
	Socket trimmers	7-24			7-25
	Alignment, parts list	7-25			4-11
	Alignment—See model 700	4-11			5-19
	Schematic, data	4-11			7-26
	Parts list	4-12			8-35
	Schematic	5-19			8-36
	Schematic, parts, alignment	7-26			8-37
	Schematic, voltage, parts	8-35			9-9, 10
	Switch and coil assembly	8-36			9-11, 12
	Socket, trimmers, chassis	8-36			
	Alignment, notes	8-37			
	Schematic, parts	9-9, 10			
	Schematic, parts	9-11, 12			

EARLY PAGE	RADIOTRON	COMPLETE PAGE
---------------	-----------	------------------

EARLY PAGE	RADIOTRON	COMPLETE PAGE
---------------	-----------	------------------

GOODYEAR TIRE & RUBBER CO., INC. (Cont.)			RADIOTRON	
MODEL	GOODYEAR TIRE & RUBBER CO., INC. (Cont.)	REVISI	EARLY COMPLETE	PAGE
Wings All Weather	See model 101501			
Wings Junior	See model 101500			
404	Schematic, voltage, socket, trimmers, alignment	10-1		
415A Chassis	See Model 010219, Run 1			
415B Chassis	See Model 010219, Run 2			
459 Chassis	See Model 010219, Run 3, 4			
504	Schematic, voltage, socket, trimmers, alignment	10-2		
505 Chassis	See Model 01554			
523 Chassis	See Model 010220, Run 2			
528 Chassis	See Model 010220, Run 2			
528F Chassis	See Model 010220, Run 2			
528F Chassis	See Model 010220, Run 2			
540	Schematic, voltage, socket, alignment, parts	6-1		
550	Schematic, voltage, socket, trimmers, alignment	10-3		
575	Schematic, voltage, socket, trimmers, alignment	6-2		
578, Series A	Schematic, voltage, socket, trimmers, alignment	10-4		
580 Chassis	See Model 01030			
585	Schematic, voltage, socket, trimmers, alignment	10-5		
585, Run 1	Schematic, voltage	9-1		
585, Run 2	Schematic, voltage	9-1		
585, Run 1, Run 2	Socket, trimmers, alignment	9-2		
587	Schematic, voltage, socket, trimmers, alignment	10-6		
588 Chassis	See Model 010212			
601, Runs 1, 2	Schematic, voltage, socket, trimmers, alignment	10-7		
602	Schematic, socket, trimmers, alignment, voltage, parts	8-2		
602, Runs 1, 2	Schematic, voltage, socket, trimmers, alignment	10-8		
602F Chassis	See Model 010211			
602F Chassis	See Model 010222			
601 Chassis	See Model 01019			
606, Runs 1, 2	Schematic, voltage, socket, trimmers, changes	10-9		
667 Chassis	Speaker connections, alignment	10-10		
670	See Model 010110			
675	Schematic, voltage, socket, trimmers	6-3		
675	Alignment, elimination notes	6-4		
691	Schematic, voltage, socket, trimmers	6-5		
691	Alignment	6-6		
741	Schematic, voltage, socket, trimmers	10-11		
741	Alignment	10-12		
749	Schematic, voltage, socket, trimmers, parts	8-7		
777, Run 1	Alignment, trimmers	8-8		
787	Schematic, voltage, socket, trimmers, tuner	10-20		
804 Chassis	Schematic, voltage	7-1		
800 Chassis	Trimmers, socket, parts, layout	7-2		
880 Chassis	Alignment	7-3		
888, 889	Schematic, voltage, socket, trimmers	10-16		
01009, Ch. 526E	Alignment	10-12		
01010, Ch. 526I	See Model 010221			
01018, Runs 1, 2	See Model 01029			
01019 Chassis 661	See Model 01018			
01019 Chassis 661	See Model 01020			
01019 Chassis 661	Schematic, voltage, socket, trimmers, parts	9-3		
01010, Ch. 526I	Schematic, socket, voltage, trimmers, alignment, tuner	10-21		
01018, Runs 1, 2	Schematic, socket, voltage, trimmers, alignment, tuner	10-21		
01019 Chassis 880	Schematic, voltage, socket, trimmers, alignment	10-22		
01019 Chassis 880	Schematic, voltage, socket, trimmers, alignment, parts	8-5		
01020, Chassis 881	Schematic, socket, trimmers, alignment	10-23		
01029, Chassis 860	Schematic, voltage, socket, trimmers	10-24		
01030, Runs 1, 2	Tuner, alignment	10-19		
Oh. 582, Series A.B	Schematic, voltage, socket, trimmers, alignment	10-34		
1070, Runs 1, 2	Tuner	10-21		
1170, 1171	Schematic, socket, trimmers, changes	10-13		
1173 Chassis	Alignment, parts	10-14		
1174 Chassis	Schematic, socket, trimmers, alignment	10-15		
1175	See Model 010217			
01554, Chassis 505	See Model 010218			
010110, Chassis 667	Schematic, voltage	10-17		
010211, Chassis 602E	Socket, trimmers, tuner data	10-18		
010212, Chassis 588	Alignment	10-19		
010217, Chassis 1173	Schematic, voltage, socket, trimmers	10-25		
010218, Chassis 1174	Schematic, voltage, socket, trimmers, parts	8-6		
010219, Run 1	Schematic, voltage, socket, trimmers, alignment	10-26		
Chassis 415-A	Schematic, voltage, socket, trimmers, parts	8-3		
010219, Run 2	Alignment, notes	8-4		
Chassis 415-B	Schematic, socket, trimmers, parts	8-9		
010219, Runs 3, 4	Alignment, notes	8-9		
Chassis 489, Series A	Schematic, voltage, socket, trimmers	10-29		
Issues A and B	Alignment, notes	8-10		
010220, Chassis 523	Schematic, voltage, socket, trimmers, parts	9-5		
010220, Run 2	Alignment	9-6		
Chassis 528B	Schematic, voltage, socket, trimmers, alignment	10-27		
010221, Chassis 804	Schematic, voltage, socket, trimmers, alignment	10-23		
010222, Chassis 6021	Schematic, voltage, socket, trimmers	10-29		
015040	Trimners, alignment	10-31		
015050	Schematic, voltage, socket, trimmers, alignment	10-32		
015060	Schematic, voltage, socket, trimmers, alignment	10-26		
015070	Schematic, voltage, socket, trimmers, alignment	10-35		
015080	Tuner data	10-37		
015090	Schematic, voltage, socket, trimmers, alignment	10-36		
015090	Tuner data	10-37		
015100	Schematic, voltage, socket, trimmers	10-38		
015110	Alignment	10-41		
015120	Schematic, voltage, socket, trimmers	10-39		
015130	Tuner data	10-42		
	Schematic, voltage, socket, trimmers, alignment	10-43		
	Tuner data	10-44		
	Schematic, voltage, socket, trimmers, alignment	10-37		
	Tuner data	10-45		
	Schematic, voltage, socket, trimmers, alignment	10-37		
	Socket, trimmers	10-46		
	Alignment	10-43		
	Tuner data	10-41		
	Schematic, voltage	10-49		

**GOODYEAR TIRE & RUBBER CO., INC.—(Cont.)**

MODEL	EARLY COMPLETE PAGE	REVISED PAGE
015130	Alignment	10-41
100502, Double Eagle	Tuner data	10-37
Above Serial 42,000	Schematic, changes, tuner	10-47
101500, Wings Junior	Early schematic of coils, early, late alignment, socket, trimmers	10-48
101501, Wings All Weather	Schematic, voltage, alignment, tuner, socket, trimmers	9-7
101503	Installation, parts	9-8
103553	Tuner data	9-10
	Schematic, voltage, alignment, socket, trimmers	9-9
	Installation, tuner, parts	9-10
	Schematic, voltage	9-11
	Socket, trimmers, chassis, alignment, tuner, coils, parts	9-12
	Tuner data	9-10
	Schematic, socket, trimmers, voltage, alignment	10-50

**GRAYBAR ELECTRIC CO.**

GB-4	See RCA Radiola R-5
GT-7	See RCA Radiola R-4
GB-8	See RCA Radiola R-7
GB-8-A	See RCA Radiola R-7-A
GT-8	See RCA Radiola R-8
GT-8-56	See RCA Radiola R-71
GT-8-69	See RCA Radiola R-72
GB-9	See RCA Radiola R-11
GT-10-69	See RCA Radiola R-74
GT-10-88	See RCA Radiola R-76
GT-10-99	See RCA Radiola R-77
GO-18	See RCA R-5
GO-14	See RCA Radiola R-12
GO-15	See RCA Radiola R-6
GB-100	See RCA Radiola R-55
GB-300	See RCA Radiola R-16
GB-810	See RCA Radiola R-18
811	See RCA Radiola R-33
GB-811	See RCA Radiola R-33
GB-380	See RCA Radiola R-60
840	See RCA Radiola R-62
GB-340	See RCA Radiola R-62
600	See RCA Radiola R-44
GB-500	See RCA Radiola R-44
550	See RCA Radiola R-46
GB-550	See RCA Radiola R-46
600	See RCA Radiola R-66
GB-600	See RCA Radiola R-66
GB-678	See RCA Radiola R-48
GB-700	See RCA Radiola R-80
GB-770	See RCA Radiola R-82
GB-900	See RCA Radiola R-86
GB-989	See RCA Radiola R-10

**A. H. GREBE & CO.**

Broadcast Receiver	Schematic	1-6
Synchrophase 1925	Schematic	1-11
RORB	Schematic	1-11
RORD	Schematic	1-11
RORE	Schematic	1-11
RORF	Schematic	1-11
RORG	Schematic	1-11
RORH	Schematic	1-12
RORJ	Schematic	1-12
RORK	Schematic	1-12
RORL	Schematic	1-12
RORN	Schematic	1-12
RORO	Schematic	1-12
RORQ	Schematic	1-12
AR-1	Schematic, socket, voltage	1-20
Synchrophase MU-1	Schematic	1-11
CR-2	Schematic	1-11
Synchrophase MU-2	Socket layout	1-12
CR-3	Schematic, socket, voltage	1-12
	Schematic	1-14

**RADIOTRON**

MODEL	EARLY COMPLETE PAGE	REVISED PAGE
015130	Alignment	10-41
100502, Double Eagle	Tuner data	10-37
Above Serial 42,000	Schematic, changes, tuner	10-47
101500, Wings Junior	Early schematic of coils, early, late alignment, socket, trimmers	10-48
101501, Wings All Weather	Schematic, voltage, alignment, tuner, socket, trimmers	9-7
101503	Installation, parts	9-8
103553	Tuner data	9-10
	Schematic, voltage, alignment, socket, trimmers	9-9
	Installation, tuner, parts	9-10
	Schematic, voltage	9-11
	Socket, trimmers, chassis, alignment, tuner, coils, parts	9-12
	Tuner data	9-10
	Schematic, socket, trimmers, voltage, alignment	10-50

**A. H. GREBE & CO.—(Cont.)**

MODEL	EARLY COMPLETE PAGE	REVISED PAGE
HS-3	Schematic	3-1
CR-4	Schematic	1-4
HS-4, 1 Pentode	Schematic, socket, voltage	1-21
HS-4 with '45 Pushpull	Schematic, socket, voltage	1-22
Synchrophase SK-4, Early	Schematic, socket, voltage	1-19
Synchrophase SK-4, Late	Schematic	3-2
CR-5	Schematic	1-5
HS-5	Schematic, socket, voltage	1-23
Synchrophase 5, 671 SPU	Schematic, socket, voltage	1-10
Synchrophase AC-6	Schematic, socket, voltage	1-15
Synchrophase AC-6 SPU	Chassis wiring (2 types)	1-16
CR-6	Schematic	1-5
HS-6	Schematic, socket	3-3
HS-7	Schematic, socket	1-5
CR-7	Schematic, socket	3-4
Synchrophase 7 Battery	Schematic, socket, voltage	1-17
Synchrophase 7 AO	Schematic, socket, voltage	1-18
CR-8	Schematic, socket	1-5
HS-8	Schematic, socket	3-5
CR-9	Schematic	1-7
HS-11	Schematic	4-5
CR-12	Schematic, socket	1-6
HS-12	Schematic	3-6
CR-13	Schematic	1-8
CR-14	Schematic, socket	1-8
CR-18 (Special)	Schematic, socket	1-7
CR-18 (1 A-F Stage)	Schematic	1-9
61-R	Socket, alignment data, vibrator data	4-2
89	Schematic	4-3
111-B	Schematic	4-4
412 Pushpull Amplifier	Schematic, chassis wiring	4-1
428 Deluxe Console	Schematic	1-13
671 SPU	Schematic	1-14
671-B Power Unit	See model Synchrophase 5	1-17
<b>GRIGSBY-CRUNOW CO.</b>		
7-P-6, 7-P-3 (2 types)	Schematic	1-2
7-P-6, 7-P-3 (Old wiring)	Chassis wiring	1-3
7-P-6, 7-P-3	Chassis wiring	1-4
7-BP-6, 7-BP-3	Schematic	1-6
8-P-6, 8-P-3	Chassis wiring	1-7
9-P-3, 9-P-6	Schematic, chassis wiring	1-9
10 Chassis, 11, 59, 204,	Schematic, socket, voltage, data	1-24
294 G-13-C, PM Speakers	Schematic, voltage	3-14
G-13, G-19-B, G-19-O	Alignment notes	3-15
G-14-F, G-19-B, G-19-O	Two views, data	3-9
15, 15-B, 150 Chassis,	Notes	3-18
151, 153, 154, 155, 156	Schematic, data	2-4
Below Serial #65,149,	Voltage, chassis views	2-5
15, 15-B, 150 Chassis,	Schematic	2-6
Above Serial #65,150	Chassis views	2-7
15-B Chassis	See model G-14-F	
G-19-B, G-19-O	Schematic, socket, voltage, data	1-14
20 Chassis, 21, 22, 23	Chassis views	1-15
25 Service Notes	See model 120	
25 Chassis, 251, 258, 264	Schematic	2-8
25-B Chassis, 251-B,	Voltage, chassis views	2-9
253-B, 254-B	Schematic, voltage, data	2-10
30 Chassis, 31	Chassis views, parts list	2-11
35 Chassis, 351, 353	Alignment data	2-13
44, 49, 194 (Chassis 440)	Speaker connections	2-15
50 Chassis, 51, 53	Schematic, socket	1-16
	Voltage, data	1-17
	Schematic, voltage, data	2-12
	Chassis views	2-14
	Alignment data, chassis	2-13
	Speaker connections	2-15
	Chassis views, voltage, parts list	4-11
	Schematic, parts list, point-to-point data, socket	4-12
	Schematic, socket, voltage	1-18

GRIGSBY-GRUNOW CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
50 Chassis, 51, 52			200 Chassis, 201, 203, 204		
55 Chassis, 56, 57, 58			204		
55, 59, 75, 195, 560, 566 (Chassis 500)			210 Chassis, 211, 214, 215		
55, 57, 59			220 Chassis, 221, 228		
58			230-A, 238		
59 (Chassis 500)			251, 253, 254		
60 Chassis, 61, 62			251-B, 253-B, 254-B		
66			290 Chassis, 291, 293, 294		
70 Chassis, 71, 72			294		
70-B Chassis, 71, 72			300 Chassis, 303, 304, 307		
75 (Chassis 500)			310-A Chassis, (2 types), 311		
77			310-A		
85, 86, 998 (Chassis 800)			310-A, 310-B		
90 Chassis, 91, 92			310-B		
90-B Chassis, 90, 91, 98			310-B Chassis, (2 types), 314, 315		
95, 105 (Chassis 520)			320 Chassis, 324		
100 Chassis, 101			330 Chassis, 331, 336, 77		
100-B Chassis, 102, 103			340 Chassis, 344		
105			351, 353		
110 Auto Set			353 Record Changer		
1114			360 Chassis, 363		
1116			370 Chassis, 371, 373		
Duro-Mite for 116			400 Chassis, 411, 413		
116, Type 1			400-A Chassis, 411-A, 413-A		
116, Type 3			Chassis 440		
1116, Type 4			460, 461, 469		
1118			490, 491, 493		
1120 Chassis, 121					
120-B Chassis, 123					
130-A, 130, 131, 132					
150					
151, 153, 154, 156					
160 Chassis, 163					
180 Chassis, 181					
194					
195 (Chassis 500)					

## GRIGSBY

MODEL	GRIGSBY-GRUNOW CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
490, 491, 493	Alignment, voltage, condenser assembly	4-18		
	Schematic, socket, condenser	4-19		
	Point-to-point data	4-20		
	Parts list	4-21		
	Parts list concluded	4-22		
	See model 55			
Chassis 500	See model 55 (Chassis 500)	5-3		
Chassis 520	Schematic	5-4		
560, 566	See model 85			
570	See model 85			
600 AO-DO				
Chassis 800				
998				
<b>DAVID GRIMES, INC.</b>				
Inverse Duplex, type 4-DL	Schematic	Misc. 1-9	*388	
Inverse Duplex, 1927	Schematic	Misc. 1-9	*988	
New Yorker, 110-volt DO	Schematic	Misc. 1-9	*388	
<b>GRUNOW</b>				
<b>See GENERAL HOUSEHOLD UTILITIES CO.</b>				
<b>GULBRANSEN CO.</b>				
06-W	Schematic, voltage, socket	4-9		
	Alignment	4-10		
	Mounting data	4-11		
	Speaker data	4-12		
	Flexible drive notes	4-13		
	Wiring notes, maintenance	4-14		
	Service notes	4-15		
	Schematic, voltage, socket	4-16		
	Alignment, wiring	4-17		
	Antenna, mounting notes	4-18		
	Mounting notes	4-19		
	Control unit	4-20		
	Flexible drive	4-21		
	Service notes	4-22		
	Parts list	4-23		
	Schematic, voltage	4-24		
	Alignment, antenna notes	4-1		
	Service notes	4-2		
	Service notes	4-3		
	Parts list	4-4		
	Mounting notes	4-5		
	Flexible drive notes	4-6		
	Control unit data	4-7		
	Schematic	4-8		
	Voltage, condenser data	4-9		
	Schematic, socket	4-10		
	Chassis wiring	2-1		
	Voltage, data, phonograph schematic	2-2		
	Color code, installation data	2-3		
	Alignment data	2-4		
	Schematic	2-5		
	Voltage, alignment data	2-6		
	Chassis layout, parts list	2-7		
	Schematic, socket	2-8		
	Chassis wiring	2-9		
	Voltage, notes, phonograph schematic	2-10		
	Parts list, phonograph data	2-11		
	Alignment data	2-12		
	Chassis layout, revisions	2-13		
	Chassis wiring	2-14		
	Schematic, voltage, data	3-1		
	Schematic, socket, notes	3-2		
	Voltage, parts	3-3		
	Schematic, socket, voltage	3-4		
	Chassis wiring, data	3-5		
	Schematic, chassis wiring, data	3-6		
	Voltage, data	3-7		
	Schematic, data	3-8		
	Schematic, voltage	1-3		
	Schematic, voltage	1-4		
10 Series				
18				
20 Series, Early, Late				
20 Series				
28				
53 Battery				
53 A. C.				
60, 63				
92, 98				
160, 161 (60 cycles)				
160, 163 (25 cycles)				

# HALLICRAFTERS HARRIS

RADIOTRON  
EARLY COMPLETE  
PAGE

1273

REVISÉ  
PAGE

HALSON RADIO CORP.—(Cont.)

MODEL

615 Schematic ..... 3-3  
620 Socket layout ..... Changes 7-9  
630 Schematic, socket, alignment ..... 5-5  
711 Schematic, socket, alignment ..... 5-5  
770-AW See model 310  
770-AW Schematic, socket ..... 6-6  
1200 Schematic, socket ..... 9-8  
1900 Schematic, parts ..... 9-9, 10

## HAMMARLUND MFG. CO.

AC & DC Converters ..... 1-1  
Comet Pro, Dec., '31 ..... 3-1  
Comet Pro, July, '32 ..... 3-1  
Comet Pro, Sept., '32 ..... 3-2  
Comet Pro, Oct., '32 ..... 3-2  
Comet Pro, Feb., '33 ..... 3-1  
"Comet Pro" AVO ..... 5-1  
"Comet Pro" (Crystal) ..... 5-2  
Schematic ..... 4-5  
Chassis view ..... 4-6  
Service notes ..... 4-7  
Schematic ..... 4-3  
Chassis view ..... 4-3  
Service notes ..... 4-4  
Schematic ..... 4-1  
Schematic ..... 1-1  
Schematic, voltage, trimmers ..... 7-1, 7-2  
Parts list ..... 7-3, 7-4  
Alignment, part 1 ..... 7-5  
Alignment, part 2, socket, chassis ..... 7-6  
Circuit data, operating notes ..... 7-7  
Schematic ..... 1-1  
Schematic ..... 1-1  
Schematic, trimmers, crystal circuit, terminal voltages 9-1, 2

## "Comet Pro" (Standard)

DeLuxe  
Hawk  
Super Pro

Trans-Oceanic Two  
Z-4 Commander  
SPI110X, SPI20X,  
SPR110X, SPR120X  
Super Pro Standard  
Model SPI110 Series

HQ-120X, Crystal

## HAMMARLUND-ROBERTS, INC.

H-R 5-tube ..... 1-1  
H-R "Hi-Q" ..... 1-1  
H-R "Hi-Q" 6 ..... 1-2  
H-R "Hi-Q" 29 Jr. ..... 1-4  
H-R "Hi-Q" 29 Master ..... 1-5  
H-R "Hi-Q" 30 (30-R Battery) ..... 1-5  
H-R "Hi-Q" 30 AC ..... 1-5  
H-R "Hi-Q" 30 DO ..... 1-6  
H-R "Hi-Q" 81 ..... 1-6  
100, "A" ..... Misc. 9-4  
500, 600, 700 ..... Schematic, socket, trimmers, voltage ..... 8-1  
501W, 701W, 900, 1201W ..... Schematic, socket, trimmers, voltage ..... 8-2  
800 ..... Schematic, socket, trimmers, voltage ..... 8-3  
1000 ..... Schematic, socket, trimmers, voltage ..... 8-4  
1201W ..... See model 501W

## HARRIS MFG. CO.

100, "A" ..... Misc. 9-4  
500, 600, 700 ..... Schematic, socket, trimmers, voltage ..... 8-1  
501W, 701W, 900, 1201W ..... Schematic, socket, trimmers, voltage ..... 8-2  
800 ..... Schematic, socket, trimmers, voltage ..... 8-3  
1000 ..... Schematic, socket, trimmers, voltage ..... 8-4  
1201W ..... See model 501W

RADIOTRON  
EARLY COMPLETE  
PAGE

1273

REVISÉ  
PAGE

THE HALLICRAFTERS INC.—(Cont.)

MODEL

SX23, Super Skyriders, R-F switching schematic ..... 10-12  
Skyriders 23  
Socket, trimmers, parts ..... 10-13  
Alignment, notes ..... 10-14  
Schematic ..... 10-15  
Antenna notes ..... 10-10  
Socket, trimmers, alignment, parts ..... 10-16

## HALSON RADIO CORP.

Dual Range "Roadmaster" ..... 3-2  
Schematic ..... 4-5  
Socket layout ..... Changes 7-9  
I-F Peaks ..... Changes 7-4  
A-5 Schematic, socket, trimmers, alignment ..... 9-1  
A-5S, S-5 Schematic, socket, alignment, trimmers ..... Misc. 10-6  
51E Schematic, socket ..... 7-1  
MG-5 Schematic, socket ..... 7-1  
AW6 Schematic, socket, trimmers, alignment ..... 7-2  
C-6, 163 Schematic, socket, trimmers, alignment ..... 9-1  
61G Schematic, socket ..... 7-3  
10 Schematic, socket, trimmers, alignment, parts ..... 9-2  
20 Schematic, socket, trimmers, alignment, parts ..... 9-3  
20-A Schematic ..... 4-1  
Socket layout ..... Changes 7-9  
20-B Schematic ..... 4-1  
Socket layout ..... Changes 7-9  
20-B European Schematic ..... 4-2  
25 Schematic, socket, trimmers, alignment, voltage, parts ..... 8-1  
30 Schematic, socket, trimmers, alignment, parts ..... 9-4  
35 Schematic, socket, trimmers, alignment, voltage, parts ..... 8-2  
N.S. 40 Schematic ..... 4-3  
Socket layout ..... Changes 7-9  
45 Schematic, socket ..... 6-1  
N.S. 60 Schematic ..... 4-3  
Socket layout ..... Changes 7-9  
50S Schematic, socket ..... 7-4  
50X Schematic, socket ..... 7-5  
52 Schematic, socket ..... 6-1  
54 Schematic, socket ..... 6-2  
60L Schematic ..... 7-7  
60M Schematic ..... 7-6  
MAG3 Schematic, socket ..... 7-8  
66-AW Schematic, socket, notes, parts ..... 6-3  
100, 100M Schematic, socket, trimmers ..... 7-9  
102, 103 Schematic, socket, trimmers, alignment, parts ..... 8-3  
104, 106 Schematic, socket, trimmers, alignment, parts ..... 8-4  
161, 162 Schematic, socket, trimmers, alignment, voltage, parts ..... 8-5  
163 See model C-6  
310, 711 Schematic, socket, trimmers, alignment, voltage, parts ..... 8-6  
410 Schematic, socket, parts ..... 5-1  
412 Schematic, socket, trimmers, alignment, parts ..... 9-5  
515 SW Schematic ..... 3-1  
515 Schematic ..... 3-1  
Socket layout ..... Changes 7-9  
516 Schematic ..... 3-3  
520 Schematic, socket, alignment ..... 5-2  
520 Schematic, socket, alignment ..... 5-3  
525 Schematic, socket, parts ..... 6-4  
526 Schematic, socket ..... 7-10  
530 Schematic, socket, parts ..... 6-5  
606 Schematic, socket, trimmers, alignment, parts ..... 9-6  
610 Dual Wave Schematic, socket, alignment ..... 5-4  
610 Schematic ..... 4-4  
612 Schematic, socket, trimmers, alignment, parts ..... 9-7

1271

1271

1273



HATRY & YOUNG			RADIOTRON		
MODEL	REVISION	PAGE	EARLY COMPLETE	PAGE	
H-Y 7	Schematic, parts list	Misc. 1-10	*784	2754	
H-X 7, Battery	Schematic	Misc. 1-10	*784	2754	
H-Y 7-B	Schematic	Misc. 1-10	*784	2754	
HETRO ELECTRICAL INDUSTRIES					
A, B Tuners	Installation data	9-5			
	Installation, concluded, adjustments, operating data	9-6			
6-Tube AO	Schematic, voltage, socket, trimmers, alignment	6-11			
6-Tube, AC-DO	Schematic, voltage, socket, trimmers, alignment	6-12			
8-Tube Superhet	Schematic, alignment	6-13			
	Voltage, socket, parts, trimmers	6-14			
9-Tube Air-Ace	Schematic, socket, trimmers, voltage	6-15			
	Alignment	6-16			
F5, F6, F7, F8	Changes	7-4			
6LB, 6SB	Schematic, alignment	Misc. 8-2			
	Schematic, socket, trimmers, alignment, battery connections	8-2			
F-9 to F-12 incl. Series FA	Schematic	6-4			
F-13 to F-20 incl. Series FA	Schematic	7-1			
F-21 to F-28 incl. Series FA	Schematic	7-2			
22, 2 types	Schematic, voltage	6-1			
31, 2 types	Schematic, voltage	6-2			
H47, H48	Schematic	9-12			
H61, H62, HP61, HP62	Schematic, voltage, parts, phonograph circuit	9-1			
	Socket, trimmers, alignment	9-2			
H63, H64, HP63, HP64	Schematic, voltage, parts, phonograph circuit	9-3			
	Socket, trimmers, alignment	9-4			
H67	Schematic, voltage	9-5			
71	Schematic, voltage	9-6			
H85, H93, HP85, HP93	Schematic, voltage, parts, phonograph circuit	9-7			
	Socket, trimmers, alignment	9-8			
H87, HP87	Schematic, voltage, parts, phonograph circuit	9-9			
	Socket, trimmers, alignment	9-10			
207, 257	Schematic, parts	6-5			
209, 259	Schematic, parts	6-6			
251	Schematic	6-7			
293, Series V	Schematic	7-4			
295	Schematic, parts	6-8			
297	Schematic, parts	6-9			
412	Schematic, socket	6-10			
468	Schematic, socket	6-11			
10310, 10410, 10510, 10610, Series B	Schematic	9-11			
14610, 14710, 15010, 15110, 15210, 15010, 14810, 14690, 14910, 14990	Schematic	9-13			
	Schematic	9-14			
HICKOK ELECTRICAL INSTRUMENT CO.					
48 Volt-Ohmmeter	Schematic	3-1			
4600 Tester	Schematic	3-1			
4700 Tester	Schematic	3-1			
4949 Volt-Ohm-Capacity Meter	Schematic	3-2			
HIGH FREQUENCY LABORATORIES					
A-C Special	Schematic	1-1	*787	1287	
Mastertone 1929	Schematic	1-2	*890	1288	
4-Tube Pentode	Schematic voltage	Misc. 6-12			
9-in-Line	Schematic	1-1	*787	1287	
Isotone 10	Schematic	1-2	*890	1288	
117-4	Schematic	3-1			
160-6	Schematic	3-2			
200	Schematic	3-2			
222	Schematic	3-1			
CHARLES HOODWIN CO.					
MODEL	REVISION	PAGE	EARLY COMPLETE	PAGE	
Aero A-F Amplifier	Schematic	4-7			
Aero Auto Set	Schematic	2-1			
Aero 1932 Converter	Schematic	3-1			
A (1932), Aero Pentode	Schematic	3-2			
Auto	Schematic	4-1			
B (1932), Aero Pentode	Schematic	4-1			
Auto	Schematic	4-1			
1-Tube SW	Schematic	4-1			
2-Tube SW	Schematic	4-2			
4-Tube SW	Schematic	4-6			
4-Tube TRF	Schematic	4-6			
5-Tube TRF	Schematic	4-7			
5-Tube DO	Schematic	4-7			
5-Tube AC	Schematic	4-7			
6-Tube DO Superhet	Schematic	4-2			
6-Tube AC Superhet	Schematic	4-3			
6-Tube 32-volt DC Super	Schematic	4-4			
6-Tube 110-volt DC Super	Schematic	4-5			
"International Aero" 11-Tube All-Wave	Schematic	4-8			
HERBERT H. HORN					
1934	Schematic	5-2			
4T	Schematic	9-1			
5	Schematic	6-1			
5A	Schematic	7-1			
5MT	Schematic	6-2			
5MTD	Schematic	7-2			
7MT	Schematic	6-3			
9MT, 9MTC	Schematic	6-4			
9MT, 9MTC, Revised	Schematic	7-3			
10MT	Schematic	7-4			
11A	Schematic	9-2			
15	Schematic, voltage, data	3-1			
15M	Service data	3-2			
	Schematic, voltage, socket, notes	6-5			
16MT	Schematic	8-1			
17MT	Schematic	7-5			
21, 25	Schematic	4-1			
24	Schematic	4-2			
36	Schematic	4-2			
50, 50B	Schematic	9-1			
51	Schematic	7-6			
52	Schematic	7-7			
55	Schematic	6-1			
58	Schematic	4-3			
58, 158	Schematic, socket	5-2			
59, 69, 90	Schematic, socket, voltage	3-3			
62	Schematic	7-6			
63	Schematic	7-8			
66	Schematic	6-6			
66MT	Schematic	6-9			
66MT, Revised	Schematic	7-1			
67	Schematic	9-3			
69	See model 59				
70, 71	Schematic	3-4			
	Voltage, socket, data	3-5			
76	Schematic	6-1			
77	Schematic	6-7			
79, 99, 109	Schematic, voltage, socket	6-7			
83	Alignment, changes	6-8			
87	Schematic	7-8			
90	Schematic	9-4			
97	See model 59				
101, 110	Schematic	9-4			
	Schematic, socket, data	2-1			
101-B, 102	Voltage, alignment data	2-2			
	Schematic	3-6			
	Voltage, socket	3-7			
	Condenser adjustments	3-8			
109	See model 79				
110	See model 101				
112-A	Schematic	5-1			
156	Schematic	5-2			
156AW	Schematic	4-4			
	Schematic	6-2			
RADIOTRON					
MODEL	REVISION	PAGE	EARLY COMPLETE	PAGE	
Aero A-F Amplifier	Schematic	4-7			
Aero Auto Set	Schematic	2-1			
Aero 1932 Converter	Schematic	3-1			
A (1932), Aero Pentode	Schematic	3-2			
Auto	Schematic	4-1			
B (1932), Aero Pentode	Schematic	4-1			
Auto	Schematic	4-1			
1-Tube SW	Schematic	4-1			
2-Tube SW	Schematic	4-2			
4-Tube SW	Schematic	4-6			
4-Tube TRF	Schematic	4-6			
5-Tube TRF	Schematic	4-7			
5-Tube DO	Schematic	4-7			
5-Tube AC	Schematic	4-7			
6-Tube DO Superhet	Schematic	4-2			
6-Tube AC Superhet	Schematic	4-3			
6-Tube 32-volt DC Super	Schematic	4-4			
6-Tube 110-volt DC Super	Schematic	4-5			
"International Aero" 11-Tube All-Wave	Schematic	4-8			
HERBERT H. HORN					
1934	Schematic	5-2			
4T	Schematic	9-1			
5	Schematic	6-1			
5A	Schematic	7-1			
5MT	Schematic	6-2			
5MTD	Schematic	7-2			
7MT	Schematic	6-3			
9MT, 9MTC	Schematic	6-4			
9MT, 9MTC, Revised	Schematic	7-3			
10MT	Schematic	7-4			
11A	Schematic	9-2			
15	Schematic, voltage, data	3-1			
15M	Service data	3-2			
	Schematic, voltage, socket, notes	6-5			
16MT	Schematic	8-1			
17MT	Schematic	7-5			
21, 25	Schematic	4-1			
24	Schematic	4-2			
36	Schematic	4-2			
50, 50B	Schematic	9-1			
51	Schematic	7-6			
52	Schematic	7-7			
55	Schematic	6-1			
58	Schematic	4-3			
58, 158	Schematic, socket	5-2			
59, 69, 90	Schematic, socket, voltage	3-3			
62	Schematic	7-6			
63	Schematic	7-8			
66	Schematic	6-6			
66MT	Schematic	6-9			
66MT, Revised	Schematic	7-1			
67	Schematic	9-3			
69	See model 59				
70, 71	Schematic	3-4			
	Voltage, socket, data	3-5			
76	Schematic	6-1			
77	Schematic	6-7			
79, 99, 109	Schematic, voltage, socket	6-7			
83	Alignment, changes	6-8			
87	Schematic	7-8			
90	Schematic	9-4			
97	See model 59				
101, 110	Schematic	9-4			
	Schematic, socket, data	2-1			
101-B, 102	Voltage, alignment data	2-2			
	Schematic	3-6			
	Voltage, socket	3-7			
	Condenser adjustments	3-8			
109	See model 79				
110	See model 101				
112-A	Schematic	5-1			
156	Schematic	5-2			
156AW	Schematic	4-4			
	Schematic	6-2			

# HORN HOWARD

MODEL	HERBERT H. HORN—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
158	Schematic .....4-4	4-4		
518	Socket, schematic—See model 58			
585	Schematic .....7-7	7-7		
587, 588	Schematic .....5-2	5-2		
<b>HOWARD RADIO CO.</b>				
Intermediate Frequencies				
A (SW Converter)	I-F Peaks .....Changes 7-4	7-4		
AVH, AVH-P Chassis	Schematic, socket .....3-9	3-9		
AVO Chassis	See models 45 & 60			
D-F	See model 35-A			
EX, Dual Range	Chassis wiring .....6-5	6-5		
F	Alignment .....6-6	6-6		
F Pentode	Schematic, socket .....3-2	3-2		
H Chassis (35-40)	Schematic, voltage .....6-4	6-4		
Pushpull 47s	Schematic .....2-1	2-1		
	Chassis views .....2-5	2-5		
H Chassis, (35, 40) Push- pull 45	Schematic, socket .....2-3	2-3		
	Adjustment data .....2-4	2-4		
	Schematic, socket .....3-3	3-3		
K Chassis	Alignment data .....3-4	3-4		
L Chassis	See model 400			
M Chassis	Revisions .....3-6	3-6		
M Chassis 1st type	Revisions .....3-6	3-6		
O Chassis	Schematic .....3-7	3-7		
Q	See model 20			
SG "A" RF Chassis	Alignment data .....4-2	4-2		
SG "C" RF Chassis	Schematic, voltage .....4-3	4-3		
SG "A" RF Chassis	Socket layout .....Changes 7-9	7-9		
SG "A" RF Chassis	Schematic .....1-6	1-6		
SG "C" AF Chassis	Schematic .....1-6	1-6		
SG "C" AF Chassis	Schematic .....1-7	1-7		
SG "B" (Miniature)	Schematic, socket .....2-14	2-14		
SG-T	Schematic, socket .....2-10	2-10		
	Chassis views, parts list, data .....2-11	2-11		
T Chassis	See model 10			
W, Explorer, (Type 1)	Schematic .....5-4	5-4		
W, Explorer (Type 2)	Schematic .....5-5	5-5		
W, Explorer Power	Schematic .....5-6	5-6		
W, Amplifier	Socket layout, trimmers .....5-7	5-7		
W, Explorer Receiver	Socket layout, trimmers .....5-8	5-8		
	Notes, alignment .....5-9	5-9		
	I-F, Alignment, R-F, Oscillator alignment .....5-10	5-10		
	Power amplifier notes, parts list .....5-11	5-11		
	Parts list .....5-12	5-12		
	Schematic, voltage .....6-13	6-13		
	Power pack schematic .....6-14	6-14		
	Socket layout .....Changes 7-9	7-9		
	Schematic .....6-15	6-15		
	Amplifier & SPU schematic .....6-16	6-16		
Grand, Series 1	Schematic .....7-1	7-1		
Grand, Series 2	Socket, trimmers, alignment data .....7-2	7-2		
Green Diamond "8"	Schematic, socket, voltage data .....1-3	1-3		
(Mag. Spkr.)	Schematic, socket, voltage data .....1-4	1-4		
Green Diamond "8"	Schematic, socket, voltage data .....1-5	1-5		
(Dynam. Spkr. "71")	Adjustments .....10-16	10-16		
Green Diamond "8"	Changes .....10-17	10-17		
(Dynam. Spkr. "45")	See model 670-A			
1, 2, "Penn-A-Matic"	See model 52			
Tuner	Schematic .....4-1	4-1		
HA-1	Socket layout .....Changes 7-9	7-9		
HA-2	Alignment data .....4-4	4-4		
S-2, S-7	Schematic, voltage .....4-5	4-5		
X-2, X-3, Y-3	Socket layout .....Changes 7-9	7-9		
HA-3	Schematic, socket, alignment, notes .....6-11	6-11		
<b>HOWARD RADIO CO.—(Cont.)</b>				
MODEL		REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
J-8 Compact	Schematic, changes .....3-12	3-12		
4B	Schematic, voltage, notes .....10-1	10-1		
	Alignment .....10-7	10-7		
	Socket, trimmers, tuner data, dial .....10-8	10-8		
4BT	Schematic, voltage, notes .....10-2	10-2		
	Alignment .....10-7	10-7		
	Socket, trimmers, tuner data, dial .....10-8	10-8		
Cable-Nelson D-4	Schematic, socket, voltage .....2-12	2-12		
HA-4	Schematic, socket, alignment .....6-12	6-12		
Z-4	Alignment data .....4-6	4-6		
A-5	Schematic, voltage .....4-7	4-7		
E5B	Schematic, socket .....1-1	1-1		
	Schematic, phonograph and headphone circuits .....9-1	9-1		
5B	Alignment, trimmers .....9-3	9-3		
	Schematic .....8-1	8-1		
	Trimmers .....8-2	8-2		
A-6	Alignment, notes .....8-3	8-3		
HA-6, Early	Schematic, socket .....1-1	1-1		
	Schematic, parts list .....7-3	7-3		
	Alignment, notes, socket, trimmers .....7-4	7-4		
	Installation data, noise notes .....7-5	7-5		
	Parts list, notes .....7-6	7-6		
	Installation data .....7-7, 7-8	7-7, 7-8		
HA-6, Late	Schematic, voltage, parts list .....7-9	7-9		
	Alignment, socket, trimmers, speaker .....7-10	7-10		
6B	Schematic, parts .....9-4	9-4		
6B-A	Schematic, alignment, parts .....9-5	9-5		
HA-7, HA-9	Schematic, voltage, alignment .....10-3	10-3		
S-7	See model S-2			
SN-7	Schematic, socket .....1-2	1-2		
7BT	Schematic, voltage .....9-6	9-6		
D-8	Schematic, voltage .....6-17	6-17		
HA-8	Schematic, voltage, alignment .....10-3	10-3		
X-8	See model X-2			
HA-9	See Model HA-7			
R-9	Schematic .....5-1	5-1		
	Parts layout, socket, trimmers .....5-2	5-2		
10 (T)	Alignment data .....5-3	5-3		
	Schematic, socket .....2-10	2-10		
	Chassis views, parts list, data .....2-11	2-11		
A-12	Schematic, socket .....6-1	6-1		
R-13	Schematic, socket .....6-1	6-1		
E-14, E-107	Schematic, alignment .....6-2	6-2		
20, 25, 30, 32 (O)	Schematic, socket .....2-8	2-8		
	Chassis views .....2-13	2-13		
	Voltage, service data .....2-9	2-9		
OC-23, OC-34	Schematic, socket .....6-3	6-3		
AA-25	Schematic, socket .....6-3	6-3		
G-26	Schematic, socket .....6-3	6-3		
30, 32	See model 20			
35, 40	See chassis H			
35-A (Chassis AVO)	Schematic .....3-11	3-11		
45, 60 (AVH)	Schematic, socket .....2-7	2-7		
	Alignment data .....2-6	2-6		
	Chassis view .....3-10	3-10		
45, 60 (AVH-P)	Data .....3-10	3-10		
47-A	Schematic, voltage .....7-11	7-11		
50	Alignment, parts .....7-12	7-12		
	Schematic, voltage .....7-11	7-11		
50-SW	Alignment, parts .....7-12	7-12		
	Schematic, voltage .....7-11	7-11		
52, 502, HA-2	Alignment, parts .....7-12	7-12		
	Schematic, socket, trimmers, notes .....6-10	6-10		
56	Schematic, voltage .....8-2	8-2		
57-A	Schematic, voltage .....7-13	7-13		
	Parts list .....7-12	7-12		
	Notes .....7-14	7-14		
57-AUS	Schematic, voltage .....7-13	7-13		
E-57	Schematic, voltage .....7-13	7-13		
58	Alignment, parts .....7-12	7-12		
	Schematic, voltage .....7-15	7-15		
	Alignment, socket, trimmers, parts list .....7-16	7-16		

HOWARD RADIO CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
59	Schematic, voltage	9-26	260, S260	Trimmers, alignment, Part 2	9-14
60	Schematic, voltage, socket, notes	7-14	266	Socket, trimmers	8-4
60 (AVH)	See model 45		268	Alignment	8-6
60-SW	Phonograph data	3-1		Schematic	8-1
	Schematic, voltage, socket, notes	7-12		Socket, trimmers	8-4
67C, 67T	Parts list	7-14		Alignment	8-6
68	See model 626		270	See model 220	
68 (Revised)	Schematic, voltage	7-17	271	Schematic, trimmers	9-11
	Circuit data, notes, parts	7-18	275C, 275T, 280	Socket, trimmers	9-12
	Schematic, voltage	8-5		Alignment, Part 1	9-13
	Socket, trimmers	8-4	X275	Alignment, Part 2	9-14
	Alignment	8-6		Schematic, voltage	10-11
77 Long Wave	Alignment	8-6	285	Schematic, trimmers, parts	10-12
	Schematic, voltage, socket, notes	7-21		Schematic, voltage, notes	10-13
77-C, 77-T	Schematic, voltage, socket, trimmers	7-19	318, 325	Alignment, trimmers, part	10-12
	Alignment, chassis	7-20		Schematic	9-15
99 Long Wave	Schematic, voltage, notes, alignment	7-22		Parts list	9-16
99-C, 99-T	Schematic, voltage, socket, parts	7-23	318D, 325D, 375	Socket, trimmers, voltage	9-17
	Alignment, chassis	7-24		Alignment, notes	9-18
E-107	See model E-14			Schematic	10-14
118, 218	Schematic, voltage	8-7		Alignment, socket, trimmers	10-15
	Socket, trimmers	8-8		"Perm-A-Matic" tuner adjustments	10-16
	Alignment	8-9		Phonograph data	10-20
135 A. C.	See model 395		368	Schematic	9-15
135 DO	Schematic, socket, data	2-2		Parts list	9-16
200	Schematic, voltage	9-26		Socket, trimmers, voltage	9-17
210, Push-Button Adapter	Schematic, instructions, parts	10-5	377	Alignment, notes	9-18
211, Push-Button Converter	Instructions, tuner	10-7	395, 445, 470, 495 (135 AC)	Schematic, voltage, socket	10-15
214	Schematic	10-7	400	Schematic, socket	1-8
	Instructions, tuner	10-7		Schematic, voltage	9-19
	Schematic, voltage	8-11		Phonograph data, notes, parts	9-21
	Socket, trimmers, alignment, parts	8-12		Antenna data, notes, tuner	9-22
218	See model 118			Alignment	9-23
220, 270	Schematic, voltage, notes	10-9		Phonograph notes, parts	9-20
	Alignment	10-7	400-A	Antenna notes, tuner	9-21
	Socket, trimmers, tuner data, dial	10-8		Tuner data	9-23
221, 271	Schematic, voltage, notes	10-10		Socket, trimmers	9-24
	Alignment	10-7		Alignment	9-25
	Socket, trimmers, tuner data, dial	10-8	400 (K)	Schematic, voltage	8-8
	Schematic, voltage	10-8	400X	Schematic, voltage	10-4
225, S225, 250, S250	Socket, trimmers, alignment	9-9	418	Schematic, voltage	10-18
	Parts	9-9		Socket, trimmers, alignment, phono. data	10-20
	Socket, trimmers, alignment	9-13		"Perm-A-Matic" tuner adjustments	10-16
240-1	Trimmers, alignment	9-13	420 (L) 1st type	Schematic, socket	8-5
	Schematic, voltage	9-14	425	Schematic, voltage	9-19
	Phonograph data, tuner data, parts	9-7		Phonograph notes, parts	9-21
240-2	Alignment, notes	9-8		Antenna notes, tuner	9-22
	Schematic, voltage	9-18		Socket, trimmers	9-24
	Phonograph data, tuner data, parts	9-7	425-A	Alignment	9-25
	Alignment, notes	9-8		Schematic, voltage	9-20
250, S250	See model 225			Phonograph notes, parts	9-21
E256	Schematic, voltage	9-2		Antenna data, notes, tuner	9-22
	Phonograph and headphone circuits	9-1		Tuner data	9-23
	Schematic, voltage	8-10		Socket, trimmers	9-24
S-256	Trimmers	8-2	430, Series 2	Alignment	9-25
	Schematic, voltage	8-10		Schematic, voltage	9-25
256	Alignment	8-3	438	Alignment, socket, trimmers, dial data	10-21
	Schematic, voltage	8-10		Schematic	10-22
	Trimmers	8-2		Dial data	10-22
E259	Schematic, voltage	8-3	440, Series 1, 2	Alignment, socket, trimmers	10-24
	Phonograph and headphone circuits	9-1		Schematic, voltage	10-25
	Schematic, voltage	8-13	450	Crystal alignment	10-24
S-259	Trimmers	8-2		Alignment, socket, trimmers	10-26
	Schematic, voltage	8-3		Schematic, voltage	10-27
259	Alignment	8-2		Socket, trimmers, chassis	10-28
	Trimmers	8-3		Antenna data, color code, notes	10-30
360, S260	Schematic, voltage, phonograph data, parts	9-10	450A	Notes	10-31
	Trimmers, alignment, Part 1	9-13		Alignment	10-31

1806

\*400

1892

1899

# HOWARD INTERNATIONAL

MODEL	HOWARD RADIO CO.—(Cont.)	REVISED PAGE	EARLY PAGE	RADIOTRON COMPLETE PAGE
468	Schematic, voltage .....10-19 Socket, trimmers, alignment, "Perm-A-Matic" tuner ad- justments .....10-20 See model 52 .....10-16 Schematic, voltage, socket .....10-32 "Perm-A-Matic" tuner ad- justments .....10-16 Socket, trimmers, alignment, phono, data .....10-20 Schematic, voltage, parts .....8-15 Socket, trimmers, chassis .....8-14 Alignment .....8-16 Schematic, voltage, parts .....6-7 Alignment, notes .....6-8 Socket, trimmers, parts details .....6-9 See model 626			
626, 1626, 67-O, 67-F				
670-A, HA-1				
1626				
OB-6				
H-6				
DB-37				
SA-37				
DB-38				
SA-38				
650HD, 651HE, 660TD, 661TE				
680				
Legion 88 48 59 69 80				

## HUDSON MOTOR CAR CO.

OB-6	Schematic, socket, trimmers, alignment data .....9-1 Chassis wiring .....9-2 Voltage, alignment .....9-3 Alignment, concluded .....9-4 See RCA model H-6 Schematic, socket, trimmers, specifications .....9-5 Alignment, Part 1 .....9-3 Alignment, Part 2 .....9-4 Chassis wiring .....9-6 Voltage, parts .....9-7 Schematic, socket, trimmers, specifications .....9-9 Voltage, parts .....9-8 Alignment, Part 1 .....9-3 Alignment, Part 2 .....9-4 Chassis wiring .....9-10 Schematic, socket, trimmers, alignment .....10-1 Chassis wiring, voltage, con- nections .....10-2 Alignment procedure .....10-4 Schematic, socket, trimmers, alignment .....10-1 Chassis wiring, voltage, con- nections .....10-3 Alignment procedure .....10-4 See Zenith model 650HD 680 See Zenith model 680			
------	---	--	--	--

## HUDSON-ROSS

Legion 88 48 59 69 80	Schematic ..... Misc. 6-13 Schematic .....5-1 Schematic .....6-1 Schematic .....5-2 Schematic .....5-3 Schematic .....5-4			
--------------------------------------	--	--	--	--

## HUPMOBILE

See PHILCO RADIO & TELEVISION CORP.

## IOA

See INSULINE CORP. OF AMERICA

## IMPERIAL

See TRIANGLE ELECTRIC CO.

## INSULINE CORP. OF AMERICA

Auxiliary Tube Checker	Schematic .....4-1 Chart .....4-2			
"Classic" Conqueror SW AC Conqueror, SW Batt.	Schematic .....5-6 Schematic .....2-6 Schematic .....2-10			

## INTERNATIONAL INDUSTRIES, INC.

Classic	See model 10			
A, B Kaydette	Schematic, parts list .....4-1 Alignment data .....4-2			
BW, CD	See model A-7			
OB (Battery)	Schematic .....5-3			
CM	Alignment, voltage .....5-4 Schematic, data .....5-8 Schematic .....5-3			
OMS	Alignment data .....3-3			
CS (SW)	Schematic, socket, voltage, data .....8-4			
CS	See model DA-8			
D, DSP Chassis	See model A-7			
DAO Chassis	See model A-8			
DAS Chassis				

## HOWARD RADIO CO.—(Cont.)

MODEL	INSULINE CORP. OF AMERICA—(Cont.)	REVISED PAGE	EARLY PAGE	RADIOTRON COMPLETE PAGE
DC 110-volt AVC, Super Broadcast	Schematic .....4-3			
"Elite"	Schematic .....5-5			
Envoy 6 Tube AO	Schematic .....2-1	1-405		1341
Envoy Midget	Schematic .....2-1	1-405		1341
Envoy Midget DO	Schematic .....2-2	2-405		1342
(Rev) 1st				
Envoy Midget DO	Schematic .....2-2	2-405		1342
(Rev) 2nd				
Envoy Brdcast-LW DO	Schematic .....2-3	3-405		1343
Envoy Brdcast-LW AO	Schematic .....2-4	4-405		1344
Envoyette	socket .....6-14			
Envoyette, 5-tube AO	Schematic .....3-2			
Envoyette, 5-tube DO	Schematic .....3-2			
Envoyette, Long Wave AO	Schematic .....3-2			
IOA-tube	Schematic .....6-14			
"Icasix" (2 bands)	Schematic, socket .....5-3			
"Icasix" (3 bands)	Schematic, socket .....5-4			
Insuletta-4 Tube Midget	Schematic .....2-5	5-405		1345
Insuletta Brdcast-LW AO	Schematic .....2-5	5-405		1345
Mascot, Brdcast-Long Wave, 4-tube Midget	Schematic .....2-5	5-405		1345
Mascot 4 Tube Midget AO	Schematic .....2-5			
Super-Conqueror, Short- Long Wave	Schematic .....2-7	5-405		1345
"Super-Conqueror" AC, 108-250 volts, W/Noise Suppressor	Schematic .....4-14			
Super Six AVC, Long Wave	Schematic .....4-4			
Super Six AVC, Broad- cast	Schematic .....4-5			
"Superseven" AO, Long Wave	Schematic .....4-16			
"Trans-Atlantic"	Schematic, socket .....5-1			
"Trans-Pacific"	Schematic, socket .....5-2			
"Una-Radio Nine" AC-DO	Schematic .....4-15			
Universal Companion, AC-DC-Batt.	Schematic .....2-8			
Universal Companion, AC- DC-Batt. (Revised)	Schematic .....2-9	6-405		1346
Universal Mascot	Schematic .....2-8			
5-Tube Unaradio Super AC-DO "Americus"	Schematic .....4-6			
5-Tube Unaradio Super AC-DO "Aiglon"	Schematic .....4-7			
5-Tube Unaradio Super AC-DO "Atlantic"	Schematic .....4-8			
5-Tube Unaradio Super AC-DO "Bijon"	Schematic .....4-9			
5-Tube Unaradio Super AC-DO "Latinic"	Schematic .....4-10			
5-Tube Unaradio Super AC-DO "Migron"	Schematic .....4-11			
5-Tube Unaradio Super AC-DO "Gnome"	Schematic .....4-12			
5-Tube Unaradio Super AC-DO "Pacific"	Schematic .....4-13			
6-tube Superhet. AC	Schematic .....3-1			
7-tube Superhet. 220-v. DO	Schematic .....3-1			

8-405  
7-405

1346  
1353

INTERNATIONAL INDUSTRIES, INC.—(Cont.)			RADIOTRON			INTERNATIONAL INDUSTRIES, INC.—(Cont.)		
MODEL	REVISION	PAGE	MODEL	REVISION	PAGE	MODEL	REVISION	PAGE
ES Chassis	See model ES-19		76X, 676X			76X, 676X		
F Kaydetto, Jr. (Four types)	Schematic, parts list	4-3	77, 777, 778, 779			77, 777, 778, 779		
F Kaydetto, Jr.	Voltage, condensers, notes	4-4	85			85		
J	Parts list, notes	4-5	86	1957		86		
JS (SW)	Schematic, socket, voltage	3-5	86X	1954		86X		
KS	Alignment data	3-2	87	1953		87		
L Chassis	Schematic, socket, voltage	3-1						
N Chassis	See model 10							
P	See model K-40							
T, TS	Schematic, notes	9-8						
Jewel	Schematic, socket	3-5						
Kadette	See model 40							
Regal	Schematic, chassis views, adjustments	3-2						
St. Regis	See model K-40							
KRO-2, Tunemaster	Schematic	10-1						
K-6 Chassis	Alignment	10-2						
A-7, BW, OD (DAO)	See model K-60							
A-8, A-9, A-10, AD-11, AD-12 (Chassis DAS)	Schematic, voltage	5-5						
DA-8, DA-9, DA-10, D-11, D-12, D-14 (Chassis D, DSP)	Alignment data	5-8						
10, 11, 12, 13, 14, 15, 16, 10 (1938)	Schematic, voltage	8-1						
AD-11, AD-12	Schematic, socket, alignment, voltage	9-1						
ES-19, ES-20, ES-80 (Chassis ES)	See model A-8							
KR 20, Attune	Schematic, alignment	5-8						
21, 22, 23	Schematic, voltage, alignment	10-2						
25, 26, 27, 28 (1938)	Schematic, socket, alignment, voltage	6-3						
ES-25	Schematic	9-1						
26, 226	Schematic, parts list	6-1						
35	Voltage, alignment data	6-2						
36	Schematic, voltage, alignment	8-2						
40, Jewel (Early)	Schematic, socket, alignment, voltage	8-3						
40, 41, 43, 44, 45, 46, 47, K-40 Regal (M)	Schematic, parts	7-1						
41, 43 (1938)	Schematic, voltage, data	3-6						
50	Schematic, voltage, socket, alignment	9-2						
52	Schematic, parts	6-4						
53, 553, Early and late	Schematic, voltage, alignment	6-5						
53, 553	Voltage, alignment	6-6						
55	Alignment	6-7						
AW-55	Schematic	6-8						
56	Trimmers, parts, voltage	6-9						
56X, 86X	Changes	7-7						
60	Schematic	6-10						
K-60, St. Regis (Chassis K-6)	See model 25	3-4						
61, 661	Schematic, voltage	8-4						
65	Schematic	6-10						
66X, 86, 96	Schematic	5-1						
70	Voltage, alignment	5-2						
71	Schematic, parts	6-11						
710	Voltage, trimmers, alignment	6-12						
72	Schematic	6-13						
	Schematic, parts	7-2						
	Socket, voltage, alignment	7-1						
	Schematic	6-13						
	Schematic	6-14						
	Schematic	6-15						
	Parts list	6-16						

INTEROCEAN RADIO CORP.

202	Schematic, voltage, socket, alignment, trimmers	10-1
204	Schematic, socket, trimmers, voltage, alignment	10-2
2037	Schematic, socket	7-1
505	Voltage, alignment, parts list	7-2
508, 522, 525, 525A	Schematic, alignment	10-2
Chassis 508	Socket, trimmers	10-4
511, 524, 527, 527A	Schematic, voltage, trimmers	10-3
Chassis 511	Alignment, socket	10-4
520, 521 (Chassis 2035)	Schematic, voltage, trimmers	10-3
530, 531, 538 (Chassis 2088)	Alignment, socket	10-4
	Schematic	5-1
	Voltage, socket, parts list	5-2
	Schematic	5-3
	Voltage, socket, alignment	5-4

# JACKSON-BELL KENNEDY

MODEL	REVISID PAGE	EARLY COMPLETE PAGE	RADIOTRON
4	Schematic	7-1	
5-A	Schematic	5-1	
24	Schematic	3-1	1359
25	Schematic	3-1	1360
25-A, 25-U	Schematic	3-2	1361
26	Schematic	3-3	1362
26-SBL	Schematic	3-4	1363
27, 1st type	Schematic	3-5	1364
27, 2nd type	Schematic	3-6	1365
28	Schematic	3-7	1366
29	Schematic	3-8	1367
33	Schematic	3-9	1368
Junior 50	Schematic	3-10	1369
59	Schematic	2-1	
60	Schematic	7-2	
	Schematic	7-3	
	Schematic	7-5	
	Schematic	3-3	
62, 68, 64, (Early)	Schematic	7-4	
Under Serial #120,000	Schematic	7-5	1361
62, 2nd & 3rd Series	Schematic	7-6	
68	Schematic	7-5	
	Schematic	7-6	
84	Schematic	7-5	
	Schematic	6-1	
86	Schematic	5-2	
87	Schematic	6-2	
88	Schematic	6-3	
89	Schematic	4-1	
89-A	Schematic	6-4	
96	Schematic	5-2	
99	Schematic	5-1	
205 Auto Set	Schematic	7-1	1359
245S	Schematic	7-1	

## JACKSON RADIO & TELEVISION CO.

J-104, 401-A, 447	Schematic	Misc. 5-8
J-105, 504-B, SF-547	Schematic	Misc. 4-4

## JACKSON RESEARCH LABORATORY

NJ-8	Schematic	Misc. 6-15
------	-----------	------------

## J. E. JENKINS & S. E. ADAIR

A (2 types)	Schematic	1-2
Level Indicator	Schematic	*702
Monitor Amplifier	Schematic	*702
Pushpull Amplifier	Schematic	*702
SB Mixing Panel	Schematic	*701
30 Mixing Panel	Schematic	*701

## KADETTE

See INTERNATIONAL INDUSTRIES, INC.

## KARADIO CORP.

56	Schematic, socket	Misc. 5-9
----	-------------------	-----------

## KEILER-FULLER

F	Schematic	3-1
M	Schematic	3-1
Radlette F-12	Schematic	3-2
Radlette F-14	Schematic	3-2
Radlette F-14-A	Schematic	3-3
Radlette F-14-B	Schematic	3-3
Radlette 20	Schematic	3-4
Radlette 40	Schematic	3-5
Radlette 50	Schematic	3-5
Radlette 60	Schematic	3-6
Radlette 70	Schematic	3-6

## KELLOG SWITCHBOARD AND SUPPLY CO. REVISED PAGE

MODEL	REVISID	PAGE	EARLY COMPLETE PAGE
Chassis B			
Wave Master	Schematic, voltage	1-2	*408
6-tube Battery	Schematic	1-1	*407
7-tube Cascade	Schematic	1-1	*407
AC-7-tube	Schematic	1-1	*407
528, 524, 525, 526, 527, 528 RF	Schematic, voltage	1-2	*408
528, 526 Power Unit	Schematic	1-3	*409
524, 525, 527, 528 Power Unit	Schematic, socket, voltage	1-4	*410
538, 534, 535, 536, RF	Schematic, socket, voltage	1-5	*411
Chassis	Schematic, socket	1-6	*410-A
RFL 701	Schematic		*407

## COLIN B. KENNEDY CORP.

Coronet	See model 42 & 7 DO		
Globe Trotter	See model 54		
Royal	Schematic	1-5	*416
6, Type 420	Schematic	1-2	*418
7, Type 421	Schematic	1-2	*418
7-Coronet DO	Schematic	1-2	*413
10	Schematic, socket	1-3	*414
15, 16 (Type 480-43)	Schematic, socket, voltage	1-4	*415
20, Type 440	Schematic	1-1	*412
22, 36, 38, 40 DO	Schematic, socket, voltage	1-3	*414
24	Chassis layouts	1-4	*415
	Schematic, parts list, data	2-1	416-2
	Schematic, voltage, chassis, data	2-2	416-1
26	Schematic, chassis, notes	2-3	416-3, 4
30, Type 485	Schematic, voltage	1-6	*416-C
30, 32	Schematic, chassis	1-3	*414
34	Schematic, voltage	1-7	*416-A
	Chassis wiring	1-8	*416-F
	Changes, data	1-9	*416-B
Coronet 42	Schematic, chassis, voltage	1-10	*416-H
42-B	Schematic	1-11	*416-E
44	Schematic	4-1	
48	Schematic	2-4	
50	Schematic, chassis, alignment	2-5	
52	Schematic, socket, voltage, data	2-6	416-K
58-SW, 54-SW	Parts list, data	2-7	416-L
	Schematic, chassis calibration	2-8	416-L-2
54 "Globe Trotter"	Schematic, chassis, data	2-9	416-L-1
54-A	Schematic, chassis, data	2-10	416-M
55	Voltage, socket, data, schematic	2-11	416-L-3
56	Schematic, socket, voltage, parts list	2-12	
Royal 60	Schematic, socket	1-5	416-N
62	Schematic, voltage, parts list	2-13	*416
62-A	Chassis alignment data	2-14	416-O
62-D Chassis	Schematic, data	3-1	416-P
63, 63-A Chassis	Chassis views, alignment data	3-2	
64	See model 563-A		
64-B Chassis	Schematic, socket, alignment	Misc. 8-4	
66, 66-A	Schematic, data	8-11	1428
66-B Chassis	Chassis views, alignment data	8-12	1424
Royal 60	See model 266-B		
164-B (Chassis 64-B)	Schematic, socket	1-12	1427
	Schematic, data	3-7	1419
	Chassis layout, alignment	3-8	
175 to 25,000 Meters	Schematic	1-1	1420
220	Schematic	1-1	1385
266-B, 366-B (Chassis 66-B)	Schematic, data	3-13	1426
281	Chassis layout, alignment	3-14	1426
420, 421 Type	Schematic	1-1	1385



**MODEL** **LAFAYETTE RADIO MFG. CO.—(Cont.)** **REVISED**  
**PAGE**

P.A. Tuner	Schematic	7-1
P.C. Receiver	Schematic	9-5
P.W. Converter	Schematic	7-1
L-1, L-2, L-3, L-4	Schematic, voltage, socket, trimmers	5-9
2A5, First Minstrel	Schematic	9-1
2A5, First Minstrel	Schematic	9-2
2A5, First Minstrel	Schematic, alignment trimmers	9-3
2A5, First Minstrel	Schematic, alignment trimmers	9-3
2A5, First Minstrel	Schematic, parts list	5-2
2A5, First Minstrel	Schematic, parts list	5-1
2A5, First Minstrel	Schematic, socket, parts	8-2
2A5, First Minstrel	Schematic, socket, parts	8-2
2A5, First Minstrel	Schematic, parts list	5-1
2A5, First Minstrel	Schematic	8-3
2A5, First Minstrel	Schematic	5-7
2A5, First Minstrel	Socket, alignment, parts	5-8
2A5, First Minstrel	Schematic, data	6-3
2A5, First Minstrel	Condenser data, notes, parts (early)	6-2
2A5, First Minstrel	Schematic, socket, voltage	6-5
2A5, First Minstrel	Alignment, parts data	6-4
2A5, First Minstrel	Schematic	7-2
2A5, First Minstrel	Schematic	Misc. 4-5
2A5, First Minstrel	Schematic	8-3
2A5, First Minstrel	Schematic, voltage, socket, trimmers	5-10
2A5, First Minstrel	Schematic	Misc. 4-5
2A5, First Minstrel	Schematic	Misc. 4-6
2A5, First Minstrel	Schematic	6-6
2A5, First Minstrel	Schematic, parts list	5-2
2A5, First Minstrel	Schematic	7-7
2A5, First Minstrel	Schematic, socket, changes, trimmers	5-11
2A5, First Minstrel	Alignment, voltage, parts list	5-12
2A5, First Minstrel	Schematic	8-4
2A5, First Minstrel	Schematic	Misc. 4-6
2A5, First Minstrel	Schematic	6-7
2A5, First Minstrel	Schematic, voltage, alignment	6-8
2A5, First Minstrel	Schematic	10-1
2A5, First Minstrel	Schematic	7-3
2A5, First Minstrel	Alignment, voltage, socket, parts	7-4
2A5, First Minstrel	Schematic, alignment, parts	8-5
2A5, First Minstrel	Schematic	9-4
2A5, First Minstrel	Schematic	9-4
2A5, First Minstrel	Schematic, parts list	5-3
2A5, First Minstrel	Schematic	8-4
2A5, First Minstrel	Schematic, parts list	5-3
2A5, First Minstrel	Schematic	10-3
2A5, First Minstrel	Alignment, resistances	10-2
2A5, First Minstrel	Voltage, socket, coils, trimmers, phono, data	10-4
2A5, First Minstrel	Schematic	8-6
2A5, First Minstrel	Schematic, socket, trimmers, voltage	5-13
2A5, First Minstrel	Alignment data	5-14
2A5, First Minstrel	Schematic	8-6
2A5, First Minstrel	Data	9-8
2A5, First Minstrel	Changes	9-8
2A5, First Minstrel	Schematic	9-5
2A5, First Minstrel	Schematic	9-6
2A5, First Minstrel	Schematic	10-5
2A5, First Minstrel	Voltage, socket, coils, trimmers, phono, data	10-6
2A5, First Minstrel	Alignment, resistances, changes	10-7
2A5, First Minstrel	Schematic	6-9
2A5, First Minstrel	Schematic	8-7
2A5, First Minstrel	See model 80M	
2A5, First Minstrel	Schematic, alignment	8-8
2A5, First Minstrel	Schematic	10-8
2A5, First Minstrel	Schematic	8-7
2A5, First Minstrel	Schematic, alignment	8-8
2A5, First Minstrel	Schematic	10-10
2A5, First Minstrel	Schematic	10-1
2A5, First Minstrel	See model AM20	
2A5, First Minstrel	Schematic, socket, parts, voltage, alignment, trimmers	6-4
2A5, First Minstrel	See Model AM20	

B-60	Schematic, voltage, socket, parts	5-5
O-60	Alignment, parts list	5-6
S-61	Schematic, socket, alignment	6-11
B-62	Schematic, socket, trimmers, voltage, resistance test	9-7
M55	Schematic, resistance test	6-12
M-69	See model A-7	10-9
RV1	Schematic	8-9
SL71	Schematic	8-9
A7	Schematic, socket	10-10
B78	Schematic	10-11
	S.P.U. schematic	10-12
	Voltage, trimmers, chassis	10-13
	Trimmers, color code, changes	10-14
	Alphano.	10-15
	Alignment, resistances	10-15
C-78	Schematic	9-8
G-78L	Schematic	7-5
O-C-79	Alignment, voltage, socket	7-6
	Schematics	6-13
80-M, 2 types, 40A	Alignment parts	6-14
	Socket voltage, alignment, pickup data	6-15
A81, A81L	Schematic, socket	10-10
B90(R) Early	Schematic	10-17
B90(N) Late	Voltage, socket trimmers, coils, resistances	10-16
B92(K) Early	Schematic, socket, trimmers	10-18
B97-98	Voltage, alignment, coils, resistances	10-19
	Socket voltage, alignment, voltage, alignment, coils	10-20
	Schematic	8-11
	Socket, trimmers, coils, phono.	8-10
M-99, Pigmy	Alignment, voltage, notes	8-12
100A	Schematic	9-7
G02A	Schematic	6-16
G06-A	Schematic	6-16
1115A	Schematic	6-17
120-A	Schematic, voltage	6-18
132-A, 133-A	Schematic	6-17
135-A	Schematic	7-8
136-A	Schematic	7-8
137-A	Schematic	7-9
137-X, 150-X, 171-X	alignment, notes	7-10
143, 144, 149	Schematic, alignment, notes	7-11
U-145	Schematic	9-9
151, 154, 156, 158	Schematic, voltage	7-13
	Chassis layout	7-12
	Alignment	7-14
U-155	Schematic	9-9
158P	Schematic, voltage	6-18
171-X	See model 137-X	
186, 188	See model 151	
E-204	See model E-20	
324	Schematic	7-15
430	Schematic	9-10
200L, Minstrel (1932)	Schematic	9-1
P-16754	Schematic	7-16
XP-15949	Schematic	7-16
S-17762	Schematic	5-15
	Socket, alignment, trimmers	5-16

LANG RADIO CO.		*444
BA-5	Schematic, socket	1-1
UG-5B	Schematic, alignment, parts list	5-1
BA-5-P	Schematic, socket	2-2
BD-5-P	Schematic, socket	1-1
BD-6	Schematic, socket	1-1
BD-6-P	Schematic, socket	1-2
F-7, 110-volt DO	Schematic, socket	2-1
J-7	Schematic, socket	1-2
M-7	Schematic, socket	1-3
MA-7	Schematic, socket	2-3

BA-5	*444
UG-5B	
BA-5-P	444-B
BD-5-P	444-A
BD-6	*444
BD-6-P	444-A
F-7, 110-volt DO	444-A
J-7	*445
M-7	446
MA-7	446-A



MODEL	LANG RADIO CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
MD-7	Schematic, socket	2-3	1482	
SA-7	Schematic	2-4	446-A	
MA-8	Schematic, socket	3-1	446-B	
MD-8	Schematic, socket	3-1		
R-8	Schematic, socket	1-3	*446	
SA-8	Schematic, socket	2-4	446-B	
F-9	Schematic, socket	1-2	*445	
40-UL	Schematic, alignment	6-1		
50-AS	Schematic, alignment	6-2		
50-UP, 60-UP	Schematic, alignment	6-2		
50-US	Schematic, alignment	6-1		
60-AA	Schematic	6-3		
80-UA	Schematic, alignment, parts	6-4		
502-US	List	5-2		
503-US	Schematic, alignment	5-1		
503-AS	Schematic, alignment, parts	5-3		
503-UT, 538-UT	Schematic, alignment	6-5		
703-US	Schematic, alignment, parts	5-4		
LAERIN CO., INC.				
84	Schematic	Misc. 6-20		
88	Schematic	5-1		
90	Schematic, socket	5-1		
91	Schematic	5-2		
LA SALLE				
See CADILLAC MOTOR CAR CO.				
LAUREHK MFG. CO.				
L4B "Laurette"	Misc.	10-7		
L44-T	Schematic	Misc. 7-8		
L55-T	Schematic	Misc. 7-8		
L-69 Musique	Schematic, alignment	Misc. 8-5		
L600 Musique	Schematic, alignment	Misc. 8-5		
LEAR-WUERFUL CO.				
Suprex Six	Schematic	Misc. 5-11		
C. R. LEUTZ, INC.				
C	Schematic	1-1	*788	
Seven Seas	Schematic	1-2	*447	
Silver Ghost	Schematic	1-1	*788	
Trans-Oceanic	Schematic	1-2	*447	
C-10 Navy Model	Schematic	1-1	*788	
LEWOL MFG. CORP.				
LW-4	Schematic, voltage	5-1		
LW-4-DW	Schematic, voltage	5-1		
60-MS	Schematic, socket	5-2		
63	Schematic	5-3		
64	Alignment, voltage	5-4		
	Schematic, socket	5-2		
LINCOLN RADIO CORP.				
DC SW-8	Schematic	4-1		
Hollister AO 8	Schematic, chassis wiring	4-4		
Hollister DO 8	Schematic	4-4		
8-80	Schematic	1-1		
R-9	Schematic	4-1		
DeLuxe 10	Schematic	3-1		
31	Schematic	3-1		
SW-32	Schematic, socket, coil	3-1		
DeLuxe SW 38	Schematic, assembly	4-2		
	Bottom view, terminal connections	4-3		
LOFTIN-WHITE				
See ELECTRAD, INC.				
LYRIO				
See ALL AMERICAN MOHAWK CORP.				
R. H. MAOY & CO.				
MB-5	Schematic, socket	3-1		1487
MB-56, MB-58	Schematic	3-1		1487
MB-92	Schematic	3-3		1489
410 AC-DC	Schematic, trimmers, alignment	7-1		
708-70623	Schematic, alignment	7-2		
MB-710	Schematic	3-2		1488
MADISON-MOORE				
One-Spot Super	Schematic	Misc. 1-12	*790	2757
Superheterodyne	Schematic	Misc. 1-12	*790	2757
THE MAGNAVOX CO.				
A	Schematic	Misc. 1-13	*449	1491
D	Schematic	Misc. 1-13	*449	1491
One Dial	Schematic	Misc. 1-13	*449	1491
THE MAGNOVOX CO., INC.				
Model numbers in which the figure 30 appears are housed in the Playfellow cabinet				
Model numbers in which the figure 31 appears are housed in the Concerto cabinet				
Model numbers in which the figure 32 appears are housed in the Chairside cabinet				
Model numbers in which the figure 33 appears are housed in the Duette cabinet				
Model numbers in which the figure 34 appears are housed in the Berkeley cabinet				
Model numbers in which the figure 35 appears are housed in the Regent cabinet				
Model numbers in which the figure 36 appears are housed in the Windsor cabinet				
Model numbers in which the figure 38 appears are housed in the Hepplewhite cabinet				
Model numbers in which the figure 40 appears are housed in the Swedish Console				
OR101 Chassis				
Model 37				
Style RTR308				
OR101M Chassis				
Model 35				
Style CPAR301				
Model 35A				
Style CPAR312				
Model 36				
Style CPAR302				
CR102 Chassis				
Model 31				
Style TPR307				
OR103 Chassis				
Model 32				
Style EPR306				
OR104 Chassis				
Model 31				
Style TPR309				
OR105 Chassis				
Model 32				
Style EPR 310				
OR106 Chassis				
Model 31				
Style TPR316				
OR109 Chassis				
Model 32				
Style EPR313				
Model 33				
Style CPR305				
Schematic, voltage				
Socket, trimmers, chassis, dial				
Alignment, dial data				
Changes, notes				
Schematic				
Socket, voltage, chassis, trimmers				
Alignment				

EARLY PAGE	RADIOTRON COMPLETE PAGE
1	1
2	2
3	3
100	100

MODEL	THE MAGNAVOX CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON COMPLETE PAGE
CR111 Chassis				
Model 34,				
Style CPAR315				
Model 34A,				
Style CPAR321				
CR107 Chassis				
Model 31,				
Style TPR335				
Model U31,				
Style TPUR311				
Model U31				
Style TPUR361				
Model U31B				
Style TPUR339				
CR110 Chassis				
Model 32,				
Style EPR336				
Model U32,				
Style EPR314				
Model U32,				
Style EPR355				
Model U33,				
Style OPUR317				
CR112 Chassis				
Model U34,				
Style OPAUR318				
CR119 Chassis				
Model U34A,				
Style OPAUR 328				
Model U34B,				
Style OPUR 332				
CR120 Chassis				
Model U30,				
Style PRU331				
CR126 Chassis				
Model U34A,				
Style OPAUR 359				
CR127 Chassis				
Model U38,				
Style OPUR 344				
Model U38,				
Style OPUR 375				
Model U38B,				
Style OPAUR 347				
Model U38B,				
Style OPAUR 374				
UR103M Chassis				
Model 35,				
Style CPAR319				
Model 35A,				
Style CPAR329				
Model 36				
Style CPAR320				
Model 36A,				
Style PAR333				
CR122 Chassis				
Model 35A,				
Style CPAR 356				
Model 36,				
Style CPAR 352				
UR113 Chassis				
Model 31,				
Style TPR323				
Model 31A,				
Style TPR349				
UR114 Chassis				
Model 32,				
Style EPR324				
Model 32				
Style EPR358				
Model 32A,				
Style EPR334				

**MAJESTIC**  
See GRIGSBY-GRUNOW CO.

MAJESTIC RADIO & TELEVISION CO.—(Cont.)			RADIOTRON		
MODEL	MAJESTIC RADIO & TELEVISION CO.—(Cont.)	REVISED	EARLY COMPLETE	PAGE	PAGE
1656X, Chassis 11656X	Socket, trimmers, alignment, photo., tuner data	10-13			
1673 Chassis	Parts list	10-14			
1870 Chassis	See model 67				
11056, 11057, 11058	Schematic, voltage	9-9			
	Tuner data	9-8			
	Socket, trimmers, alignment, parts	9-10			
11356	Alignment	10-2			
	Schematic, voltage	9-11			
	Tuner data	9-8			
	Socket, trimmers, alignment, parts	9-12			
	Tuner data	Changes 10-2			
11356X Chassis	See model 1356X				
11656	Schematic, voltage	9-13			
	Socket, trimmers, alignment, parts	9-14			
11656X Chassis	Tuner data	9-8			
	See model 1656X				
MAJOR LABORATORIES					
12	Schematic	Misc. 1-14			2758
ML-210 Amplifier	Schematic	Misc. 1-14			2758
250 Amplifier	Schematic	Misc. 1-14			2758
250 Amplifier Power Unit	Schematic	Misc. 1-14			2758
P. R. MALLORY & CO.					
Elkon Auto "B" Eliminator	Power Connections	4-4			
Elkon Standard Type, Auto "B" Eliminator	Schematic	4-1			
Elkon Type "C" Eliminator	Schematic	4-2			
	Notes	4-3			
Elkonode	Notes	5-5			
50 Series Elkonodes	Repairs	5-7			
60, 70, 80 Series Elkonodes	Repairs	5-6			
60, 70, 80 Series Elkonodes	Repairs, Part 2	5-8			
B. Eliminator Types					
1932 Type	Singlereed Elkonodes Data	5-1			
1933-34 Type	Dualreed Elkonodes Data	5-2			
1935-34 Type Dualreed Elkonodes	Diamonding, repairs	5-3			
	Dismantling, adjustments	5-4			
MARCONIPHONE INC.					
D. DE (1937)	Schematic	10-2			
Vanity 1937	Schematic	10-1			
Vanity 1938	Schematic	10-1			
D8 1938	Schematic	10-3			
D10, 1938	Schematic	10-4			
MARTY RADIO					
"T"	Schematic	Misc. 4-10			
2R-10	Schematic	Misc. 4-10			
MASTER RADIO & MFG. CO.					
50, 70 "Mighty Midget"	Schematic, voltage	Misc. 8-9			1493
McMILLAN RADIO CO.					
8 (2 types) AC Series 900	Schematic, socket, voltage	1-1			1495
	Schematic, socket, voltage	1-2			1496
McMURDO SILVER, INC.					
World-Wide Nine	Schematic, socket	Misc. 5-12			
MID-WEST RADIO CORP.					
Imperial	See 18(1935) Imperial				
Regal (1936)	Schematic, voltage	8-65, 8-66			
	Alignment, trimmers	8-67			
	Socket, chassis	8-68			

# SERVICING ESSENTIALS

## The CATHODE-RAY TUBE AT WORK



Over 450 illustrations  
336 Pages, Price \$4.00

The second half is devoted to practical applications of commercial oscillographs to servicing and adjustment problems. Each example is made clear by the use of oscillograms photographed in the author's "Successful Servicing" Laboratory.

This book and an oscillograph will enable you to speed up the servicing of jobs in your shop—this means greater profits.

**T**HE cathode-ray oscillograph is rapidly becoming one of the most important tools in the serviceman's kit. It is essential that the progressive serviceman be thoroughly familiar with all the phases of this instrument, so that he can service complicated sets by modern methods.

The theory underlying the functioning of the cathode-ray tube and the circuits that accompany it receive full consideration. One idea alone was kept foremost: the man who works with the cathode-ray oscillograph must know what is occurring within the tube and in the associated apparatus. This is covered in the first part of the book.

By  
**John F. Rider**


## SERVICING SUPERHETERODYNES

**M**ORE than 90% of the receivers coming into service shops are superheterodynes. If you are going to locate the trouble in these sets quickly, you must be familiar with every part of the circuit. . . . You must diagnose quickly in order to show a profit on every job.

First you should know how the various parts of the set function—the first detector—the oscillator—the i-f. amplifier—the second detector, etc. Then you should be familiar with the many variations of the fundamental circuits, . . . the various combinations of oscillator and first detector—second detector, a.v.c., and first audio combinations, etc.

"Servicing Superheterodynes" not only gives you all this, but much more. An entire chapter is devoted to the generation and relation of harmonics. This subject is all-important in superheterodynes and it has to be understood. Then the subject of signal generators is covered and the various types of vibrator units.

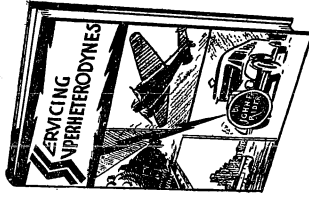The most important portion of the book is that which is devoted to the various troubles that occur in superheterodynes and how these troubles are discovered and fixed. These pages have helped thousands of servicemen all over the world to speed up their work and to turn sets back to the customers in first-class condition. Get "Servicing Superheterodynes" at your jobbers and let it help you, too.



Profusely Illustrated  
307 Pages, Price \$2.00

### CONTENTS

Chapter 1—The Theory of the Tube
Chapter 2—Sweep Circuits
Chapter 3—A-C. Voltages on Both Sets of Plates
Chapter 4—Commercial Cathode-ray Tube Oscillographs
Chapter 5—Practical Application of the Cathode-ray Oscillograph
Chapter 6—Alignment of Tuned Circuits
Chapter 7—The A-F. Frequency Modulator
Chapter 8—Auto Radio Vibrator Testing
Chapter 9—Transmitter Adjustment
Chapter 10—Other Applications of the Cathode-ray Oscillograph

### CONTENTS

Chapter 1—The Principles Underlying the Operation of the Superheterodyne Receiver
Chapter 2—The Generation of and the Relation between Harmonics
Chapter 3—Explanation of the Different Types of Superheterodyne Circuits
Chapter 4—Function and Characteristics of Individual Parts of the Superheterodyne Receiver
Chapter 5—Special Circuits and Tube Applications
Chapter 6—Troubles and Symptoms Encountered in Superheterodynes
Chapter 7—Application of Test Oscillators
Chapter 8—Vibrator Units
Appendix —Intermediate Peak Frequencies of Commercial Receivers with Model Numbers

**John F. Rider Publisher, Inc., 404 Fourth Ave., New York 16, N. Y.**



EARLY PAGE	RADIOTRON COMPLETE PAGE
---------------	-------------------------------

WARD & CO.—(Cont.)

# MONTGOMERY MODEL

EARLY PAGE	RADIOTRON COMPLETE PAGE
---------------	-------------------------------

**REVISED  
PAGE**

MID-WEST RADIO CORP.-(Cont.)

**MONEY.**

[illegible][illegible]

MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON.		
MODEL			EARLY COMPLETE PAGE		
62-89	Voltage, alignment data.....	4-3			
62-91	Schematic, socket.....	4-4			
62-93	Voltage, alignment.....	4-13			
62-96	Schematic, voltage, socket.....	4-5			
62-97	Noise elimination.....	4-6			
62-99	Schematic, socket, voltage.....	4-7			
62-99X	Schematic, socket.....	4-10			
62-98	Voltage, alignment.....	4-11			
62-101	Schematic, hum notes.....	4-8			
62-101X	Voltage, alignment, socket.....	4-9			
62-101	Schematic, socket.....	4-12			
62-108	Voltage, alignment.....	4-13			
62-108	Schematic, socket, changes.....	4-14			
62-104	Voltage, alignment.....	4-15			
62-106	Schematic, socket, voltage.....	4-16			
62-107	Schematic, socket, voltage.....	4-17			
62-114	Schematic, socket, parts.....	6-1			
62-116	Voltage, resistance test, alignment data.....	6-2			
62-118	Wiring changes, schematic.....	6-3			
62-120	Chassis view of changes, data.....	6-4			
62-122	Schematic, voltage, socket, parts.....	5-1			
62-124	Alignment, data.....	5-2			
62-126	Schematic, socket, parts.....	5-3			
62-128	Alignment, voltage.....	5-4			
62-131	See model 62-106				
62-133	Schematic, socket, trimmers, alignment, Part 1.....	10-1			
62-134	Alignment, Part 2, voltage, drive data, changes, parts.....	10-2			
62-135	Schematic, parts, coil resistance.....	5-5			
62-136	Alignment.....	5-6			
62-138	Voltage, socket, drive-cord data.....	5-7			
62-140	See model 62-120				
62-142	Schematic, voltage, socket, trimmers, parts.....	8-14			
62-143	See model 62-123				
62-144	Schematic, parts.....	5-8			
62-147	Alignment, voltage.....	5-9			
62-149	Socket, trimmers, drive-cord data.....	5-10			
62-151	See model 62-123				
62-153	Schematic, parts.....	6-5			
62-154	Resistance test, socket, trimmers, voltage.....	6-6			
62-155	Alignment, data.....	6-7			
62-156	Schematic, voltage, parts.....	6-9			
62-157	Socket, trimmers, alignment.....	6-10			
62-158	Schematic, parts.....	6-11			
62-159	Voltage, socket, data, alignment.....	6-12			
62-160	See model 62-132				
62-161	See model 62-134				
62-162	Schematic, socket.....	5-11			
62-163	Alignment, parts list.....	5-12			
62-164	See model 62-123				
62-165	Schematic, voltage, alignment, trimmers, socket.....	6-13			
62-166	Alignment.....	6-14			
62-167	Schematic, voltage, socket, trimmers.....	6-15			
62-168	Alignment, notes.....	6-16			
62-169	Parts list.....	6-17			
62-170	See model 62-140				
62-171	Data.....	Changes 7-3			
62-172	See model 62-135				
62-173	See model 62-186				
62-174	See model 62-140				
62-175	See model 62-140				
62-176	See model 62-140				
62-373	See model 62-140				

MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY	COMPLETE	PAGE
62-215	Coil data, resistance	7-21			
	Alignment, drive cord, parts	7-22			
62-216, 62-218	See model 62-179				
62-217, 62-219	See model 62-203				
62-221	See model 62-207				
62-226, 62-228, 62-259,	Schematic	8-5			
62-308, 62-318, 62-408,					
62-418	Trimmers, voltage, socket, coils, sensitivity, phono. data	8-6			
	Alignment, notes	8-7			
62-220	Schematic	7-23			
	Alignment, parts, drive cord, and noise data	7-24			
	Voltage, socket, resistance, coil data	7-25			
62-230, 62-240	Schematic, voltage, socket, trimmers, alignment	9-2			
62-232	See model 62-030				
62-238	Schematic, socket, trimmers, alignment	7-26			
62-235, 62-245	Schematic, voltage, socket, trimmers	7-27			
62-236	Schematic, socket, trimmers	7-28			
	Voltage, coils, panel mtg. kits	8-8			
	Alignment, notes	8-10			
62-242	Schematic	8-11			
	Resistance, voltage, coils, socket, trimmers	8-12			
	Alignment, notes, panel mtg. kits	8-13			
62-251, 62-255, 62-328, 62-338, 62-428	Schematic, socket, trimmers, parts	9-3			
62-254	Alignment	9-14			
	Schematic, voltage, socket, trimmers	8-15			
	Alignment, parts, battery data	8-16			
62-259	See model 62-226				
62-261, 62-311, 62-411	Schematic	9-5			
	Socket, trimmers, voltage, coils	9-6			
62-264	Alignment, phonograph notes	9-7			
	Notes, parts	9-8			
62-267, 62-277	Schematic, voltage, parts, socket, trimmers, alignment	9-4			
	Schematic	8-17			
	Trimmers, socket, voltage, coils	8-18			
	Alignment, circuit data	8-19			
	Movie dial data	8-20			
	Movie dial adjustments and replacements	8-21			
62-273, 62-283	Schematic, chassis wiring	8-30			
62-274, 62-288, 62-290, Issue A	Tuning Eye Installation	8-29			
	Schematic, socket, trimmers, voltage, parts	9-9			
	Alignment	9-10			
62-274, 62-288, 62-290, Issue B Above Serial 207500	Tuner data	9-11			
	Schematic, voltage, socket, trimmers, parts, alignment	9-10			
62-276	Tuner data	9-11			
	Schematic, voltage, socket, trimmers, parts	9-13			
	Trimmers, alignment	9-14			
62-277	See model 62-267				
62-280 Series A	Schematic, voltage, socket, trimmers, alignment, parts	9-12			
	Tuner data	9-11			
62-280, 62-282, 62-284, Series B Above serial 439000	Schematic, voltage, socket, alignment, trimmers	10-3			
62-288, 62-290	Tuner data	10-4			
62-292, 62-294, 62-373, 62-374	See model 62-274, Early or Late Schematic	10-5			
	Alignment, voltage, coils,				
MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY	COMPLETE	PAGE
62-292, 62-294, 62-373, 62-374	socket, trimmers, drive data, notes	10-6			
62-297, 62-357, 62-367, 62-457, 62-467, 62-497	Schematic, phonograph data, specifications	9-15			
	Socket, trimmers, alignment, voltage, coils, notes	9-16			
	Description	9-17			
62-298, Remote Control Unit	Assembly, schematic, parts, data	9-20			
	Schematic, socket, trimmers	9-21			
	Alignment	9-22			
	Schematic, voltage, socket	9-23			
	Coils, trimmers, alignment	9-24			
	Schematic, coils, battery data, drive cord data	9-25			
	Socket, trimmers, voltage, alignment	9-24			
	Schematic, socket, trimmers, parts	9-26			
	Trimmers, alignment	9-22			
	Schematic, voltage, socket, alignment, trimmers	10-9			
	Schematic, voltage, parts	9-27			
	Socket, trimmers, alignment	9-28			
	See model 62-226				
	Schematic	8-23			
	Battery data	8-22			
	Socket, trimmers, coils, voltage, sensitivity	8-24			
	Alignment, data	8-25			
	See model 62-261				
	See model 62-302				
	Schematic	8-27			
	Voltage, socket, trimmers, coils, phono. data	8-26			
	Alignment, notes	8-28			
	Schematic, voltage, socket, trimmers, parts	9-29			
	Alignment	9-61			
	Schematic, voltage, parts	9-30			
	Socket, trimmers, alignment, notes	9-31			
	See model 62-226				
	Schematic, voltage, socket, alignment	9-32			
	Schematic, socket, tuner, voltage	9-33			
	Trimmers, alignment	9-34			
	Schematic, voltage, socket, trimmers	10-7			
	Alignment, notes	10-8			
	Tuner data	10-4			
	Schematic, voltage, socket, alignment, trimmers	10-10			
	Tuner data	10-4			
	See model 62-320				
	Schematic, voltage, socket, trimmers	8-31			
	Coils, battery connections	8-32			
	Alignment, notes	8-33			
	Battery data, Drive cord replacements	8-34			
	Circuit data, parts	8-35			
	Schematic, sensitivity	8-37			
	Socket, trimmers, coils, voltage, battery connections	8-36			
	Alignment, data, parts	8-38			
	See model 62-251				
	Schematic, specifications	9-35			
	Socket, trimmers, coils, voltage, alignment, vibrator data	9-36			



MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON		
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
62-334	Schematic, socket, trimmers, alignment, coils, specifications	9-37			
	Antenna, mounting data, tuner, notes	9-38			
62-336	See model 62-326				
62-337	See model 62-327				
62-338	Schematic, voltage, socket, trimmers, parts, alignment	9-39			
62-345	See model 62-251				
62-346	Schematic, voltage, socket, trimmers, parts, alignment	9-40			
62-350, 62-351, 62-352	Schematic, voltage, parts, socket, trimmers, alignment	9-41			
	Tuner data	9-11			
62-353	See model 62-323				
62-357	Schematic, socket, trimmers, voltage, parts	9-42			
62-361, Issue A	Alignment, notes	9-44			
	Tuner data	9-11			
62-361, Issue B	Schematic, socket, parts, trimmers, voltage	9-43			
	Alignment, notes	9-44			
62-362	Schematic, voltage, socket, trimmers, parts	9-45			
	Alignment	9-46			
62-363, 62-463, 62-650	Schematic, voltage, socket	9-48			
62-364	Trimmers, alignment	9-46			
	Schematic, voltage, socket, trimmers, alignment	10-11			
62-367	See model 62-297				
62-369	Schematic, socket, trimmers, alignment	10-12			
62-370, 62-470, 62-700	Schematic, voltage, socket, coils, phono. data	10-13			
	Alignment, trimmers	10-14			
62-372	Tuner data	10-15			
	Schematic, socket, voltage, parts	9-49			
	Tuner data	9-47			
	Alignment, trimmers	9-50			
62-373, 62-374	See model 62-292				
62-377, 62-387, 62-477, 62-487, 62-607, 62-617	Schematic, specifications	9-51			
62-380, Series A	Socket, trimmers, alignment, coils, voltage, dial drive data	9-52			
Above serial 90618200	Schematic, voltage, socket	10-16			
62-381 S.P.U.	Alignment, trimmers	10-8			
62-385	Schematic	10-61			
62-386, 62-636, 62-646	Chassis	10-62			
	See model 62-305				
62-387	Schematic, voltage, alignment, resistances	10-17			
62-390, 62-490, 62-900	See model 62-377				
	Schematic, socket, trimmers, voltage, parts	9-53			
	Alignment	9-54			
	Remote control installation data	9-18			
62-401, 62-1100	Tuner data	9-47			
	Schematic, coils, socket, specifications, phonograph data, tuner data	9-55			
	Remote control installation data	9-19			
62-402, 62-1101	Trimmers, alignment	9-54			
	Schematic, voltage, socket, phonograph data	9-56			
62-403	Trimmers, coils, alignment, notes	9-34			
	Schematic, voltage, socket, alignment notes	9-59, 60			
	Remote control installation data	9-19			
62-404	Trimmers, alignment	9-61			
62-405	See model 62-304				
62-406	See model 62-305				
	See model 62-306				
MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON		
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
62-407	See model 62-307				
62-408	See model 62-226				
62-410	See model 62-310				
62-411	See model 62-261				
62-414	See model 62-305				
62-416	See model 62-315				
62-418	See model 62-316				
62-419	See model 62-226				
62-422	See model 62-322				
62-423	Schematic, voltage, alignment, parts	9-57			
62-426, 62-436	See model 62-326				
62-428	See model 62-251				
62-432	Schematic, voltage, parts, socket, trimmers	9-58			
62-434, 62-435	Alignment, tuner	9-50			
62-441	See model 62-331				
62-442	Schematic, socket, voltage, trimmers, parts, alignment	9-63			
62-445, 62-455, 62-475	See model 62-302				
62-452	Schematic, voltage, socket, trimmers, alignment	10-18			
62-453, Series A	Tuner data	10-4			
Above serial 489500	See model 62-445				
62-455	See model 62-297				
62-457	Schematic, voltage, socket, trimmers	10-21			
62-459, Series A	Tuner data	10-4			
	Alignment	10-18			
62-463	See model 62-363				
62-465	Schematic, voltage, socket, trimmers, notes, parts	9-64			
	Alignment	9-50			
62-467	See model 62-297				
62-470	See model 62-370				
62-471, 62-472	Schematic	10-19			
62-473, 62-701, Early	Socket, trimmers, alignment, voltage, drive cord data	10-20			
62-473, 62-701, Late	Schematic, voltage, socket, coils, parts	9-65			
	Alignment, trimmers	9-67			
62-475	Schematic, voltage, socket, coils, parts	9-66			
62-476, 62-606, 62-616	Alignment, trimmers	9-67			
62-477	See model 62-445				
62-479	Schematic, socket, trimmers, alignment, voltage, parts	9-68			
	See model 62-377				
	Schematic, voltage, socket	9-69			
	Trimmers, coils, alignment, specifications	9-70			
62-487	See model 62-377				
62-490	See model 62-390				
62-495	See model 62-305				
62-497	See model 62-297				
62-500	Schematic, socket, parts	9-71			
62-501, 62-502, Series A	Alignment, trimmers	9-72			
Above serial 286700	Schematic, voltage, socket, trimmers, alignment	10-22			
62-504, 62-505, Series A	Tuner data	10-4			
Issues A, B Above serial 623100	Schematic, voltage, socket, trimmers, alignment, changes	10-23			
62-506, 62-516	Tuner data	10-4			
	Schematic, trimmers, socket, voltage, parts	9-62			
62-550, 62-1550, 62-2550	Alignment, trimmers	9-72			
Series A, Above serial 83312900	Schematic, voltage, socket, trimmers	10-25			
62-551, 62-1551, 62-2551	Alignment	10-26			
Series A, Above serial 81475800	Schematic, voltage, socket, trimmers, alignment	10-24			
62-552, Series A	Schematic, voltage, socket, trimmers	10-27			
	Tuner data	10-4			
62-553	Alignment	10-18			
	Schematic, voltage, socket, trimmers	10-28			
	Tuner data	10-4			
	Alignment	10-18			

# MONTGOMERY-WARD

MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON	
MODEL	REVISÉD PAGE	EARLY COMPLETE PAGE	RADIOTRON	
MODEL	REVISÉD PAGE	EARLY COMPLETE PAGE	RADIOTRON	
62-554	Schematic, socket, trimmers, voltage, alignment .....10-29	See model 1355	452-B-8	1518
62-555, 62-557, 62-2555, 62-2557	Tuner data .....10-30	See model 62-550		
62-558, 62-1558, 62-2558	Schematic, voltage, socket, alignment, trimmers .....10-31	See model 62-551	452-B-7	1517
Series A, Issue A, Above serial 591000	Schematic, voltage, socket, trimmers .....10-32	See model 62-555		
62-601, Series A, Above serial 645900	Tuner data .....10-4	See model 62-654	452-B-3	1519
62-606	Alignment .....10-26	See model 62-558		
62-607	Schematic, voltage, socket, trimmers .....10-33	Schematic, voltage, socket, alignment data .....4-18	452-B-14	1522
62-617	Tuner data .....10-4	Schematic, voltage, socket, alignment, wiring .....4-19		
62-636, 62-646	Alignment .....10-18	Antenna, mounting notes .....4-20	452-B-13	1521
62-650	See model 62-476	Mounting notes .....4-21		
62-651, 62-652, Series A, Above serial 8M498700	See model 62-377	Control unit .....4-22	452-B-18	1523
62-653	See model 62-377	Extra drive notes .....4-23		
62-654, 62-655, 62-1654, 62-1656, 62-2654, 62-2656, Series A, Above serial 509200	See model 62-386	Parts list .....4-24	452-B-22	1524
62-700	See model 62-363	Schematic, voltage, socket, trimmers .....10-51		
62-701, Early or Late Issue B, Above serial 8H262200	Schematic, socket, trimmers .....10-35	Alignment .....10-40	452-B-9	1527
62-704, 62-705, 62-706, 62-707, 62-708, 62-709, 62-710, 62-711, 62-712	Tuner data .....10-34	Schematic, voltage, socket, trimmers .....10-52		
62-750, 62-751, Series A, Above serial 8M499800	Voltage, alignment, trimmers .....10-36	Alignment, battery data .....10-56	452-B-15	1529
62-752, 62-753	Schematic, socket, voltage, trimmers .....10-37	Schematic, voltage, socket, trimmers .....10-53		
62-900	Tuner data .....10-30	Alignment .....10-54	452-B-6	1536
62-901, Issues A, B	Schematic, socket, trimmers .....10-38	Tuner data .....10-4		
62-902	Schematic, voltage, socket, trimmers .....10-41	Schematic, voltage, socket, alignment, trimmers .....10-57	452-B-7	1537
62-905	Voltage, alignment, trimmers .....10-36	Tuner data .....10-30		
62-1100	Schematic, voltage, socket, trimmers .....10-42	Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-8	1538
62-1101	Alignment .....10-40	Schematic, voltage, socket, alignment, trimmers .....10-59		
62-1150	Tuner data .....10-34	Alignment .....10-55	452-B-9	1539
62-1151	See model 62-370	Tuner data .....10-56		
62-1158	See model 62-473 Early or Late	Schematic, voltage, socket, trimmers .....10-57	452-B-10	1540
62-1611, 62-1711	Schematic, voltage, socket, trimmers .....10-41	Alignment .....10-54		
62-1654, 62-1655	Alignment, trimmers .....10-44	Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-11	1541
62-1656	Tuner data .....10-36	Alignment .....10-55		
62-1658	Schematic, voltage, socket, trimmers .....10-34	Tuner data .....10-56	452-B-12	1542
62-1659	Alignment, trimmers .....10-45	Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1660	Schematic, voltage, socket, trimmers .....10-46	Tuner data .....10-58	452-B-13	1543
62-1661	Alignment, trimmers .....10-47	Schematic, voltage, socket, alignment, trimmers .....10-59		
62-1662	See model 62-390	Alignment .....10-55	452-B-14	1544
62-1663	Schematic, voltage, socket, changes .....10-47	Tuner data .....10-56		
62-1664	Alignment, trimmers, dial, phono, data .....10-42	Schematic, voltage, socket, alignment, trimmers .....10-57	452-B-15	1545
62-1665	Notes .....10-48	Alignment .....10-54		
62-1666	Schematic, voltage, phono, data .....10-42	Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-16	1546
62-1667	Notes .....10-48	Alignment .....10-55		
62-1668	Alignment, trimmers, dial, data .....10-49	Tuner data .....10-56	452-B-17	1547
62-1669	Tuner data .....10-15	Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1670	Schematic, socket, voltage, coils .....10-50	Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-18	1548
62-1671	Alignment, trimmers .....10-49	Schematic, voltage, socket, alignment, trimmers .....10-59		
62-1672	See model 62-401	Alignment .....10-55	452-B-19	1549
62-1673	See model 62-402	Tuner data .....10-56		
62-1674	See model 62-550	Schematic, voltage, socket, alignment, trimmers .....10-57	452-B-20	1550
62-1675	See model 62-551	Schematic, voltage, socket, alignment, trimmers .....10-58		
62-1676	See model 62-558	Alignment .....10-54	452-B-21	1551
62-1677	See model 1111	Schematic, voltage, socket, alignment, trimmers .....10-59		
62-1678	See model 62-654	Alignment .....10-55	452-B-22	1552
62-1679	See model 62-656	Tuner data .....10-56		
62-1680	See model 1288	Schematic, voltage, socket, alignment, trimmers .....10-57	452-B-23	1553
62-1681		Schematic, voltage, socket, alignment, trimmers .....10-58		
62-1682		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-24	1554
62-1683		Alignment .....10-55		
62-1684		Tuner data .....10-56	452-B-25	1555
62-1685		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1686		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-26	1556
62-1687		Alignment .....10-54		
62-1688		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-27	1557
62-1689		Alignment .....10-55		
62-1690		Tuner data .....10-56	452-B-28	1558
62-1691		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1692		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-29	1559
62-1693		Alignment .....10-54		
62-1694		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-30	1560
62-1695		Alignment .....10-55		
62-1696		Tuner data .....10-56	452-B-31	1561
62-1697		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1698		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-32	1562
62-1699		Alignment .....10-54		
62-1700		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-33	1563
62-1701		Alignment .....10-55		
62-1702		Tuner data .....10-56	452-B-34	1564
62-1703		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1704		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-35	1565
62-1705		Alignment .....10-54		
62-1706		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-36	1566
62-1707		Alignment .....10-55		
62-1708		Tuner data .....10-56	452-B-37	1567
62-1709		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1710		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-38	1568
62-1711		Alignment .....10-54		
62-1712		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-39	1569
62-1713		Alignment .....10-55		
62-1714		Tuner data .....10-56	452-B-40	1570
62-1715		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1716		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-41	1571
62-1717		Alignment .....10-54		
62-1718		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-42	1572
62-1719		Alignment .....10-55		
62-1720		Tuner data .....10-56	452-B-43	1573
62-1721		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1722		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-44	1574
62-1723		Alignment .....10-54		
62-1724		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-45	1575
62-1725		Alignment .....10-55		
62-1726		Tuner data .....10-56	452-B-46	1576
62-1727		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1728		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-47	1577
62-1729		Alignment .....10-54		
62-1730		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-48	1578
62-1731		Alignment .....10-55		
62-1732		Tuner data .....10-56	452-B-49	1579
62-1733		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1734		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-50	1580
62-1735		Alignment .....10-54		
62-1736		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-51	1581
62-1737		Alignment .....10-55		
62-1738		Tuner data .....10-56	452-B-52	1582
62-1739		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1740		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-53	1583
62-1741		Alignment .....10-54		
62-1742		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-54	1584
62-1743		Alignment .....10-55		
62-1744		Tuner data .....10-56	452-B-55	1585
62-1745		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1746		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-56	1586
62-1747		Alignment .....10-54		
62-1748		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-57	1587
62-1749		Alignment .....10-55		
62-1750		Tuner data .....10-56	452-B-58	1588
62-1751		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1752		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-59	1589
62-1753		Alignment .....10-54		
62-1754		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-60	1590
62-1755		Alignment .....10-55		
62-1756		Tuner data .....10-56	452-B-61	1591
62-1757		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1758		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-62	1592
62-1759		Alignment .....10-54		
62-1760		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-63	1593
62-1761		Alignment .....10-55		
62-1762		Tuner data .....10-56	452-B-64	1594
62-1763		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1764		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-65	1595
62-1765		Alignment .....10-54		
62-1766		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-66	1596
62-1767		Alignment .....10-55		
62-1768		Tuner data .....10-56	452-B-67	1597
62-1769		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1770		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-68	1598
62-1771		Alignment .....10-54		
62-1772		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-69	1599
62-1773		Alignment .....10-55		
62-1774		Tuner data .....10-56	452-B-70	1600
62-1775		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1776		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-71	1601
62-1777		Alignment .....10-54		
62-1778		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-72	1602
62-1779		Alignment .....10-55		
62-1780		Tuner data .....10-56	452-B-73	1603
62-1781		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1782		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-74	1604
62-1783		Alignment .....10-54		
62-1784		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-75	1605
62-1785		Alignment .....10-55		
62-1786		Tuner data .....10-56	452-B-76	1606
62-1787		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1788		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-77	1607
62-1789		Alignment .....10-54		
62-1790		Schematic, voltage, socket, alignment, trimmers .....10-59	452-B-78	1608
62-1791		Alignment .....10-55		
62-1792		Tuner data .....10-56	452-B-79	1609
62-1793		Schematic, voltage, socket, alignment, trimmers .....10-57		
62-1794		Schematic, voltage, socket, alignment, trimmers .....10-58	452-B-80	1610
62-1795		Alignment .....10-54		
62-1				

MONTGOMERY-WARD & CO.—(Cont.)			RADIOTRON		NOBLITT SPARKS INDUSTRIES		EARLY COMPLETE				
MODEL	REVISION	PAGE	MODEL	PAGE	MODEL	PAGE	MODEL	PAGE			
14,000 Commander, 62,000 Cavalier 15,000	Schematic, socket, voltage, notes .....2-22 See model 1500	452-B-16	1580	1935 Receivers General Service Notes Arvin	See Arvin Pages	6-4	Installation data .....6-4 Data .....5-20 Car data .....4-13 Car data, part 2 .....4-14 Instructions, notes .....9-19 Schematic, parts, alignment .....9-19 Socket, trimmers, voltage, lay- out, specifications .....9-2 Schematic, parts, voltage, specifications, tuner, align- ment .....9-3 Socket, trimmers, layout .....9-4 Schematic, voltage, resistance, parts .....6-1 Parts, changes .....6-2 Chassis layouts .....6-3 Schematic, voltage .....10-1 Alignment, socket, trimmers, sensitivity .....10-2 Antenna data .....10-3 Schematic, alignment, socket, trimmers .....10-4 Antenna data .....10-3 Schematic, parts .....8-9 Alignment .....9-9 Voltage .....10-5 Socket, trimmers, chassis .....10-5 Schematic .....4-1 Notes .....4-2 Notes .....4-3 B supply schematic .....4-15 Alignment data .....5-14 Schematic .....5-1 Voltage, test data, coil resist- ance .....5-2 Schematic, parts list .....5-3 Voltage, test data, coil resist- ance .....5-4 Installation notes .....5-6 Alignment data .....5-18 Schematic, parts list .....5-19 Voltage, test data .....6-5 Installation data, parts list .....6-6 Schematic, voltage, resistance, parts .....6-7 Chassis layouts .....6-8 Changes .....6-9 Alignment, parts, voltage, resistance, coil data .....7-1 Socket, trimmers, chassis, alignment .....7-2 Schematic, voltage, resistance, parts .....8-1 Socket, trimmers, chassis, alignment .....8-2 Schematic .....4-5 Schematic .....4-4 Control schematic .....4-15 Voltage .....5-5 Alignment data .....5-14 Notes .....4-10 Notes, part 2 .....4-11 Notes, part 3 .....4-12 Schematic .....4-16 Voltage, test data, coil resist- ance .....5-5 Schematic, parts, voltage, alignment .....9-5 Socket, trimmers, layout, specifications .....9-6 Installation notes .....5-6 Schematic, parts list .....5-7 Voltage, test data, coil resist- ance .....5-8 Alignment data .....5-18 See model 68	1935 Receivers General Service Notes Arvin	See Arvin Pages	6-4	Installation data .....6-4 Data .....5-20 Car data .....4-13 Car data, part 2 .....4-14 Instructions, notes .....9-19 Schematic, parts, alignment .....9-19 Socket, trimmers, voltage, lay- out, specifications .....9-2 Schematic, parts, voltage, specifications, tuner, align- ment .....9-3 Socket, trimmers, layout .....9-4 Schematic, voltage, resistance, parts .....6-1 Parts, changes .....6-2 Chassis layouts .....6-3 Schematic, voltage .....10-1 Alignment, socket, trimmers, sensitivity .....10-2 Antenna data .....10-3 Schematic, alignment, socket, trimmers .....10-4 Antenna data .....10-3 Schematic, parts .....8-9 Alignment .....9-9 Voltage .....10-5 Socket, trimmers, chassis .....10-5 Schematic .....4-1 Notes .....4-2 Notes .....4-3 B supply schematic .....4-15 Alignment data .....5-14 Schematic .....5-1 Voltage, test data, coil resist- ance .....5-2 Schematic, parts list .....5-3 Voltage, test data, coil resist- ance .....5-4 Installation notes .....5-6 Alignment data .....5-18 Schematic, parts list .....5-19 Voltage, test data .....6-5 Installation data, parts list .....6-6 Schematic, voltage, resistance, parts .....6-7 Chassis layouts .....6-8 Changes .....6-9 Alignment, parts, voltage, resistance, coil data .....7-1 Socket, trimmers, chassis, alignment .....7-2 Schematic, voltage, resistance, parts .....8-1 Socket, trimmers, chassis, alignment .....8-2 Schematic .....4-5 Schematic .....4-4 Control schematic .....4-15 Voltage .....5-5 Alignment data .....5-14 Notes .....4-10 Notes, part 2 .....4-11 Notes, part 3 .....4-12 Schematic .....4-16 Voltage, test data, coil resist- ance .....5-5 Schematic, parts, voltage, alignment .....9-5 Socket, trimmers, layout, specifications .....9-6 Installation notes .....5-6 Schematic, parts list .....5-7 Voltage, test data, coil resist- ance .....5-8 Alignment data .....5-18 See model 68
MOTO-METER GAUGE & EQUIPMENT CO.			MOTOROLA		7A, Chassis RE44		8A, Chassis RE45				
14,000 Commander, 62,000 Cavalier 15,000			See GALVIN MFG. CO.								
Schematic, socket, voltage, notes .....2-22 See model 1500			Schematic, socket, voltage, notes .....2-22 See model 1500								
Schematic, socket, voltage, notes .....2-22 See model 1500			Schematic, socket, voltage, notes .....2-22 See model 1500								
Schematic, socket, voltage, notes .....2-22 See model 1500			Schematic, socket, voltage, notes .....2-22 See model 1500								
Schematic, socket, voltage, notes .....2-22 See model 1500			Schematic, socket, voltage, notes .....2-22 See model 1500								
Schematic, socket, voltage, notes .....2-22 See model 1500											

MODEL	NOBLITT SPARKS INDUSTRIES—(Cont.)	REVISED PAGE
58, 58A, 88, Chassis RE29, RE35	Schematic, parts, voltage, alignment, specifications	9-11
Arvin 61, 62	Socket, trimmers, layout	9-12
	Schematic, parts	6-19
	Voltage, resistance, alignment, coils	7-9
Arvin 61-B, 62-B	Socket, trimmers, chassis	7-10
	Schematic, voltage, alignment, resistance, coils, parts	7-11
Arvin, 61M, 62M	Socket, trimmers, chassis	7-12
	Schematic, parts	6-20
	Voltage, resistance, alignment, coils	7-9
68, Chassis RE26	Socket, trimmers, chassis	7-13
	Schematic, voltage, parts, alignment, specifications	9-13
78, Chassis RE37	Socket, trimmers, layout	9-14
	Tuner data	9-19
Arvin 81	Schematic, voltage, trimmers, alignment, parts	9-15
	Socket, layout	9-16
	Schematic, parts	6-21
	Voltage, resistance, alignment, coils	7-9
Arvin 81M	Socket, trimmers, chassis	7-14
	Voltage, resistance, coil data	7-16
	Schematic, parts	6-22
	Voltage, resistance, alignment, coils	7-9
89, 91, Chassis RE27	Socket, trimmers, chassis	7-15
92, Chassis RE31	Voltage, resistance, coil data	7-16
Arvin 417, 467	Schematic, voltage, alignment, trimmers, sensitivity	10-7
	Schematic, alignment, trimmers, sensitivity	10-8
	Schematic, voltage, resistance, coils, parts list	7-17
508 AC-DC	Socket, trimmers, chassis, alignment	7-18
Arvin 517, 527	Schematic, voltage, resistance, parts	8-7
	Socket, trimmers, alignment	8-8
	Schematic, voltage, resistance, coils, parts	7-19
Arvin 517-B, 527-B	Socket, trimmers, chassis, alignment	7-20
	Schematic, voltage, resistance, coils, parts	7-21
518, 518A, 518DW, 528CS, 568, 568A, 568DW	Socket, trimmers, chassis, alignment	7-22
	Schematic, parts	8-10
	Socket, trimmers, chassis	8-12
	Voltage, resistance, alignment, sensitivity	8-13
518B, 518B	Data	Changes 9-3
	Schematic, parts	8-11
	Schematic, parts	8-10
608	Socket, trimmers, chassis	10-10
	Alignment, voltage, data	10-5
	Schematic, parts	8-14
	Voltage, alignment, resistance, specifications	9-17
Arvin 617, 627	Socket, trimmers, layout	9-18
	Schematic, voltage, resistance, coils, parts	7-23
Arvin 617-B, 627-B	Socket, trimmers, chassis	7-24
	Alignment	7-32
	Schematic, voltage, resistance, coils, parts	7-25
618, 618A, 628, 628CS, 638, 638CS	Socket, trimmers, chassis	7-26
	Alignment	7-32
	Schematic, parts	8-10
618B, 628B	Voltage, resistance, alignment, sensitivity	8-15
	Socket, trimmers, chassis	8-16
	Data	Changes 10-1
	Schematic, voltage, alignment, parts	8-17

MODEL	NOBLITT SPARKS INDUSTRIES—(Cont.)	REVISED PAGE
Arvin 27	Schematic, voltage, resistance, parts	6-11
RE27 Chassis	Chassis layouts	6-13
Arvin 28	Changes—See model 17	6-13
	See model 89	
29	Schematic, voltage, resistance, changes	7-3
	Alignment	7-2
	Socket, trimmers, chassis	7-4
	Schematic, voltage, resistance, parts	8-3
	Socket, trimmers, chassis, alignment	8-4
RE29 Chassis	See model 58	
Arvin 80-A, Type 1	Schematic	4-6
Arvin 80-A, Type 2	Schematic	4-7
Arvin 80-A	Resistance data, voltage	4-8
	Condenser data, control data	4-9
Arvin 80-A (3rd Type)	Schematic	5-9
	Voltage, test data, coil resistance	5-10
	Alignment data	5-14
32	Notes—See model 20-A	5-14
	Schematic, parts, voltage, alignment	9-7
Arvin 33	Socket, trimmers, layout, specifications	9-8
	Schematic, voltage, resistance, coils, parts	7-5
	Alignment	7-2
	Changes	7-3
Arvin 35 below serial #E31577H	Socket, trimmers, chassis	7-6
Arvin 35, above serial E31577H	Schematic, parts list	5-11
Arvin 85	Voltage, resistances	6-10
	Schematic, parts list	5-12
	Voltage, test data, coil resistance	5-13
Arvin 87	Alignment data, notes	5-18
	Schematic, voltage, resistance	5-18
	ancies, parts	6-13
RE37 Chassis	Chassis layouts	6-14
39	Alignment—See model 17	6-15
	See model 78	
	Schematic, voltage, resistance, parts	8-5
Arvin 41	Socket, trimmers, chassis, alignment	8-6
	Schematic, parts	6-16
42	Voltage, resistance, socket, trimmers, alignment, coil	7-7
	Schematic, parts, voltage	9-9
	Socket, trimmers, layout, specifications	9-10
440, Chassis RE46	Alignment	9-7
	Schematic, voltage	10-1
	Alignment, socket, trimmers, sensitivity	10-2
RE44 Chassis	Antenna data	10-3
Arvin 45 below serial #E40568L	See model 7A	
Arvin 45, above serial E40568L	Schematic, parts list	5-15
Arvin 45	Voltage, resistances	6-17
	Schematic, parts list	5-16
	Voltage, test data, coil resistance	5-17
	Alignment, notes	5-18
RE45 Chassis	See model 8A	
RE46 Chassis	See model 44C	
Arvin 51	Schematic, parts	6-18
	Voltage, resistance, socket, trimmers, alignment, coil	7-7
Arvin 51-B	Schematic, socket, trimmers, voltage, resistance, coils, alignment, parts	7-8

RADIOTRON					
MODEL	NOBLITT SPARKS INDUSTRIES—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON	
318B, 628B	Socket, trimmers, chassis, alignment.....	8-18			
918, 828, 828A, 838OS	Schematic, voltage, alignment sensitivity, resistance, parts.....	8-19			
	Socket, trimmers, chassis.....	8-20			
	Data.....	Changes 10-1			
228AT, 838AT, Chassis 818AT	Schematic, voltage, resistances.....	10-9			
	Alignment, tuner data, sensitivity.....	10-3			
848OS	Socket, trimmers, chassis.....	10-6			
Arvin 927	Schematic, alignment parts.....	8-21			
	Schematic, voltage, resistance, coils, parts.....	7-27			
	Socket, trimmers, chassis.....	7-28			
	Alignment.....	7-32			
Arvin 1127	Schematic, voltage, resistance, parts.....	7-29			
	Socket, trimmers, chassis.....	7-30			
	Coil data, data, power supply layout.....	7-31			
1237, 1247, 1247A	Alignment.....	7-32			
1237, 1237D, 1247, Chassis 1237D	Schematic, alignment, parts.....	8-22			
	Alignment, notes.....	9-20			
1427, 1427D	Schematic, parts, voltage, coils.....	9-21, 22			
	Classis views.....	9-23			
	Trimners.....	9-24			
	Schematic, alignment.....	10-1, 12			
	Trimners, socket.....	10-13			
	Voltage, resistances.....	10-13			
	Classis views.....	10-14			
<b>NORCO MFG. CO.</b>					
Also see REMPLER CO., LTD.					
4 Combination Dual Wave	Schematic, voltage, notes.....	3-1			
4 Super	Schematic, voltage, notes.....	3-2			
<b>NORDEN-HAUCK, INC.</b>					
Super DX-5	Schematic.....	1-1	*455		
Super DX-5A	Schematic.....	1-1	*455		
O-7	Schematic.....	1-3	*457		
Super 10	Schematic.....	1-3	*457		
Admiralty Super 12	Schematic.....	1-2	*456		
Super 15, RF Chassis	Schematic.....	8-2			
Super 15, Power Pack and Amplifier	Schematic.....	3-1			
<b>OLDSMOBILE DIV.—GENERAL MOTORS</b>					
See UNITED MOTORS SERVICE					
982043 Early	See BUICK 980393				
	Schematic, trimmers, voltage, notes.....	9-1			
	Socket, trimmers, chassis, voltage changes.....	9-2			
	Alignment, parts.....	9-4			
	Data.....	Changes 10-1			
	Serial Schematic, socket, voltage, chassis.....	9-3			
982043 Late, Above Serial A20,000	Alignment, parts.....	9-4			
	Schematic, voltage, changes.....	9-5			
982044 (3 Types)	Socket, trimmers, alignment.....	9-6			
	Schematic, voltage.....	9-7			
982045 (3 Types)	Socket, trimmers, chassis notes.....	9-8			
	Alignment.....	9-6			
	Schematic.....	10-1			
982083, Early, Late	Socket, trimmers, chassis, condenser schematic.....	10-2			
	Remote control head details, parts.....	10-3			
	"Hash," elimination, changes, notes.....	10-4			
	Voltage, alignment.....	10-17			
	Conversion control units, assembly, parts.....	10-18			
	Schematic, notes.....	10-5			
982084, Early, late	Socket, trimmers, chassis.....	10-6			
	Alignment, voltage.....	10-7			
<b>OLDMOBILE DIV.—GEN. MOTORS.—(Cont.)</b>					
MODEL	REVISIONS	PAGE	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
982084, Early, Late	Remote control head assembly, details, condenser schematic "Hash," elimination, changes, notes.....	10-8			
	Conversion control units assembly, parts.....	10-18			
	Schematic, changes.....	9-9			
	Socket, trimmers, notes, chassis.....	9-10			
	Alignment, voltage.....	9-11			
	Parts, data.....	9-12			
	Remote control head details, parts.....	10-3			
	Conversion control units assembly, parts.....	10-18			
	Schematic.....	10-9			
982126 (3-wire speaker)	Schematic.....	10-10			
982126 (4-wire speaker)	Socket, trimmers, chassis, alignment.....	10-11			
982126 (3 and 4-wire speaker models)	Voltage, chassis, control assembly.....	10-12			
	bly.....	10-13			
982127	Schematic.....	10-13			
	Socket, trimmers, alignment.....	10-14			
	Control assembly.....	10-12			
982153	Schematic.....	10-15			

# PACENT PACKARD

RADIOTRON  
EARLY COMPLETE  
PAGE

REVISÉ  
PAGE

PACIFIC RADIO CORP.—(Cont.)

MODEL

102 (Late)	Schematic	8-6
110	Schematic	8-7
150	Schematic	8-8
302	Schematic	8-9
	Alignment	9-5
321-86	Schematic, alignment	8-9
321-87	Schematic, alignment	8-10
601	Schematic, socket, trimmers	9-8
	Alignment	9-6
682	Schematic, alignment	7-4
702	Schematic, socket, trimmers	10-9
	Alignment	9-6
915	Schematic, alignment	10-10
3280	Schematic, alignment	7-5
6320	Schematic, alignment	7-6
6322	Schematic, alignment	7-7
6370	Schematic, alignment	7-8
7370	Schematic, alignment	7-9
14870	Schematic, alignment	7-10

## PACKARD BELL CO.

5B	Schematic	10-1
5D	Schematic, socket, trim-	10-2
5 Kompak	mers	8-1, 8-2
5M, 35M	Schematic	9-1
5MP	Schematic	10-3
5N	Schematic	10-4
5NP	Schematic	10-4
5TP	Schematic	9-1
15	Schematic	10-1
25, Early & late	Schematic	6-1
34	Schematic	6-4
	Additional data	Changes 7-13
35	Schematic	6-4
	Alignment data	Changes 7-5
35A	Schematic, socket	7-1
35H	Schematic, socket	6-2
35L	Schematic, socket, trimmers	8-3
35M	See model	10-5
35N	Schematic	9-1
36	Schematic, socket, trimmers	10-4
38	Schematic, socket	10-2
40 Portable	Schematic, socket, trimmers	10-1
41	Schematic	6-4
45M	Alignment data	Changes 7-5
46	Schematic, socket, alignment	7-2
46B	Schematic, socket	8-3
46D	Schematic	9-1
46DP	Schematic	9-2
47M	Schematic, socket	7-1
48	Schematic, socket	7-3
48B	Schematic	9-2
48D	Schematic	10-7
48DC, 48DK	Schematic	10-2
50 High Fidelity	Schematic, socket, trimmers	10-2
	alignment	8-1, 8-2
58	Schematic	10-6
65	Schematic, socket, notes	7-4
65 Auto	Schematic	6-2
66	Schematic, socket, tuner	9-3
67	Schematic, socket, notes	7-4
75 Auto	Schematic, socket, trimmers	10-5
	alignment	10-5
76	Schematic	6-5
76 Auto	Schematic, socket, trimmers	8-4
78	Schematic, socket, alignment	9-4
86	Schematic	6-6
120 Console	Schematic, alignment	8-1, 8-2
120-AB	Schematic	9-3
160	Schematic	10-7
	Socket, trimmers, alignment, tuner	10-8

See PHILCO RADIO & TELEVISION CORP.

RADIOTRON  
EARLY COMPLETE  
PAGE

REVISÉ  
PAGE

PACIFIC REPRODUCER CORP.—(Cont.)

MODEL

Fader Units, (Two types)	Schematics	4-1
Pacnet Rectifiers, (Two types)	Schematic	4-6
Spkr-Amplifier AO Service	Schematic	4-4
2-MDA-F	Schematic	4-5
2-MDA-F Control Box	Assembly wiring	4-16
2-MDA-F Harness	Schematic	4-2
	Layout	4-4
2-MDA-F Piping	Layout	4-18
2-MDA-F Piping for Disc-Film	Schematic	4-5
	Layout	4-22
4-MDA Piping for Disc	Layout	4-20
4-MDA-F Harness	Layout	4-14
4-MDA-F Amplifier	Assembly wiring	4-15
4-MDA-F Piping	Layout	4-17
4 Spkr-MDA Service	Schematic	4-13
C-63 (102), C-66 (20)	Schematic	4-10
63 PEO Amplifier	Schematic	4-9
65 Amplifier	Schematic	4-10
70 Amplifier	Schematic	4-11
112	See model HFA	4-11
500 DDA-Jr. Piping for Disc	Layout	4-19
500 DDA-Jr. Piping for Disc-Film	Layout	4-21
C-1000 Jr.	Schematic	4-9
1005 Amplifier	Schematic	4-8
1010 SPU	Schematic	4-8
1015 Amplifier	Schematic	4-7
1020 SPU	Schematic	4-7
1063 PEO Amplifier	Schematic	4-12
1070 Amplifier	Schematic	4-13

## PACIFIC RADIO EXCHANGE



Spero Four	Schematic	Misc. 6-24
Spero Super	Schematic	Misc. 6-25

## PACIFIC RADIO CORP.

Midnet Super	Schematic, socket, alignment	9-4
TR-F Midnet	Schematic	10-10
3	Schematic	9-1
5SW	Schematic, alignment	9-2
H6	Schematic	8-1
H7	Schematic, alignment	7-1
M7	Schematic	8-1
8T-6V	Schematic	9-3
	Socket, trimmers, parts	9-4
	Alignment	9-6
11	Schematic	9-1
12	Schematic	10-1
14	Schematic	10-1
15, 16 Series 37	Schematic	10-2
20, Series 37	Schematic	10-2
21, 22, 23	Schematic, alignment	9-5
25	Schematic	10-3
30	Schematic, socket, trimmers	8-2
35	alignment	9-6
36	Schematic, socket	10-4
	Alignment	9-6
40	Schematic	10-5
41	Schematic, socket, trimmers	10-6
	Alignment	9-6
42	Schematic, socket, trimmers	10-7
	Alignment	9-6
43	Schematic, socket, trimmers	9-7
	Alignment	9-6
50	Schematic	8-3
60	Schematic, alignment	10-5
A60B	Schematic, alignment	7-2
61	Schematic	8-5
81A	Schematic, alignment	7-3
101, Early 1935	Schematic, alignment	10-8
101 (Late)	Schematic, socket	8-6

[illegible]

# RIDER Publications

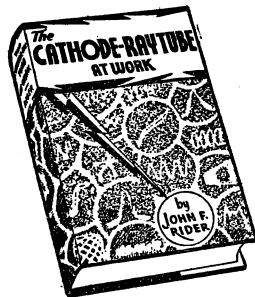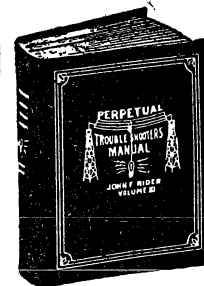

## THE CATHODE-RAY TUBE AT WORK

A new era in the servicing of radio receivers, public-address systems, transmitters, etc., is in the offing. It is the use of the cathode-ray tube and the progressive serviceman will prepare himself now for the change that is coming. The theory underlying the functioning of the cathode-ray tube and the circuits that accompany it receives full consideration in this book. The second half of the volume is devoted to specific and practical applications of commercial oscilloscopes to servicing and adjustment problems. Order your copy today!

### CONTENTS

I—The Theory of the Tube. A complete explanation of the different types of cathode-ray tubes. How the spot is focussed and how the beam of electrons is deflected. II—Sweep Circuits. How and why the spot moves across the screen and forms the image. III—A-C. Voltages on Both Sets of Plates. An explanation of the patterns formed on the cathode-ray tube screen when a.c. voltages are applied. IV—Commercial Cathode-Ray Oscillographs. A detailed description of the various cathode-ray oscillographs that are on the market. V—Practical Application of the Cathode-Ray Oscillograph. General directions for adjusting the cathode-ray oscillograph for all tests. VI—Alignment of Tuned Circuits. Understandable explanation of the theory of the frequency modulated oscillator and how it is used in testing with the cathode-ray oscillograph. VII—The A-F. Frequency Modulator. How overall a.f. response curves of audio units are developed and what they mean. VIII—Auto Radio Vibrator Testing. The connections for testing vibrators with the cathode-ray tube oscillograph. IX—Transmitter Adjustment. How the modulation of a wave is measured and the trapezoidal pattern is developed on the screen. X—Other Applications of the Cathode-Ray Oscillograph. Beat patterns, c-w. reception and detection.

338 Pages . . Profusely Illustrated . . Net Price \$4.00



## SERVICING SUPERHETERODYNES

No other circuit in the radio field has undergone all the changes that have been incorporated in the superheterodyne. In order to service these receivers with profitable speed, you must be able to analyze the different portions of the circuit quickly and this is just what Rider tells you how to do in this book. Not only is the theory of all types of Superhets thoroughly covered, but actual servicing details are most complete. Many thousands of Servicemen are using "Servicing Superheterodynes" daily and are finding the investment one that paid dividends in increased profits.

### CONTENTS

I—The Principles Underlying the Operation of the Superheterodyne Receiver. II—The Generation of and the Relation Between Harmonics. III—Explanation of the Different Types of Superheterodyne Circuits. IV—Function and Characteristics of Individual Parts of the Superheterodyne Receiver. V—Special Circuits and Tube Applications. VI—Troubles and Symptoms Encountered in Superheterodynes. VII—Application of Test Oscillators. VIII—Vibrator Units. Appendix—Intermediate Peak Frequencies of Commercial Receivers with Model Numbers.


288 Pages . . Profusely Illustrated . . Net Price \$2.00

### Alternating Currents in Radio Receivers

Are you familiar with the different forms of alternating currents which are present in a radio receiver? When once you understand the basic facts relating to the cycle—frequency—sine waves—harmonics—complex waves—modulated waves—phase relations—you will have no trouble in understanding the servicing problems which involve these factors.
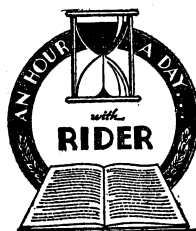
### D.C. Voltage Distribution

Only a casual glance at the schematics of some of the 1939 multi-tube sets will convince you that the distribution of the D.C. voltage to the tube elements is complicated. The many different forms these systems take should be recognized at a glance and understood. You should know thoroughly how the value of resistance and wattage rating of each resistor is calculated and why.



96 Pages Each  
Net Price \$1.25 Each

### Resonance and Alignment

Do you know what happens when you tune a circuit to resonance? In order to align a receiver, oscillator, or transformer properly, so that maximum efficiency is attained, you must be familiar with more than just the mechanical operation. Are you familiar with I.F., oscillator, R.F. and detector alignment for all types of circuits—single, double and triple tuned systems?

### Automatic Volume Control


Automatic volume control has now become a standard feature of every well made receiver. Are you familiar with every type in use and can you recognize one system from another by examining the schematic? Do you know how various types of tubes are used in each circuit? Noise suppression systems, time delay circuits—audio-frequency volume expansion systems and other such networks have greatly increased servicing problems.

HARD COVERS . . . . . TYPE SET . . . . . PROFUSELY ILLUSTRATED . . . . . HANDY POCKET SIZE

## SERVICING RECEIVERS BY MEANS OF RESISTANCE MEASUREMENT

Take the guesswork out of servicing by using an ohmmeter in your trouble shooting. This book tells you how to make and correctly interpret point to point resistance measurements. It will simplify your servicing problems and enable you to use the resistance data furnished in RIDER MANUALS to the best advantage. Now that more and more manufacturers are supplying resistance data, you need this book to speed up your servicing with greater accuracy. Let Rider show you how to use a modern servicing procedure on the complicated receivers—you will find in this book the usual Rider clarity of explanation of how theory is applied to practice.

203 Pages . . . . . Net Price \$2.00

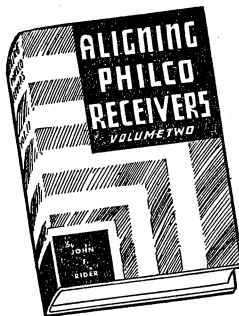

## ALIGNING PHILCO RECEIVERS Two Volumes

Everything you need for aligning Philco receivers . . . I.F. peaks—adjustment frequencies—trimmer and padder locations—complete and detailed information for aligning every Philco model from 1929 to 1941. These two volumes, prepared with the co-operation of the engineering staff of the Philco Radio & Television Corp., are the authentic source of alignment information and the data are presented in a brand new way that makes alignment easier and quicker. You will find all the necessary data arranged so that every step in the alignment procedure is carried out in a definite systematic time-saving manner. The necessity for referring back and forth is eliminated completely in this radically new style of presenting alignment data.

Vol. I — 1929 to 1936 — 176 pages — \$2.00  
Vol. II — 1937 to 1941 — 200 pages — \$2.00

## AUTOMATIC FREQUENCY CONTROL SYSTEMS

From the simplest type of A.F.C. circuit to the most complicated push pull control circuit . . . you will find them all clearly explained in Rider's book. The first part of the book is devoted to a review of the combination of D.C. voltages, the phase relations in inductive, capacitive, and transformer circuits, with particular reference to the manner in which these principles appear in A.F.C. circuits. The remaining chapters cover the operation of all types of discriminator circuits, the operation of the various types of control tube circuits, including the push-pull type, the reflected reactance type, and the mutual inductance type. Let Rider tell you all about A.F.C. in this up-to-the-minute book that combines theory and practice.

144 Pages . . . . . Net Price \$1.75



PHILCO RADIO & TELEVISION CORP.—(Cont.)	REVISI PAGE	RADIOTRON EARLY COMPLETE PAGE
MODEL		
Condensers	2-25	1686
Dial Drive Assemblies	7-151	
Grand Father Clock	8-46	1690
Increasing Range and		
Interference Notes		
Lazy X		1714
Philco Speakers		
Philco Tubes		
Shadow Tuning		1678
Standard Bypass		1684
Condensers		
Superheterodynes		1680
Transistors		
B part of AB Unit		
DB		
DP, DPV		
EA, EG		
EA Dynamotor		
EF Full-wave Vibrator		
G		
G (Code 122)		
J, R		
RP-1 Wireless Record		
Player		
3 Transistors		
4, 40 SW Converter		
5 Transistors		
5, 6, 7, 8, 9, 12		
5, 6, 9		
6, B6, 6F Transistors		
7 Transistors		
7, 10		
TV-NT7, T8-NT8		
8, 12		
9, 12 (123)		
10, O, E		
10, O, E (Code 123)		
11, J, R		
11, J, R (Code 122)		
1A		
Connections, color code.....	2-25	1686
Data.....	7-151	
Details, notes.....	7-151	
See model 570.....	7-151	
Data.....	8-46	1690
Changing I.F. Peaks.....	8-46	
Installation notes.....	8-46	
Data, part 1.....	8-46	1714
Data, part 2.....	8-46	
Data, part 3.....	8-46	
Data, part 4.....	8-46	
Data, part 5.....	8-46	
Data, part 6.....	8-46	
Data, part 7.....	8-46	
Data, part 8.....	8-46	
Data, part 9.....	8-46	
Data, part 10.....	8-46	
Adjustment notes.....	8-46	
Data.....	2-17	
Adjustment notes.....	2-17	
Vibrator data, steering	4-47	
column.....	4-47	
Drive controls.....	4-48	
Drive controls, part 2.....	4-48	
Control shafts data.....	4-49	
Control shafts, part 2.....	4-50	
Chassis layout.....	1-2	1592
See model 10.....	1-2	
C.....		
Specifications—See model AB-468		
Schematic, chassis, parts,	8-136	
changes.....	8-136	
Socket, trimmers, alignment.....	8-137	
See model 10.....	8-137	
Data.....	4-52	
Wiring, diagram, values.....	3-5	1599
Terminal arrangements.....	3-6	1600
Data.....	3-7	1601
Schematic, parts list.....	3-9	
Installation data.....	5-1	
Installation data, service data.....	5-2	
Alignment, adjustment, socket.....	5-3	
Schematic, chassis layout, parts.....	5-4	
Additional data.....	7-1	
See model 11.....	7-1	
See model 700.....	7-1	
Schematic, instructions.....	10-12	
Voltage, electrical values.....	3-1	1595
Schematic, compensating data.....	3-2	1596
Chassis layout, parts list,	2-1	1605
data.....	2-1	
Schematic, socket, voltage,	2-2	1604
data.....	2-2	
Schematic, chassis layout,	3-8	
data.....	3-8	
Parts list.....	3-9	
Changes.....	4-55	
Speaker cones, adjustments.....	4-51	
Schematic, voltage, socket.....	3-55	
Schematic, chassis layout.....	3-3	1596-A
Alignment data.....	3-4	1597
Adjustments.....	4-54	1598
See model 806.....	4-54	
Schematic, data.....	3-5	1599
Chassis layout, alignment	3-6	
data.....	3-6	
Condenser data.....	3-7	1600
Schematic, layout, parts list.....	3-56	1601
Data.....	4-52	1596-B
Adjustments—See model 5.....	4-52	
Schematic, chassis, parts list.....	4-56	
Service notes, chassis layout.....	4-57	
Adjustments—See model 7.....	4-57	
Changes.....	7-12	
Alignment, socket.....	5-5	
Schematic, chassis, parts.....	5-6	
Changes.....	5-7	
Alignment, socket.....	5-7	
Schematic, chassis, parts.....	5-8	
Alignment, parts, chassis, data.....	6-43	
Alignment, socket, trimmers.....	6-44	
Schematic, chassis, notes—See	model 8	
PHILCO RADIO & TELEVISION CORP.—(Cont.)	REVISI PAGE	RADIOTRON EARLY COMPLETE PAGE
MODEL		
Adjustments—See model 5		
Additional data.....	Changes 7-2	
See model 9.....	3-29	1649
Chassis layout, voltage, speaker	3-30	1650
connections, data.....	3-30	
Schematic, parts list.....	4-1	
Voltage, chassis view, socket,	4-2	
data.....	4-17	
Schematic, parts list.....	4-17	
Changes—See model 91.....	3-50	1718
Changes.....	3-10	1606
Voltage, socket data.....	3-11	1607
Schematic, changes.....	3-11	
Chassis layout, speaker data,	3-12	1608
notes.....	3-12	
Alignment, trimmers.....	8-10	
Schematic, voltage, data.....	4-3	
Chassis view, socket.....	4-4	
Parts list.....	4-5	
Adjustment notes.....	4-6	
Adjustment notes.....	4-7	
Changes.....	4-9	
Changes.....	4-10	
Changes.....	5-15	
Changes.....	4-8	
Schematic, socket, voltage.....	6-1	
Chassis, parts.....	6-3	
Alignment, trimmers.....	6-2	
Changes.....	Changes 7-8	
Changes.....	4-9	
Changes.....	4-10	
Voltage, chassis view, socket,	4-11	
data.....	4-12	
Schematic, trimmer data.....	4-13	
Alignment, parts list.....	4-13	
Changes, parts list.....	4-14	
Changes, parts list.....	4-14	
Schematic, data, voltage,	4-15	
socket.....	4-15	
Chassis view, alignment, parts	4-16	
list.....	4-17	
Changes.....	5-9	
Alignment, voltage, parts.....	5-9	
Schematic, socket, chassis	5-10	
layout.....	5-10	
Changes.....	5-15	
See model 89 Early.....	5-16	
Notes.....	4-43	
Changes.....	4-18	
Socket, voltage, data.....	4-19	
Schematic, parts list.....	4-19	
Chassis view, trimmer notes,	4-20	
adjustments.....	4-20	
Changes, See model 14LZX.....	1-6	1610
Schematic, chassis view.....	2-3	1609
Voltage, socket, values.....	2-3	1610
Circuit changes, chassis views.....	2-4	
Schematic similar to model 20		
Same as model 71(221) but with		
phonograph.....	3-43	
Schematic, changes.....	8-10	1688
Alignment, trimmers.....	8-10	
Changes—See model 14-LZX.....	3-45	1685
Schematic, changes.....	3-45	
Alignment—See model 91(221)		
See model 51.....	5-11	
See model 43-AC.....	5-12	
Similar to model 89 Early.....	5-13	
Alignment, parts list.....	5-14	
Schematic, layouts, voltage.....	5-14	
Schematic, voltage, layouts.....	5-14	
Alignment, layout, parts list.....	5-15	
Schematic, layout, parts list.....	5-15	
Changes.....	1-7	1612
Schematic, socket, chassis	2-5	1611
views.....	2-5	
Voltage, values, data.....	2-5	

[illegible]

RADIOTRON  
EARLY COMPLETE  
PAGE

PHILCO RADIO & TELEVISION CORP.—(Cont.)  
MODEL  
38-116 (125)

Schematic, coils	9-11, 12
Chassis layouts, speaker wiring	9-13
Transformer data	9-14
Socket voltage, specifications	9-15
Notes	9-16
Alignment, tuner	9-17
Trimmers, parts	9-18
Schematic, coils	9-19
Parts list	9-20
Alignment, tuner	9-21
Schematic, coils	9-22
Chassis layouts, socket	9-23
Trimmers	9-24
Voltage, socket, trimmers	9-25
Alignment	9-26
Schematic	9-27
Alignment, part 2, chassis	9-28
Schematic, voltage, socket	9-29
Trimmers	9-30
Alignment, parts	9-31
Schematic, chassis, parts	9-32
Socket, trimmers, alignment	9-33
Voltage	9-34
Schematic, chassis, parts	9-35
Socket, trimmers, alignment	9-36
Voltage	9-37
Schematic	9-38
Alignment, chassis, tuner	9-39
Socket, trimmers, voltage	9-40
Parts	9-41
Schematic	9-42
Voltage, socket, trimmers	9-43
Alignment	9-44
Tuner data	9-45
Schematic, voltage	9-46
Alignment, socket, trimmers	9-47
Chassis, parts, tuner chassis	9-48
Tuner data	9-49
Schematic, voltage	9-50
Alignment, tuner data	9-51
Socket, trimmers, chassis, tuner	9-52
Chassis, drive data, parts	9-53
Schematic, voltage	9-54
Alignment, tuner data	9-55
Socket, trimmers, chassis, tuner	9-56
Chassis, drive data, parts	9-57
Schematic	9-58
Parts list	9-59
Control frequency	9-60
amplifier adjustments	9-61
Chassis layout, trimmers, dial	9-62
drive, "Mystery Control"	9-63
schematic	9-64
Alignment	9-65
Specifications, "Mystery Control"	9-66
Adjustments	9-67
Schematic, socket, trimmers	9-68
Chassis	9-69
Alignment, parts	9-70
Schematic, voltage, socket	9-71
alignment, trimmers, chassis, parts	9-72
Schematic socket, trimmers	9-73
Chassis, parts	9-74
Alignment	9-75
Schematic	9-76
Control frequency amplifier	9-77
Adjustments	9-78
"Mystery Control" schematic	9-79
trimmers, dial drive	9-80
Alignment	9-81
Chassis, parts list	9-82
"Mystery Control" adjustments, specifications	9-83
Schematic, voltage, data	9-84

RADIOTRON  
EARLY COMPLETE  
PAGE

PHILCO RADIO & TELEVISION CORP.—(Cont.)  
MODEL  
38-2670

Alignment, trimmers	8-50
Chassis, parts	8-51
Chassis view, socket	8-52
alignment	8-53
Schematic, changes, parts list	8-54
Notes	8-55
Changes	8-56
Changes	8-57
Changes	8-58
Schematic	8-59
Chassis, parts	8-60
Alignment, trimmers, voltage	8-61
Schematic	8-62
Alignment, trimmers, voltage	8-63
Chassis, parts	8-64
Changes	8-65
Schematic	8-66
Chassis, parts	8-67
Alignment, voltage, trimmers	8-68
Schematic, notes	8-69
Alignment, parts	8-70
Trimmers, voltage, chassis	8-71
Changes	8-72
Data	8-73
Schematic	8-74
Voltage, socket, trimmers	8-75
tuner, parts	8-76
Schematic, chassis, parts	8-77
Socket, trimmers, alignment	8-78
notes, voltage	8-79
Changes	8-80
Schematic, chassis, parts	8-81
Socket, trimmers, voltage	8-82
Specifications, voltage	8-83
Socket, trimmers, alignment	8-84
Specifications, voltage	8-85
Schematic, voltage, trimmers	8-86
Chassis	8-87
Alignment, parts	8-88
Schematic, voltage, chassis	8-89
Alignment, trimmers, parts	8-90
Schematic	8-91
Trimmers, alignment, Part 1	8-92
Alignment, Part 2, voltage	8-93
Chassis, notes	8-94
Parts	8-95

PHILCO RADIO & TELEVISION CORP.—(Cont.)			RADIOTRON		
MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
40-120, 40-125	Schematic, voltage, parts ..... 10-28	10-28			
40-150, 40-155	Alignment, trimmers ..... 10-16	10-16			
	Schematic, socket, trimmers ..... 10-29	10-29			
	Alignment ..... 10-30	10-30			
	Socket, trimmers, chassis, parts ..... 10-31	10-31			
40-160	Tuner data ..... 10-16	10-16			
	Schematic, socket, trimmers, chassis, voltage, parts ..... 10-33	10-33			
	Tuner data ..... 10-16	10-16			
	Alignment ..... 10-34	10-34			
40-180, 40-185, 40-190	Schematic, socket, trimmers ..... 10-29	10-29			
	Alignment ..... 10-30	10-30			
	Socket, trimmers, chassis, parts ..... 10-31	10-31			
	Tuner data ..... 10-16	10-16			
40-195, 40-200	Schematic, voltage, socket, trimmers ..... 10-35	10-35			
	Tuner data ..... 10-16	10-16			
	Chassis, tuner chassis, parts ..... 10-36	10-36			
	Alignment ..... 10-37	10-37			
41 DO, 42 DO	Schematic, socket, voltage, data ..... 1-11	1-11			
	Chassis, data ..... 2-8	2-8			
	Voltage, socket, data, notes ..... 3-13	3-13			
	Schematic, changes ..... 3-14	3-14			
	Chassis layout, single and twin speaker connections ..... 3-15	3-15			
	Alignment data ..... 3-16	3-16			
	Changes ..... 4-36	4-36			
48-121	Voltage, trimmers, socket ..... 4-23	4-23			
44	Schematic, condensers ..... 4-24	4-24			
	Chassis view, adjustment data ..... 4-25	4-25			
	Parts list ..... 4-26	4-26			
	Alignment, voltage, layouts ..... 5-25	5-25			
	Changes ..... 5-15	5-15			
	Chassis, parts, socket ..... 5-24	5-24			
	Chassis, voltage, parts list ..... 1-12	1-12			
46, 46-E DO	Schematic, voltage, data ..... 1-13	1-13			
47 DO (121-221)	Schematic, voltage, resistor data ..... 3-47	3-47			
	Chassis layout, speaker connections ..... 3-48	3-48			
	Alignment, trimmers ..... 8-87	8-87			
48 DO	Socket, resistor data, voltage, notes ..... 3-21	3-21			
	Schematic, chassis layout ..... 3-22	3-22			
	Alignment, trimmers ..... 8-87	8-87			
49	Alignment, parts list ..... 5-27	5-27			
	Schematic, voltage, layouts ..... 5-28	5-28			
	Changes ..... 5-33	5-33			
50, 50-A	Schematic, chassis, data ..... 1-14	1-14			
	Voltage, values ..... 1-15	1-15			
	Adjustments, parts list ..... 2-9	2-9			
	Test data ..... 2-10	2-10			
51, 51-A, 52, 24, 551	Schematic, socket, data ..... 2-11	2-11			
	Voltage, data ..... 2-12	2-12			
	Chassis, adjustment, parts list, notes ..... 2-13	2-13			
58 A-C DO	Schematic, alignment ..... 3-17	3-17			
	Chassis layout, voltage for AO and DC ..... 3-18	3-18			
54	Voltage, data ..... 3-57	3-57			
	Schematic ..... 3-58	3-58			
	Changes ..... 4-36	4-36			
	Alignment, trimmers ..... 7-147	7-147			
57	Voltage, parts view ..... 4-27	4-27			
	Schematic, parts list ..... 4-28	4-28			
	Trimmers, alignment ..... 4-29	4-29			
58	Similar to model 57				
59	Alignment, voltage, parts list ..... 5-29	5-29			
	Schematic, chassis, parts list ..... 5-30	5-30			
	Changes ..... 5-30	5-30			
60	Changes ..... 5-40	5-40			
	Voltage, parts view, adjustment ..... 4-31	4-31			
	Schematic, parts list ..... 4-32	4-32			
	Changes ..... 7-147	7-147			
PHILCO RADIO & TELEVISION CORP.—(Cont.)			RADIOTRON		
MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
65	Schematic, socket, voltage, changes ..... 1-16	1-16			
	Alignment, trimmers ..... 5-31	5-31			
66	Schematic, voltage, parts ..... 5-32	5-32			
	Changes ..... 5-33	5-33			
70, 70-A (Below #B-22,000)	Schematic, socket, voltage, data ..... 1-17	1-17			
	Chassis, parts values ..... 1-18	1-18			
	Parts list, data ..... 2-5	2-5			
	Alignment, trimmers ..... 8-88	8-88			
	Voltage, values ..... 3-32	3-32			
70, 70-A (Above #B-22,000)	Chassis layout ..... 2-16	2-16			
	Alignment ..... 2-17	2-17			
	Schematic, wiring changes ..... 3-31	3-31			
71 Series, 22	Voltage, socket, twin speaker connections ..... 3-23	3-23			
	Schematic, notes ..... 3-24	3-24			
	Alignment, trimmers ..... 8-10	8-10			
	Shadow tuning data ..... 4-35	4-35			
	Changes ..... 4-43	4-43			
76	Schematic, socket, voltage, data ..... 2-19	2-19			
	Chassis, socket, alignment ..... 1-20	1-20			
77, 77-A	Voltage, values ..... 4-60	4-60			
80	Socket, voltage, electrical data ..... 3-25	3-25			
	Schematic, chassis layout, notes ..... 3-26	3-26			
81	Alignment, trimmers ..... 8-88	8-88			
	Chassis layout, voltage, data ..... 3-27	3-27			
	Schematic, parts list ..... 3-28	3-28			
	Alignment, trimmers ..... 8-88	8-88			
82, 86	Schematic, socket, voltage ..... 1-21	1-21			
84	Adjustment, voltage, parts view ..... 4-33	4-33			
	Schematic, parts list ..... 4-34	4-34			
87	Schematic, socket ..... 1-22	1-22			
	Voltage, data ..... 2-20	2-20			
89	Notes ..... 5-16	5-16			
	Changes ..... 5-40	5-40			
89, 19 (121-2-3)	Schematic, alignment data, changes ..... 3-33	3-33			
	Chassis layout, socket, voltage, data ..... 3-34	3-34			
89 (Code 123)	Schematic, socket, trimmers ..... 7-77	7-77			
	Voltage, trimmers, alignment ..... 7-78	7-78			
89 (126-126B)	Chassis, parts list ..... 7-79	7-79			
90, 90-A (with two '45s)	Changes ..... 4-43	4-43			
	Chassis layout, parts values, data ..... 2-22	2-22			
	Schematic, socket, voltage ..... 2-23	2-23			
	Parts list, data ..... 2-24	2-24			
	Alignment data with Jewell 560 Oscillator ..... 2-30	2-30			
90, 90-A (with one '47)	Schematic, socket, voltage ..... 2-26	2-26			
	Chassis layout, parts values, data ..... 2-27	2-27			
	Socket, test data ..... 2-28	2-28			
	Parts list ..... 2-29	2-29			
	Alignment, trimmers ..... 8-87	8-87			
	Schematic, changes, data ..... 3-35	3-35			
	Voltage data ..... 3-36	3-36			
	Chassis, parts list ..... 3-37	3-37			
	Changes ..... 4-43	4-43			
90, 90-A (with two '47s)	Changes—See model 14-LZX ..... 3-39	3-39			
91, 14, 91-122	Schematic, data ..... 3-40	3-40			
91 (121-221)	Voltage, socket, speaker connections ..... 3-40	3-40			
	Chassis layout, adjustment notes ..... 3-41	3-41			
91 (126-226)	Parts list ..... 3-42	3-42			
91-A (121)	See model 14				
95	Changes ..... 4-43	4-43			
	Schematic, socket, voltage, data ..... 1-23	1-23			
	Alignment, trimmers ..... 8-89	8-89			
	Schematic socket ..... 1-24	1-24			
	Chassis ..... 2-31	2-31			
96, 96-A	Alignment, trimmers ..... 8-89	8-89			
97	Schematic, voltage, socket, data ..... 6-7	6-7			



MODEL	PHILCO RADIO & TELEVISION CORP.—(Cont.)	REVISED PAGE
660	Socket, chassis, parts.....	6-42
	Parts catalog changes.....	7-150
AB-669	Schematic, Power Unit—See model AB-423.....	7-117
665	Specifications—See model AB-463 Schematic.....	7-117
	Socket, voltage, trimmers, alignment.....	7-118
680	Chassis, parts.....	7-119
	Schematic.....	7-121
	Chassis.....	7-120
	Socket, voltage, alignment.....	7-122
	Trimmers, parts list.....	7-123
	Parts catalog changes.....	7-150
680 (Code 122)	Alignment, socket.....	5-47
700, Q	Schematic, chassis layout, parts.....	5-48
800	Schematic, parts list, chassis layout.....	4-51
	Socket, trimmers, alignment.....	4-62
800 (Code 123)	Schematic, chassis, parts.....	5-49
802	Alignment, socket layout.....	5-50
	Schematic, parts.....	6-45
	Alignment—See model 800 (Code 122).....	
805	Additional data.....Changes 7-2 Alignment, socket, trimmers.....	6-46
	Schematic, chassis, parts.....	6-47
	Parts details, parts.....	6-52
806, TV-NT7, T7-S77, T8- NT8	Schematic, parts, chassis, alignment.....	6-49
	Socket, trimmers, alignment, data.....	6-48
	Changes, parts numbering system.....	6-52
808	Schematic, parts, notes.....	7-26
	Installation data.....	6-51
	Parts details, parts.....	6-50
	Trimmers, alignment.....	6-52
	Changes, parts numbering system.....	6-54
809	Chassis.....	7-26
	Schematic, chassis, parts.....	7-16
	Parts details, parts.....	6-53
	Trimmers, alignment.....	6-52
	Changes, parts numbering system.....	6-54
810PA, 810PB 810PV, 810PB, 810PV	Schematic, trimmers, data.....	7-26
	Schematic, chassis.....	6-57
	Parts list.....	6-55
811PA, 811PB	Data, alignment.....	6-55
	Schematic, parts.....	6-56
	Notes.....	7-123
	Socket, trimmers, chassis, alignment.....	7-124
811PV	Schematic, parts.....	7-126
	Alignment, notes.....	7-125
816	Socket, trimmers, chassis.....	7-126
	Schematic, socket, trimmers, chassis.....	7-126
	Alignment.....	7-127
	Remote controls, parts list, part 1.....	7-129
	Remote controls, parts list, part 2.....	7-135
817	Remote controls, parts list, part 2.....	7-136
	Schematic, chassis, notes, parts list.....	7-128
	Socket, trimmers, alignment.....	7-129
	Remote controls, parts list, part 1.....	7-135
	Remote controls, parts list, part 2.....	7-136
818	Schematic, chassis, notes, parts.....	7-131
	Socket, trimmers, alignment.....	7-130
	Remote controls, parts list, part 1.....	7-135
	Remote controls, parts list, part 2.....	7-136

MODEL	PHILCO RADIO & TELEVISION CORP.—(Cont.)	REVISED PAGE
611F	Changes.....	7-148
620	Schematic, voltage, data.....	6-25
	Chassis, parts.....	6-26
	Alignment, data, socket, trimmers.....	6-27
620, Late	Schematic.....	7-59
	Changes, parts.....	7-90
628	Changes.....	7-148
	Chassis, parts.....	6-28
	Schematic, socket, trimmers.....	6-29
	Alignment, data.....	6-30
AB-628	Changes.....	7-148, 7-149
	Schematic, Power Unit—See model AB-423.....	
628B	Specifications—See model AB-463 Changes.....	7-149
628F	Schematic.....	7-149
624	Chassis.....	7-51
	Voltage, socket, trimmers, alignment.....	7-92
625	Chassis, parts list.....	7-92
	Schematic, transformer data.....	7-95
	Socket, chassis, parts list.....	7-94
680	Trimmers, voltage, alignment.....	7-96
	Schematic.....	6-51
	Voltage, trimmers, chassis, alignment, data.....	6-52
	Alignment, part 2, socket, parts.....	6-33
680, 680PF, 2nd Type	Changes.....	7-149
685	Schematic.....Changes 8-2	7-97
	Changes, parts.....	7-98
	Schematic.....	7-99
640	Socket, trimmers, voltage, align- ment, transformer data.....	7-100
	Chassis, parts list.....	7-101
	Schematic.....	6-35
	Chassis, parts.....	6-34
	Socket, voltage, trimmers, alignment.....	6-36
640B	Changes.....	7-149
641	Changes.....	7-149
	Schematic.....	7-103
642	Chassis, parts list.....	7-102
	Socket, voltage, trimmers, notes, alignment.....	7-104
	Changes.....	7-149
	Schematic.....	8-109
	Chassis, parts.....	8-108
648	Voltage, socket, trimmers, alignment.....	8-110
	Changes.....	7-149
	Schematic.....	7-105
	Socket, voltage, trimmers, notes, alignment.....	7-106
645	Chassis, parts list.....	7-107
	Changes.....	7-149
	Schematic.....	7-109
	Socket, voltage, chassis, parts list.....	7-108
	Trimmers, coil data, alignment.....	7-110
650	Changes.....Changes 8-2	6-57
	Schematic.....	6-57
	Alignment, trimmers, voltage, data.....	6-58
	Chassis, sockets, parts, data.....	6-59
651	Changes.....	7-149
	Parts catalog changes.....	7-150
	Schematic.....	7-111
	Socket, trimmers, alignment.....	7-112
655	Voltage, chassis, parts list.....	7-113
	Changes.....	8-2
	Schematic, voltage.....	7-115
	Coil data, parts.....	7-114
	Socket, trimmers, chassis, alignment.....	7-116
660	Changes.....Changes 8-2	6-41
	Schematic.....	6-41
	Alignment, trimmers.....	6-40

[illegible]

NASH-PHILCO

D (122)-NDD, Nash (AC-989)	Schematic, parts ..... 6-78 Installation data ..... 6-80 Alignment, trimmers ..... 8-3 Schematic, parts ..... 8-4 Installation data ..... 6-83 Alignment, trimmers ..... 8-4 Schematic, parts ..... 8-4 Alignment, trimmers ..... 8-4 See model 11 (122) Schematic, parts ..... 6-85 Installation data ..... 6-86 Alignment, trimmers ..... 8-4 See model 806 Schematic, chassis, parts ..... 7-5 Socket, trimmers, alignment ..... 7-6 Schematic, chassis, parts ..... 7-11 Socket, trimmers, alignment ..... 7-12 Schematic, chassis, parts ..... 8-131 Socket, trimmers, alignment ..... 8-129 Control, parts ..... 8-130 Schematic, chassis, parts, changes ..... 8-140 Socket, trimmers, alignment ..... 8-137 Control, parts ..... 8-130 Schematic, chassis, parts ..... 8-141 Socket, trimmers, alignment ..... 8-137 Schematic, parts, chassis ..... 9-34 Socket, trimmers, alignment ..... 9-40 Controls details ..... 10-45 Schematic, parts, chassis ..... 9-39 Socket, trimmers, alignment ..... 9-40 Controls details ..... 10-45
T7-NT7; T8-NT8 T12-NT12X, NT12X3, Lafayette	
T15-NT15, NT15X, Nash, Lafayette	
N-1418	
N-1498H	
N-1494H (Two-antennae) N1514	
N1524	

PACKARD-PHILCO

A-PAD, A-PAL	Schematic, chassis, parts ..... 6-87 Installation data ..... 6-88 Alignment, trimmers ..... 8-3 Schematic, chassis, parts, socket ..... 6-89 Installation data ..... 6-90 Alignment, trimmers ..... 8-3 Schematic, chassis, socket, parts ..... 6-91 Installation data ..... 6-92 Changes, parts numbering system ..... 7-26 Alignment, trimmers ..... 8-3 Schematic, chassis, parts ..... 6-93 Socket, trimmers, alignment ..... 6-94 Schematic, socket, chassis, parts ..... 6-95 Installation data ..... 6-96 Changes ..... 7-11 Alignment, trimmers ..... 8-6 Schematic, chassis, parts ..... 6-97 Alignment, socket, trimmers ..... 6-98 Schematic, chassis, parts, changes ..... 8-127 Control, parts ..... 8-128 Socket, trimmers, alignment ..... 8-129 Schematic, chassis, parts list ..... 7-143 Socket, trimmers, alignment ..... 7-144 Socket, alignment, trimmers ..... 8-133 Schematic, chassis, parts, changes ..... 8-134 Socket, alignment, trimmers ..... 8-133 Schematic, chassis, parts ..... 8-137 Socket, trimmers, alignment ..... 8-137 Control, parts ..... 8-128 Schematic, chassis, parts, changes ..... 8-139 Socket, trimmers, alignment ..... 8-137 See model P-1422
B-PBD	
H (122)-PHD	
PHXD	
T6-PT5, Packard 120 Cars	
T14-PT14	
P-1417	
P-1421	
P-1422, P-1439	
P-1426	
P-1430	
P-1432H	
P-1439	

DODGE-PHILCO

R-ORD T2-OT2 T11-OT11 See Chrysler R-ORD See Chrysler T2-OT2 See Chrysler T11-OT11	
N-FND (V8, 1984)	Schematic, chassis, parts, changes ..... 8-5 Alignment, trimmers ..... 8-4 Schematic, chassis, parts, socket ..... 6-59 Trimmers, alignment ..... 6-58 Changes, parts numbering system ..... 7-26 Schematic, chassis, parts ..... 6-61 Alignment, data, chassis, trimmers ..... 6-60 Schematic, chassis, parts, changes ..... 8-144 Socket, trimmers, alignment ..... 8-133 Schematic, chassis, parts, changes ..... 8-145 Socket, trimmers, alignment ..... 8-133 Schematic, parts, chassis ..... 9-49 Socket, trimmers, alignment ..... 9-52 Control details, antenna ..... 9-50 Schematic, chassis, parts ..... 10-59 Alignment, socket, trimmers ..... 10-60
T9-F79, F70X	
F-1440	
F-1442	
F1540	
F-1640	
G-1418	
G-1486	
G1528	

GRAHAM-PHILCO

G-1418	Schematic, chassis, parts ..... 8-131 Socket, trimmers, alignment ..... 8-129 Schematic, chassis, parts ..... 8-142 Socket, trimmers, alignment ..... 8-137 Schematic, parts, chassis ..... 9-43 Socket, trimmers, alignment, control, parts ..... 9-44
--------	--

HUPMOBILE-PHILCO

G (121)-GGD G (122)-GGD, Hupmobile for J, T & W Cars	See Chrysler G (121)-GGD Schematic, chassis, parts ..... 6-72, 6-73 Installation data ..... 6-76 Alignment, trimmers ..... 8-4 Schematic, chassis, parts ..... 6-75 Changes ..... 6-76 Installation data ..... 6-76 Alignment, trimmers ..... 8-3 Schematic, chassis, parts ..... 6-74 Installation data ..... 6-76 Changes ..... 6-76 Alignment, trimmers ..... 6-77 Schematic, chassis, parts ..... 6-76 Installation data ..... 6-76 Alignment, trimmers ..... 8-4 See model 11 (122) See Chrysler T2-OT2 Schematic, chassis, parts, changes ..... 8-9 Alignment, trimmers ..... 8-8
H-HHD, Hupmobile for J, T & W Cars	
H (122)-HHD, Hupmobile for J, T & W Cars	
R-HRD, Hupmobile for J, T & W Cars	
R (122)-HRD T2-HT2 HT11X See Chrysler T2-OT2	

LINCOLN-PHILCO

LT14X3 Lincoln	Schematic, chassis, parts list ..... 7-9 Socket, trimmers, alignment ..... 7-10 Schematic, chassis, parts ..... 8-132 Socket, trimmers, alignment ..... 8-133 Schematic, chassis, parts ..... 8-135 Socket, trimmers, alignment ..... 8-133 Schematic, parts, chassis ..... 9-51 Controls details, parts ..... 9-48 Socket, trimmers, alignment ..... 9-52 Schematic, chassis, parts ..... 10-61 Alignment, socket, trimmers ..... 10-62
L-1420, L-1424, L-1425	
L-1427, L-1429, L-1460	
L1560 (Lincoln Zephyr)	
L-1660 Lincoln Zephyr	

NASH-PHILCO

O-NCD; D-NDD, Nash (AC-989)	Schematic, parts ..... 6-79 Installation data ..... 6-80 Alignment, trimmers ..... 8-3
--------------------------------	--



PACKARD-PHILCO

P1517	Schematic, parts, chassis	9-37
	Socket, trimmers, alignment	9-38
P1530	Controls details	10-46
	Schematic, parts, chassis	9-46
P1535	Socket, trimmers, alignment	9-38
	Schematic, parts, chassis	9-47
	Socket, trimmers, alignment	9-48
	Controls details	10-47
P-1617	Schematic, chassis, parts	10-53
	Socket, trimmers, alignment	10-54
P-1630	Schematic, chassis, parts	10-56
	Alignment, socket, trimmers	10-54
P-1635	Schematic, chassis, parts	10-57
	Alignment, socket, trimmers	10-58

PIERCE-ARROW-PHILCO

E-MED, Pierce-Arrow	Schematic, parts	6-79
	Installation data	6-82
F(122) MED	Alignment	6-82
T9-MT3, Pierce-Arrow	See model 10 (122)	
DeLuxe	Schematic, socket, chassis, parts	6-99
	Installation data, service notes	6-102
	Changes	6-102
	Alignment, trimmers	6-102
	See Packard T14-PT14	6-102

PLYMOUTH-PHILCO

G(121)-CGD, Plymouth	Schematic, chassis, parts	5-4
Codes PE & PF	Installation data	5-1
	Installation data, notes	5-2
	Alignment, adjustment, socket	5-2
G(122)-CGD, Plymouth	Schematic, chassis, parts	6-82
Codes PE & PF	Installation data	5-1
	Installation data, notes	5-2
	Alignment, trimmers	5-4
	Schematic, chassis, parts	6-88
	Installation data	6-87
	Similar to T2-CT2	
	Alignment, trimmers	8-6
	See Chrysler R-CD	
	See Chrysler T2-CT2	

REO-PHILCO

T3-RT3, Reo DeLuxe,	Schematic, socket, chassis, parts	6-99
(Part No. 5485)	Installation data, parts	6-101
	Changes	6-101
	Alignment, trimmers	8-6
T11-CT11	See Chrysler T11-CT11	
T14-RT14X	See Packard T14-PT14	
R-1415	Schematic, chassis, parts	8-125
	Socket, trimmers, alignment	8-126

STUDEBAKER-PHILCO

C(122)-SOD	See model 10(122)	
C-SCD	See Nash C-ND	
D-SDD	See Nash model D-ND	
J-SJD (121)	Schematic, chassis, parts	6-103
	Installation data	6-104
	Alignment, trimmers	8-4
J(122)-SJD	See model 11 (122)	
Q-SJD	See Nash Q-ND	
T3-ST3	See Pierce-Arrow T3-MT3	
	Changes, parts numbering system	7-26
	See model 806	
T7-ST7	Schematic, alignment	7-7
T12-ST12, Studebaker	Socket, trimmers, chassis, parts	7-8
	Alignment, part 2	7-13
T15-ST15, Studebaker	Schematic, chassis, parts list	7-13
	Socket, trimmers, alignment	6-79
AC-206, Studebaker	Schematic, parts	6-81
	Installation data	6-81
	Alignment, similar to AC-206, Code 122	

STUDEBAKER-PHILCO

AC-206 (Code 122),	Schematic, chassis, parts	5-6
Studebaker DeLuxe	Alignment, socket	5-5
	Similar to model 10 (122)	5-5
AC-236, Studebaker Junior	Schematic, parts	6-84
	Installation data	6-81
	Similar to J-NJD	
AC-266, Studebaker	Schematic, socket, parts	6-99
	Installation data	6-100
	Similar to T3-ST3	
S-1431, Studebaker	Schematic, chassis, parts list	7-145
	Socket, trimmers, alignment	7-146
S-1437 (Two units)	Schematic, chassis, parts	8-143
	Socket, trimmers, alignment	8-137
S1516	Schematic, parts, chassis	9-35
	Socket, trimmers, controls, alignment, parts	9-36
S1526	Schematic, parts, chassis	9-41
	Socket, trimmers, controls, alignment, parts	9-42
S-1616	Schematic, chassis, parts	10-48
	Socket trimmers, alignment	10-52
S-1622	Schematic, chassis, parts	10-55
	Alignment, socket, trimmers	10-15

WILLIS-OVERLAND

W-1419	Schematic, chassis, parts	8-125
	Socket, trimmers, alignment	8-126

PIERCE-AIRO, INC.

See DE WALD RADIO

PIERSON-DELANE CO.

PR150, PR15M, PR15R,	Schematic, data	9-1
PR15UH, PR15X	Trimmers, socket	9-2
	Alignment, filter data, oscillograms	9-3
	Noise-suppressor notes	9-4

PILGRIM ELECTRIC CORP.

D, DE	Schematic, voltage	10-1
DA, DAE	Schematic	9-1
DE, DF	Schematic	9-1
GE	Schematic, voltage	10-2
GB, GBE, GF, GFE	Schematic, voltage	10-2
GH, GHE	Schematic, voltage	10-1
NT, NTE	Schematic, voltage	8-1
NTH, NTHE	Schematic, voltage	8-2
RJ, RJE	Schematic, voltage	8-2
RJH, RJHE	Schematic	10-3
200	Schematic	8-1
313, 314	Schematic	8-2
623, 624, 643, 644	Schematic	10-3
713, 714, 753, 754	Schematic	10-3
860	Schematic	10-4
930	Wireless Record Player Schematic	10-1

PILOT RADIO & TUBE CORP.

4-Tube DC Superhet	Schematic	4-3
Air Hound (All Electric)	Schematic	1-3
Air Scout (All Electric)	Schematic	1-3
Captain Kidd Chest	See model 55	
Country Special	See model K-121	
Dragon 8 tube	See model L-8	
Dragon AC Super	See model 10	
Dragon AW	See model 1010	
Dragon AW Super	See model 8	
Dragon DC	See model 11, 41 series	
Dual-Wave Midret, (200-2,000 Meters)	Schematic	2-1
Junco ABC	Schematic	1-2
Junco Power Pack	Schematic	1-2
Pilotone (Electric)	Schematic	1-3
Pilotone B Pack	Schematic	1-2
Public-Address System	Schematic	1-1
Rainbow	See model 31-81, 81	



258, 255	Schematic, socket, trimmers, voltage	7-9
G284	Alignment	7-8
	Schematic, parts	9-3
	Alignment, notes	9-4
298, 295	Schematic, socket, trimmers, voltage	7-11
	Alignment	7-12
S-295	Schematic, socket, trimmers, parts	8-15
	Alignment	8-17
304, 805	Schematic, parts	7-13
	Voltage, alignment	7-14
X-304, X-305	Schematic, parts	8-14
	Voltage, alignment	8-17
G352, G353	Schematic, socket, trimmers, parts	9-5
	Voltage, alignment	9-2
364, 365	Schematic, parts	7-15
	Socket, trimmers, voltage, alignment	7-16
H372, H373, Chassis H370	Schematic	10-7
	Voltage, socket, alignment, trimmers	10-8
H384, H385, Chassis H380	Schematic, voltage	10-17
	Socket, alignment, trimmers	10-18
398, 395	Schematic, parts	7-10
	Alignment	7-14
S-393	Schematic, trimmers, alignment, parts	8-18
403, 405	Schematic, socket, trimmers, parts	9-6
	Voltage, alignment	9-8
423, 425	Schematic, parts	9-7
	Alignment	9-8
H454, H455, Chassis H450	Schematic	10-10
	Socket, trimmers, voltage	10-11
	Alignment	10-12
H474, H475, Chassis H470	See model H134	
H484, H485, Chassis H480	See model H384	
G-528, G-529	Schematic, parts, changes	8-19
	Socket, trimmers, phono. data	8-20
H554, H555	Schematic, parts	9-11
	Socket, trimmers, specifications	9-12
	Voltage, alignment	9-13
BG562, BG563	Schematic, socket, trimmers, parts	9-9
	Voltage, alignment	9-10
G-576, G-577	Schematic, socket, trimmers, parts	8-23
	Alignment	8-30
G-584, G-585	Schematic, trimmers, parts	8-21
	Alignment	8-22
H594, H597	Schematic, tuner, parts	9-15
	Voltage, alignment	9-14
	Socket, trimmers, specifications	9-16
623, 625	Schematic, parts	8-24
	Alignment	8-27
S-623, S-623-J	Schematic, parts	8-25
	Alignment	8-27
H650, H651, Chassis H650	Schematic, voltage, socket, alignment, trimmers	10-16
H664, H665	Schematic, parts	9-17
	Alignment	9-13
	Socket, trimmers, voltage, specifications	9-18
H710	Schematic, voltage	10-19
	Socket, trimmers, alignment	10-20
G-752, G-753	Schematic, socket, trimmers, parts	8-26
	Alignment	8-27
H762, H763, Chassis H760	Schematic	10-21
	Voltage, socket, trimmers, alignment	10-22
H874, H875, Chassis H870	Schematic, voltage	10-23
	Alignment procedure	10-24
	Socket, trimmers	10-25
H974, H975, Chassis H970	See model H874	
1010 All-Wave Dragon	Schematic, voltage	3-6
T1252	Schematic, socket, trimmers, alignment	10-25

T1452	Schematic, trimmers, alignment, changes	10-26
M-2203, M-2205	Schematic, socket, trimmers, alignment, voltage, parts	8-28
X-2253, X-2255	Schematic, socket, trimmers, parts	8-29
	Alignment	8-30
H6204, Chassis H6200	Schematic, voltage	10-27
	Alignment, socket, trimmers	10-28
<b>PIONEER RADIO CORP.</b>		
60-A Series	Schematic	Misc. 6-37
<b>PLA-RIGHT</b>		
500	See United Motors model 630 Delco	
<b>PLAZA MUSIC CO.</b>		
6-Tube Long Wave	Schematic	3-2
6-Tube TRF	Schematic	3-3
7-Tube Super	Schematic	3-3
24 Standard	Schematic	3-4
49-A	Schematic	3-1
549	Schematic	3-1
711 Junior	Schematic	3-2
711 Super	Schematic	3-2
<b>PONTIAC</b>		
	See UNITED MOTORS SERVICE	
	See BUICK 980893	
<b>PORT-O-MATIC CORP.</b>		
18A, 18C, 18R, 80A, 80F, 80C, 210C, 210F, 210R, 212C, 212F, 212R,	Schematic, alignment	10-1
Chassis P8		
25A, 25C, 25R, 250C, 250F, 250R, Chassis P8LW	Schematic, alignment	10-2
<b>POWERTONE</b>		
500	See United Motors model 630 Delco	
<b>PRECISION RADIO PRODUCTS MFG. CO.</b>		
6-Tube A-W Superhet	Schematic	6-1
8-Tube A-W Superhet	Schematic	6-2
511	Schematic	6-3
<b>RCA MFG. CO., INC.</b>		
Antenna Length	Chart	5-210
Automatic Record Changer	See RE-73	
Premax	See P-1	
Public Address Notes	Part #1	4-119
	Part #2	4-120
Radiola Balanced Am-	Schematic, socket	1-6
plifier		
Radiola Senior Amplifier	Schematic, socket	1-6
Radiola Grand	Schematic, socket	1-5
Radiola Senior	Schematic, socket	1-5
Radiola Superette	See model R-7	
Radiola RS	Schematic, socket	1-5
Radiola II (AR-800)	Schematic, socket	1-6
Radiola III-A	Schematic, socket	1-7
Radiola III	Schematic, socket	1-7
Radiola IV (AR-885)	Schematic, socket	1-7
Radiola V (AR-897)	Schematic, socket	1-7
Radiola VI	Schematic, socket	1-8
Radiola VII	Schematic, socket	1-8
Radiola VIII-B	Schematic, socket	1-8
Radiola Super VIII	Schematic, socket	1-9
Radiola IX	Schematic, socket	1-8
Sealed Vibrator Test	Data	5-244
Short Wave Adapter	See model SW-10	
Theremin	See models SWA-2 & SW-3	
Tuning Condensers	Realignment data	1-70
Victor Alhambra I (7-1)	Schematic, socket	2-78
Victor Alhambra II (7-2)	Schematic, socket	1-57

# FREQUENCY MODULATION

The latest development in radio—**FREQUENCY MODULATION**—is on the air. More and more stations all over the country are making provision for “static-less” broadcasting and the number of F-M receivers on the market is increasing. . . . Here is your chance to get in at the start—Rider’s newest book explains the transmission and reception of frequency-modulated signals with especial attention given to the different types of f-m receivers now available—their adjustments and maintenance. . . . This is a “must” for every serviceman who has an eye on the future. . . . It is an investment that will pay real dividends!




## CONTENTS

**Chapter I. Frequency Modulation.**—An introduction to the subject with comparisons drawn between the frequency-modulation and amplitude-modulation forms of transmission and reception. **Chapter II. What Happens at the Transmitter.**—A non-mathematical explanation of how frequency-modulated signals are broadcast, including a discussion of phase modulation. **Chapter III. What Happens in the Receiver.**—How the f-m signal progresses through the receiver and how it is affected by the limiter discriminate tubes. **Chapter IV. Wave Propagation and Service Areas.**—How the ultra-high frequency waves are used for f-m transmission and the area covered. **Chapter V. F-M Receiving Antennas.**—Explanations and data concerning the best types of antennas for the reception of f-m signals. **Chapter VI. Servicing F-M Receivers.**—Valuable instructions for the adjusting and maintenance of the receiver including numerous oscillograms that will guide you in your servicing problems.

136 PAGES . . . . TYPE SET . . . . FLEXIBLE CLOTH . . . . PROFUSELY ILLUSTRATED . . . . NET PRICE \$2.00

## THE METER AT WORK

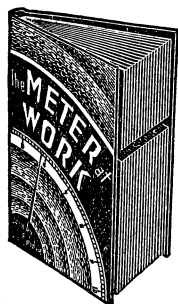

Here is a practical book for all who employ electric meters in radio and the allied electronic arts.

It is only through knowledge of the principles underlying the functioning of any piece of apparatus that a man can get the utmost use from it. To that end, it will be found that the subject matter of this book is treated from an entirely new angle, the theory upon which each meter is based is separate and distinct from any other type and complete in itself. Inasmuch as some types of meters can do several jobs, the practical aspects of the meter are confined to the latter portion of the book. Thus, you can cover whichever phase of the subject you are interested in, and with the new construction of the book—the separation of text and illustrations—you will be able to obtain the information quickly and with the minimum of effort.

## CONTENTS


I—General Considerations. II—Moving-Iron Meters. III—Moving-Coil Meters. IV—Electrodynamometer Meters. V—The Electrostatic Meter. VI—Thermal Meters. VII—Components of Meters. VIII—Characteristics of Meters. IX—Rectifiers and Thermocouples. X—Practical Applications of Meters.

152 Pages . . . 138 Illustrations . . . \$2.00
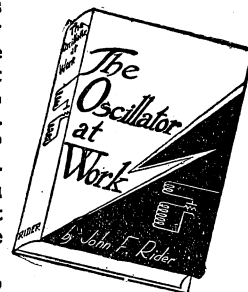
## THE OSCILLATOR AT WORK

Do you get your money’s worth out of your present-day oscillator? Do you derive maximum utility from that unit? Do you know how to test your oscillator and establish if it is working properly? Would you know how to repair it if it went bad? Do you know how many different types of oscillators can be used in the servicing field?

Here is your opportunity to get the true facts about oscillators! Rider’s “The Oscillator at Work” is worth many times the price asked because it helps protect the investment you have made in oscillator equipment.



## CONTENTS

I—How an oscillator works. II—Alternating Currents. III—Triode Oscillators. IV—Electron-Coupled Oscillators. V—Ultra-High Frequency Oscillators. VI—Negative-Resistance Oscillators. VII—Electro-Mechanical Oscillators. VIII—Relaxation Oscillators. IX—Superheterodyne Oscillators. X—R-F Signal Generators. XI—Audio-Frequency Oscillators. XII—Modulation of Oscillators. XIII—Wobblers. XIV—Adjustment of Transmitters. Bibliography.

256 Pages . . . 167 Illustrations . . . \$2.50

## A.C. CALCULATION CHARTS

146 charts 7" x 11" printed in two colors, covering all alternating current calculations from 10 cycles to 1000 megacycles. A tremendous time saver for all engineers and others who work on power, audio, supersonic, high frequency and ultra high frequency problems.

160 PAGES . . . . 9½ x 12 INCHES . . . . CLOTH BINDING . . . . \$7.50

RCA MFG. CO., INC.—(Cont.)			RCA MFG. CO., INC.—(Cont.)			RCA MFG. CO., INC.—(Cont.)					
MODEL	REVISION	REVISION	MODEL	REVISION	REVISION	MODEL	REVISION	REVISION			
EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE	EARLY COMPLETE PAGE			
Victor Borgia (9-40)	Schematic	515	1981	Victor Borgia I (9-3)	Schematic, socket	515	1981	Victor Borgia I (9-3)	Schematic, socket	515	1981
Victor Borgia II (9-2)	Schematic, socket	508	1974	Victor Borgia II (9-2)	Schematic, socket	508	1974	Victor Borgia II (9-2)	Schematic, socket	508	1974
Victor Cromwell (12-1)	Schematic, socket	510	1976	Victor Cromwell (12-1)	Schematic, socket	510	1976	Victor Cromwell (12-1)	Schematic, socket	510	1976
Victor Firenze (9-1)	Schematic, socket	509	1973	Victor Firenze (9-1)	Schematic, socket	509	1973	Victor Firenze (9-1)	Schematic, socket	509	1973
Victor Hyperion (15-1)	Schematic, socket	508	1974	Victor Hyperion (15-1)	Schematic, socket	508	1974	Victor Hyperion (15-1)	Schematic, socket	508	1974
Victor Tuscany (12-2)	Installation data	5211	1976	Victor Tuscany (12-2)	Installation data	5211	1976	Victor Tuscany (12-2)	Installation data	5211	1976
World Wide Antenna	Notes, parts list	5212		World Wide Antenna	Notes, parts list	5212		World Wide Antenna	Notes, parts list	5212	
9-Tube General Purpose	Schematic, voltage	5165		9-Tube General Purpose	Schematic, voltage	5165		9-Tube General Purpose	Schematic, voltage	5165	
A-W, AR-5A	Chassis wiring	5166		A-W, AR-5A	Chassis wiring	5166		A-W, AR-5A	Chassis wiring	5166	
	Coils' wiring diagram	5167			Coils' wiring diagram	5167			Coils' wiring diagram	5167	
	Alignment data	5168			Alignment data	5168			Alignment data	5168	
	Transformer data, trimmer locations	5169			Transformer data, trimmer locations	5169			Transformer data, trimmer locations	5169	
AVR-1	Parts list	5170		AVR-1	Parts list	5170		AVR-1	Parts list	5170	
HF-1	See model 140			HF-1	See model 140			HF-1	See model 140		
	Schematic, fidelity switch data	9-1			Schematic, fidelity switch data	9-1			Schematic, fidelity switch data	9-1	
	Socket, trimmers, voltage, chassis wiring, specifications, notes	9-2			Socket, trimmers, voltage, chassis wiring, specifications, notes	9-2			Socket, trimmers, voltage, chassis wiring, specifications, notes	9-2	
	Alignment, tuner, parts	9-3			Alignment, tuner, parts	9-3			Alignment, tuner, parts	9-3	
	Data	4-1			Data	4-1			Data	4-1	
	Schematic, voltage, data	4-2			Schematic, voltage, data	4-2			Schematic, voltage, data	4-2	
	Tuner adjustments, specifications	9-4			Tuner adjustments, specifications	9-4			Tuner adjustments, specifications	9-4	
	Schematic	9-5			Schematic	9-5			Schematic	9-5	
	Chassis wiring, voltage, transformer data, lead dress	9-6			Chassis wiring, voltage, transformer data, lead dress	9-6			Chassis wiring, voltage, transformer data, lead dress	9-6	
	Socket, trimmers, tuner, dial drive data, notes	9-7			Socket, trimmers, tuner, dial drive data, notes	9-7			Socket, trimmers, tuner, dial drive data, notes	9-7	
	Alignment, tuner	9-8			Alignment, tuner	9-8			Alignment, tuner	9-8	
	Antenna notes	9-9			Antenna notes	9-9			Antenna notes	9-9	
	Automatic record changer notes	9-10			Automatic record changer notes	9-10			Automatic record changer notes	9-10	
	Parts list	2-96			Parts list	2-96			Parts list	2-96	
SWA-2, SW Converter	Chassis wiring, parts list, data	2-97		SWA-2, SW Converter	Chassis wiring, parts list, data	2-97		SWA-2, SW Converter	Chassis wiring, parts list, data	2-97	
2-19 Portable Victrola	Schematic, data	2-98		2-19 Portable Victrola	Schematic, data	2-98		2-19 Portable Victrola	Schematic, data	2-98	
	Notes	5-213			Notes	5-213			Notes	5-213	
2-25 Portable Victrola	Parts list	5-214		2-25 Portable Victrola	Parts list	5-214		2-25 Portable Victrola	Parts list	5-214	
	Parts list, assembly	2-98			Parts list, assembly	2-98			Parts list, assembly	2-98	
2-65 Turntable	Notes	2-99		2-65 Turntable	Notes	2-99		2-65 Turntable	Notes	2-99	
KC-3 Television chassis	See model TRK-5	2-100		KC-3 Television chassis	See model TRK-5	2-100		KC-3 Television chassis	See model TRK-5	2-100	
SW-3 AC	Schematic	4-5		SW-3 AC	Schematic	4-5		SW-3 AC	Schematic	4-5	
	Chassis wiring	4-9			Chassis wiring	4-9			Chassis wiring	4-9	
SW-3 Batt.	Schematic	4-9		SW-3 Batt.	Schematic	4-9		SW-3 Batt.	Schematic	4-9	
	Chassis wiring	4-9			Chassis wiring	4-9			Chassis wiring	4-9	
SW-3 Converter	Notes on oscillator	4-9		SW-3 Converter	Notes on oscillator	4-9		SW-3 Converter	Notes on oscillator	4-9	
	Detector adjustment	4-7			Detector adjustment	4-7			Detector adjustment	4-7	
	General notes	4-8			General notes	4-8			General notes	4-8	
	Data	4-3			Data	4-3			Data	4-3	
	Parts list	4-14			Parts list	4-14			Parts list	4-14	
SW-3 W/R-24	Assembly wiring	4-4		SW-3 W/R-24	Assembly wiring	4-4		SW-3 W/R-24	Assembly wiring	4-4	
SW-3 W/R-24A	Assembly wiring	4-10		SW-3 W/R-24A	Assembly wiring	4-10		SW-3 W/R-24A	Assembly wiring	4-10	
SW-3 W/R-24B	Assembly wiring	4-11		SW-3 W/R-24B	Assembly wiring	4-11		SW-3 W/R-24B	Assembly wiring	4-11	
SW-3 W/R-78 SW	Assembly wiring	4-12		SW-3 W/R-78 SW	Assembly wiring	4-12		SW-3 W/R-78 SW	Assembly wiring	4-12	
SW-3 W/RE-81	Assembly wiring	4-13		SW-3 W/RE-81	Assembly wiring	4-13		SW-3 W/RE-81	Assembly wiring	4-13	
SW-3 W/RAE-84	Assembly wiring	4-13		SW-3 W/RAE-84	Assembly wiring	4-13		SW-3 W/RAE-84	Assembly wiring	4-13	
HF-4	See model TRK-2			HF-4	See model TRK-2			HF-4	See model TRK-2		
KC-4 Television chassis	See model TRK-12			KC-4 Television chassis	See model TRK-12			KC-4 Television chassis	See model TRK-12		
RC-4A Television chassis	See model TRK-9			RC-4A Television chassis	See model TRK-9			RC-4A Television chassis	See model TRK-9		
R-4, R-6	Chassis wiring, voltage, data	2-1		R-4, R-6	Chassis wiring, voltage, data	2-1		R-4, R-6	Chassis wiring, voltage, data	2-1	
	Schematic, parts list	2-2			Schematic, parts list	2-2			Schematic, parts list	2-2	
	Test data	2-3			Test data	2-3			Test data	2-3	
	Schematic, socket, chassis wiring, trimmers, loud speaker, transformer	7-1			Schematic, socket, chassis wiring, trimmers, loud speaker, transformer	7-1			Schematic, socket, chassis wiring, trimmers, loud speaker, transformer	7-1	
	Voltage, resistance, transformer	7-2			Voltage, resistance, transformer	7-2			Voltage, resistance, transformer	7-2	
	Circuit data, alignment, parts list	7-3			Circuit data, alignment, parts list	7-3			Circuit data, alignment, parts list	7-3	
	Schematic, socket, interference note	6-78			Schematic, socket, interference note	6-78			Schematic, socket, interference note	6-78	
	Alignment, trimmers, voltage	6-74			Alignment, trimmers, voltage	6-74			Alignment, trimmers, voltage	6-74	
	Alignment part 2, parts list	6-75			Alignment part 2, parts list	6-75			Alignment part 2, parts list	6-75	
4T				4T				4T			
	Chassis wiring, voltage, data	10-1			Chassis wiring, voltage, data	10-1			Chassis wiring, voltage, data	10-1	
	Operating notes, Kinescope installation	10-3, 4			Operating notes, Kinescope installation	10-3, 4			Operating notes, Kinescope installation	10-3, 4	
	Antenna, transmission line	10-5			Antenna, transmission line	10-5			Antenna, transmission line	10-5	
	Socket, voltage data, antenna data, rear view of model	10-6			Socket, voltage data, antenna data, rear view of model	10-6			Socket, voltage data, antenna data, rear view of model	10-6	
	TRK-5	10-7			TRK-5	10-7			TRK-5	10-7	
	Test patterns	10-21			Test patterns	10-21			Test patterns	10-21	
	Video band switch wiring	10-23			Video band switch wiring	10-23			Video band switch wiring	10-23	
	Parts list	10-12			Parts list	10-12			Parts list	10-12	
	Specifications, dial data	10-8			Specifications, dial data	10-8			Specifications, dial data	10-8	
	Schematic, lead dress	10-9			Schematic, lead dress	10-9			Schematic, lead dress	10-9	
	Socket, trimmers, tuner, alignment	10-10			Socket, trimmers, tuner, alignment	10-10			Socket, trimmers, tuner, alignment	10-10	
	R-F chassis wiring, voltage	10-11			R-F chassis wiring, voltage	10-11			R-F chassis wiring, voltage	10-11	
	Schematic	10-11			Schematic	10-11			Schematic	10-11	
	Schematic, socket, trimmers, chassis wiring	8-5			Schematic, socket, trimmers, chassis wiring	8-5			Schematic, socket, trimmers, chassis wiring	8-5	
	Voltage, alignment	8-6			Voltage, alignment	8-6			Voltage, alignment	8-6	
	Victrola, attachment data	10-101			Victrola, attachment data	10-101			Victrola, attachment data	10-101	
	Schematic, socket, speaker, data	6-79			Schematic, socket, speaker, data	6-79			Schematic, socket, speaker, data	6-79	
	Chassis wiring	6-80			Chassis wiring	6-80			Chassis wiring	6-80	
	Alignment, trimmers, voltage	6-81			Alignment, trimmers, voltage	6-81			Alignment, trimmers, voltage	6-81	
	Alignment part 2, parts list	6-82			Alignment part 2, parts list	6-82			Alignment part 2, parts list	6-82	
504-J-18		1952		504-J-18		1952		504-J-18		1952	
504-J-17		1951		504-J-17		1951		504-J-17		1951	
504-W		1960		504-W		1960		504-W		1960	
504-W		1959		504-W		1959		504-W		1959	
504-W		1961		504-W		1961		504-W		1961	
TRK-5 Television, Chassis Nos. KC-3A, RC-429, RS-89A				TRK-5 Television, Chassis Nos. KC-3A, RC-429, RS-89A				TRK-5 Television, Chassis Nos. KC-3A, RC-429, RS-89A			
TT-5 Television, Chassis KC-3				TT-5 Television, Chassis KC-3				TT-5 Television, Chassis KC-3			
Receiver Chassis RC-429				Receiver Chassis RC-429				Receiver Chassis RC-429			
S.P.U. Chassis RS-39A				S.P.U. Chassis RS-39A				S.P.U. Chassis RS-39A			
504-11		1759		504-11		1759		504-11		1759	
504-10		1758		504-10		1758		504-10		1758	
504-9		1760		504-9		1760		504-9		1760	
504-8				504-8				504-8			
504-7				504-7				504-7			
504-6				504-6				504-6			
504-5				504-5				504-5			
504-4				504-4				504-4			
504-3				504-3				504-3			
504-2				504-2				504-2			
504-1				504-1				504-1			
504-0				504-0				504-0			
504-A				504-A				504-A			
504-B				504-B				504-B			
504-C				504-C				504-C			
504-D				504-D				504-D			
504-E				504-E				504-E			
504-F				504-F				504-F			
504-G				504-G				504-G			
504-H				504-H				504-H			
504-I				504-I				504-I			
504-J				504-J				504-J			
504-K				504-K				504-K			
504-L				504-L				504-L			
504-M				504-M				504-M			
504-N				504-N				504-N			
504-O				504-O				504-O			
504-P				504-P				504-P			
504-Q				504-Q				504-Q			
504-R				504-R				504-R			
504-S				504-S				504-S			
504-T				504-T				504-T			
504-U				504-U				504-U			
504-V				504-V				504-V			
504-W				504-W				504-W			
504-X				504-X				504-X			
504-Y				504-Y				504-Y			
504-Z				504-Z				504-Z			
504-AA				504-AA				504-AA			
504-AB				504-AB				504-AB			
504-AC				504-AC				504-AC			
504-AD				504-AD				504-AD			
504-AE				504-AE				504-AE			
504-AF				504-AF				504-AF			
504-AG				504-AG				504-AG			
504-AH				504-AH				504-AH			
504-AI				504-AI				504-AI			
504-AJ				504-AJ				504-AJ			
504-AK				504-AK				504-AK			
504-AL				504-AL				504-AL			
504-AM				504-AM							



MODEL	RCA MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
7T, 7K, 8T, 8K	Schematic, socket, trimmers, phono, wiring	7-56		
	Chassis wiring	7-57		
	Voltage, socket, trimmers, resistance, loudspeaker	7-58		
	Circuit data, alignment, part 1	7-59		
	Alignment, part 2, parts list	7-60		
	Victrola attachment data	10-101		
7T1	See model 6K3			
7U	Victrola attachment data	10-101		
	Schematic, chassis wiring	7-61		
	Resistance, voltage, socket, trimmers, speaker, transformer	7-62		
	Motor board adjustments	7-63		
	Assembly wiring, pickup details	7-64		
	Circuit data, alignment, pickup data, part 1	7-65		
	Pickup data, part 2, socket, parts list	7-66		
7U2	Schematic, socket, trimmers	8-29		
	Phono, data, notes	8-28		
	Chassis wiring	8-30		
	Parts	8-31		
7X	Schematic, voltage, socket, trimmers, alignment, resistance	8-33		
	Alignment, parts	8-32		
	Chassis wiring	8-34		
	Victrola attachment data	10-101		
	Changes	9-6		
7X1	Victrola attachment data	10-101		
Victor 7-1	See Victor Alhambra I			
Victor 7-2	Schematic, socket, trimmers	1-62		
Victor 7-3, 7-30, R-20	Schematic, socket, trimmers	7-67		
T7-5	Chassis wiring	7-68		
	Voltage, socket, trimmers, transformer, loudspeaker	7-69		
	Circuit data, parts, alignment, data	7-70		
	Speaker data	7-70		
	Victrola attachment data	10-101		
67-5	Schematic, socket, trimmers	7-67		
	Chassis wiring	7-68		
	Voltage, socket, trimmers, transformer, loudspeaker	7-69		
	Circuit data, parts, alignment, data	7-70		
	Victrola attachment data	10-101		
	Schematic, socket, trimmers	7-71		
	Chassis wiring, pickup	7-72		
	Assembly wiring, voltage, speaker, transformer, circuit, alignment, part 1	7-73		
	Alignment, part 2, parts list	7-74		
	Additional data	Changes 7-6		
	Schematic, socket, trimmer, data	6-95		
	Chassis wiring	6-96		
	Parts, circuit data, alignment	6-97		
	Alignment part 2, voltage, trimmers	6-98		
BT7-8, B07-9	See model TRK-12			
	Schematic, chassis wiring	7-75		
	Data, parts list	7-76		
	Victrola attachment data	10-101		
	Schematic, socket	1-59		
	Schematic, socket, voltage	1-59		
	Schematic, socket	1-59		
	Schematic, socket	1-59		
	See Victor 7-3			
	Schematic, socket, trimmers, phono, data, speaker wiring	8-35		
	Resistance, voltage	8-37		
	Alignment	8-38		
	Notes, parts	8-39		
	Battery cable, chassis wiring	8-36		
	Power unit and chassis wiring	8-36		
8BT, 8BK				
8BT6, 8BK6				
BT7-8, B07-9				
KK-7, S.P.U. Chassis				
KK-7A, S.P.U. Chassis				
TT-12, C7-14				
Victor 710				
Victor 711				
Victor 725				
Victor 726				
Victor 730				
8BT, 8BK, 8BT6, 8BK6				
8BT, 8BK				
8BT6, 8BK6				
OS-15	Schematic, socket, trimmers, speaker	7-77		
	Chassis wiring	7-78		
	Voltage, transformer, visual alignment, data	7-79		
	Circuit data, alignment	7-80		
	Parts list	7-81		
	Victrola attachment data	10-101		
OS-17	Schematic, socket, trimmers	7-83		
	Chassis wiring	7-84		
	Voltage, trimmers, transformer, visual alignment	7-85		
	Alignment, parts	7-86		
	Schematic, chassis wiring, parts	8-52		
	Schematic, socket, trimmers	7-89		
D8-28	Chassis wiring pickup	7-90		
	Voltage, assembly, wiring, phono, adjustments, data	7-91		
	Alignment, parts, loudspeaker, transformer	7-92		
HF-8, U				





MODEL	RCA MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
TEK-9: TRK-12 Television S.P.U. Chassis RS33E	Schematic .....	10-23		
9TX1, 9TX2, 9TX3, 9TX4, 9TX5, "Little Nipper 2nd"	Schematic, voltage, socket, alignment, trimmers .....	10-40		
9TX21, 9TX22, Chassis RC403, 9TX23, Chassis RC403A	Parts .....	10-38		
	Schematic, voltage, socket, trimmers, data, alignment .....	10-41		
9TX31, Chassis RC405, 9TX32, Chassis RC405A, 9TX33, Chassis RC405B	Parts .....	10-42		
	Schematic, voltage, socket, trimmers, alignment, data .....	10-43		
9TX50, Chassis RC435	Parts .....	10-42		
	Schematic, voltage, socket, trimmers, alignment, data, parts 10-44			
9U, 9U2	Schematic .....	8-67		
	"Magic Brain" wiring .....	8-69		
	Assembly wiring, dial data .....	8-71		
	Socket, trimmers, voltage, resistance .....	8-72		
	Automatic record changer, details, notes .....	8-73		
	Alignment, page 1 .....	8-74		
	Alignment, page 2, notes, page 1 .....	8-75		
	Notes, page 2, parts, page 1 .....	8-76		
	Parts, page 2 .....	8-77		
	Parts, page 3, circuit data .....	8-78		
	Chassis wiring .....	8-83		
	Chassis wiring .....	8-80		
9U2	See Victor Florenza			
Victor 9-1	See Victor Borgia, I			
Victor 9-2	See Victor Borgia, II			
Victor 9-3	Schematic, socket .....	1-63		
Victor 9-15	Schematic, socket .....	1-64		
Victor 9-25	Schematic, socket .....	1-65		
Victor 9-40 Borgia	Schematic .....	1-65		
Victor 9-54	Schematic, socket, voltage .....	1-66		
Victor 9-55	Schematic, socket .....	1-67		
9X, 9X1, 9X2, 9X3, 9X4	Schematic, socket, voltage, specifications, lead dress, notes, chassis wiring .....	9-30		
10K, 10T	Schematic .....	7-130		
	Chassis wiring .....	7-131		
	"Magic Brain" chassis wiring .....	7-132		
	Socket, trimmers dial mechanism, loudspeaker data .....	7-133		
	Resistance, voltage, transformer .....	7-134		
	Circuit data, alignment, part 1 .....	7-135		
	Alignment, part 2, parts list .....	7-136		
	Victrola attachment data .....	10-101		
10K1, 10T (2nd Production)	Schematic .....	8-79		
	Chassis wiring .....	8-80		
	Socket, voltage, trimmers, notes .....	8-81		
	Parts .....	8-82		
	Victrola attachment data .....	10-101		
	Data .....	Changes 8-4		
10K11, 10T11	Schematic, chassis wiring, voltage, data .....	2-16		
R-10 AO	Resistance data, socket, voltage .....	2-17		
	Resistance data, socket, voltage .....	2-17		
	Data .....	Changes 10-2		
PLF-10 Filter Coupling Unit	See model 5X51			
R-10 DC	Data .....	Changes 7-15		
SW Adaptor SW-10	Schematic, chassis wiring .....	1-53		
10T Early	Voltage, chassis views, data .....	1-54		
T10-1	See model 10K			
	Trimmers, socket, voltage, speaker data, transformer data .....	6-104		
	Schematic .....	6-105		
	Chassis wiring .....	6-106		
	Alignment, parts list .....	6-107		
	Alignment, part 2 .....	6-108		
MODEL	RCA MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
T10-1	Speaker data .....	7-82		
	Victrola attachment data .....	10-101		
	Schematic .....	6-109		
T10-3	Chassis wiring .....	6-110		
	Socket, trimmers, speaker data, voltage .....	6-111		
	Circuit data, alignment .....	6-112		
	Alignment, part 2 .....	6-113		
	Parts list .....	6-114		
Victor 10-51-A	Speaker data .....	7-82		
Victor 10-69	Schematic, socket .....	1-57		
	Schematic, socket, chassis wiring .....	1-58		
	Schematic, socket .....	1-59		
	Schematic, socket .....	1-59		
	Schematic .....	6-115		
	Trimmers, voltage, speaker data, alignment .....	6-116		
	Circuit data, alignment, socket .....	6-117		
	Alignment, part 2 .....	6-118		
	Alignment, part 3; parts list .....	6-119		
	Victrola attachment data .....	10-101		
O11-3	Similar to C11-1			
	Data .....	7-156		
D11-2	Victrola attachment data .....	10-101		
	Schematic .....	7-137		
	Chassis wiring .....	7-138		
	Voltage, socket, trimmers, pickup, transformer, speaker, dial mechanism .....	7-139		
	Assembly wiring, record changer .....	7-140		
	Circuit data, notes .....	7-141		
	Alignment .....	7-142		
	Parts list .....	7-143		
	Changes .....	Changes 8-4		
R-11 AC, Early	Schematic, socket, voltage .....	2-18		
	Chassis wiring, data .....	2-19		
	Chassis wiring .....	2-20		
	Parts list, notes .....	2-21		
R-11 AC, Late	Resistance data, socket, voltage .....	2-22		
R-11 AC	Schematic, phono, pickup .....	7-144		
	Chassis wiring .....	7-145		
	Socket, trimmers, voltage, speaker, transformer .....	7-146		
	Circuit data, alignment, part 1 .....	7-147		
	Alignment, part 2, parts list .....	7-148		
	Changes .....	Changes 8-4		
	See model R-8			
R-12 AO	See Victor Tuscany			
Victor 12-1	Schematic, socket .....	1-61		
Victor 12-2	Schematic, socket .....	1-61		
Victor 12-15	Schematic, socket .....	1-69		
Victor 12-15-O	Schematic .....	6-121		
C18-2	Chassis wiring .....	6-122		
	Trimmers, voltage, circuit data .....	6-123		
	Circuit data, part 2; alignment, socket .....	6-124		
	Alignment, part 2 .....	6-125		
	Alignment, part 3; dial data, transformer data .....	6-126		
	Parts list .....	6-127		
	Victrola attachment data .....	10-101		
O18-3	Similar to C13-2			
	Data .....	7-156		
	Victrola attachment data .....	10-101		
	Schematic, speaker wiring, transformer wiring .....	8-83		
13X	Chassis wiring .....	8-84		
	"Magic Brain" chassis wiring .....	8-85		
	Resistance, voltage, socket, trimmers .....	8-86		
	Dial change mechanism, notes, socket, trimmers .....	8-87		
	504-G	1783		
	504-H	1783		
	504-I	1784		
	504-J	1785		
	Front	1786		
	*517	1988		
	*518	1984		
	*519	1985		
	*519	1986		
	*520	1977		
	*520	1977		
	*519	1985		
	504-F-1	1780		
	Front	1781		
	*504-E	1949		
	*504-F	1950		

RCA MFG. CO., INC.—(Cont.)			RCA MFG. CO., INC.—(Cont.)			
MODEL	REVISI PAGE	EARLY COMPLET PAGE	MODEL	REVISI PAGE	EARLY COMPLET PAGE	
13K	Alignment, page 1, oscillograms.....8-88 Alignment, page 2.....8-89 Alignment, page 3, notes, parts.....8-90 Victrola attachment data.....10-101 See Radiola 42 Schematic.....6-129 Parts list.....6-128 Chassis wiring.....6-130 Trimmers, voltage, speaker data, transformer data.....6-131 Circuit data, alignment.....6-132 Alignment part 2; cathode-ray, oscillograph alignment.....6-133 Alignment, part 3; phono-graph, dial, transformer notes.....6-134 Victrola attachment data.....10-101 Similar to O15-3 Victrola attachment data.....10-101 Data.....7-156 Schematic, pickup.....7-149 Chassis wiring.....7-150 "Magic Brain" chassis wiring.....7-151 Resistance, voltage.....7-152 Socket, trimmers, transformer, speaker, visual alignment, dial mechanism.....7-153 Circuit data, alignment, part 1.....7-154 Alignment, part 2, parts list.....7-155 Victrola attachment data.....10-101 Schematic, parts list.....4-131		RE-18-A RE-18-W RE-19 AC (AVO) R-20 Radiola 20 RE-20 Electrola RE-20 Electrola SPU PK 21 A1 Speaker Field Supply Radiola 21, 22 R-21 R-22 D22-1	Parts list, specifications.....2-26 Parts list, concluded.....2-27 Notes.....4-23 Schematic, chassis, voltage, parts list.....4-24 Schematic, socket, chassis wiring, data.....2-28 Assembly wiring, parts list.....2-29 See Victor 7-3 Schematic, socket data.....1-17 Chassis wiring, parts list.....2-30 Schematic, socket, data.....2-31 Assembly wiring, parts list.....2-32 Chassis wiring, parts list.....2-33 Panel wiring, schematic.....4-133 Schematic, socket, voltage.....1-18 Schematic, changes, parts list.....2-34 Chassis wiring, parts list.....2-35 Resistance data, socket, voltage.....2-36 Schematic, voltage, parts list.....4-25 Chassis wiring, alignment.....4-26 Schematic.....6-135, 6-136 Chassis wiring.....6-137 Power amplifier, chassis wiring.....6-138 Voltage, socket.....6-139 Dynamic amplifier wiring, pickup details, transformer, dial mechanism details.....6-140 General description, circuit data.....6-141 Circuit data, part 2; alignment, socket.....6-142 Alignment, part 2; cathode-ray oscillograph alignment images.....6-143 Alignment, part 3; output meter alignment, speaker wiring.....6-144 Alignment, part 4; automatic record changer, notes.....6-145 Phonograph data, assembly wiring, cable connectors.....6-146 Phonograph data, part 2; change-over switch wiring, parts list.....6-147 Parts list, part 2.....6-148 Parts list, part 3.....6-149 Changes.....Changes 9-6 Revised voltage.....10-46 Schematic changes, parts.....10-45 Voltage.....10-46 Schematic, voltage, parts list.....4-121 Chassis wiring.....4-122 Schematic.....5-225 Schematic wiring.....5-226 Schematic, parts.....4-125 Chassis wiring.....4-126 Schematic, socket.....2-37 Chassis wiring, data.....2-38 Converter chassis wiring, data.....2-39 Alignment notes.....2-40 Assembly wiring, voltage notes.....2-41 Parts list.....2-42 Schematic, voltage, parts list.....4-127 Chassis wiring.....4-128 See model SW-3 Schematic, socket.....1-19 Schematic, parts, chassis wiring assembly.....6-150 Schematic, chassis wiring, voltage.....5-56 Schematic, chassis wiring.....2-107 Schematic, socket, wiring.....1-20 Schematic, voltage.....1-21		1796 1797 1798 1800 1799 1802 1801 1803 1804 1805 1806
PK 15 B1 Speaker Field Supply	Assembly wiring.....4-132 Schematic.....3-59 Schematic, socket, voltage, data.....1-14 Schematic, socket, trimmers.....8-91, 8-92 Chassis wiring.....8-93 "Magic Brain" chassis wiring, pickup.....8-94 Power amplifier wiring, pickup, speaker wiring.....8-95 Specifications, notes.....8-96 Resistance.....8-97 Voltage, socket, trimmers.....8-98 Automatic record changer, details, notes.....8-99 Alignment, page 1.....8-100 Alignment, page 2.....8-101 Alignment, page 3, notes, oscillograms.....8-102 Parts, page 1.....8-103 Parts, page 2, dial change mechanism.....8-104 Schematic, assembly wiring.....5-219 Pickup data.....5-220 Parts list.....5-221 Pickup data.....5-221 Schematic, socket, data.....1-15 Data.....Changes 4-19 Schematic, notes.....4-20 Assembly wiring.....5-220 Schematic, parts list.....5-222 Pickup data.....5-223 Schematic.....5-224 Pickup data, parts list.....5-224 Schematic, socket, voltage, data.....1-15 Notes.....4-21 Combination R-15 and RE-57 parts list.....4-22 Schematic, chassis, voltage, parts list.....1-16 Schematic, socket.....1-16 Schematic, socket, voltage.....2-23 Assembly wiring.....2-24 Resistance data, socket, voltage.....2-25		PT-16-A1, PT-16-A2 Radiola 16 RE-16 RE-16-A PT-17-A1, PT-17-A2 Radiola 17 RE-17 R-17-M Radiola 18 AC Radiola 18 DO RE-18	1962 1787 *521 1789 *477 *477 1789 *478 *478 504-F-3 504-F-4 Front 1798		2001 1814 1815

RCA MFG. CO., INC.—(Cont.)			RADIOTRON			RCA MFG. CO., INC.—(Cont.)			RADIOTRON		
MODEL	REVISION	PAGE	EARLY COMPLETE	PAGE	REVISION	MODEL	REVISION	PAGE	EARLY COMPLETE	PAGE	REVISION
Radiola 26	1-19	1813	*481	1813	1-19	P-31 Portable	Schematic, chassis, socket, voltage	2-59	504-Y-13	1848	1848
RAE-26	2-44	1816	504-K	1816	2-44	M-32 Auto Set	Chassis wiring, data	2-60	504-Y-13	1844	1844
	2-43	1817	504-L	1817	2-43		Notes, part 1	2-61			
	2-45	1818	Front	1818	2-45		Notes, part 2	2-62			
R-27 AC-DO	3-2	1819		1819	3-2		Notes, part 3	2-63			
	3-3	1820		1820	3-3		Notes, part 4	2-64			
R-27, Revised	5-1	1821		1821	5-1		Service data, voltage	2-65			
	5-2				5-2		Chassis wiring	2-67			
R-28	3-4	1822		1822	3-4	M-32 Battery Operated	Schematic, control box wiring	2-68			
	3-5	1823		1823	3-5	Photophone PG-82	Parts list	2-69			
	1-23	1825	*485	1825	1-23		Terminal data	2-101			
	1-22	1824	*484	1824	1-22		Schematic	2-102			
	5-3				5-3		Change-over panel wiring	2-103			
R-28-BW	5-4				5-4		Voltage, exciter-lamp chassis wiring	2-104			
R-28-BWC	5-5				5-5		Panel wiring	2-103			
R-28-P	5-6				5-6		Amplifier	2-104			
OE-29	4-30				4-30		Photophone PG-32, Voltage	1-27			
	3-56				3-56			Schematic, socket, data	1-27		
	3-57				3-57			Schematic, socket	3-6		
	3-58				3-58			General service notes, voltage	3-7		
	3-68				3-68			Schematic, socket, voltage, data	1-26		
	3-69				3-69			Alignment data	3-8		
	2-47				2-47			Schematic, socket, voltage	1-28		
	2-48				2-48			Assembly wiring, notes	3-9		
	2-49				2-49			Notes, part 1	3-10		
	2-50				2-50			Notes, part 2	3-11		
	2-51				2-51			Notes, part 3, voltage	3-12		
	2-52				2-52			Vibrator notes	3-13		
	2-53				2-53			Schematic, wiring	3-14		
	2-54				2-54			Cable wiring	1-61		
	2-55				2-55			A-F. Chassis wiring, socket, voltage data	1-29		
	3-70				3-70			Schematic, data	1-30		
	2-56				2-56			Voltage, adjustment data	3-15		
	2-57				2-57			Alignment, voltage	4-31		
	2-58				2-58			Schematic, chassis	4-32		
	1-24				1-24			Schematic	2-105		
	3-72				3-72			See model R-35	2-106		
	3-73				3-73			Schematic, voltage, socket, trimmers, alignment, parts	10-54		
	3-74				3-74			Schematic, chassis wiring	3-17		
	3-75				3-75			Voltage, service data	8-18		
	1-25				1-25			Schematic, chassis	4-33		
	1-26				1-26			Alignment, voltage, pickup data	4-34		
	3-7				3-7			Parts list	4-36		
	10-47				10-47			Chassis wiring, voltage	1-31		
	10-28				10-28			Schematic, socket, data	1-32		
	10-48				10-48			Receptor SPU wiring	1-32		
	10-49				10-49			Sterling SPU wiring	1-32		
	10-50				10-50			Schematic, notes	3-19		
	10-51				10-51			Schematic, socket, voltage, chassis wiring	1-33		
	10-52				10-52			Service notes	3-19		
	10-53				10-53			Terminal voltage	1-35		
	3-71				3-71			Schematic, socket, voltage	1-35		
	3-76				3-76			Schematic	1-36		
	3-77				3-77			Schematic	1-36		
	3-78				3-78			Parts list, data	1-36		
	3-79				3-79			Chassis wiring	4-129		
	3-80				3-80			See Victor R-32	4-130		
	3-81				3-81			Schematic	1-35		
	3-82				3-82			Schematic, socket, voltage	1-36		
	3-83				3-83			Terminal voltage	1-35		
	3-84				3-84			Schematic	1-36		
	3-85				3-85			Schematic, socket, voltage	1-36		
	3-86				3-86			Parts list	1-36		
	3-87				3-87			Resistance data, voltage, chassis	1-38		
	3-88				3-88			Schematic	2-70		
	3-89				3-89			Schematic, voltage, data	10-55		
	3-90				3-90			See Photophone PG-31			
	3-91				3-91			Schematic, socket	492		
	3-92				3-92			Terminal voltage	493		
	3-93				3-93			Schematic	493		
	3-94				3-94			Schematic, socket, voltage	494		
	3-95				3-95			Resistance data, voltage, chassis	495		
	3-96				3-96			Schematic	496		
	3-97				3-97			See Photophone PG-31			
	3-98				3-98			Schematic, socket	497		
	3-99				3-99			Resistance data, voltage, chassis	498		
	3-100				3-100			Schematic	499		
	3-101				3-101			See Photophone PG-31			
	3-102				3-102			Schematic, socket	500		
	3-103				3-103			Resistance data, voltage, chassis	501		
	3-104				3-104			Schematic	502		
	3-105				3-105			See Photophone PG-31			
	3-106				3-106			Schematic, socket	503		
	3-107				3-107			Resistance data, voltage, chassis	504		
	3-108				3-108			Schematic	505		
	3-109				3-109			See Photophone PG-31			
	3-110				3-110			Schematic, socket	506		
	3-111				3-111			Resistance data, voltage, chassis	507		
	3-112				3-112			Schematic	508		
	3-113				3-113			See Photophone PG-31			
	3-114				3-114			Schematic, socket	509		
	3-115				3-115			Resistance data, voltage, chassis	510		
	3-116				3-116			Schematic	511		
	3-117				3-117			See Photophone PG-31			
	3-118				3-118			Schematic, socket	512		
	3-119				3-119			Resistance data, voltage, chassis	513		
	3-120				3-120			Schematic	514		
	3-121				3-121			See Photophone PG-31			
	3-122				3-122			Schematic, socket	515		
	3-123				3-123			Resistance data, voltage, chassis	516		
	3-124				3-124			Schematic	517		
	3-125				3-125			See Photophone PG-31			
	3-126				3-126			Schematic, socket	518		
	3-127				3-127			Resistance data, voltage, chassis	519		
	3-128				3-128			Schematic	520		
	3-129				3-129			See Photophone PG-31			
	3-130				3-130			Schematic, socket	521		
	3-131				3-131			Resistance data, voltage, chassis	522		
	3-132				3-132			Schematic	523		
	3-133				3-133			See Photophone PG-31			
	3-134				3-134			Schematic, socket	524		
	3-135				3-135			Resistance data, voltage, chassis	525		
	3-136				3-136			Schematic	526		
	3-137				3-137			See Photophone PG-31			
	3-138				3-138			Schematic, socket	527		
	3-139				3-139			Resistance data, voltage, chassis	528		
	3-140				3-140			Schematic	529		
	3-141				3-141			See Photophone PG-31			
	3-142				3-142			Schematic, socket	530		
	3-143				3-143			Resistance data, voltage, chassis	531		
	3-144				3-144			Schematic	532		
	3-145				3-145			See Photophone PG-31			
	3-146				3-146			Schematic, socket	533		
	3-147				3-147			Resistance data, voltage, chassis	534		
	3-148				3-148			Schematic	535		
	3-149				3-149			See Photophone PG-31			
	3-150				3-150			Schematic, socket	536		
	3-151				3-151			Resistance data, voltage, chassis	537		
	3-152				3-152			Schematic	538		
	3-153				3-153			See Photophone PG-31			
	3-154				3-154			Schematic, socket	539		
	3-155				3-155			Resistance data, voltage, chassis	540		
	3-156				3-156			Schematic	541		
	3-157				3-157			See Photophone PG-31			
	3-158				3-158			Schematic, socket	542		
	3-159				3-159			Resistance data, voltage, chassis	543		
	3-160				3-160			Schematic	544		
	3-161				3-161			See Photophone PG-31			
	3-162				3-162			Schematic, socket	545		
	3-163				3-163			Resistance data, voltage, chassis	546		
	3-164				3-164			Schematic	547		
	3-165				3-165			See Photophone PG-31			
	3-166				3-166			Schematic, socket	548		
	3-167				3-167			Resistance data, voltage, chassis	549		
	3-168				3-168			Schematic	550		
	3-169				3-169			See Photophone PG-31			
	3-170				3-170			Schematic, socket	551		
	3-171				3-171			Resistance data, voltage, chassis	552		
	3-172				3-172			Schematic	553		
	3-173				3-173			See Photophone PG-31			
	3-174				3-174			Schematic, socket	554		
	3-175				3-175			Resistance data, voltage, chassis	555		
	3-176				3-176			Schematic	556		
	3-177				3-177			See Photophone PG-31			
	3-178				3-178			Schematic, socket	557		
	3-179				3-179			Resistance data, voltage, chassis	558		
	3-180				3-180			Schematic	559		
	3-181				3-181			See Photophone PG-31			
	3-182				3-182			Schematic, socket	560		
	3-183				3-183		</				

MODEL	RCM MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIO TRON COMPLETE PAGE	MODEL	RCM MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIO TRON COMPLETE PAGE
PG-65	Chassis wiring, socket, trimmers	10-56			PG-65	Panel wiring	5-243		
	Alignment	10-57				Units specifications	5-241		
	Tuner and antenna data	10-58				Back assembly wiring	5-242		
	Drive data, parts	10-59				Schematic, socket, voltage, data	1-42		
	Schematic, chassis wiring	2-71				Schematic, socket, trimmers, speaker and transformer connections	9-47		
	Chassis layouts, voltage, socket notes	2-72				Chassis wiring	9-48		
	Schematic, voltage, R-F chassis wiring	10-61				Voltage, alignment	9-51		
	Speaker connections, switch mechanism, parts	10-60				Parts list	9-52		
	Socket, trimmers, dial data, alignment, chassis	10-62				Schematic, socket, trimmers, speaker	9-49		
	Voltage, alignment, parts list	4-38				Chassis wiring, transformers and vibrator connections	9-50		
	See Victor R-32					Voltage, alignment, trimmers	9-51		
	See Victor R-50					Parts list	9-52		
	See Victor R-95					Changes 7-3			
	Units specifications	5-228				Schematic, data	1-43		
	Chassis wiring	5-229				Schematic, socket, condenser connections	3-24		
	Schematic	5-230				Data	Changes 7-14		
	Schematic, socket, data	2-73				Schematic	10-65		
	Assembly wiring	2-74				Voltage, chassis wiring, tuner	10-66		
	Schematic	10-63				Alignment, socket, trimmers, tuner adjustments, antenna and drive cord data	10-67		
	Chassis wiring, socket, trimmers, voltage	10-64				Data, parts list	4-39		
	Alignment	10-67				Schematic, voltage, chassis wiring	4-40		
	Tuner and antenna data	10-58				Voltage, data	3-25		
	Drive data, parts	10-59				Schematic	3-26		
	Schematic, socket, voltage, data	1-39				Chassis wiring	3-27		
	Assembly wiring	4-134				Parts list	3-28		
	Chassis views	4-135				Voltage, data	3-29		
	Notes	4-136				Schematic	3-30		
	Notes	4-137				Chassis wiring	3-31		
	Loud speaker wiring	4-138				Parts list	3-32		
	Microphone notes	4-139				Schematic, chassis wiring	5-7		
	Multiple operation of amplifiers	4-140				Alignment, voltage	5-8		
	Schematic	4-141				Parts list	5-9		
	Chassis wiring	4-142				Alignment, voltage, speaker data	4-41		
	Voltage, notes, phasing speakers	4-145				Schematic, chassis wiring	4-42		
	Replacement parts	4-146				Parts list	4-43		
	Schematic	3-60				Schematic—Similar to R-35			
	Chassis wiring	3-61				Assembly wiring, data	2-75		
	Voltage, notes	3-62				Parts list	2-76		
	Installation data	5-233				Record changer, part 1	2-79		
	Operating notes, chassis views, speaker data	5-234				Record changer, part 2	2-80		
	Operating notes, chassis views, speaker data	5-235				Record changer, part 3	2-81		
	Voltage, parts list	5-236				Record changer, part 4	2-82		
	Schematic	5-237				Locations of parts	2-77		
	Chassis wiring	5-238				Chassis wiring	3-34		
	Schematic	4-143				Schematic, socket	3-35		
	Chassis wiring	4-144				Voltage, speaker wiring	3-36		
	Schematic	5-239				Parts list	5-10		
	Chassis wiring	5-240				Schematic, chassis wiring	5-11		
	Schematic, chassis	1-71				Alignment, voltage	5-12		
	Schematic, socket, voltage, data	1-40				Parts list	5-13		
	Additional data	Changes 7-14				Schematic, chassis wiring	5-13		
	Notes	4-147				Alignment, voltage	5-14		
	View	4-148				See Victor R-32	3-33		
	Chassis view	4-149				Schematic, socket	3-34		
	Notes	4-150				Chassis wiring	3-35		
	Schematic	4-151				See model R-38	3-36		
	Notes	4-152				Specifications, notes	3-37		
	Voltage, parts list	4-153				Schematic, socket	3-38		
	Chassis wiring	4-154				Socket, wiring changes, service data	3-39		
	Schematic	4-155				Chassis wiring	3-40		

RCA MFG. CO., INC.—(Cont.)			RADIOTRON	
MODEL	REVISION	EARLY COMPLETE	PAGE	PAGE
RAE-79	2-83	504-9-A	1915	1915
	2-84	504-9-B	1916	1916
	2-85	504-9-C	1917	1917
	2-86	504-9-D	1918	1918
	2-87	504-9-E	1919	1919
	2-88	504-9-F	1920	1920
	2-89	504-9-G	1921	1921
	2-90	504-9-H	1922	1922
	2-91	504-9-I	1923	1923
	2-92	504-9-J	1924	1924
	2-93	504-9-K	1925	1925
	2-94	504-9-L	1926	1926
	2-95	504-9-M	1927	1927
	2-96	504-9-N	1928	1928
	2-97	504-9-O	1929	1929
	2-98	504-9-P	1930	1930
	2-99	504-9-Q	1931	1931
	2-100	504-9-R	1932	1932
	2-101	504-9-S	1933	1933
	2-102	504-9-T	1934	1934
	2-103	504-9-U	1935	1935
	2-104	504-9-V	1936	1936
	2-105	504-9-W	1937	1937
	2-106	504-9-X	1938	1938
	2-107	504-9-Y	1939	1939
	2-108	504-9-Z	1940	1940
	2-109	504-10-A	1941	1941
	2-110	504-10-B	1942	1942
	2-111	504-10-C	1943	1943
	2-112	504-10-D	1944	1944
	2-113	504-10-E	1945	1945
	2-114	504-10-F	1946	1946
	2-115	504-10-G	1947	1947
	2-116	504-10-H	1948	1948
	2-117	504-10-I	1949	1949
	2-118	504-10-J	1950	1950
	2-119	504-10-K	1951	1951
	2-120	504-10-L	1952	1952
	2-121	504-10-M	1953	1953
	2-122	504-10-N	1954	1954
	2-123	504-10-O	1955	1955
	2-124	504-10-P	1956	1956
	2-125	504-10-Q	1957	1957
	2-126	504-10-R	1958	1958
	2-127	504-10-S	1959	1959
	2-128	504-10-T	1960	1960
	2-129	504-10-U	1961	1961
	2-130	504-10-V	1962	1962
	2-131	504-10-W	1963	1963
	2-132	504-10-X	1964	1964
	2-133	504-10-Y	1965	1965
	2-134	504-10-Z	1966	1966
	2-135	504-11-A	1967	1967
	2-136	504-11-B	1968	1968
	2-137	504-11-C	1969	1969
	2-138	504-11-D	1970	1970
	2-139	504-11-E	1971	1971
	2-140	504-11-F	1972	1972
	2-141	504-11-G	1973	1973
	2-142	504-11-H	1974	1974
	2-143	504-11-I	1975	1975
	2-144	504-11-J	1976	1976
	2-145	504-11-K	1977	1977
	2-146	504-11-L	1978	1978
	2-147	504-11-M	1979	1979
	2-148	504-11-N	1980	1980
	2-149	504-11-O	1981	1981
	2-150	504-11-P	1982	1982
	2-151	504-11-Q	1983	1983
	2-152	504-11-R	1984	1984
	2-153	504-11-S	1985	1985
	2-154	504-11-T	1986	1986

RCA MFG. CO., INC.—(Cont.)			RADIOGRAM		
MODEL		REVISED PAGE	MODEL		REVISED PAGE
PA 90 A1 Amp.			95X, 95XL		
R-90	Schematic, voltage, parts list.....4-123		95X1	Schematic, socket, alignment, chassis wiring, lead dress, parts.....9-108	
R-90-P	Chassis wiring.....4-124	1947		Alignment, chassis wiring, specifications, tuner, lead dress.....9-113	
	Voltage, trimmers, speaker wiring, voltage.....3-53	1948	96BK6, 96BT6, Chassis RC-392 with model OV-9 A-O S.P.U.	Schematic, tuner data.....10-77	
	Alignment, data.....4-49				
	Schematic, voltage, trimmers, speaker.....4-50				
91-B	Chassis wiring.....4-51				
R-92 Recorder	Parts list.....4-52		96E, 96T, 96T1	Alignment, voltage, chassis wiring.....10-78	
	Schematic, chassis wiring.....5-15			Socket, trimmers, alignment.....10-76	
	Capacitor adjustment, voltage, parts.....5-17			Procedure.....10-79	
	Schematic, voltage.....5-18			Parts.....10-94	
	Assembly wiring, pickup.....5-19			Schematic, socket, trimmers, chassis wiring.....9-94	
R-98 Phonograph	Pickup adjustments.....5-20			Alignment, tuner, specifications.....9-95	
	Service notes.....5-21			Push-button assembly, parts.....9-96	
	Pickup data, parts list.....5-22			Schematic, lead dress.....10-51	
	Models listing, connections.....5-23				
R-98	Schematics.....5-24		96K2, 96T3, 97E, 97KG, 97T	Alignment, socket, trimmers, tuner adjustments.....10-80	
	Schematic, motor details, wiring, diagram, pickup.....7-157			R-F chassis wiring, data.....10-82	
	Motor details (Late), typical layout.....7-158			Parts.....10-79	
	Lead connections.....7-159			Schematic, specifications, drive data.....9-97	
	Connection data, pickup data, parts.....7-160			Voltage, chassis wiring, socket, trimmers, transformer data.....9-98	
R-98 (3rd Production), R-98A, R-98-2, R-98-S, R-94	Pick-up details, schematics.....8-187			Schematic, socket, trimmers, transformer data.....9-102	
	Notes.....8-138			Chassis wiring, voltage, lead dress, drive cord data, transformers data.....9-102	
	Specifications, parts, page 1.....8-140			Alignment, tuner, parts.....9-103	
R-98-A, R-98-2	Parts, page 2.....8-141			Schematic, chassis wiring.....8-143	
R-98-S, R-94	Motor details.....8-136			Automatic record changer, adjustment, assembly.....8-144	
	Notes, details of receiver connections.....8-137			Parts.....8-142	
	Sections.....8-139			Pick-up and motor details, voltage, notes, socket, adjustments.....8-145	
94BK, 94BT	Schematic, socket, trimmers, voltage, alignment, lead dress.....9-90			Notes.....8-145	
	Parts list.....9-90			Schematic, voltage, R-F chassis wiring.....10-83	
94BK1, 94BT1, Chassis RC-383B	Schematic, voltage, socket, alignment, trimmers.....10-68			Alignment, socket, trimmers, tuner, lead dress, drive data.....10-84	
94BK2, 94BT2, Chassis RC-390	Parts.....10-74			Tuner adjustments, parts.....10-85	
	Schematic, voltage, chassis wiring.....10-69			Schematic, voltage, socket, trimmers, alignment, data.....10-87	
94BP4, Chassis RC-410	Socket, trimmers, alignment, drive cord data, lead dress.....10-70			Parts.....10-86	
	Schematic, voltage, alignment, trimmers, lead dress.....10-71			Chassis wiring.....5-215	
94BP61, 94BP62, 94BP64, 94BP66, 94BP80, 94BP81, Chassis RC-407	Parts list.....10-73			Schematic.....5-216	
94BT6	Schematic, voltage, alignment, trimmers, lead dress, battery data, parts.....10-72			Schematic.....10-89	
	Schematic, socket, trimmers, voltage, alignment, lead dress.....9-91			Voltage, chassis wiring, transformer, speaker data.....10-90	
94BT61, Chassis RC-339C	Parts list.....9-90			Specifications, calibration scale.....10-88	
	Schematic, voltage, alignment, chassis wiring, socket, trimmers.....10-75			Alignment, socket, trimmers, tuner adjustments.....10-93	
94X	Lead dress, parts.....10-76			Parts.....10-94	
94X1, 94X2	Schematic, socket, trimmers, voltage, parts, alignment.....9-92			Schematic.....10-91	
	Schematic, socket, trimmers, voltage, tuner, chassis wiring, notes.....9-100			Voltage, chassis wiring, transformer, speaker.....10-92	
95T	Schematic, socket, trimmers, voltage, chassis wiring, alignment, parts.....9-104			Specifications, calibration scale.....10-88	
95T5	Schematic, socket, trimmers, chassis wiring, voltage.....9-93			Alignment, socket, trimmers, tuner adjustments.....10-98	
	Alignment, tuner, specifications.....9-95			Parts.....10-98	
	Push-button assembly, parts.....9-96			See model 96E2	

MODEL	ROA MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
97X	Schematic, specifications, lead dress, notes ..... 9-105 Socket, trimmers, alignment, tuner ..... 9-106 Voltage, chassis wiring, parts 9-107 Schematic, lead dress ..... 9-109			1838 1839
97Y, Chassis RC952A, 98BY, 98Y, 98YG, Chassis RC 352	Voltage, chassis wiring, drive cord data, notes, specifications ..... 9-110 Socket, trimmers, parts, alignment, tuner ..... 9-111 Schematic, socket, trimmers, specifications ..... 9-113 Voltage, lead dress, chassis wiring, notes, transformers 9-114 Electric tuning, notes, mechanism, adjustments ..... 9-115 Alignment, antenna data, parts ..... 9-116 Schematic, voltage, socket, speaker connections ..... 10-95 Motor data, switch assembly, parts ..... 10-96 Schematic, socket, trimmers, transformer, speaker data ..... 10-97 Voltage, chassis wiring, alignment, drive data ..... 10-98 Dial calibration ..... 10-8 Tuner adjustments, parts ..... 10-99 Schematic, socket, trimmers, transformers ..... 9-117 Voltage, chassis wiring, tuner 9-118 Lead dress, alignment, electric tuning data, specifications 9-119 Drive data, parts, notes ..... 9-120 Schematic, loudspeaker ..... 7-161 Chassis wiring, pickup, socket 7-162 Resistance, voltage ..... 7-163 Motor adjustments, assembly wiring ..... 7-164 Circuit data, adjustments, parts ..... 7-165 Motor data, tone compensation, parts ..... 10-100 Motor, pickup details, receiver connections ..... 10-101 Alignment, speaker, schematic, voltage ..... 4-53 Chassis wiring, parts list ..... 4-54 Schematic, socket, data ..... 1-55			
98K	See Model Univ. Amp. PG 63 Schematic, transformer data ..... 6-1 Alignment, voltage, socket, trimmers ..... 6-2 Chassis wiring, service notes ..... 6-3 Parts ..... 6-4 Schematic ..... 8-147 Alignment, socket, trimmers ..... 8-148 Voltage ..... 8-149 Parts ..... 8-152 Chassis wiring ..... 8-147 Motor details ..... 8-149 Changes ..... 9-6 Schematic, chassis wiring ..... 5-25 Voltage, parts list ..... 5-26 See model 85E Schematic, voltage ..... 6-5 Circuit data, socket, trimmers, voltage, alignment, parts ..... 6-6 See 100-A Speaker Schematic, voltage, parts list ..... 5-281 Panel wiring ..... 5-282 Chassis wiring ..... 8-148 Automatic record changer, adjustments, details ..... 8-150 Motor details, notes ..... Changes 8-151			
R98, Chassis RS-77				
98T, 98K2, Chassis RC-386A				
99K, 99T				
R-99				
R-100 Victrola attachment				
RCA-100, 101				
100-A, 100-B, 103, 104 AC, Loudspeakers				
PB 100 B1				
M-101				
U-101, U-103				
U-101				
102				
U102E				
103				
103, 104 AO Speakers PA-103-A1				
U-108				
MODEL	ROA MFG. CO., INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
104 DO Speaker	Schematic, socket, notes ..... 3-6 General service notes, voltage ..... 3-7 See Radiola 25, 28, 30 Circuit notes ..... 6-8 Schematic, speaker wiring ..... 6-9 Chassis wiring, notes ..... 6-10 Alignment, voltage, socket, trimmers, notes ..... 6-11 Parts list ..... 6-12 Schematic, voltage, chassis wiring, alignment procedure 10-102 Chassis wiring, lead dress, pickup, phono ..... 10-103 Parts ..... 10-86 Schematic, socket, wiring ..... 1-56 Alignment data, voltage, service data ..... 5-27 Installation data ..... 5-28 Schematic, installation details ..... 5-29 Installation details ..... 5-30 Chassis wiring ..... 5-31 Parts list ..... 5-32 Chassis wiring ..... 5-32 Automatic record changer details, adjustments and details ..... 9-123 Schematic ..... 9-124 Circuit data, lead dress, pickup data, specifications 9-122 Socket, trimmers, voltage, pickup data, phonograph motor data ..... 9-126 Alignment ..... 9-127 Parts list ..... 9-128 Schematic, specifications ..... 9-129 Chassis wiring ..... 9-130 Socket, trimmers, circuit data, notes ..... 9-131 Automatic record changer adjustments, views, tuner ..... 9-132 Alignment, transformer data, parts ..... 9-133 Schematic, service details ..... 5-33 Chassis wiring ..... 5-34 Alignment data ..... 5-35 Voltage data, trimmer location, socket ..... 5-36 Voltage, chassis wiring ..... 5-37 Parts list ..... 5-38 Chassis wiring, coils ..... 9-125 Automatic record changer adjustments, views, tuner, 9-132 See Model M-104 Schematic ..... 6-18 Chassis wiring ..... 6-14 Alignment, notes ..... 6-15 Socket, trimmers, circuit notes, power unit wiring ..... 6-16 Parts list ..... 6-17 Circuit data ..... 9-134 Schematic ..... 9-135 R-F Chassis wiring, coils, specifications ..... 9-136 Power amplifier, chassis and tuner wiring ..... 9-137 Voltage, socket, trimmers ..... 9-138 Socket, trimmers, current readings ..... 9-139 Lead dress, amplifier adjustments ..... 9-140 Tuner mechanism, principles, adjustments ..... 9-141 Tuner adjustments, Part 2 ..... 9-142 Alignment ..... 9-143 Assembly wiring, compensator connections ..... 9-144 Automatic record changer views ..... 9-145 Automatic record changer adjustments, data, pickup data ..... 9-146			
104 DO Speaker				
104 Power Pack M-104, M-108				
U-104, Chassis RC-345H				
105, 108 Speakers M-105				
U105				
U105, U107				
U106				
M-107				
U107				
M-108				
M-109				
U109				

MODEL	RCA MFG. CO., INC.—(Cont.)	REVISION PAGE	RADIO TRON EARLY COMPLETE PAGE
U109	Parts list ..... 9-147	9-147	
ACR111	Parts list, concluded ..... 9-148	9-148	
	Chassis wiring, coils ..... 9-149	150	
	Schematic ..... 9-151		
	Tuner unit, chassis wiring, coils ..... 9-152		
	Socket, trimmers, voltage, ..... 9-153		
	R-F and I-F trimmers, sockets ..... 9-154		
	Alignment table ..... 9-155		
	Selectivity control curves ..... 9-156		
	Dial data, selectivity, speaker wiring ..... 9-157		
	Notes, operation ..... 9-158		
	Adjustment, notes ..... 9-159		
	Circuit data, transformer data ..... 9-160		
	Parts list ..... 9-161		
RCA 110, 111, 115	Alignment, voltage, parts list ..... 4-55		
U111	Schematic, data, chassis wiring ..... 4-56		
	Schematic, voltage, chassis wiring ..... 9-169		
	Socket, trimmers, alignment, lead dress, phonograph data, parts ..... 9-170		
112 AC-DO 220 volts	Alignment, parts list ..... 4-57		
	Schematic, voltage, trimmer locations ..... 4-58		
U-112, Late U-111 and U-112	Chassis wiring ..... 4-59		
114	Data ..... Changes 10-4		
U-115, Chassis RC-348E, RC-348E "M," RC-348E "MOD"	Voltage, alignment ..... 4-60		
	Schematic, chassis wiring ..... 4-61		
	Parts list ..... 4-62		
	socket, trimmers, voltage, transformer data ..... 10-105		
	Alignment, phono. data, tuner adjustments ..... 10-106		
M-116	Parts ..... 10-104		
	Voltage, alignment data ..... 5-39		
	Chassis wiring ..... 5-40		
	Schematic ..... 5-41		
117, 214	Installation notes, parts list ..... 5-42		
	Circuit notes, loud speaker data, voltage, trimmers, socket ..... 6-18		
	Chassis wiring ..... 6-20		
	Schematic ..... 6-19		
118, 211	Alignment, parts ..... 6-21		
	Schematic, trimmer locations ..... 5-43		
	Chassis wiring ..... 5-44		
	Voltage, socket, loud speaker wiring ..... 5-45		
118, 211 (1935 Production)	Alignment data, parts list ..... 5-46		
	Parts list ..... 6-22		
	Schematic, voltage, speaker wiring ..... 6-23		
TMV-118-B	Chassis wiring ..... 6-24		
	Schematic, socket, voltage, data ..... 7-167		
119	Chassis wiring, transformer, data, regulating circuits ..... 7-168		
	Schematic ..... 6-25		
	Chassis wiring ..... 6-26		
	Trimmers, socket, voltage, alignment, circuit data ..... 6-27		
	Alignment, part 2; speaker wiring ..... 6-28		
U119, U122E, U124	Schematics, specifications ..... 9-171		
	Voltage, chassis wiring, lead dress, transformer data ..... 9-172		
	Tuner and phonograph data ..... 9-173		
	Alignment, motor data, parts ..... 9-174		
120	Alignment, voltage, speaker data ..... 4-63		
	Schematic, chassis ..... 4-64		
	Parts list ..... 4-65		
	Alignment, voltage, trimmer locations ..... 4-66		
	Schematic ..... 4-67		
	Chassis wiring ..... 4-68		
	Parts list ..... 4-69		
	Schematic, chassis wiring, voltage ..... 10-107		
U-121, Chassis RC-348J	Alignment, socket, trimmers, phono. data ..... 10-109		
U-123, Chassis RC-348H (Single Band), U-127E, Chassis RC-348L	Automatic record changer adjustments, notes ..... 10-110		
	Specifications, tuner data, record changer details ..... 10-111		
	Parts ..... 10-112		
	See model U119 ..... 10-113		
U122E	Alignment data, voltage, trimmers ..... 5-47		
M-123	Schematic, socket layout ..... 5-48		
	Service details ..... 5-49		
	Chassis wiring ..... 5-50		
	Vibrator data ..... 5-51		
	Parts list ..... 5-52		
	Schematic, chassis wiring, voltage ..... 10-108		
U-123, Chassis RC-421 (2 Bands)	Alignment, socket, trimmers, phono. data ..... 10-109		
	Automatic record changer, adjustments, notes ..... 10-110		
	Specifications, tuner data, record changer details ..... 10-111		
124	Parts ..... 10-112		
	Alignment data, voltage ..... 5-53		
	Schematic, chassis wiring ..... 5-54		
	Parts list ..... 5-55		
U124	See model U119		
125, 225	Schematic, speaker data ..... 6-29		
	Chassis wiring ..... 6-30		
	Alignment, transformer data ..... 6-31		
	Socket, trimmers, voltage, parts, speaker wiring ..... 6-32		
	Victrola attachment data ..... 10-101		
	Schematic, voltage ..... 10-115		
	Alignment, tuner data ..... 10-114		
	Chassis wiring, voltage ..... 10-116		
	Socket, trimmers, speaker connections, drive data, transformer data, parts ..... 10-118		
	Automatic record changer adjustments, data ..... 10-51		
	Record changer assembly, details ..... 10-52		
U-127E	Parts ..... 10-117		
128-B	See model U-121		
	Schematic, socket layout ..... 5-57		
	Chassis wiring ..... 5-58		
	Alignment data, voltage ..... 5-59		
U126	Parts list ..... 5-60		
127	See model 910KG		
	Schematic, trimmer locations ..... 5-61		
	Chassis wiring, voltage ..... 5-62		
	Socket layout, voltage ..... 5-63		
	Alignment data, parts list ..... 5-64		
	Schematic, transformer data ..... 5-65		
128, 224 (1934 Production)	Chassis wiring ..... 5-66		
	Trimmer layout, socket layout, circuit data ..... 5-67		
	Alignment data ..... 5-68		
	Alignment data, part 2 ..... 5-69		
	Voltage, parts list ..... 5-70		
	Victrola attachment data ..... 10-101		
128, 226 (1935 Production)	Schematic, parts, speaker wiring ..... 6-33		
	Chassis wiring ..... 6-34		
	Victrola attachment data ..... 10-101		



[illegible]



RCA MFG. CO., INC.—(Cont.)			RADIOTECH		RCA MFG. CO., INC.—(Cont.)		RADIOTECH	
MODEL			EARLY COMPLETE PAGE	REVISED PAGE	MODEL		EARLY COMPLETE PAGE	REVISED PAGE
RC-429 chassis	See model TRK-5				910KG, U126, U128	Alignment, turntable data	9-204	
RC-435 chassis	See model 9TX50					Tuner mechanism data	9-205	
AP-736	Data	Changes 8-4				Automatic record changer	9-9	
AP-736B	Schematic, chassis wiring	1-1	1749			Parts list	9-206	
AP-777-O	Schematic, chassis wiring	1-1	1749			Schematic, lead dress	9-207	
AR-200	See Radiola II	1-2	1750			Chassis wiring, transformer		
810K, 810K1, 810T	Schematic notes	9-175				data, voltage, specifications	9-208	
	Chassis wiring, coils	9-176				Tuner mechanism, data	9-209	
	Voltage, trimmers, specifica-	9-177				Alignment, socket, trimmers,		
	tions	9-177				Parts	9-210	
	Alignment, socket, phono-					Schematic	1-3	*748
	graph notes	9-178				Schematic	1-3	*748
	Lead dress, parts	9-179				Schematic	1-2	*708
	Victrola attachment data	10-101				Schematic	1-2	*708
	Schematic, socket, trimmers,					Schematic	1-2	*708
	type specifications					Schematic	1-4	*709
	Parts list	9-181				Schematic	1-4	*709
	Chassis wiring, coils	9-180				Schematic	1-4	*709
	Lead dress, voltage, notes,	9-182				Schematic	1-3	*748
	trimmers	9-183				Socket, reproducer distribution	8-63	1967
	Alignment	9-184				table notes	3-64	
	Victrola attachment data	10-101				AP Amplifier Chassis wiring	3-65	1968
	Schematic, notes	8-153				Receiver Chassis wiring	3-65	1969
	Chassis wiring	8-154				Voltage	8-67	1970
	Socket, trimmers, voltage	8-155				Schematic, chassis details	5-203	
	Specifications, "Electric Eye"	8-156				Chassis wiring	5-204	
	"Electric Tuning" adjust-					Alignment data, voltage	5-205	
	ments, assembly	8-157				Parts list	5-208	
	"Electric Tuning" notes,					Changes	8-4	
	alignment	8-158				Schematic, voltage	5-207	
	Notes, parts	8-159				Alignment data, parts list	5-208	
	Victrola attachment data	10-101				Chassis wiring	5-209	
	Schematic	8-161						
	Parts, notes	8-160						
	Chassis wiring	8-162						
	Socket, trimmers, voltage	8-163						
	"Electric Tuning" assembly,							
	details, adjustments	8-164						
	"Electric Tuning" wiring,							
	alignment	8-165						
	Circuit data, adjustment							
	Notes	8-166						
	Victrola attachment data	10-101						
	Schematic	9-185						
	Chassis wiring, transformer							
	data	9-186						
	Voltage, trimmers, socket,							
	data	9-187						
	Socket, trimmers, tuner							
	wiring	9-188						
	Alignment	9-189						
	Circuit data, adjustments,							
	lead dress	9-190						
	Tuner data, specifications	9-191						
	Tuner mechanism, adjust-							
	ments	9-192						
	Parts list	9-193						
	Victrola attachment data	10-101						
	Tuner mechanism, adjust-							
	ments	9-192						
	Parts list	9-194						
	Schematic	9-195						
	Chassis wiring, transformer							
	data	9-196						
	Socket, trimmers, voltage	9-197						
	Electric tuning wiring,							
	specifications	9-198						
	Alignment	9-199						
	Tuner notes, lead dress,							
	phonograph data	9-200						
	Victrola attachment data	10-101						
	See Radiola V							
	See Radiola VI							
	Schematic, socket, trimmers,							
	drive data	9-201						
	Chassis wiring, voltage, trans-							
	former data, specifications	9-202						
	Circuit data, antenna, lead							
	dress, tuning dial	9-203						

AR-885  
AR-895  
910KG, U126, U128

816K

818K

819K

811K

810T4

3749

\*709

1745  
1746  
1748  
1748  
1747  
1748  
1745

\*748  
\*748  
\*708  
\*708  
\*708  
\*709  
\*709  
\*748  
1967  
1968  
1969  
1970  
1971

RADIO CIRCULAR CO.

V Schematic, voltage, alignment 7-1  
W Schematic, voltage, alignment 7-2  
5-Tube Dual Battery A-W Schematic, alignment 6-1  
5-Tube Dual A-O A-W Schematic, alignment 6-1  
5-Tube AC-DO Dual A-W Schematic, alignment 6-2  
Superhet Schematic, alignment 6-2  
317

RADIART LABORATORIES

Magnaformer 9-8 Schematic Misc. 1-4

RADIETTE

See KELLER FULLER

RADIO CHASSIS, INC.

Auto Receiver  
A-5-D Schematic 4-1  
L-5-D Schematic 4-2  
A-6-D Schematic 4-3  
L-6-D Schematic 4-5  
L-6-W Schematic 4-6  
SMA-24 Schematic 3-1  
AC-25, SMA-25 Schematic 3-2  
AC-35, QAC-35 Schematic 3-4  
AC-36, QAC-36, LSA-36 Schematic 3-4  
SDC-36 Schematic 3-2  
LSA-37 Schematic 3-1  
HOAR-48

R K RADIO LABORATORIES, INC.

4-Tube Receiver  
RK-4 Schematic 5-1  
RK-4 Schematic Misc. 7-11  
RK-5 S-5 Radiokog Schematic 5-4  
RK-5 S-5 Radiokog Schematic 4-9  
RK-5 S-5 Radiokog Schematic 5-2  
RK-5 S-5 Radiokog Schematic 5-3  
RK-5 S-5 Radiokog Schematic 6-1  
421, 422, 423, 424 Schematic, voltage 6-1  
425, 426, 427, 428 Schematic, voltage 6-1  
521, 522 Schematic, voltage 6-1  
534 Schematic, voltage 6-3  
631, 633 Schematic, voltage 6-3

EARLY PAGE	RADIOTRON COMPLETE PAGE
1	1
2	2
3	3
100	100

REVISION NO.	REVIEWED	PAGE
1		1
2		2
3		3
100		100

## 1441

**Schematic**  
**Schematic**

Schematic

Schematic	3-1
Schematic	1-1

**Schematic,  
trimmers  
Alignments**

## A-1 Chassis

Schematic,  
alignmen  
Nee model

EARLY PAGE	RADIOTRON COMPLETE PAGE
1	1
2	2
3	3
100	100

Schematic  
Socket. tr

## Day 2: 31 Oscilla

Schematic  
ment ...

## Dayrad 4000

Schematic	2-1
Schematic	3-1
Schematic	3-1

### 3-Tube AC

## Schematic

## Chassis

Schematic  
Schematic  
Schematic

### M-1 Chase

Schematic, socket .....	3-2
Schematic, wiring diagram.....	3-2

## U-4 Chassis

Schematic	3-4
Schematic	3-4

RADOLEK—(Cont.)			REMLER CO., LTD.—(Cont.)			RADIOTRON		
MODEL	REVISID PAGE	EARLY COMPLETE PAGE	MODEL	REVISID PAGE	EARLY COMPLETE PAGE	MODEL	REVISID PAGE	EARLY COMPLETE PAGE
7-tube Super	Schematic	8-3	11	Schematic, socket, voltage, chassis layouts	3-4	11	Schematic, socket, voltage, chassis layouts	2026
Marvelo 7-tube Super	Schematic	8-2	14	Schematic, socket, voltage, chassis layouts	3-4	14	Schematic, socket, voltage, chassis layouts	2027
9-tube Battery Super	Schematic	8-1	15	Schematic, socket, voltage, chassis layouts	3-4	15	Schematic, socket, voltage, chassis layouts	2028
Radolek 10-tube Super	Schematic	2-1	16	Schematic, socket, voltage, chassis layouts	3-4	16	Schematic, socket, voltage, chassis layouts	2029
Marvelo 6 Midget	Schematic	4-1	17	Schematic, socket, voltage, chassis layouts	3-4	17	Schematic, socket, voltage, chassis layouts	2030
Marvelo-Monroe 6-7	Schematic	4-1	19, 21	Chassis layout	3-5	19, 21	Chassis layout	2031
Monroe-Marvelo 8-9	Schematic	2-1	19	Schematic, socket, voltage, chassis layouts	3-2	19	Schematic, socket, voltage, chassis layouts	2032
Monroe-Marvelo 80	Schematic	8-1	21	Schematic, socket, voltage, chassis layouts	3-3	21	Schematic, socket, voltage, chassis layouts	2033
35 Common Talk System	Schematic	4-1	21-3	Schematic, socket, voltage, chassis layouts	3-6	21-3	Schematic, socket, voltage, chassis layouts	2034
45 Selective System	Schematic	4-2	21-4	Schematic, socket, voltage, chassis layouts	3-6	21-4	Schematic, socket, voltage, chassis layouts	2035
SR-230	Schematic	4-2	26 AC-DO	Notes	3-6	26 AC-DO	Notes	2036
SR-233	Schematic	4-2	26	Above Serial 54760	6-1	26	Above Serial 54760	2037
SR-234	Schematic	4-2	27	"Scottie," Above Serial 77059	4-2	27	"Scottie," Above Serial 77059	2038
SR-236	Schematic	4-2	28	"Scottie," Above Serial 77059	4-2	28	"Scottie," Above Serial 77059	2039
SR-241 Amplifier	Schematic	8-2	29	Schematic	1-2	29	Schematic	2040
SR-247 Amplifier	Schematic	8-2	30, 40	Schematic, voltage, alignment	4-3	30, 40	Schematic, voltage, alignment	2041
951	Alignment, voltage	5-1	35 Auto	Schematic, socket, voltage, installation	5-3	35 Auto	Schematic, socket, voltage, installation	2042
956	Alignment, voltage	5-3	36	Schematic, chassis, voltage	6-2	36	Schematic, chassis, voltage	2043
958	Alignment, voltage	5-4	37	Schematic, socket, voltage, alignment	7-1	37	Schematic, socket, voltage, alignment	2044
10926	Schematic, notes	7-1	39, Above serial 115439	Schematic, voltage, alignment	10-1	39, Above serial 115439	Schematic, voltage, alignment	2045
10927	Schematic, notes	7-2	40 KC	Schematic	2-1	40 KC	Schematic	2046
10928	Schematic, notes	7-3	40, Above Serial 53410	Schematic, voltage, alignment	6-3	40, Above Serial 53410	Schematic, voltage, alignment	2047
10931	Schematic, notes	7-4	40 (Late), Beginning Serial #66746	Schematic, voltage, data	7-2	40 (Late), Beginning Serial #66746	Schematic, voltage, data	2048
10943	Schematic, notes	7-5	41, Beginning Serial #60411	Schematic, voltage, data	7-2	41, Beginning Serial #60411	Schematic, voltage, data	2049
10951	Schematic, voltage	5-7	42, Above Serial 53968	Schematic, voltage, alignment	6-4	42, Above Serial 53968	Schematic, voltage, alignment	2050
10953	Schematic	5-11	42SW, Beginning Serial #37061	Schematic, voltage, data	7-3	42SW, Beginning Serial #37061	Schematic, voltage, data	2051
10956	Schematic	5-10	43, Beginning Serial #62761	Schematic, voltage, changes, data	7-4	43, Beginning Serial #62761	Schematic, voltage, changes, data	2052
10962	Alignment, voltage	5-12	44, Early, Serial #68915, Late, Serial #69773	Schematic, voltage, trimmers, alignment	8-1	44, Early, Serial #68915, Late, Serial #69773	Schematic, voltage, trimmers, alignment	2053
10963 (60 cycles)	Schematic, voltage, alignment	5-13	45, Beginning Serial #72409	Schematic, voltage, alignment	9-1	45, Beginning Serial #72409	Schematic, voltage, alignment	2054
10964 (25 cycles)	Schematic, voltage, alignment	5-13	46, Above Serial #83786	Schematic, voltage, alignment	9-2	46, Above Serial #83786	Schematic, voltage, alignment	2055
10966	Schematic, voltage	5-14	46, "Scottie," Serials 98515 to 107767	Schematic, voltage, alignment	9-2	46, "Scottie," Serials 98515 to 107767	Schematic, voltage, alignment	2056
10967	Schematic, alignment, voltage	5-12	46, "Scottie," Above Serial 107767	Schematic, voltage, alignment	9-2	46, "Scottie," Above Serial 107767	Schematic, voltage, alignment	2057
10968	Schematic, voltage, alignment	5-13	47, "Worldwide Scottie," Above Serial 92942	Schematic, voltage, alignment	9-3	47, "Worldwide Scottie," Above Serial 92942	Schematic, voltage, alignment	2058
10969	Schematic, service data	5-11	49, 171 Beginning Serial 115014	Schematic, parts	8-3	49, 171 Beginning Serial 115014	Schematic, parts	2059
10970	Schematic, voltage, alignment	5-14	M-50 Communication System	SC-50, SWC-50 call-back connections	8-3	M-50 Communication System	SC-50, SWC-50 call-back connections	2060
11908	Schematic, socket	7-6		X-50 Switch wiring	8-4		X-50 Switch wiring	2061
11910	Schematic, notes	7-7		Box wiring, data	8-5		Box wiring, data	2062
11911	Schematic, alignment	7-8		Master unit, call-back switch wiring, data	8-6		Master unit, call-back switch wiring, data	2063
11935	Schematic, alignment	7-9		Installation, operation	8-8		Installation, operation	2064
11947	Schematic, alignment	7-10		Schematic, voltage, trimmers, alignment	8-1		Schematic, voltage, trimmers, alignment	2065
READRITE METER WORKS				Schematic, voltage, alignment	6-5		Schematic, voltage, alignment	2066
6	Schematic	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2067
15	Schematic	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2068
245	Schematic	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2069
400 Tube Tester	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2070
405 Tube Checker	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2071
407 Tube Tester	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2072
410 Tube Checker	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2073
502 Ohmmeter	Schematic	4-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2074
550 Oscillator	Schematic	2-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2075
600, 700 Testers	Schematic	2-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2076
610, 710 Set Analyzer	Schematic	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2077
705 Set Tester Adapter	Schematic	3-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2078
710 Set Tester	Schematic	4-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2079
800 Capacity Meter	Schematic	2-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2080
850 Capacity Meter	Schematic	2-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2081
900 Elec. Refrigerator Tester	Schematic	3-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2082
1000 Set Tester	Schematic	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2083
REMLER CO., LTD.				Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2084
Best 115 KC.	Schematic	1-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2085
"Scottie"	See model 28 or 46			Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2086
"Worldwide Scottie"	See model 47			Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2087
1827 Infradyne	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2088
1828 Infradyne	Schematic	2-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2089
10, 11, 15, 19, 21 Super	Schematic, socket, voltage, chassis layouts	3-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2090
10-3	Schematic, voltage	2-2		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2091
10-4	Alignment, data	4-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2092
	Schematic, voltage, socket, alignment	5-1		Schematic, voltage, alignment	6-6		Schematic, voltage, alignment	2093

<b>RADIOTRON</b>	<b>2050</b>
<b>COMPLETE</b>	<b>2051</b>
<b>PAGE</b>	<b>2051</b>
	<b>2051</b>
	<b>2051</b>
	<b>2052</b>
	<b>2052</b>
	<b>2053</b>
	<b>2053</b>
	<b>2054</b>
	<b>2055</b>
	<b>2055</b>
	<b>2048</b>

MODEL	REMIRE CO., LTD.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
63, Beginning Serial #69116	Schematic, voltage, data	7-7	
64, Beginning Serial #73914	Schematic, voltage, data	7-7	
65, Above Serial 109217	Schematic, voltage, alignment	9-4	
66, Master unit and S-50 secondary unit wiring	Installation, operation	8-7	
67, M-70 Communication System	Schematic, voltage, data	8-8	
71, Beginning Serial #75639	Schematic, voltage, alignment, data	9-5	
72, Above Serial 104459	Schematic, voltage, tuner,		
73			

88	Schematic, data	7-8
89, 89C	Schematic, voltage	
92582	alignment, phonograph	9-6
91, Beginning Serial	Schematic, data	7-8
#72759		
140, 170 Norco	Schematic, voltage, alignment	Misc. 8-8
171	See model 49	
173 Norco	Schematic, voltage, alignment	Misc. 8-8
1779, Above Serial 113701	Schematic, alignment	10-4

**REO**

See PHILCO RADIO & TELEVISION CORP.

**REPUBLIC INDUSTRIES**

MS & Jr.	Schematic, notes	Misc. 3-7
SL-5E Hawk Patrician	Schematic	Misc. 6-12
RE-5E	Schematic, voltage, socket	5-1
"Skyhawk"	Schematic, voltage, socket	5-4
RC-5, RC-6	Schematic	4-1
"Skyhawk" SL-5-D	Schematic	4-2
OS-6	Schematic, voltage, socket	5-2

"Skyhawk" SL-6D	
TL-60	4-4
42	Schematic, voltage, socket.....5-3
51	Schematic, socket, voltage, paris.....7-1
	Schematic, socket, voltage, paris.....7-2
<b>ROOKE INTERNATIONAL ELECTRIC CORP.</b>	
Arlab 51	Schematic ..... Misc. 4-8
<b>ROOT'S AUTO RADIO MFG. CORP.</b>	
55 Auto	Schematic, data ..... Misc. 5-16
<b>ROYAL</b>	
A	Schematic ..... Misc. 5-17

SAMSON ELECTRIC CO.			
Amplifier	Schematic	1-1	*713
MIK-1	Schematic	2-12	712-L
MIK-1D	Schematic	2-12	712-L
PAM-1	Schematic	2-1	712-A
HA-2	Schematic	2-12	712-L
PABO-2	Schematic	2-2	*711
PABO-3	Schematic	2-2	*711
PAM-3	Schematic	2-2	712-B
PABO-4	Schematic	2-2	*712
PABO-5	Schematic	1-3	*712
PAM-5	Schematic	1-3	712-C
PAM-5-D	Schematic	2-3	712-C
PAM-8	Schematic	2-3	712-D
PAM-9	Schematic	2-4	712-D
PAM-11, 12, 13, 14	Schematic	2-4	712-D
PAM-16, 17	Schematic	2-5	712-E
PAM-16-N, 17-N	Schematic	2-6	712-F
PAM-19	Schematic	2-6	712-F
PAM-19-N	Schematic	1-1	*713
PAM-19-N	Schematic	2-7	712-G
PAM-19-Q	Schematic	2-7	712-G

MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE
218	See model 109						
334, 334X	Chassis						
334X	Chassis						
345X	Chassis						
359	Chassis						
359X	Chassis						
388	Chassis						
388X	Chassis						
391Y	Chassis						
550	Chassis						
709, 719	International						
802, 812							
1150, 1170							
1152, 1174, 1420							
1250							
1252							
1280							
1280, 1300							
1290, 1292, 1300, 1302							
1292, 1302							
1310, 1312							
1390, 1322, 1324, 1326, 1386, 1450, 1452							
1370, 1371							
1370, 1400, 1402, 1404, 1406							
1400, 1406							
1480, 1510							
1480, 1452							
1482							
1480, 1482, 1484							
1506							
1510							
1510X, 1520, 1522, 1522X, 7000, 7001, 7002, 7012							
1564							
1570, 1572, 1574							
1580, 1582, 1584							
1590, 1592							
1597, 1598, 7050							
1600							
1620, 1622							
1626							
1630							
1640							
1650							
218	See model 109						
334, 334X	Chassis						
334X	Chassis						
345X	Chassis						
359	Chassis						
359X	Chassis						
388	Chassis						
388X	Chassis						
391Y	Chassis						
550	Chassis						
709, 719	International						
802, 812							
1150, 1170							
1152, 1174, 1420							
1250							
1252							
1280							
1280, 1300							
1290, 1292, 1300, 1302							
1292, 1302							
1310, 1312							
1390, 1322, 1324, 1326, 1386, 1450, 1452							
1370, 1371							
1370, 1400, 1402, 1404, 1406							
1400, 1406							

EARLY PAGE	RADIOTRON COMPLETE PAGE
1	1
2	2
3	3
100	100

MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
1760	Schematic, voltage.....	4-31	
	Socket, trimmers, chassis	.....4-31	
	Schematic	.....4-32	
1760 (Type 1)	Voltage	.....5-26	
1760 (Type 2)	Schematic, voltage	.....5-27	
1760	Socket layout, chassis, parts.....	5-28	
1800	Schematic, notes, parts.....	5-29	
1801, 1801A	Schematic, alignment, parts.....	5-30	
1802, 1803	Schematic, voltage	.....5-3	
	Socket layout, alignment.....	5-4	
1802-A, 1803-A, 1807	Schematic	.....5-31	
	Voltage, alignment, socket.....	5-32	
1804, 1805, 1808, 1820, 1826	Schematic, circuit changes.....	5-33	
	Wavetrap data, voltage, align- ment, socket, parts	.....5-34	
1805A, 1808A, 1826A, 1841	Alignment	.....6-20	
	Schematic, voltage	.....6-21	
1806, 1823, 1829	Schematic	.....5-35	
	Alignment, voltage, socket.....	5-36	
1809, 1811, 1833, 1845	Alignment, socket, trimmers, voltage	.....6-22	
	Schematic	.....6-23	
1820	See model 1804		
1821, 1827	Schematic	.....5-37	
	Alignment, voltage, socket, parts.....	5-38	
1822, 1881, 7164	Socket, trimmers, transformer data	.....6-24	
	Schematic	.....6-25	
	Alignment, parts	.....6-26	
1824, 1890	Additional data	.....Changes 7-1, 7-6	
	Schematic	.....6-27	
	Alignment, parts	.....6-28	
	Socket, trimmers, transformer	.....6-29	
	Additional data.....	Changes 7-1	
1825, 1828	Schematic	.....5-39	
	Voltage, alignment, socket, parts	.....5-40	
1825-A	Alignment, voltage, socket, trimmers	.....6-80	
	Schematic	.....6-81	
1826	See model 1804		
1826-A	See model 1805-A		
1827	See model 1821		
1828	See model 1825		
1829	See model 1806		
1830	See model 1824		
1831	See model 1822		
1832	Socket, trimmers, clock unit tests, drive unit test	.....6-32	
	Schematic	.....6-33	
	Alignment, pre-selector data.....	6-34	
1832-A	Schematic	.....6-35	
	Alignment, socket, trimmers, voltage	.....6-36	
1833	See model 1809		
1835	Schematic, voltage	.....7-5	
	Socket, trimmers, alignment.....	7-6	
1840, 1842	Schematic	.....6-37	
	Wave trap data, alignment, voltage	.....6-38	
	Socket, trimmers	.....6-39	
	Additional data.....	Changes 7-15	
1841	See model 1805-A		
1845	See model 1809		
1850, 1851, 1862, 1868, 1870	Schematic	.....5-41	
	Voltage, alignment, socket, parts	.....5-42	
1852, 1859	See model 1711-A		
1854	Schematic	.....5-43	
	Alignment, voltage, socket.....	5-44	
1854A	Schematic, voltage	.....7-7	
	Socket, trimmers, chassis, alignment, parts	.....7-8	
1855	Schematic	.....5-45	
1855A	See model 1804		
1855B	See model 1805		
1855C	See model 1806		
1855D	See model 1807		
1855E	See model 1808		
1855F	See model 1809		
1855G	See model 1810		
1855H	See model 1811		
1855I	See model 1812		
1855J	See model 1813		
1855K	See model 1814		
1855L	See model 1815		
1855M	See model 1816		
1855N	See model 1817		
1855O	See model 1818		
1855P	See model 1819		
1855Q	See model 1820		
1855R	See model 1821		
1855S	See model 1822		
1855T	See model 1823		
1855U	See model 1824		
1855V	See model 1825		
1855W	See model 1826		
1855X	See model 1827		
1855Y	See model 1828		
1855Z	See model 1829		
1856	See model 1830		
1856A	See model 1831		
1856B	See model 1832		
1856C	See model 1833		



[illegible]

SEARS-ROEBUCK & CO.—(Cont.)			RADIOTRON		EARLY COMPLETE PAGE	
MODEL			REVISED PAGE		EARLY COMPLETE PAGE	
4426A, 4526A, 4546A	Alignment, sensitivity, interference data .....	8-26				
4428	Socket, trimmers, chassis .....	8-27				
4428A, 4448A, 4528A, 4548A	See model 4405 .....	7-61				
	Schematic voltage .....	7-61				
4430	Alignment, data, transformer .....	7-62				
4431, 4432, 4435, 4436, 4531	Socket, trimmers, chassis .....	8-5				
	Changes .....	8-5				
4432A (Late)	See model 4405A .....	9-11				
4439, 4449, 4529, 4549	Schematic, voltage, specifications speaker connections .....	9-11				
	Socket, trimmers, chassis .....	9-12				
4430	Alignment, notes .....	9-13				
4431, 4432, 4435, 4436, 4531	See model 4418 .....	9-13				
	Schematic, voltage, specifications .....	9-15				
4433	Alignment, sensitivity, socket, trimmers, chassis .....	9-16				
4437, 4438, 4477, 4478, 4537, 4577	See model 4405A .....	9-17				
	Notes, parts .....	9-17				
4439, 4440, 4455, 4456, 4539	Socket, trimmers, chassis, parts .....	9-18				
4441, 4451	Schematic, voltage, notes .....	9-19				
	Alignment, sensitivity, notes .....	9-20				
	Schematic, voltage, data .....	8-28				
4442, 4443	Socket, trimmers, chassis, alignment, sensitivity .....	8-29				
4444	Schematic, voltage, alignment, sensitivity, interference data .....	8-31				
4445	Socket, trimmers, chassis, notes .....	8-30				
4446, 4447	See model 4409 .....	8-30				
4448	See model 4410 .....	8-30				
4448A (Late)	See model 4405 .....	8-30				
4449	See model 4429 .....	8-33				
4450, 4550	Schematic, voltage, data .....	8-33				
	Socket, trimmers, chassis, sensitivity notes, data .....	8-32				
4451	Alignment, sensitivity, whistle elimination .....	8-34				
4453	See model 4441 .....	8-34				
4455, 4456	See model 4405A .....	8-34				
4459	See model 4439 .....	8-34				
4461, 4462	See model 1983 .....	8-34				
4463	See model 1986 .....	8-34				
4464 (Chassis 100150)	See model 1986 (Chassis 100150) .....	8-34				
4465, 4485, 4565, 4585	Schematic, socket voltage, specifications, speaker connections .....	9-21				
Chassis 100.151	Socket, trimmers, chassis, alignment, sensitivity .....	9-22				
4465, 4485, 4565, 4585	Schematic, voltage, notes .....	8-35				
Chassis 101.410	Distortion elimination, sensitivity data .....	8-36				
4466, 4467, 4469, 4567	Alignment, socket, trimmers, chassis .....	8-37				
	Phono, jack connections, interference data, notes .....	8-38				
4468, 4470, 4490	Schematic, specifications .....	9-23				
	Alignment, sensitivity, voltage .....	9-24				
	Socket, trimmers, chassis .....	9-25				
	Schematic, voltage, data .....	8-39				
	Alignment, sensitivity, notes .....	8-40				
4469	Socket, trimmers, chassis .....	8-41				
4472, 4473, 4533	See model 4466 .....	8-41				
	Schematic, voltage, specifications, socket, trimmers, chassis .....	9-27				
	Alignment, sensitivity, notes, parts .....	9-28				
4477, 4478	See model 4437 .....	8-43				
4481	See model 1986 .....	8-44				
4486, 4586, 4586A	Schematic, voltage, phono, pick-up data, interference data .....	8-42				
	Whistle elimination, data .....	8-44				
	Socket, trimmers, chassis, alignment, sensitivity .....	8-44				
4487	Schematic, changes .....	9-29				
	Changes, notes .....	9-30				
4488, 4588	Data .....	Changes 10-5				
	Schematic, voltage .....	8-45				
	Socket, trimmers, chassis, color code .....	8-46				
	Alignment, sensitivity, dial drive parts .....	8-48				
	AFO notes, page 1 .....	8-49				
	AFO notes, page 2, dial lamp data .....	8-50				
	Interference elimination, phono, pick-up jack data .....	8-51				
	Changes notes .....	8-52				
	Changes schematics .....	8-53				
	Changes .....	8-56				
	Revised alignment, AFO adjustment .....	8-57				
	justment .....	8-57				
	Schematic, voltage .....	8-57				
	Color code .....	8-46				
	Socket, trimmers, chassis .....	8-47				
	Alignment, sensitivity, dial drive parts .....	8-48				
	AFO notes, page 1 .....	8-49				
	AFO notes, page 2, dial drive data .....	8-50				
	Interference elimination, phono, pick-up jack data .....	8-51				
	Changes notes .....	8-52				
	Changes schematics .....	8-53				
	Changes .....	8-56				
	Revised alignment, AFO adjustment .....	8-57				
	justment .....	8-57				
	Schematic, voltage .....	8-57				
	Socket, trimmers, chassis .....	8-58				
	Changes .....	8-56				
	Alignment, AFO adjustment .....	8-57				
	See model 4468 .....	8-59				
	Schematic, voltage, notes, alignment, sensitivity .....	8-60				
	See model 4414 .....	8-61				
	Schematic, voltage, notes .....	8-61				
	Socket, trimmers, parts, alignment, notes .....	8-62				
	Schematic, voltage, notes .....	8-58				
4488B, 4588B	Socket, trimmers, chassis, alignment, parts .....	9-26				
	Data .....	Changes 10-5				
4490	See model 4414 .....	9-26				
4498, 4499, 4593	See model 4501 .....	9-26				
	See model 4502 .....	9-26				
	See model 4419 .....	9-26				
	See model 1989 .....	9-26				
	See model 4421 .....	9-26				
	See model 4409 .....	9-26				
	See model 4404 .....	9-26				
	See model 4422 .....	9-26				
	See model 4426 .....	9-26				
	See model 4426A .....	9-26				
	See model 4428A .....	9-26				
	See model 4405A .....	9-26				
	See model 4429 .....	9-26				
	See model 4431 .....	9-26				
	See model 4422 .....	9-26				
	See model 4472 .....	9-26				
	See model 4437 .....	9-26				
	See model 4439 .....	9-26				
	See model 4409 .....	9-26				
	See model 4422 .....	9-26				
4501, 4503, 4507	See model 4414 .....	9-26				
	See model 4501 .....	9-26				
	See model 4502 .....	9-26				
	See model 4419 .....	9-26				
	See model 1989 .....	9-26				
	See model 4421 .....	9-26				
	See model 4409 .....	9-26				
	See model 4404 .....	9-26				
	See model 4422 .....	9-26				
	See model 4426 .....	9-26				
	See model 4426A .....	9-26				
	See model 4428A .....	9-26				
	See model 4405A .....	9-26				
	See model 4429 .....	9-26				
	See model 4431 .....	9-26				
	See model 4422 .....	9-26				
	See model 4472 .....	9-26				
	See model 4437 .....	9-26				
	See model 4439 .....	9-26				
	See model 4409 .....	9-26				
	See model 4422 .....	9-26				
4502, 4502A, 4504, 4508, 4512, 4513, 4514, Chassis 101.427	Socket, trimmers, chassis, alignment, parts .....	9-26				
	Data .....	Changes 10-5				
4505, 4506	See model 4414 .....	9-26				
4507	See model 4501 .....	9-26				
4508	See model 4502 .....	9-26				
4509	See model 4419 .....	9-26				
4520	See model 1989 .....	9-26				
4521	See model 4421 .....	9-26				
4522, 4523	See model 4409 .....	9-26				
4524	See model 4404 .....	9-26				
4524A	See model 4422 .....	9-26				
4526	See model 4426 .....	9-26				
4526A	See model 4426A .....	9-26				
4528A (Late)	See model 4428A .....	9-26				
4529	See model 4405A .....	9-26				
4531	See model 4429 .....	9-26				
4532	See model 4431 .....	9-26				
4533	See model 4422 .....	9-26				
4537	See model 4472 .....	9-26				
4539	See model 4437 .....	9-26				
4542, 4543	See model 4439 .....	9-26				
4542A	See model 4409 .....	9-26				

SEARS-ROEBUCK & CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
See model 4404			See model 4404		
See model 4426			See model 4426		
See model 4426A			See model 4426A		
See model 4405			See model 4405		
See model 4428A			See model 4428A		
See model 4405A			See model 4405A		
See model 4429			See model 4429		
See model 4450			See model 4450		
See model 4419			See model 4419		
See model 1986			See model 1986		
See model 4465			See model 4465		
Schematic, voltage, speaker connections, transformer		9-31	Schematic, voltage, speaker connections, transformer		9-31
Socket, trimmers, chassis, alignment, changes, sensitivity		9-32	Socket, trimmers, chassis, alignment, changes, sensitivity		9-32
Schematic, voltage		8-63	Schematic, voltage		8-63
Socket, trimmers, alignment, sensitivity		8-64	Socket, trimmers, alignment, sensitivity		8-64
See model 1986 (Colonial)			See model 1986 (Colonial)		
See model 4437			See model 4437		
See model 1986			See model 1986		
See model 4465			See model 4465		
See model 4486			See model 4486		
Schematic, voltage, data		8-65	Schematic, voltage, data		8-65
Socket, trimmers, chassis, notes		8-66	Socket, trimmers, chassis, notes		8-66
Alignment, sensitivity, jack installation		8-67	Alignment, sensitivity, jack installation		8-67
Dial data		8-68	Dial data		8-68
Circuit data		8-69	Circuit data		8-69
Dial data, flash tuning, notes		8-70	Dial data, flash tuning, notes		8-70
Changes		8-74	Changes		8-74
Changes		9-29	Changes		9-29
Changes, notes		9-30	Changes, notes		9-30
Data		10-5	Data		10-5
Schematic		8-71	Schematic		8-71
Socket trimmers, chassis		8-72	Socket trimmers, chassis		8-72
Alignment, sensitivity, notes		8-73	Alignment, sensitivity, notes		8-73
Changes		8-74	Changes		8-74
Data		Changes 10-5	Data		Changes 10-5
See model 4498			See model 4498		
See model 4488A			See model 4488A		
See model 4488B			See model 4488B		
See model 4569			See model 4569		
Schematic, voltage, transformer data, specifications		9-33	Schematic, voltage, transformer data, specifications		9-33
Socket, trimmers, alignment, chassis, sensitivity		9-34	Socket, trimmers, alignment, chassis, sensitivity		9-34
See model 4498			See model 4498		
Schematic, voltage		9-35	Schematic, voltage		9-35
Socket, trimmers, alignment, chassis, sensitivity		9-36	Socket, trimmers, alignment, chassis, sensitivity		9-36
Data		Changes 10-2	Data		Changes 10-2
Data		Changes 10-5	Data		Changes 10-5
Schematic, voltage		8-75	Schematic, voltage		8-75
Socket, trimmers, alignment, sensitivity		8-76	Socket, trimmers, alignment, sensitivity		8-76
Data		Changes 10-2	Data		Changes 10-2
Data		Changes 10-5	Data		Changes 10-5
Schematic, voltage, socket, trimmers, chassis, alignment, sensitivity, notes		8-77	Schematic, voltage, socket, trimmers, chassis, alignment, sensitivity, notes		8-77
Schematic, voltage, socket, trimmers, chassis, alignment		8-78	Schematic, voltage, socket, trimmers, chassis, alignment		8-78
Schematic, voltage, specifications		9-37	Schematic, voltage, specifications		9-37
Socket, trimmers, chassis, alignment, data, sensitivity		9-38	Socket, trimmers, chassis, alignment, data, sensitivity		9-38
Schematic, voltage, socket, trimmers, chassis		10-3	Schematic, voltage, socket, trimmers, chassis		10-3
Alignment, notes		10-4	Alignment, notes		10-4
4544			4544		
4546			4546		
4546A			4546A		
4548			4548		
4548A			4548A		
4548A (Late)			4548A (Late)		
4549			4549		
4550			4550		
4559			4559		
4569			4569		
4565			4565		
4566			4566		
4570			4570		
4571			4571		
4572			4572		
4584			4584		


## SEARS-ROEBUCK

MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	RADIO TRON EARLY COMPLETE PAGE
4681, 4781, Chassis 101.499	Phone and phono. jacks in-stallation, schematic .....10-18 Chassis, antenna, wave-trap data .....10-19 Socket, trimmers, alignment, chassis .....10-20 Schematic, voltage, phonograph installation .....9-59 Socket, trimmers, chassis, alignment, notes sensitivity.9-60 Schematic .....9-61		
4684, Chassis, 101.502	Socket, trimmers, speaker connections .....9-62 Alignment, sensitivity .....9-63 Moto-Matic Tuner adjust-ments, operation .....9-64 Moto-Matic Tuner adjust-ments, operations, concluded 9-65 Voltage, tuner motor data .....9-66 Drive data .....9-67 Switch data .....9-68 Dial mechanism .....9-69 Tuner faults and remedies, Part 1 .....9-70 Tuner faults and remedies, Part 2 .....9-71 Tuner faults and remedies, Part 3 .....9-72 Parts list, concluded .....9-73 Parts list, adjustments, Schematic, adjustments, alignment .....9-80 Alignment procedure, notes .....10-4 See model 4602-3 See model 4622 See model 4613 See model 4604-5 See model 4606-7 See model 4608A See model 4640 See model 4606-7 See model 4608A See model 4640 Schematic, voltage, socket, specifications, notes .....9-75 Socket, trimmers, chassis, alignment, sensitivity, transformer data .....9-76 See model 4664 See model 4667 See model 4610 See model 4761 Schematic, socket, voltage, specifications .....9-77 Phonograph data .....9-78 Socket, trimmers, alignment, chassis, sensitivity .....9-79 See model 4681 See model 4684 Schematic, voltage, wave-trap data, socket .....10-21, 22 Alignment, socket, trimmers, chassis, installation, color code, 10-24 Automatic tuner data, Part 1 10-25 Automatic tuner data, Part 2 10-26 Automatic tuner data, Part 3 10-27 See model 4688 See model 4690 See model 4650 Schematic, voltage .....10-29 Alignment, data .....10-30 Socket, trimmers, chassis .....10-31 Phono. wiring, details .....10-32 See model 4688 Schematic, voltage .....10-33 Schematics, details, data .....10-34		
4688, 4788, 4799 Chassis 100.159			
4700, Chassis 104.235			
4720, 4780			
4722			
4723			
4724			
4726			
4728A			
4740			
4746			
4748A			
4750			
4761, 4771, Chassis 101.490			
4764			
4767, 4777			
4769			
4771			
4776, Chassis 126.200			
4781			
4784			
4786, Chassis 100.196			
4788			
4789			
4790			
4796, Chassis 126.201			
4799			
5356A			
5731, Moto-Matic Tuner for Model 6000, 6001, 6100, 6101, Part 128.15600			
MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	RADIO TRON EARLY COMPLETE PAGE
5731, Moto-Matic Tuner for Adjustments, Part 1 .....10-35 Models 6000, 6001, 6100, Adjustments, Part 2, parts .....10-36 6101, Part 128.15600 6002, 6021, 6031, 6121, Schematic, voltage .....10-37 6131 Chassis 100.195 Socket, trimmers, chassis, alignment .....10-38 Tuner data .....10-88 Parts .....10-39 Schematic, voltage, drive data 10-41 Tuner data .....10-58 Alignment, jacks installation .....10-40 Schematic .....10-42 Socket, trimmers, chassis .....10-43 Schematic, voltage, socket .....10-43 Alignment, notes .....10-6 Socket, trimmers, chassis .....10-42 Schematic, socket, trimmers, drive data, notes .....10-45 Tuner data .....10-58 Alignment .....10-44 Chassis, data .....10-46 Schematic, voltage, socket, trimmers, changes .....10-51 Socket, trimmers, chassis, notes .....10-46 Alignment .....10-10 See model 4632A Schematic, voltage, drive data .....10-47 Alignment, notes .....10-6 Socket, trimmers, chassis .....10-48 Tuner data .....10-58 See model 6008 See model 6002 Schematic, voltage, drive data 10-49 Alignment .....10-6 Socket, trimmers, chassis .....10-50 Alignment, notes .....10-50 Tuner data .....10-58 Schematic, voltage, notes .....10-52 Socket, trimmers, chassis .....10-50 Alignment, notes .....10-6 See model 6003 Schematic, voltage, speaker wiring, motor, pick-up wiring, alignment .....10-53 Motor details, trimmers, chassis wiring, socket .....10-54 See model 6002 See model 6003 Schematic, voltage, color code, data .....10-56 Phone and phono. jacks, drive data, notes .....10-57 Alignment .....10-44 Socket, trimmers, chassis, tuner data .....10-58 Schematic, voltage, socket, drive data, color code 10-59, 60 Alignment, motor data .....10-55 Alignment .....10-44 Tuner data .....10-58 See model 6010 See model 4632A See model 6016 See model 6008 Schematic, voltage, socket, data .....10-61 Alignment .....10-10 Socket, trimmers, chassis .....10-62 Schematic, voltage, socket, trimmers, chassis .....10-65 Alignment .....10-10			
5731, Moto-Matic Tuner for Adjustments, Part 1 .....10-35 Models 6000, 6001, 6100, Adjustments, Part 2, parts .....10-36 6101, Part 128.15600 6002, 6021, 6031, 6121, Schematic, voltage .....10-37 6131 Chassis 100.195 Socket, trimmers, chassis, alignment .....10-38 Tuner data .....10-88 Parts .....10-39 Schematic, voltage, drive data 10-41 Tuner data .....10-58 Alignment, jacks installation .....10-40 Schematic .....10-42 Socket, trimmers, chassis .....10-43 Schematic, voltage, socket .....10-43 Alignment, notes .....10-6 Socket, trimmers, chassis .....10-42 Schematic, socket, trimmers, drive data, notes .....10-45 Tuner data .....10-58 Alignment .....10-44 Chassis, data .....10-46 Schematic, voltage, socket, trimmers, changes .....10-51 Socket, trimmers, chassis, notes .....10-46 Alignment .....10-10 See model 4632A Schematic, voltage, drive data .....10-47 Alignment, notes .....10-6 Socket, trimmers, chassis .....10-48 Tuner data .....10-58 See model 6008 See model 6002 Schematic, voltage, drive data 10-49 Alignment .....10-6 Socket, trimmers, chassis .....10-50 Alignment, notes .....10-50 Tuner data .....10-58 Schematic, voltage, notes .....10-52 Socket, trimmers, chassis .....10-50 Alignment, notes .....10-6 See model 6003 Schematic, voltage, speaker wiring, motor, pick-up wiring, alignment .....10-53 Motor details, trimmers, chassis wiring, socket .....10-54 See model 6002 See model 6003 Schematic, voltage, color code, data .....10-56 Phone and phono. jacks, drive data, notes .....10-57 Alignment .....10-44 Socket, trimmers, chassis, tuner data .....10-58 Schematic, voltage, socket, drive data, color code 10-59, 60 Alignment, motor data .....10-55 Alignment .....10-44 Tuner data .....10-58 See model 6010 See model 4632A See model 6016 See model 6008 Schematic, voltage, socket, data .....10-61 Alignment .....10-10 Socket, trimmers, chassis .....10-62 Schematic, voltage, socket, trimmers, chassis .....10-65 Alignment .....10-10			
6003, 6004, 6024, 6034, 6134, 6134, Chassis 101.510			
6005, 6071, 6076, 6171, 6176, Chassis 101.507			
6008, 6009, 6018, 6019, 6048, 6049, 6068, 6069, 6148, 6168, Chassis 101.524			
6010, 6040, Chassis 101.519			
6014, 6015, 6016, 6017, 6046, 6047, 6146, Chassis 101.512			
6018, 6019			
6021, 6022, 6122, 6132, Chassis 101.509			
6023, 6123, Chassis 101.506			
6024, 6028, Chassis 126.204			
6031			
6034			
6036, 6136, Chassis 101.511			
6038, 6138, Chassis 101.517			
6040, 6045, 6046, 6047, 6048, 6049, 6052, 6053, 101.525			
6054, 6055, Chassis 101.532			

RADIOTRON  
EARLY COMPLETE  
PAGESEARS-ROEBUCK & CO.—(Cont.)  
REVISED  
PAGEMODEL  
SEARS-ROEBUCK & CO.—(Cont.)  
REVISED  
PAGEMODEL  
SEARS-ROEBUCK & CO.—(Cont.)  
REVISED  
PAGERADIOTRON  
EARLY COMPLETE  
PAGEREVISED  
PAGESEARS-ROEBUCK & CO.—(Cont.)  
REVISED  
PAGEMODEL  
SEARS-ROEBUCK & CO.—(Cont.)  
REVISED  
PAGE

MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE	MODEL	SEARS-ROEBUCK & CO.—(Cont.)	REVISED PAGE
6054, 6055, Chassis 101.532	Tuner data .....	10-81	6140, Chassis 101.534, 6152, 6153, Chassis 101.537	Socket, trimmers, chassis .....	10-84
6064	See model 4632A		Alignment .....	10-44	
6068, 6069	See model 6008		Tuner data 4632A .....	10-58	
6070, 6170, Chassis 100.189	Schematic, voltage, coils .....	10-63	See model 6016 .....		
	Socket, trimmers, chassis, alignment .....	10-64	See model 6018 .....		
6071, 6076	See model 6005		See model 6040 .....		
6072, 6077, 6172, Chas- sis 101.513	Schematic, voltage .....	10-66	Schematic, voltage, switches, socket, coils .....	10-85, 86	
	Alignment, notes .....	10-6	Parts list .....	10-89	
6073, 6173, Chassis 101.528	Tuner data .....	10-58	Alignment, trimmers .....	10-87	
	Socket, trimmers, chassis .....	10-54	Tuner data, drive data .....	10-88	
6074, 6079, Chassis 101.515	Schematic, voltage, drive data .....	10-71	See model 4612A .....		
	Alignment .....	10-44	See model 4632A .....		
6077	Socket, trimmers, chassis .....	10-84	See model 6008 .....		
6079	Tuner .....	10-88	See model 6070 .....		
6100, Chassis 101.495	See model 6073		See model 6005 .....		
	See model 6074		See model 6072 .....		
	Schematic, voltage, color code 10-69		See model 6073 .....		
	Socket, trimmers, chassis, alignment .....	10-70	Schematic, voltage, socket, trimmers, alignment .....	10-91	
	"Moto-Matic" Tuner details, schematic .....	10-34	Schematic, notes .....	10-89	
	"Moto-Matic" adjustments, Part 1 .....	10-35	Operating and set-up pro- cedure notes, parts .....	10-90	
	"Moto-Matic" adjustments, Part 2 .....	10-36	Schematic changes, notes .....	10-89	
6101, Chassis 101.496	Schematic, voltage, color code .....	10-72	See Sentinel 118 .....		
	Socket, trimmers, chassis, an- tenna coil, trimmers .....	10-68	See Sentinel 518 .....		
	Alignment .....	10-70	Schematic, socket, alignment .....	5-51	
	"Moto-Matic" Tuner details, schematic .....	10-34	Voltage, parts, resistance test .....	5-52	
	"Moto-Matic" adjustments, Part 1 .....	10-35	Resistance .....	5-53	
	"Moto-Matic" adjustments, Part 2 .....	10-36	Schematic, socket, trimmer .....	5-55	
6102, 6102A, 6103, 6103A, 6105, 6105A, Chassis 101.526, 101.526-1	Schematic, voltage, alignment, tuner changes .....	10-73	Resistance test data, voltage, socket .....	5-56	
6104, Chassis 126.203	Socket, chassis .....	10-74	See model 1597 .....		
	Schematic, voltage, data .....	10-75	See Sentinel 570 .....		
	Tuner assembly, data .....	10-76	See model 1700 .....		
	Chassis wiring, socket, trim- mers, alignment .....	10-77	See model 1703 .....		
6110, 6111, Chassis 101.508	Schematic, voltage .....	10-78	See model 1720 .....		
	Socket, trimmers, chassis, alignment .....	10-82	Schematic, resistance test .....	5-57	
6112, 6113, 6118, Chas- sis 101.521	Schematic, voltage, tuner, socket, chassis .....	10-79	See model 1704 .....		
6114, 6116, Chassis 101.522	Schematic, voltage, chassis, socket, alignment, tuner .....	10-80	Schematic .....	4-88	
6118	See model 6112		Voltage, trimmers, parts location, socket .....	4-84	
6121	See model 6002		See model 1711 .....		
6122	See model 6022		See model 1711-A .....		
6123	See model 6023		Schematic, alignment, parts .....	5-63	
6124	See model 6003		See Sentinel 5000, 5100 .....		
6125, Chassis 101.527	See model 6003		Schematic, parts, service notes 5-58		
	Schematic, voltage, tuner .....	10-81	Schematic, voltage .....	5-59	
	Alignment, notes .....	10-6	Alignment, parts, installation notes .....	5-60	
	Socket, trimmers, chassis, notes .....	10-74	Schematic, voltage .....	5-61	
6131	See model 6002		Socket, chassis, parts .....	5-62	
6132	See model 6022		Schematic, notes, parts .....	5-64	
6134	See model 6003		Schematic, alignment, parts .....	5-65	
6136	See model 6036		Additional data .....	Changes 7-5	
6138	See model 6038		Schematic, parts, service notes 5-66		
6140, Chassis 101.534 6152, 6153, Chassis 101.537	Schematic, voltage, color code, notes .....	10-82	Schematic changes, socket .....	7-63	
	Phone and phono. jacks data .....	10-83	Schematic changes, socket .....	7-63	
			Data .....	Changes 10-5	
			Schematic .....	5-67	
			Alignment, voltage, socket, parts .....	5-68	
			See model 7126 .....		
			See model 7124 .....		
			See model 7127, Late .....		
			See model 1728-A .....		
			Schematic, socket, alignment .....	7-64	
			See model 1727, Late .....		
			See model 1743, 1743A .....		
			Schematic, socket, trimmers, voltage .....	6-50	

# MAKE SERVICING EASY

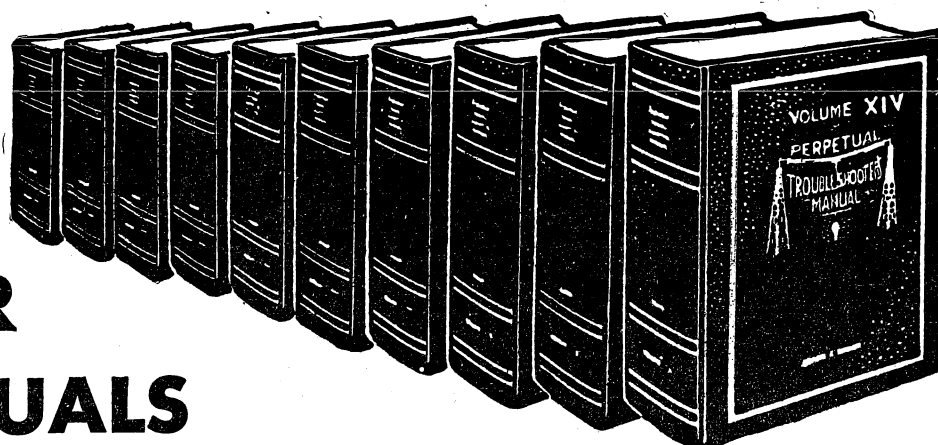

## RIDER MANUALS

The greatest collection of servicing data ever assembled. No serviceman can anticipate the year, make and model of the next set that will come to his bench. For this reason you **must** have the volume of Rider Manuals that contains the servicing information on that particular set. Benefit from the **complete**

servicing information that only Rider Manuals can give you: Data on alignment, I-F peaks, operating voltages, parts lists and parts values, voltage ratings of condensers, wattage ratings of resistors, coil resistance data, gain data, and all the other information that is vital for speedy and accurate trouble-shooting.

**VOL. XIV.** This newest Rider Manual contains servicing data on the receivers that were among the last produced in April, 1942. Every effort was made in the compilation of the data in this volume to bring them up to date for all manufacturers. This addition of Rider's Volume XIV makes available to the radio servicing industry more than 19,000 pages of authentic servicing information.

**1,376 pages, Net Price \$12.50**

**VOL. XIII.** Contains servicing data on receivers manufactured during the latter part of 1941 and early 1942. Cumulative index for Volumes XI, XII, and XIII. ....

**1,672 pages, Net Price \$12.50**

**VOL. XII.** Covers receivers manufactured up to April 1941 ..... Clarified schematics give breakdowns of complicated r-f and a-f switching circuits. ....

**1,648 pages, Net Price \$12.50**

**VOL. XI.** Covers receivers manufactured up to June 1940. Includes vest pocket manual containing push-button frequency ranges of all automatically tuned receivers and other handy servicing data.

**1,652 pages, Net Price \$12.50**

**VOL. X.** Complete information on receivers manufactured up to August, 1939. Includes a separate 188-page index covering Volume X and all preceding volumes. ....

**1,664 pages, Net Price \$12.50**

**VOL. IX.** Contains installation and servicing instructions on 1889 models manufactured up to October, 1938.

**1,672 pages, Net Price \$12.50**

**VOL. VIII.** Receivers manufactured up to October, 1937 will be found in this volume. Contains installation and servicing instructions on many types of intercommunication systems.

**1,650 pages, Net Price \$12.50**

**VOL. VII.** In this volume will be found sets manufactured up to October, 1936, together with data on older receivers hitherto unavailable.

**1,600 pages, Net Price \$12.50**

**VOL. VI.** In this volume will be found sets manufactured up to November, 1935. Data on more than 950 models.


**1,240 pages, Net Price \$9.50**

**Vols. I, II, III, IV, and V out of print—no longer available**

**RIDER'S MANUALS HAVE more schematics . . . more I.F. peaks . . . more alignment data . . . more circuit descriptions. . . . MORE EVERYTHING THAN ANY OTHER MANUALS.**

### ABRIDGED MANUAL

Volumes I-V

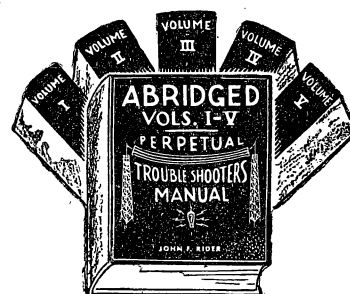

The servicing information you need to service the old receivers will be found in the Abridged Manual, Volumes I-V. It is a compilation of the most widely distributed receivers released after 1929 that formerly appeared in Volumes I-V.

In order to select the proper receivers for inclusion in the Abridged Manual, all the manufacturers who were responsible for the sale of the greatest number of sets between 1930 and 1935 were contacted and information was obtained as to the most widely distributed receivers. The Abridged Manual was then compiled.

**2,000 pages . . . Net Price \$15.00**

## SEARS-ROEBUCK &amp; CO.—(Cont.)

RADIOTRON  
EARLY COMPLETE  
PAGEREVISED  
PAGE

MODEL

7148	Schematic, voltage, socket, trimmers, alignment	8-79
7144	Schematic, socket, alignment	7-65
7150	Schematic, socket, alignment	7-67
7152	Notes, change	7-66
7153	Schematic, socket, voltage, alignment	10-92
7154	Schematic, socket, trimmers, alignment	7-9
7155	Schematic, socket	7-86
7157	Schematic, socket, alignment	7-87
7158	See model 1869X	
7164	Schematic, trimmers, socket, alignment	7-68
7165, 7166X	See model 1822	
7166, 7166X	Schematic, socket	7-65
7166A	Schematic, socket	7-63
7167	Schematic, socket, voltage	7-69
7168	Schematic, voltage, alignment, parts	7-70
7170, 7170A	Schematic, voltage, data	7-69
7171	Schematic, socket	10-93
7172	Schematic, voltage, socket, trimmers	10-95
7172X	Chassis wiring	10-94
7173, 7183	Alignment	10-96
7176	Schematic, socket, alignment	10-97
7177	Schematic, alignment	8-80
7181, 7182	Schematic, voltage, socket, alignment	9-81
7211, Chassis 110.7211	Schematic, socket, trimmers, alignment	9-81
7212, 7212A, Chassis 110.7212	Schematic, socket, trimmers, alignment	10-100
7213, Chassis 110.7213	Schematic, socket, trimmers	10-98
7214, Chassis 110.7214	Schematic, socket, trimmers	10-99
7215, Chassis 110.7215	Schematic, voltage	9-82
7220, Chassis 110.7220	Alignment	9-83
7221, Chassis 126.202	Schematic, socket, trimmers, alignment	9-84
7225, Chassis 110.255	Schematic, voltage, drive data, specifications	10-105, 106
7226, Chassis 110.880	Socket, trimmers, alignment, phono, data	10-107
	Chassis wiring	10-108
	Record changer assembly	10-109
	Schematic, socket, trimmers, voltage, alignment	10-111
	Tuner data	10-81
	Alignment	10-64
	Schematic, voltage, alignment	10-112
	Socket, trimmers, alignment, Part 2	10-104
100.150 Chassis	See model 1986	
100.151 Chassis	See model 4465	
100.157 Chassis	See model 4613	
100.159 Chassis	See model 4688	
100.179 Chassis	See model 4622	
100.189 Chassis	See model 6070	
100.195 Chassis	See model 6002	
100.196 Chassis	See model 4786	
100.198 Chassis	See model 6157	
101.410 Chassis	See model 4465	
101.458 Chassis	See model 4600	
101.472A Chassis	See model 4608A	
101.473 Chassis	See model 4606-7	
101.476 Chassis	See model 4640	
101.478 Chassis	See model 4619	
101.479 Chassis	See model 4680	
101.480 Chassis	See model 4664	
101.482 Chassis	See model 4610	
101.487 Chassis	See model 4611	

## SEARS-ROEBUCK &amp; CO.—(Cont.)

REVISED  
PAGERADIOTRON  
EARLY COMPLETE  
PAGE

MODEL

101.490 Chassis	See model 4761	
101.495 Chassis	See model 6100	
101.496 Chassis	See model 6101	
101.497 Chassis	See model 4614	
101.498 Chassis	See model 4667	
101.499 Chassis	See model 4681	
101.502 Chassis	See model 4684	
101.504 Chassis	See model 4644A	
101.505, 101.505X Chassis	See model 4632A	
101.506	See model 6028	
101.507	See model 6005	
101.508 Chassis	See model 6110	
101.509 Chassis	See model 6022	
101.510 Chassis	See model 6003	
101.511 Chassis	See model 6036	
101.512 Chassis	See model 6016	
101.513 Chassis	See model 6072	
101.515 Chassis	See model 6074	
101.517 Chassis	See model 6038	
101.519 Chassis	See model 6010	
101.521 Chassis	See model 6112	
101.522 Chassis	See model 6114	
101.524 Chassis	See model 6008	
101.525 Chassis	See model 6052	
101.526, 101.526-1 Chassis	See model 6102	
101.527 Chassis	See model 6125	
101.528 Chassis	See model 6073	
101.532 Chassis	See model 6054	
101.533 Chassis	See model 4612A	
101.534 Chassis	See model 6140	
101.537 Chassis	See model 6152	
103.AR.166 Chassis	See model 4668	
104.235 Chassis	See model 4700	
109.216 Chassis	See model 6195	
110.255 Chassis	See model 7225	
110.880 Chassis	See model 7226	
110.7211 Chassis	See model 7211	
110.7212 Chassis	See model 7212	
110.7213 Chassis	See model 7213	
110.7214 Chassis	See model 7214	
110.7215 Chassis	See model 7215	
110.7220 Chassis	See model 7220	
113.972 Chassis	See model 3972	
126.200 Chassis	See model 4776	
126.201 Chassis	See model 4796	
126.202 Chassis	See model 7221	
126.203 Chassis	See model 6104	
126.204 Chassis	See model 6028	
134.802, 134.802-1 Chassis	See model 6226	

## SENTINEL RADIO CORP.

"Automatic Tune" Wheel	Assembly, details, notes	10-1
Dial	Installation, details, parts	10-2
Push-Button Dial	Assembly, instructions, parts	10-12
6A	Schematic, voltage, trimmers, alignment, parts	8-1, 8-2
8, 9	Schematic, socket voltage	8-1
10M	Schematic, voltage, alignment, parts	8-5
10MF	Schematic, voltage, alignment, parts	8-3, 8-4
11, 12, 14, 16 (104)	Schematic, socket, voltage	1-1
11M	Schematic, voltage, alignment, parts	8-6
14A	Schematic, parts, trimmers	9-1, 2
19A	Alignment, socket, voltage	9-5
20A	Schematic, voltage, alignment, trimmers, parts	8-7
30A	Schematic, voltage, trimmers, alignment	7-1
31, 38	Schematic, alignment, voltage, parts	8-8
31B	Schematic, voltage, trimmers	2-8
32B	Alignment, parts	6-1
32B	Schematic, alignment, parts	6-2
33B	Schematic, alignment, trimmers, parts	8-9
	mer, parts	8-10

\*634

2105

2106

2116

## SENTINEL RADIO CORP.—(Cont.)

RADIOTRON  
EARLY COMPLETE  
PAGE

MODEL	REVISOR	PAGE
34B	Schematic, trimmers, alignment, parts, changes, voltage	8-11
35-B	Schematic, trimmers	6-3
36L	Alignment, parts	6-4
37B	Schematic, voltage, alignment, trimmers, parts	8-12
38B	Schematic, alignment, parts, voltage	8-13
39B	Schematic, trimmers, alignment, parts	8-14
40B	Schematic, trimmers, alignment, parts, changes, parts	8-15
44A	Schematic, parts, trimmers, voltage, parts	8-16
46A	Schematic, parts, trimmers, voltage, parts	9-7, 8
47A	Alignment, parts, trimmers, voltage, parts	9-9, 10
48A	Trimmers, alignment, parts, voltage, alignment	9-11
49B	Schematic, voltage, alignment, parts	7-3, 7-4
50B	Schematic, voltage, alignment, parts	7-2
52A	Schematic, voltage, alignment, parts	8-17
53A	Schematic, voltage, alignment, parts	8-18
54A	Schematic, voltage, alignment, parts	8-19, 8-20
55U	Schematic, voltage, alignment, parts	8-21
56U	Schematic, voltage, alignment, parts	8-22
60B	Schematic, voltage, alignment, parts	8-23
63B	Schematic, voltage, alignment, parts	8-24
65B	Schematic, voltage, alignment, parts	10-3
66B	Schematic, voltage, alignment, parts	10-4
67L	Schematic, voltage, alignment, parts	8-25
68B, 68BE	Schematic, trimmers, voltage, alignment, parts	8-26
70A	Schematic, trimmers, voltage, alignment, parts	8-27
71U	Schematic, parts, socket, voltage, trimmers	9-3, 4
72A, 72AE	Schematic, voltage, alignment, parts, socket, trimmers	9-5
73B	Schematic, voltage, alignment, parts, socket, trimmers	10-5
74A, 74AE	Schematic, voltage, alignment, parts, socket, trimmers	10-6
76A	Schematic, voltage, alignment, parts, socket, trimmers	10-7
78B, 78BE	Schematic, voltage, alignment, parts, socket, trimmers	10-8
	Schematic, voltage, alignment, parts, socket, trimmers	9-15
	Schematic, voltage, alignment, parts, socket, trimmers	9-16
	Schematic, voltage, alignment, parts, socket, trimmers	9-17
	Schematic, voltage, alignment, parts, socket, trimmers	9-18
	Schematic, voltage, alignment, parts, socket, trimmers	9-19
	Schematic, voltage, alignment, parts, socket, trimmers	10-9
	Schematic, voltage, alignment, parts, socket, trimmers	10-10
	Schematic, voltage, alignment, parts, socket, trimmers	10-1
	Schematic, voltage, alignment, parts, socket, trimmers	10-2
	Schematic, voltage, alignment, parts, socket, trimmers	10-12

MODEL	REVISOR	PAGE
80B	Schematic, voltage, socket	10-11
82A, 82AE	Alignment, trimmers, chassis	10-8
	Schematic, parts, socket, voltage	9-21
	Socket, trimmers, chassis, alignment	9-22
	"Automatic Tune" Wheel assembly, details	10-1
	"Automatic Tune" Wheel in-stallations, details	10-2
83UE	Push-Button Dial assembly, instructions, parts	10-12
85, 85UE	Schematic, voltage, socket	10-13
86AE	Alignment, trimmers, chassis	10-14
	Schematic, parts, socket, voltage, alignment	9-20
	Schematic, voltage, socket	10-15
	Alignment, trimmers, chassis	10-16
	"Automatic Tune" Wheel assembly, details	10-1
	"Automatic Tune" Wheel in-stallations, details	10-2
87AE	Push-Button Dial assembly, instructions, parts	10-12
88BE	Schematic, voltage, socket	10-17
90B	Alignment, trimmers, chassis	10-18
	Schematic, voltage, socket	10-19
	Alignment, trimmers, chassis	10-20
	Schematic, parts, socket, voltage	9-23
91B	Socket, trimmer, chassis, alignment	9-24
	Schematic, voltage, socket, alignment	10-21
	"Automatic Tune" Wheel assembly, details, notes	10-1
	"Automatic Tune" Wheel in-stallations, details	10-2
92AE	Push-Button Dial assembly, instructions, parts	10-12
93L	Schematic, voltage, socket	10-22
	Alignment, trimmers, chassis	10-23
	Schematic, parts, socket, voltage	9-25
95B	Socket trimmers, chassis, alignment, 32-volt interference data	9-26
	Schematic, voltage, socket	10-24
	Alignment, trimmers, chassis	10-23
	"Automatic Tune" Wheel assembly, details, notes	10-1
	"Automatic Tune" Wheel in-stallations, details	10-2
96BE	Push-Button Dial assembly, instructions, parts	10-12
97L	Schematic, voltage, socket	10-25
	Alignment, trimmers, chassis	10-26
	Schematic, parts, socket, voltage	9-27
98AE	Socket, trimmers, chassis, alignment	9-28
99AE	32-volt interference data	9-26
	Schematic, voltage, socket	10-27
	Alignment, trimmers, chassis	10-28
	Schematic, voltage, socket	10-29
	Trimmers, chassis	10-30
100X	Alignment, parts, socket	10-31
	Schematic, parts, socket, voltage	9-29
103-A	Socket, trimmers, chassis, alignment	9-30
104 Chassis	See model 11	
106A	Schematic, voltage, socket	10-32
	Trimmers, chassis	10-26
	Alignment	10-33
106-B	Schematic	1-2
107AE	Schematic, voltage, socket	10-34
	Alignment	10-33
	Tuner data	10-35
	Trimmers, chassis	10-36

\*628

3125



[illegible]

EARLY PAGE	RADIOTRON	COMPLETE	PAGE
1	2	3	4
5	6	7	8
9	10	11	12
13	14	15	16
17	18	19	20
21	22	23	24
25	26	27	28
29	30	31	32
33	34	35	36
37	38	39	40
41	42	43	44
45	46	47	48
49	50	51	52
53	54	55	56
57	58	59	60
61	62	63	64
65	66	67	68
69	70	71	72
73	74	75	76
77	78	79	80
81	82	83	84
85	86	87	88
89	90	91	92
93	94	95	96
97	98	99	100

MODEL	SENTINEL RADIO CORP.—(Cont.)	REvised PAGE
55500	Schematic .....	5-25
	Voltage, alignment, parts .....	5-26
56000	Socket layout.....Changes	7-7
	Schematic, voltage, alignment, socket .....	6-7
57000-B	Schematic, socket, voltage, alignment .....	6-12
57000, 5721	Schematic, voltage .....	5-27
	Alignment, parts list .....	5-28
55900	Schematic, voltage, trimmers, alignment .....	7-11, 7-12
61301, 6102	Schematic .....	5-29
	Service notes, voltage, align- ment .....	5-80
62000, 6234, 6241	Parts list .....	5-81
6315, 6317, 6321	Schematic .....	5-84
	Schematic .....	5-82
	Voltage, alignment .....	5-83
67000	Parts list .....	5-81
	Schematic, voltage, trimmers, alignment .....	7-7
68000	Schematic, voltage, trimmers, alignment .....	7-8
69000	Schematic, voltage, trimmers, alignment, parts .....	8-29, 8-30
71000	Schematic, voltage, trimmers .....	7-9
	Alignment .....	7-10
71000-B	Schematic, voltage, trimmers .....	7-13, 7-14
7200	Alignment .....	7-15
	Schematic, voltage, trimmers, alignment, parts .....	8-32
7200-B	Schematic, socket .....	6-9, 6-10
	Alignment, voltage .....	6-11
77000, 7732, 7741	Schematic .....	5-85
	Voltage, alignment, parts .....	5-86
8100B	Socket layout .....	Changes 7-7
	Schematic, voltage .....	7-17, 7-18
8200-B	Alignment, trimmers .....	7-16
	Schematic .....	6-13, 6-14
	Alignment .....	6-15
	Voltage, parts, trimmers .....	6-16
9100	Schematic, voltage, trimmers, battery data .....	7-19, 7-20
	Alignment .....	7-21

**SETOHELL-CARLSON, INC.**

PA 13 Amplifier	Schematic	8-1
PA 25 Amplifier	Schematic	8-1
555 Portable	Schematic, socket, trimmers	Misc. 10-8
PA 115 Amplifier	Schematic	8-2
3832	Schematic	9-1
400	Schematic	9-2
402	Schematic	9-2
3832	Schematic	9-2
322	Schematic	9-1

Shamrock "38-29"	Schematic	Misc. 4-10
------------------	-----------	------------

5 Kompak	Schematic	7-1
36-Q	Schematic	Misc. 9-3
350-AW, 97-0	Schematic, socket	8-1
48	Schematic, socket, alignment	8-2
48-A	Schematic, socket	7-1
65	Schematic, socket	8-1
65	Schematic, socket	7-2
07	Schematic, socket	7-2
75 Auto	Schematic, socket, alignment	8-2

**SILVER KING**

Bearcat	See model 787	<b>SILVER-MARSHALL, INC.</b>
Bearcat Midget	See model 37	
Broadcast-Long Wave	See model 773	

See model 737

**Bearcat Midget** See model 757  
**Broadcast-Long Wave** See model 37  
**Broadcast-Long Wave** See model 773

**SILVER-MARSHALL, INC.—(Cont.)** **REVISED**

MODEL	REVISION	PAGE	REVISION	PAGE	REVISION	PAGE
Little Red Rooster						
Long-Wave Receiver						
Sergeant Raymond 7						
SW Converter						
Superhet Converter						
Time Signal Amplifier						
A						
B						
C						
O						
C w/AVO						
D						
E						
F						
G						
H						
I						
J						
K						
Q DeLuxe						
"Q" Type 1						
"Q" Type 2						
"Q" Type 3						
R						
V						
W						
X						
Y						
Z						
DeLuxe						
Z-10						
Z-11						
Z-12						
Z-86						

## RADIOTRON

EARLY COMPLETE PAGE	RADIOTECH PAGE
	2169
*542-C	2163
542-B	2164
542-K	2165
542-L	2168
*542-D	2167
*542-O	2163
542-M	2168
542-G	2169
542-P	2173
542-O	2172
542-R	2175
542-Q	2174
	2176
	2177
*597	2127
*598	2129
*598	2129
*599	2130
*599	2130
*540	2128
*541	2131
*542	2132
*542	2132
*543	2133
*542-A	2134
*597	2127
*526	2178
*527	2178
*527	2178
*749	2136
*714	2135
*749	2136
*714	2135
*714	2136
*749	2136
*750	2137
*750	2137
*751	2138
*716	2140
*529	2145
*717	2141
*717	2141
*717	2141
542-F-1	2147
*718-A	2142
*718	2143
*718	2143
*718	2143
*528	2144
*529	2145
*530	2146
542-F-1	2147
*531	2148
*531	2148
*532	2149
*532	2150



# SPARKS WITHINGTON

MODEL	SPARKS WITHINGTON CO.—(Cont.)	REVISID PAGE	RADIOTRON EARLY COMPLETE PAGE
6-15, 6-26	Schematic	1-3	2233
AC-7, AC-62, AC-68	Schematic, socket, voltage	1-5	2209
9	See model 5		
9-A, 600-A, 610-A, 620-A	Schematic, socket, voltage	2-2	2211
9X, 13, 14, 14-A, 15X, 620X	Schematic	2-7	2215
10	Voltage, chassis, data	2-6	2216
12	Alignment data	4-1	
14, 14A	Chassis, voltage, data	2-3	2213
16	Schematic	2-4	2212
16X	Schematic, chassis, voltage	2-5	2214
16-AW, 26-AW (SW Rec.)	See model 9X		
17, 18, 28X, 111X, 750-A, 750X, 870-A, 870X	Chassis, voltage, data	2-8	2218
AR-19, 19-A	Schematic	2-9	2217
25, 26	See model 9X		
26 AW (SW Rec.)	Schematic, voltage	2-11	2219
26-AW, Revised #2	Additional data	Changes 7-4	2220
27, 27-A, 28	Schematic	4-2	2221
27X	Voltage, chassis, trimmers	4-3	2222
28	Alignment data	4-1	2223
28X, 30A, 80B,	Schematic	1-1	2224
30-A, 80-B	Chassis view	2-12	2226
31, 32	Schematic	2-14	2227
33	Schematic—See model 16-AW (SW Rec.)	2-15	
38-A, 88-B	Schematic	2-16	2228
34	Chassis, voltage	3-1	2231
35	Schematic	3-2	2230
36	Alignment data	4-1	2232
39	Schematic	4-4	2233
40, 40-A	Voltage, socket, trimmers	4-5	
41	Data	Changes 7-13	
41-A, 43	Additional data	Changes 7-4	
41A	See model 17		
42	Chassis, voltage	2-17	2235
43	Schematic	2-18	2234
45	Service notes, part 1	2-19	2236
	Service notes, part 2	2-20	2237
	Parts list	2-21	2239
	Chassis views	2-22	2238
	Alignment data	4-1	
	Schematic	1-4	2240
	Chassis views	2-23	2241
	Schematic	4-7	
	Voltage, notes, socket	4-8	
	Schematic, voltage, resistance	7-1	
	Trimmers, alignment	7-2	
	Schematic	8-3	
	Voltage, battery and assembly connections, notes	3-4	
	Alignment data	4-1	
	Service data	2-24	
	Service data, continued	2-25	
	Service data, concluded	2-26	
	Chassis views	2-27	
	Schematic	3-5	
	Chassis layout, voltage	3-6	
	I.F. Peak	Changes 7-8	
	Schematic, voltage, resistance data	4-9	
	Changes	7-8	
	Trimmers, alignment	7-2	
	Schematic	1-4	
	Schematic, voltage, socket	2-30	
	Alignment, trimmers	7-3	
	Schematic, socket, voltage	2-31	
	Alignment, trimmers	7-3	
	Alignment data	4-1	
	Trimmers, additional alignment	7-3	
	Schematic, voltage	8-8	
	Schematic, voltage	8-8	
	Voltage	4-8	
	Schematic, changes	4-10	
	Alignment, trimmers	7-3	
	Schematic	2-32	
	Chassis, voltage, data	2-33	
	Schematic, parts, voltage, resistance, trimmers	9-1	
	Schematic	1-5	
	Chassis	1-1	
	Schematic, socket, voltage	2-12	
	Service data	2-85	
	Schematic	5-1	
	Voltage, chassis view	5-2	
	Alignment data	5-3	
	Voltage, chassis layout	3-8	
	Schematic	3-7	
	Alignment data	4-1	
	Schematic	2-36	
	Alignment, trimmers	7-8	
	Schematic	2-37	
	Voltage, chassis, data	2-38	
	Schematic	5-4	
	Alignment data	5-3	
	Voltage, chassis view	5-5	
	Additional data	Changes 7-14	
	Schematic, parts	6-1	
	Voltage, socket, trimmers	6-2	
	Schematic, socket, voltage	2-39	
	Additional data	Changes 7-4	
	Schematic, voltage	4-11	
	Changes	Changes 7-15	
	See model AC-7		
	Schematic	5-7	
	Voltage, chassis view	5-8	
	Alignment data	5-9	
	Additional data	Changes 7-8	
	Note	5-7	
	Alignment data	5-9	
	Schematic	5-11	
	Alignment data	5-10	
	Voltage, chassis view	5-12	
	Data	Changes 7-13	
	Schematic, voltage	1-7	
	Schematic, parts	6-3	
	Voltage, socket, trimmers	6-4	
	Schematic, voltage, resistance data	4-12	
	Trimmers, alignment	7-2	
	Schematic, voltage, resistance data	4-13	
	Trimmers, alignment	7-2	
	Schematic, trimmers	7-4	
	Voltage, alignment	7-6	
	Schematic, trimmers, parts	7-5	
	Voltage, socket, trimmers, alignment	7-6	
	Data	Changes 7-13	
	Schematic, voltage, resistance data	4-14	
	Schematic	5-13	
	Voltage, notes	5-14	
	Alignment	8-2	
	Schematic, voltage, socket, trimmers, changes, parts	8-1	
	Alignment	8-2	
	Schematic	7-7	
	Voltage, resistance, socket, trimmers, speaker wiring	7-8	
	See model 70		
	Schematic, voltage, resistance data	4-16	
	See model 69		
	Schematic	5-15	
	Voltage, chassis view, notes	5-16	
	Alignment data	5-17	
	Trimmer locations, frequency tables	5-18	
	Additional data	Changes 7-4	
	Data	Changes 7-13	
	Schematic, voltage, resistance data	4-16	
	Schematic, socket, voltage, resistance	7-18	
	See model 69		
	Schematic	5-15	
	Voltage, chassis view, notes	5-16	
	Alignment data	5-17	
	Trimmer locations, frequency tables	5-18	
	Additional data	Changes 7-4	
	Data	Changes 7-13	
	Schematic, voltage, resistance data	4-16	
	Schematic, socket, voltage, resistance	7-18	

SPARKS WITHINGTON CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
81-A	Additional data	Changes 7-14			
81-X	Data	Changes 7-13			
82	Schematic, voltage, resistance	4-17			
82-X	Data	Changes 7-13			
83, 84	See model 80				
85-X	Schematic	5-15			
	Voltage, chassis view, notes	5-16			
	Alignment data	5-17			
	Trimmer locations, frequency	5-18			
	tables				
	Phonograph data, part 1	7-9			
	Phonograph data, part 2	7-10			
85-XS, 86-X	See model 80				
89	See model 69				
89-A	Schematic, voltage	1-7			
99	Ensemble wiring	1-10			
101	Schematic	1-11			
	Voltage, assembly wiring	4-18			
	Schematic	4-19			
103, 578	Assembly wiring, voltage, chassis	2-40			
	Schematic	2-41			
104, 135	Schematic	5-19			
	Voltage, chassis view, notes	5-20			
	Alignment	5-17			
105	Additional data	Changes 7-14			
105-X, 105-XS	Schematic	5-19			
	Voltage, chassis view, notes	5-20			
	Alignment	5-17			
	Phonograph data, part 1	7-9			
	Phonograph data, part 2	7-10			
109 Deluxe	Schematic	1-12			
110, 111, AO (2 types)	Schematic	1-13			
111-A, 574, 870	Schematic	2-43			
111-X	See model 17				
	Alignment data	4-1			
134, 136	Schematic, parts	6-5			
	Voltage, socket, trimmers	6-6			
135	See model 104				
219-P, 219-PD, Wireless	Schematic, voltage, adjustments, changes	10-1			
Phonograph	Schematic	2-44			
235	Schematic, voltage	1-14			
301 AO	Schematic, voltage	2-45			
301 DO	Schematic, voltage, resistance	4-20			
383	Schematic, voltage, resistance	4-20			
409-GL	Schematic, voltage, socket, trimmers, alignment	10-2			
410, 420 AO	Chassis layout	2-46			
410, 420 DO	Schematic	2-47			
417-X	Chassis layout	2-48			
	Schematic	2-49			
427-X, 437-X, 457-X	Schematic, parts, voltage, resistance, socket, trimmers, alignment	8-3			
	Socket, trimmers, alignment	8-4			
475-A, 475-A	See model 75-A				
475-A, 475-A	See model 75-A				
478	See model 78				
500DG, 500DR, 500W, 500BV, 500BW	Schematic, voltage, socket, trimmers, alignment	10-3			
506, 566, 594	Schematic, parts	6-7			
510DG, 510DR, 510W, 510BV, 510BW	Voltage, socket, trimmers	6-8			
516, 516X, 546X	Schematic, voltage, socket, trimmers, alignment	10-4			
	Schematic, parts, transformer	7-11			
	Voltage, alignment, socket, trimmers, resistance	7-12			
517, 517B, 517W, 517X, 557, 567	Schematic, trimmers, resistance, voltage, parts	8-5			
	Socket, trimmers, alignment	8-6			
518, 518X, 558B, 558BX, 558C, 558CX, 568, 568X, 578 (1938), 578X	Schematic, parts, voltage	9-2			
527-2, 587-2	Alignment, socket, trimmers	9-3			
	Schematic, voltage, socket, trimmers	10-5			
	Alignment	10-10			
SPARKS WITHINGTON CO.—(Cont.)			RADIOTRON		
MODEL	REVISION	REVISION	EARLY	COMPLETE	PAGE
528-2, 588-2	Socket, trimmers, alignment	9-3			
566, 566X	Schematic, parts, voltage, resistance, socket, voltage	9-4			
597, 577	Alignment, trimmers	7-13			
	Schematic, socket, trimmers, voltage, resistance, parts	8-7			
538, 538X, 628, 628X, 668, 668X, 678, 678X, 678A (Selectronne)	Alignment	8-6			
	Schematic, parts	9-5			
	Voltage, alignment, socket, trimmers	9-6			
540X	Selectronne data	9-22			
547X	See model 516				
	Schematic, voltage, socket, trimmers, resistance, parts	8-11			
548X	Alignment, parts	8-14			
	Schematic, parts	9-7			
549-1	Voltage, alignment, socket, trimmers	9-8			
557	Schematic, voltage	10-7			
558	Alignment, socket, trimmers	10-8			
564, 570, 740, 750 AO, 564, 570, 600, 610, 620, 737, 740, 750 DO	See model 518				
566	See model 506				
567	See model 517				
568	See model 518				
570	See model 564				
574	See model 111-A				
577	See model 537				
578	See model 103 or 518				
587-2	See model 507-2				
588-2	See model 528-2				
589 AO	Schematic, voltage	1-19			
591, 593 AO	Schematic	2-52			
594	See model 506				
600, 610, 620 DO	Schematic, see model 564 DO				
600, 610, 620, 737 AO	Schematic, voltage	1-20			
600-A, 610-A	See model 9-A				
608, 608B, 608G, 608W, 608R, 608K, 608V	Schematic, parts, voltage	9-10			
616, 616-X, 666, 666-X	Socket, trimmers, alignment	9-11			
	Schematic, parts	8-9			
616-M, 616-MX, 666-M, 666-MX	Voltage, socket, trimmers	6-10			
	Alignment, trimmers	7-16			
	Schematic, parts	7-16			
617, 617-X, 667, 667-X	Alignment, trimmers	7-18			
	Socket, voltage, resistance	7-17			
	Schematic, socket, voltage, trimmers, parts	8-8			
620	Alignment	8-10			
620-A	See model 564				
620 AO, Below #6502	See model 8-A				
620 DO	See model 600 AO				
620X	See model 604 DO				
628	See model 538				
636-MX	Alignment data	4-1			
	See model 538				
637-6, 687-6	Voltage, resistance, socket, trimmers, alignment	7-19			
638-6, 688-6	Schematic, voltage	7-20			
	Alignment, socket, trimmers	10-9			
649-6L, 649-6S	Socket, trimmers, voltage, alignment	10-10			
	Schematic, parts	9-11			
655	Schematic	9-12			
	Voltage, socket, chassis	10-11			
	Alignment, trimmers	10-12			
	Schematic, parts	10-13			
666, 666X	Voltage, socket	6-11			
666-M, 666-MX	See model 616				
667, 667X	See model 616-M				
668	See model 617				
	See model 538				

# SPARKS WITHINGTON SPIEGEL

RADIOTRON  
EARLY COMPLETE  
PAGE

SPARKS WITHINGTON CO.—(Cont.)  
REVISÉD  
PAGE

MODEL  
1089

Schematic .....10-17  
Socket, trimmers, chassis .....10-16  
Voltage, alignment, trimmers .....10-18  
Electronne tuner, trimmer .....10-14  
Adjustments .....7-23  
Schematic, parts .....7-23

Voltage, resistance, socket,  
trimmers .....7-24  
Alignment, phonograph, data .....7-25  
Schematic, parts .....7-23

Voltage, resistance, socket,  
trimmers .....7-24  
Alignment, phonograph, data .....7-25  
Phonograph, data, part 1 .....7-9  
Phonograph, data, part 2 .....7-10  
Schematic, voltage, parts .....8-16, 8-14  
Alignment .....8-14

See model 1116X  
Schematic, parts, voltage .....9-25  
Socket, trimmers, alignment .....9-26  
Electronne tuner, trimmers, .....10-14  
adjustments .....10-14

See model 1268  
Schematic .....10-19  
Electronne tuner trimmers,  
adjustments .....10-14  
Alignment, trimmers .....10-20  
Schematic, parts .....7-26  
Alignment, phonograph, data .....7-25  
Voltage, resistance, socket,  
trimmers .....7-24

Schematic, parts, voltage 9-27, 28  
Socket, chassis .....9-29  
Schematic .....10-21  
Alignment, voltage, socket,  
trimmers, chassis .....10-22  
Electronne tuner trimmers,  
adjustments .....10-14  
Schematic, changes, voltage 10-25

Alignment, trimmers .....10-26  
Socket layout .....10-20  
Schematic, changes .....10-23, 24  
Alignment, trimmers .....10-26  
Socket layout .....10-20  
Schematic, voltage, alignment,  
trimmers, socket .....10-27  
Schematic, voltage, alignment,  
chassis .....10-28  
Schematic, voltage, trimmers,  
socket, alignment .....10-33  
Schematic, voltage, trimmers 10-29  
Alignment, tuner .....10-30  
Chassis .....10-34  
Schematic, voltage .....10-31  
Alignment, chassis, trimmers 10-32  
Tuner data .....10-32  
Schematic, trimmers,  
socket, chassis .....10-34  
Voltage, alignment, tuner .....10-30  
Schematic, voltage .....10-35  
Alignment, socket, trimmers,  
chassis .....10-35  
Electronne tuner, trimmers,  
adjustments .....10-14

1867, Below Serial 000751  
Early, Late Productions

1867, Above Serial 000751

5008  
5018  
5028  
5218

5518, 5518A, 5518AX  
6218, 7618  
8618

2290  
2391  
2391

\*565  
\*566  
\*566

990 AO  
931 AO  
931 DO  
906, 966X

968, 965X

977  
987

997X  
1068, 1068X, 1078, 1078X

1078

See model 1068

See model 1068

RADIOTRON  
EARLY COMPLETE  
PAGE

SPARKS WITHINGTON CO.—(Cont.)  
REVISÉD  
PAGE

MODEL  
676 (Late) 686, D686,  
H686

Schematic, parts, socket, trim-  
mers, voltage, alignment, .....9-30  
resistance .....9-30  
See model 676  
See model 676  
See model 686  
See model 686-6  
Schematic, speaker connec-  
tions .....10-6  
Voltage, alignment .....10-3  
Schematic, parts .....6-13  
Voltage, socket, trimmers, pho-  
nograph data .....6-14  
Alignment, trimmers .....6-14  
Schematic, voltage, socket,  
trimmers, parts .....8-12  
Alignment .....8-14  
Schematic, voltage .....10-15  
Alignment, trimmers, socket,  
chassis .....10-16  
See model 600 AC, Below #6502  
Schematic .....2-55  
See model 564 DO  
Schematic, parts, socket, trim-  
mers, voltage .....9-13  
Alignment, "Selectime" data .....9-14  
See model 564  
Schematic, parts, voltage .....9-15  
Socket, trimmers, alignment .....9-16  
See model 17  
Alignment data .....4-1  
See model 716X  
Schematic, parts .....6-13  
Voltage, socket, trimmers,  
phonograph data .....6-14  
Alignment, trimmers .....7-21  
Schematic, parts .....6-13  
Voltage, socket, trimmers,  
phonograph data .....6-14  
Alignment, trimmers .....7-21  
Phonograph data, part 1 .....7-9  
Phonograph data, part 2 .....7-10  
Socket, trimmers, alignment .....9-16  
Schematic, parts, voltage .....9-17  
See model 70  
See model 768  
Schematic, socket, trimmers,  
voltage, parts .....8-17  
Alignment .....8-14  
See model 80  
Schematic, voltage, socket,  
trimmers, parts .....8-13  
Alignment .....8-14  
See model 111-A  
See model 17  
See model 727X  
Schematic, parts, voltage .....9-21  
Socket, trimmers, alignment .....9-22  
Schematic, voltage .....1-21  
Schematic, voltage .....1-22  
Schematic, parts .....7-23  
Alignment, trimmers .....7-21  
Socket, voltage, resistance .....7-17  
Schematic, parts, socket, trim-  
mers .....9-18  
Voltage, alignment .....9-19  
Schematic, parts, socket, trim-  
mers .....9-23  
Voltage, resistance, alignment 9-24  
Schematic, socket, trimmers,  
voltage, parts .....8-18  
Alignment .....8-14  
See model 827X  
Socket, trimmers, alignment .....9-19  
Schematic, parts, voltage .....9-20  
Electronne tuner, trimmers,  
adjustments .....10-14  
See model 1068

676 (Late) 686, D686,  
H686

686, 691  
686-6  
686-6  
699

716X, 766  
727X, 727XD, 877X  
728X

787 AO, Below #6502  
787 AC (Above #6502)  
737, 740, 750 DO  
738 (Selectime)

740, 750 AO  
748X

750-A, 760X  
766  
766X

766XP, 766XS

768, 768X, 778, 778X  
775  
778  
827X, 827XD, 997X

895  
867

870  
870-A, 870X  
877X  
925X

990 AO  
931 AO  
931 DO  
906, 966X

968, 965X

977  
987

997X  
1068, 1068X, 1078, 1078X

1078

See model 1068

See model 1068

See model 1068

See model 1068

SPARTON  
See SPARKS WITHINGTON CO.

SPENCER  
See TRUEVALUE

SPIEGEL, INC.  
AIR CASTLE

See model 6510  
See model 169  
Data .....Changes 10-2

B-1 Chassis  
H1 Chassis  
X1

SPINGEL, INC.—(Cont.)		REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON		
MODEL	MODEL	MODEL	SPIEGEL, INC.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
AM 3 Chassis	See model 6506	167, 182, 183, Chassis	Schematic, socket, trimmers	9-9		
Z4 Chassis	See model 102	Z-5	Alignment	9-4		
L-5 Chassis	See model 120	169, Chassis H1	Schematic, voltage, alignment	10-6		
M5 Chassis	See model 178	172	See model 102			
Z-5 Chassis	See model 167	178	See model 144			
6A60 Chassis	See model 4505	178, 6708, 6754, Chassis	Schematic, voltage, socket, trimmers	10-7		
AM 6 Chassis	See model 6508	M5 (1936)	Alignment	10-4		
L-6 Chassis	See model 130	180, 184	See model 160			
6-P Chassis	See model 4404	182, 183	See model 167			
6-Q Chassis	See model 2154	188	See model 150			
X6 Chassis	See model 2000	190	See model 130			
7A0 Chassis	See model 1901	202 Chassis	See model 1100			
AM 7 Chassis	See model 5054	211 Chassis	See model 1108			
7-J Chassis	See model 4400	212 Chassis	See model 1150			
L-7 Chassis	See model 100	216 Chassis	See model 1010			
X-8 Chassis	See model 2058	218 Chassis	See model 1052			
11-X Chassis	See model 4010	219 Chassis	See model 1002			
11-X Chassis	See model 4006	220 Chassis	See model 1104			
12AC Chassis	See model 1903	601 Chassis	See model 6504			
14A Chassis	See model 6805	603 Chassis	See model 160			
14-112S Chassis	See model 2080	608 Chassis	See model 4519 Auto			
14-127ES Chassis	See model 2212	613 Chassis	See model 5058			
14-129 Chassis (1936)	See model 6525	651 Chassis	See model 5200			
14-136EA, 14-152ES	See model 6525	700 Chassis	See model 5256			
14-142FS Chassis	See model 6512	745 (1937) Chassis	See model 2064			
16R Chassis	See model 2060	871 Chassis	See model 4004			
20C5 Chassis	See model 4508	885 Chassis	See model 4068			
22B7 Chassis	See model 4509	1002, 1003, Chassis 219	Schematic, socket, trimmers, alignment	10-8		
X23 Chassis	See model 2204	1010, 1011, Chassis 216	Schematic, socket, trimmers, alignment	10-9		
25Y Chassis	See model 9930	1052, 1053, Chassis 218	Schematic, socket, trimmers, alignment	10-10		
27D Chassis	See model 9904	1060B Chassis	See model 6600			
29B Chassis	See model 9916	1070B Chassis	See model 5102			
37B Chassis	See model 150	1072AE Chassis	See model 4002			
39B Chassis	See model 1906	1090B Chassis	See model 2108			
40 Chassis	See model 2000	1100, 1101, 1102, 1103, Chassis 202	Schematic, alignment	10-11		
BA41 Chassis	See model 1901	1104, 1105, 1106, 1107, Chassis 220	Schematic, socket, trimmers	10-12		
43 Chassis	See model 2066	1105 Chassis	Alignment	10-10		
46A Chassis	See model 134	1108, 1109, 1110, 1111, Chassis 211	See model 2070			
58 Chassis	See model 132	1150, 1151, 1152, 1153, Chassis 212	Schematic, socket, trimmers, alignment	10-13		
65B Chassis	See model 5106	1154, 1155, 1156, 1157, Chassis 220	Schematic, alignment	10-11		
66-660 Chassis	See model 4210	1901, 1907, 1911, 1921, 1932, 1955, 1957, 1961, 1981, Chassis X6, BA41	Schematic, socket, trimmers	10-10		
73 B Chassis	See model 2222	1903, 1960, Chassis 14A	Schematic, trimmers	10-15		
78-780 Chassis	See model 2302	1906, 1954, Chassis 39B	Alignment, voltage	10-16		
88-880 Chassis	See model 4212	1910	Schematic, trimmers, alignment	10-22		
90B Chassis	See model 2112	1911	See model 150			
100, Chassis X-8	Schematic, socket, voltage, trimmers	1921, 1932	See model 1901			
102, 104, 112, 114, 124, 172, 6750, 6752 Chassis Z4	Alignment, parts	1954	See model 1901			
109B Chassis	Schematic, socket, trimmers, alignment	1955, 1957	See model 1906			
120, 140, Chassis L-5	Schematic, voltage, socket, trimmers	1960	See model 1901			
124	Alignment, parts	1961, 1981	See model 1903			
130, 134, 146, 190, Chassis L-6	Schematic, voltage, socket, trimmers	2000, 2001, 2008, 2009, 2018, 2019, 2050, 2051, Chassis 40	Schematic, socket, trimmers, alignment	10-17		
132, Chassis 58	Alignment, parts	2000, 2001, 2050, 2051, 2072, 2073, Chassis 6-W	Tuner data	10-18		
134, Chassis 46A	Schematic, voltage, socket, trimmers	2058, 2059 (1938), 4054 (1937) Chassis 11-S	Schematic, socket, trimmers, alignment, parts	9-12		
144, 152, 178, Chassis L-7	Schematic, voltage, socket, tuning eye notes		Schematic, socket, parts, trimmers	9-13		
145E Chassis (1938)	Schematic, voltage, socket, trimmers		Alignment, notes	9-14		
146	Alignment		Electric tuning data	9-15		
147 Chassis (1938)	Schematic, voltage, socket, trimmers					
150, 188, 1910, Chassis 37-B	Alignment, parts					
152	See model 144					
160, 180, 184, 6500, 6504, 6518, 6546, 6550, 6562, 6564, Chassis 603 (1936)	Schematic					
	Alignment, socket, trimmers					

MODEL	REVISÉD PAGE	MODEL	REVISÉD PAGE
2060, 2061, 4056, 4074, Chassis 16R	10-19, 20	4404, 4452, Chassis 6-P	Schematic, alignment .....9-21
2064, 2065, 4014, 4064, 4066, Chassis 745 (1937)	10-21	4500 (1935), Chassis 4536	Socket, trimmers, notes, parts 9-22
2066, 2067, 2068, Chassis 43	10-23	4500 (1935), Chassis 4536	Schematic, socket, voltage, alignment .....9-20
2070, 2071, 4076, Chassis 1105	10-18	4500, 4502, 4504 (1936), See model 2154	Chassis 6-Q
2080, 2081, Chassis 147 (1938) Also chassis 14-127ES	10-10	4505, Chassis 6A60	Schematic, alignment, trim- mers, voltage .....10-41, 42
2100, 2101, 2102, 2103, Chassis 109B	10-12	4508, 9905, 9911, Chassis 2005	Schematic, parts .....9-23
2108, 2109, 2110, 2111, Chassis 1090B	10-24	4509, 9912, Chassis 22B7	Socket, voltage, resistance, alignment, drive cord data 9-24
2112, 2113, 2120, 2121, Chassis 90B	10-28	4510, 4516, 4533, 9923	Schematic, socket, trimmers, 9-25
2150, 2151, 2152, 2153, Chassis 109B	10-25	4510, 4516, 4533, 9923	Voltage, alignment, resistance, 9-26
2154, 2155 (1938), 4500, 4502, 4504, 4550, 4512, 4514 (1936) Chassis 6-Q	9-16	4512, 9914, 9915, 9932, 9933 (1935) Chassis 7700	Schematic, voltage, alignment 9-32
2200, 2201, 2202, 2203, 2220, 2221, 2230, 2231, 2232, 2233, Chassis X23	10-31	4512, 4514 (1936) Chassis 6-Q	Schematic, voltage, parts .....9-27
2204, 2205, 2206, 2207, Chassis 22E	10-36	4514, Chassis 9148	Alignment, parts .....9-28
2212, 2213, 2214, 2215, 2254, 2255, 2256, 2257, 2280, 2281, Chassis 145E (1938) Also chas- sis 14-129 (1936)	10-36	4519 Auto, Chassis 603 (1934)	Schematic, voltage, trimmers, battery data .....9-29, 30
2220, 2221, 2222, 2223, 2224, 2225, 2226, 2227, 2228, 2229 Chassis 75B	10-29	4533, Chassis 6246	Alignment, voltage .....10-43
2230, 2231, 2232, 2233	10-30	4536 Chassis	Alignment, voltage .....10-44
2302, 2303, Chassis 78- 750	10-32	4550 (1936) Chassis 6-Q	See model 4510
4002, 4050, 5020, Chassis 1072AE	10-33	5006, 5052, 6544, 6568, Chassis 14-127ES	See model 2154
4004, 4052, Chassis 871	10-34	5020	See model 2080
4006, 4070, Chassis 12AO	10-35	5054, 5062, 6570, 6580, 6582, 6590, Chassis AM 7	See model 4002
4010, Chassis 11X	10-36	5058, 5060, Chassis 613	Schematic, socket, alignment, trimmers .....10-49
4014	10-37	5062	Schematic, socket, voltage, trimmers, parts, alignment 9-35
4054	10-38	5102, Chassis 1070B	See model 5054
4056	10-39	5106, 5110, Chassis 65B	Schematic, voltage, socket .....9-33
4059	10-40	5200, 5210, 5214, 5216	Alignment, parts, battery cor- rections .....9-34
4064	10-41	5218, 6712, 6716, 6766, Chassis 651	Schematic, voltage, socket, trimmers, alignment .....10-45
4066	10-42	6772, Chassis 14-129 (1936)	Schematic, voltage .....9-36
4068, Chassis 885	10-43	6776, Chassis 700	See model 2212
4070	10-44	6776, Chassis 700	Schematic, socket, alignment 10-50
4074	10-45	6776, Chassis 700	See model 9907
4210, Chassis 66-660	10-46	6776, Chassis 700	See model 9902
4212, Chassis 88-880	10-47	6776, Chassis 700	See model 9502
4400, 4420, Chassis 7-J	10-48	6776, Chassis 700	See model 4510
	10-49	6776, Chassis 700	See model 160
	10-50	6776, Chassis 700	Schematic, socket, trimmers, alignment .....10-46
	10-51	6776, Chassis 700	Schematic, voltage, socket, trimmers, alignment, parts 9-35
	10-52	6776, Chassis 700	See model 160
	10-53	6776, Chassis 700	Schematic, socket, trimmers, alignment .....10-47
	10-54	6776, Chassis 700	Schematic, socket, trimmers, alignment .....10-48
	10-55	6776, Chassis 700	Schematic, socket, trimmers, alignment .....9-37
	10-56	6776, Chassis 700	Schematic, socket, trimmers, alignment .....10-51
	10-57	6776, Chassis 700	Schematic, socket, trimmers, alignment .....9-41
	10-58	6776, Chassis 700	See model 6512
	10-59	6776, Chassis 700	See model 2080
	10-60	6776, Chassis 700	See model 160
	10-61	6776, Chassis 700	See model 6502
	10-62	6776, Chassis 700	See model 6506



MODEL	STEINITE RADIO CO.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON PAGE
421, 425 (Chassis #21)	Chassis layout, data	2-4	576-D	2308
423 (Chassis #23)	Schematic	2-5	576-O	2307
600, 605, 630, 635, 642, 643 (Chassis #26)	Schematic	2-6	576-F	2309
642-B, 700, 705, 706, 725, 755, 760, 761 (Chassis #28)	Schematic	2-7	576-G	2311
700, 701 (Chassis #28)	Voltage, data	2-8	576-H	2312
990, 991, 992, 993	Schematic, data, voltage	2-9	576-I	2310
	Schematic, socket, voltage	1-5	576	2313
<b>STENODE RADIOSTAT</b>				
Stenode Radiostat	Schematic	Misc. 1-18		2763
<b>STERLING MFG. CO.</b>				
A (DC)	Schematic	3-1		2319
C	Schematic	3-3		2323
G	Schematic	3-5		2320
M-K-N	Schematic	1-5	*579	2321
P-Q	Schematic	3-2		2321
V-A	Schematic	3-2		2321
Miniature	Schematic	3-1		2319
8-tube Receiver	Schematic, voltage	1-3	*578-A	2317
B-A	Chassis views, data	1-4	*578-B	2318
B-B	Schematic	1-5	*579	2320
B-C	Schematic	1-1	*577	2315
4	Schematic	3-3		2323
B-A-F	Schematic	1-2	*578	2316
RET-41, R-81, R-96-M, R-96, R-97, R-98, R-100, R-100-M	Schematic	3-3		2323
R-100 MV	Schematic	3-4		2324
R-402	Schematic	2-1		2325
R-403	Schematic	2-1		2325
R-404	Schematic	2-1		2325
R-406	Schematic	2-1		2325
R-407	Schematic	2-1		2325
R-409	Schematic	2-3		2327
R-410	Schematic	2-3		2327
R-411	Schematic	2-3		2327
R-412	Schematic	2-3		2327
R-509	Schematic	2-3		2327
R-510	Schematic	2-3		2327
R-511	Schematic	2-3		2327
R-522	Schematic	1-6		2327
R-807-A	Schematic	1-6		2327
R-810 (1st type)	Schematic	2-2	*781	2322
R-810 (2nd type)	Schematic	2-2	*781	2322
R-880	Schematic	2-2		2326
	Schematic	2-2		2326
<b>STEWART-WARNER CORP.</b>				
NOTE: The second figure of the new system model numbers in Volume X indicates the voltage rating of the receiver as follows:				
1-117 volts, 50-60 cycles				
2-2 volt battery				
3-117 volts, AC-DC				
Underwriters Approved				
10-100-240 volts, 50-133 cycles				
Data	Changes 10-6			
See model A6	1-15		*580-A	2356
See models R-1322, R-1322				
Variable and fixed, part 1	1-13		*580-Q	2357
Fixed, part 2	1-14		*580-D	2358
Installation data	5-4			
Speaker cone replacements	10-14			
Schematic, voltage, sockets, coils, tuner switch	10-55			
Alignment, trimmers, tuner	10-56			
Schematic, voltage, socket, tuner switch, coils	10-57			
Alignment, trimmers	10-58			

**RADIOTRON  
COMPLETE  
PAGE**

REVISED  
PAGE

—(Cont.)

**WARNER**

STEWART  
DEL

# RADIOT Y COMPI

**REVISED  
PAGE**

2.-(Cont.)

**WARREN**

**L**  
**STRE**

Schematic, voltage, socket ....10-58

01-542S, 01-543S, 01-544S, 01-545S, 01-546S, 01-547S, 01-548S, 01-549S, Chassis 01-54S,

01-541 WT, 01-542 WT, 01-543 WT, 01-544 WT, 01-546 WT, 01-545 WT, 01-547 WT, 01-548 WT,

01-549WT, Chassis 01-54 WT	Alignment, trimmers, tuner, drive cord data .....10-59
----------------------------	--

Schematic, voltage, socket,  
coils .....10-60

01-612S, 01-613S, 01-614S, 01-615S, 01-616S, 01-617S, 01-618S, 01-619S, Chassis 01-61S

Alignment, trimmers .....	10-59
Schematic, voltage, socket, coils .....	10-61, 62
01-811, 01-812, 01-813, 01-814, 01-815, 01-816, 01-817, 01-818, 01-819,	

Alignment, trimmers .....	10-63
Pin, drive cord data .....	10-64
Schematic, voltage, socket .....	10-65

Notes .....	10-63
Chassis 02-40	
417, 02-418, 02-419,	
Chassis 02-41	
Alignment, trimmers, loop,	10-66
afterwards, data	

A6, Air Pal, Chassis 07-31	Schematic, voltage, socket ....10-1
	Alignment, trimmers, antennae .....
	Notes change .....
07-511	07-513 07-518 07-519
	Schematic, voltage, socket .....
	Notes change .....

07-519, 07-518, 07-516, 07-517, 07-515, 07-514, 07-513, 07-1, 07-0

Alignment trimmers antenna  
Chassis 07-51,  
Coils, changes .....10-67

Notes	10-68
Schematic, voltage, socket, coils, changes	10-67
07-5118, 07-5128, 07-5138, 07-5148, 07-5158, 07-5168, 07-5178, 07-5188,	

07-519S, Chassis 07-51S	Alignment, trimmers, antenna
	Notes .....
07-511H, 07-512H, 07-	Schematic, voltage, socket

.....10-69  
notes

Alignment, trimmers, antenna data .....	10-70
Schematic, voltage, socket, notes .....	10-69
07-551, 07-552, 07-553, 07-554, 07-555, 07-556,	

07-557, 07-558, Chassis 07-55	Alignment, trimmers, antenna data .....10-70
----------------------------------	---

07-631, 07-632, 07-633, 07-634, 07-635, 07-636, 07-637, 07-638, 07-639, Chassis 07-63

	Alignment trimmers, drive cord data .....	10-72
08-521,	08-522, 08-523, 08-	Schematic, voltage, socket, tuner c <sub>t</sub> , t <sub>i</sub>
524,	08-525, 08-526, 08-	
		10-55

527, 08-528, 08-529, Chassis 08-52  
Alignment, trimmers, tuner ....10-56

08-541, 08-542, 08-543, 08-544, 08-545, 08-546, 08-547, 08-548, 08-549, Chassis 08-54

Alignment, trimmers .....10-59

STEWART-WARNER CORP.—(Cont.)			STEWART-WARNER CORP.—(Cont.)		
MODEL	REVISION	EARLY COMPLETE PAGE	MODEL	REVISION	EARLY COMPLETE PAGE
91-643, Chassis 91-64 (With "S" stamped on chassis)	Schematic, voltage, socket .....10-23		98-641, 98-642, 98-643, 98-644, 98-645, 98-646, 98-647, 98-648, 98-649, Chassis 98-64	Schematic, voltage, socket, coils, notes .....10-21	
91-711, 91-712, 91-713, 91-714, 91-715, 91-716, 91-717, 91-718, 91-719, Chassis 91-71	Alignment, trimmers, tuner, phono, connections .....10-24 Schematic, voltage, coils, tuner switch, notes .....10-25		98-711, 98-712, 98-713, 98-714, 98-715, 98-716, 98-717, 98-718, 98-719, Chassis 98-71	Alignment, trimmers, phono, data, tuner .....10-22 Schematic, voltage, coils, tuner switch, notes .....10-25	
91-811, 91-812, 91-813, 91-814, 91-815, 91-816, 91-817, 91-818, 91-819, Chassis 91-81	Alignment, trimmers .....10-26 Tuner data, drive cord data, parts .....10-27 Schematic, voltage, socket, tuner switch, coils .....10-29		98-811, 98-812, 98-813, 98-814, 98-815, 98-816, 98-817, 98-818, 98-819, Chassis 98-81	Alignment, trimmers .....10-26 Tuner and drive cord data, parts .....10-27 Schematic, voltage, socket, tuner switch, coils .....10-29	
91-821, 91-822, 91-823, 91-824, 91-825, 91-826, 91-827, 91-828, 91-829, Chassis 91-82	Tuner data, drive cord data 10-28 Alignment, trimmers, parts .....10-30 Schematic, voltage, socket, tuner switch .....10-31, 32		98-821, 98-822, 98-823, 98-824, 98-825, 98-826, 98-827, 98-828, 98-829, Chassis 98-82	Tuner and drive cord data .....10-28 Alignment, trimmers, parts .....10-30 Schematic, voltage, socket, tuner switch .....10-31, 32	
91-1111, 91-1112, 91-1113, 91-1114, 91-1115, 91-1116, 91-1117, 91-1118, 91-1119, Chassis 91-111	Alignment, trimmers, antenna data .....10-33 Tuner data, phono, notes .....10-34 Schematic, voltage .....10-5, 6		98-1111, 98-1112, 98-1113, 98-1114, 98-1115, 98-1116, 98-1117, 98-1118, 98-1119, Chassis 98-111	Alignment, trimmers, antenna data .....10-33 Tuner and phono, data .....10-34 Schematic, voltage .....10-5, 6	
97-521, 97-522, 97-523, 97-524, 97-525, 97-526, 97-527, 97-528, 97-529, Chassis 97-52	Tuner, drive cord data, notes, parts .....10-7 Alignment, trimmers, coils .....10-8 Schematic, voltage, socket .....10-35		R-100-A, B, E AO R-100-A DO R-101-A, R-101-B R-101, R-102	Tuner and drive cord data, notes, parts .....10-7 Alignment, trimmers, coils .....10-8 Schematic .....10-9 Chassis wiring, voltage .....1-10 Continuity tests .....1-11 Schematic, socket, voltage .....1-12 Schematic, socket, voltage .....2-1 Chassis layout, servicing notes .....2-2 Servicing notes, concluded .....2-3 Schematic .....10-3 Schematic .....10-4 Schematic, socket, voltage .....2-4 Schematic, socket, voltage .....2-5 Schematic, socket, voltage .....3-1 Service data, parts list .....3-2 Schematic, socket, voltage, parts list .....3-3 Service data, part 1 .....3-4 Service data, part 2 .....3-5 Schematic, voltage, parts list, socket .....4-1 Alignment .....4-2 Schematic, socket, voltage, parts list .....3-6 See model 1090 Schematic, voltage, parts list, socket .....4-3 Alignment .....4-4 Schematic, voltage, socket, parts list .....4-5 Alignment .....4-6 Schematic, voltage, socket .....4-7 Alignment, notes .....4-8 Schematic, voltage .....4-9 Schematic, voltage, socket, parts list .....4-10 Alignment .....4-11 See model 1171 See model 1181 Schematic, voltage, socket, parts list .....4-12 Alignment .....4-13 Schematic, socket, voltage .....4-14 Alignment .....4-15 Alignment .....4-16	
97-551, 97-552, 97-553, 97-554, 97-555, 97-556, 97-557, 97-558, 97-559, Chassis 97-55 97-562S, 97-563S, 97-564S, 97-565S, 97-566S, 97-567S, 97-568S, 97-569S, 97-570S, 97-571S, 97-572S, 97-573S, 97-574S, 97-575S, 97-576S, 97-577S, 97-578S, 97-579S, Chassis 97-57	Alignment, trimmers .....10-36 Tuner, drive cord data .....10-37 Schematic, voltage, socket .....10-38 Alignment, trimmers .....10-39 Parts .....10-40 Schematic, voltage, socket, changes .....10-41 Tuner data .....10-38 Alignment, trimmers, parts, antenna notes .....10-42 Schematic, trimmers, alignment .....10-9 Voltage, socket, tuner, drive cord data .....10-10 Schematic, voltage, socket, tuner switch, coils .....10-11 Alignment, trimmers .....10-12 Tuner data, parts .....10-13 Schematic, socket, voltage, coils .....10-15, 16 Alignment, trimmers, tuner .....10-17 Schematic, voltage, socket, tuner switch, coils .....10-19 Tuner data .....10-17 Alignment, trimmers, parts .....10-20		102-D (7 Tubes) 102-D (8 Tubes) R-102-A, B, E (1st type) R-102-A, B, E (Revised) R-104-A, B, E 104 Chassis 105 Series		
98-531, 98-532, 98-533, 98-534, 98-535, 98-536, 98-537, 98-538, 98-539, Chassis 98-53	Alignment, trimmers .....10-12 Tuner data, parts .....10-13 Schematic, socket, voltage, coils .....10-15, 16 Alignment, trimmers, tuner .....10-17 Schematic, voltage, socket, tuner switch, coils .....10-19 Tuner data .....10-17 Alignment, trimmers, parts .....10-20		R-106 R-108, 108-X (10 to 20 incl.) R-109 Chassis R-110 R-111, R-115 R-112 Chassis R-113, R-114 R-116 R-117 Chassis R-118 Chassis R-119 R-120 (1201, 1209) R-123, R-123A Chassis R-125 Series R-126 Series		
98-611, 98-612, 98-613, 98-614, 98-615, 98-616, 98-617, 98-618, 98-619, Chassis 98-61	Alignment, trimmers, tuner .....10-17 Schematic, voltage, socket, tuner switch, coils .....10-19 Tuner data .....10-17 Alignment, trimmers, parts .....10-20				
98-621, 98-622, 98-623, 98-624, 98-625, 98-626, 98-627, 98-628, 98-629, Chassis 98-62	Alignment, trimmers, tuner .....10-17 Schematic, voltage, socket, tuner switch, coils .....10-19 Tuner data .....10-17 Alignment, trimmers, parts .....10-20				

# STEWART-WARNER

STEWART-WARNER CORP.—(Cont.)				RADIOTRON	
MODEL	REVISION	EARLY COMPLETE PAGE	REVISION	EARLY COMPLETE PAGE	
R-126-P, R-126-X	Data	6-7			
R-127, R-127-A Chassis	See model 1271				
R-127-X Chassis	Data	6-10			
R-128D Chassis	See model 1281D				
R-130 Chassis	See model 1301				
R-131 Chassis	See model 1311				
R-132 Chassis	See model 1322				
R-133 Chassis	See model 1332				
R-134 Chassis	See model 1341				
R-136, R-136P, R-136X Chassis	See model 1361				
R-137, R-137P, R-137X Chassis	See model 1371				
R-138, R-138P, R-138X Chassis	See model 1381				
R-139D Chassis	See model 1391D				
R-140 Chassis	See model 1401				
R-142A, R-142AS Chassis	See model 1421				
R-144AS Chassis	See model 1441				
R-145, R-145X Chassis	See model 1451				
R-146 Chassis	Phonograph connections, uni- versal transformer	10-18			
R-147 Chassis	See model 1471				
R-147P, R-147X Chassis	Phonograph connections, uni- versal transformer	10-18			
R-148 Chassis	Phono. connections	8-3, 8-4			
R-148X Chassis	See model 1481				
R-149, R-149X Chassis	See model 1491				
R-160 Chassis	See model 1601				
R-161-D Chassis	See model 1611-D				
R-162-D Chassis	See model 1621-D				
R-163D Chassis	See model 1631D				
R-164D Chassis	See model 1641D				
R-167S, R-168, Chassis	See model 1671				
R-169 Chassis	See model 1691				
R-171 Chassis	See model 1711				
R-172 Chassis	See model 1721				
R-172-X Chassis	Phono. connections	8-11			
R-173 Chassis	See model 1731				
R-173-X Chassis	Phono. connections, parts	8-14			
R-180 Chassis	See model 1801				
R-181, R-181A, R-181B, R-182, R-182A, R-182B, R-182W, Chassis	See model 1811				
R-183 Chassis	See model 1831				
R-184 Chassis	See model 1841				
R-185 Magic Keyboard	See "Magic Keyboard" Models 1845 etc.				
R-185, R-185A, R-185B, R-185W, Chassis	See model 1851				
R-186, R-186W Chassis	See model 1861				
R-188 Chassis	See model 1881				
R-190D Chassis	See model 1901				
R-191D Chassis	See model 1911				
R-192D Chassis	See model 1921				
800, 805	Schematic, socket	1-1			
R-301-A, B, E SW Converter	Schematic, servicing notes	2-6			
R-304, R-304A chassis	See model 3041				
805, 815, 820	Schematic, socket	1-1			
810, 825	Schematic, socket	1-1			
830	Schematic, socket	1-1			
835, 840	Schematic, socket	1-1			
845, 850, 855, 860	Schematic, socket	1-1			
865, 890	Schematic, socket	1-1			
900, 920, 925	Schematic, socket	1-2			
930, 935	Schematic, socket	1-2			
930, 935, 715, 750 SPU	Schematic	1-2			
700, 705, 710	Schematic, socket	1-3			
715, 720	Schematic, socket	1-3			
750	Schematic, socket	1-3			
801, 802	Schematic, socket	1-3			
801, 801-A, 811, 811-A (Series B)	Schematic, socket, voltage	1-4			
PU 801, 801-A, 811, 811-A	Schematic	1-4			
806 (Series A)	Schematic, socket	1-5			
				RADIOTRON	
				EARLY COMPLETE PAGE	
				REVISION	
				EARLY COMPLETE PAGE	
				REVISION	
				EARLY COMPLETE PAGE	
				REVISION	
				EARLY COMPLETE PAGE	
				REVISION	
				EARLY COMPLETE PAGE	

MODEL	STEWART-WARNER CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
1231, 1232, 1233, 1234, 1235, 1236, 1237, 1238, 1239, Chassis R-123, R-123A	Schematic, socket, voltage, parts	6-1		
Circuit data, alignment, trimmers, parts				
1251, 1252, 1253, 1254, 1255, 1256, 1257, 1258, 1259, Chassis R-125, Series Chassis R-125A and 125X	Schematic, parts list, circuit changes	6-2		
Alignment data, part 1		5-6		
Alignment data, part 2, trimmer locations		5-7		
Alignment data, part 3		5-8		
Schematic, socket, voltage, parts		6-3		
Alignment, trimmers		6-4		
Schematic, socket, changes, parts		5-9		
Alignment data, part 1		5-10		
Alignment data, part 2		5-11		
Alignment data, part 3		5-12		
Alignment data, part 4		5-13		
Schematic, socket, voltage, parts		6-5		
Circuit data, trimmers, alignment		6-6		
Alignment part 2, parts list		6-7		
Schematic, socket, voltage, parts		6-8		
Circuit data, trimmers, alignment		6-9		
Alignment part 2, parts		6-10		
Schematic, socket, circuit changes, parts		5-15		
Alignment data, part 1		5-14		
Alignment data, part 2		5-16		
Alignment data, part 3		5-17		
Alignment data, part 4		5-18		
Schematic, socket, parts		7-1		
Trimmers, alignment		7-2		
Schematic, voltage, socket, parts		6-12		
Alignment, trimmers, parts		8-6		
Schematic, voltage, socket, parts		6-13		
Circuit data, parts, alignment		6-14		
Schematic, socket, voltage, parts		6-15		
Schematic, socket, voltage, parts		6-16		
Alignment		10-6		
Schematic, voltage, socket, trimmers, parts		6-17		
Final schematic note, trimmers, alignment		7-3		
Schematic, socket, trimmers, parts		6-18		
1261, 1262, 1263, 1264, 1265, 1266, 1267, 1268, 1269, Chassis R-126, Series Chassis R-126A, R-126P, R-126X				
1261, 1262, 1263, 1264, 1265, 1266, 1267, 1268, 1269, Chassis R-126, Series Chassis R-126A, R-126P, R-126X				
1261, 1262, 1263, 1264, 1265, 1266, 1267, 1268, 1269, Chassis R-126 Late				
1271, 1272, 1273, 1274, 1275, 1276, 1277, 1278, 1279, Chassis R-127, Series Chassis R-127-X				
1271, 1272, 1273, 1274, 1275, 1276, 1277, 1278, 1279, Chassis R-127, Series Chassis R-127-X				
1281D, 1282D, 1283D, 1284D, 1285D, 1286D, 1287D, 1288D, 1289D, Chassis R-128D				
1301, 1302, 1303, 1304, 1305, 1306, 1307, 1308, 1309, Chassis R-130				
1311, 1312, 1313, 1314, 1315, 1316, 1317, 1318, 1319, Chassis R-131				
1321, 1322, 1323, 1324, 1325, 1326, 1327, 1328, 1329, Chassis R-132, Series Chassis R-132A, R-132P, R-132X				
1341, 1342, 1343, 1344, 1345, 1346, 1347, 1348, 1349, Chassis R-134, Series Chassis R-134A, R-134P, R-134X				
1361, 1362, 1363, 1364, 1365, 1366, 1367, 1368, 1369, Chassis R-136, Series Chassis R-136A, R-136P, R-136X				
1361, 1362, 1363, 1364, 1365, 1366, 1367, 1368, 1369, Chassis R-136, Series Chassis R-136A, R-136P, R-136X				
1371, 1372, 1373, 1374, 1375, 1376, 1377, 1378, 1379, Chassis R-137, Series Chassis R-137A, R-137P, R-137X				
1381, 1382, 1383, 1384, 1385, 1386, 1387, 1388, 1389, Chassis R-138, Series Chassis R-138A, R-138P, R-138X				
1391, 1392, 1393, 1394, 1395, 1396, 1397, 1398, 1399, Chassis R-139, Series Chassis R-139A, R-139P, R-139X				
1401, 1402, 1403, 1404, 1405, 1406, 1407, 1408, 1409, Chassis R-140, Series Chassis R-140A, R-140P, R-140X				
1411, 1412, 1413, 1414, 1415, 1416, 1417, 1418, 1419, Chassis R-141, Series Chassis R-141A, R-141P, R-141X				
1421, 1422, 1423, 1424, 1425, 1426, 1427, 1428, 1429, Chassis R-142, Series Chassis R-142A, R-142P, R-142X				
1431, 1432, 1433, 1434, 1435, 1436, 1437, 1438, 1439, Chassis R-143, Series Chassis R-143A, R-143P, R-143X				
1441, 1442, 1443, 1444, 1445, 1446, 1447, 1448, 1449, Chassis R-144, Series Chassis R-144A, R-144P, R-144X				
1451, 1452, 1453, 1454, 1455, 1456, 1457, 1458, 1459, Chassis R-145, Series Chassis R-145A, R-145P, R-145X				
1461, 1462, 1463, 1464, 1465, 1466, 1467, 1468, 1469, Chassis R-146, Series Chassis R-146A, R-146P, R-146X				
1471, 1472, 1473, 1474, 1475, 1476, 1477, 1478, 1479, Chassis R-147, Series Chassis R-147A, R-147P, R-147X				
1481, 1482, 1483, 1484, 1485, 1486, 1487, 1488, 1489, Chassis R				

# STEWART-WARNER STROMBERG-CARLSON

MODEL	STEWART-WARNER CORP.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
1491, 1492, 1493, 1494, 1495, 1496, 1497, 1498, 1499, Chassis R-149X, 1601, 1602, 1603, 1604, 1605, 1606, 1607, 1608, 1609, Chassis R-160	Phonograph circuit .....7-19, 7-20		
1611-D, 1612-D, 1613-D, 1614-D, 1615-D, 1616-D, 1617-D, 1618-D, 1619-D, Chassis R-161-D	Schematic, voltage, parts .....7-8		
1621-D, 1622-D, 1623-D, 1624-D, 1625-D, 1626-D, 1627-D, 1628-D, 1629-D, Chassis R-162-D	Data .....Changes 10-6 Schematic, socket, trimmers, voltage .....8-7 Alignment, parts, notes .....8-8 Schematic, socket, trimmers, voltage .....8-9 Alignment, parts, notes .....8-10 Schematic, socket, trimmers, voltage, notes .....9-1 Alignment, parts, notes .....9-2 Schematic, socket, trimmers, voltage, notes .....9-1 Alignment, parts, notes .....9-2 Schematic, voltage, socket, trimmers .....9-3 Circuit data, alignment, parts 9-4 Schematic, socket, trimmers, voltage, notes .....8-11 Alignment, parts .....8-12 Schematic, socket, voltage, trimmers .....9-5 Alignment, parts .....9-6 See model 1691 Phono. connections .....8-11 Schematic, socket, trimmers, voltage .....8-13 Alignment, parts .....8-14 Phono. connections .....8-14 Schematic, socket, voltage, parts .....9-7 Alignment, trimmers, parts .....9-8 Schematic, socket, voltage, parts .....9-9 Alignment, trimmers, parts, dial data .....9-10 Data .....9-9 Phonograph schematic .....9-9 Schematic, socket, voltage, parts .....9-11 Alignment, trimmers, dial data 9-12 Phonograph data .....9-11 Schematic, socket, voltage, parts, dimmer connections.....9-13 Alignment, trimmers, dial data 9-14 Schematic, socket, voltage, 9-15, 16 parts, data .....9-17 Alignment .....9-17 AFC data, socket, trimmers, tuner data .....9-18 Notes, trouble chart .....9-25, 26		
1631-D, 1632-D, 1633-D, 1634-D, 1635-D, 1636-D, 1637-D, 1638-D, 1639-D, Chassis R-163-D			
1641-D, 1642-D, 1643-D, 1644-D, 1645-D, 1646-D, 1647-D, 1648-D, 1649-D, Chassis R-164-D			
1671, 1672, 1673, 1674, 1675, 1676, 1677, 1678, 1679, 1680, 1681, 1682, 1683, 1684, 1685, 1686, 1687, 1688, 1689, Chassis R-167S and R-168			
1691, 1692, 1693, 1694, 1695, 1696, 1697, 1698, 1699, Chassis R-169			
1711, 1712, 1713, 1714, 1715, 1716, 1717, 1718, 1719, Chassis R-171			
1721, 1722, 1723, 1724, 1725, 1726, 1727, 1728, 1729, Chassis R-172			
Chassis 1729X, 1733, 1734, 1735, 1736, 1737, 1738, 1739, Chassis R-173			
Chassis 173X			
1801, 1802, 1803, 1804, 1805, 1806, 1807, 1808, 1809, Chassis R-180			
1811, 1812, 1813, 1814, 1815, 1816, 1817, 1818, 1819, Chassis R-181			
Chassis R-181A, R-181B, Chassis R-181W			
1821, 1822, 1823, 1824, 1825, 1826, 1827, 1828, 1829, Chassis R-182			
R-182A, R-182B, R-182W			
1831, 1832, 1833, 1834, 1835, 1836, 1837, 1838, 1839, Chassis R-183			
1841, 1842, 1843, 1844, 1845, 1846, 1847, 1848, 1849, Chassis R-184			
"Magic Keyboard" for models 1845 to 1860, Chassis R-184, R-185, R-186	Trouble chart, concluded, back switch .....9-27, 28 Bakelite and side switches 9-29, 30 Clutch, pawls, cams, keys, cam lock, bar and arm .....9-31, 32 Key stop bar, kick-out arm, star wheel motor, gears coupling, motor connections, dial mechanism .....9-33, 34 AFC and mechanism notes .....9-35, 36 Manual tuning, parts .....9-37, 38 Dial mechanism and miscellaneous parts .....9-38 Mechanism details .....9-38 Phonograph data .....9-38 Schematic, voltage, socket, dimmer data .....10-43, 44		
Chassis R-1845-W, 1851, 1852, 1853, 1854, 1855, 1856, 1857, 1858, 1859, Chassis R-185			
1851A, 1852A, 1853A, 1854A, 1855A, 1856A, 1857A, 1858A, 1859A, Chassis R-185A			
1851B, 1852B, 1853B, 1854B, 1855B, 1856B, 1857B, 1858B, 1859B, Chassis R-185B			
1851W, 1852W, 1853W, 1854W, 1855W, 1856W, 1857W, 1858W, 1859W, Chassis R-185W			
1861, 1862, 1863, 1864, 1865, 1866, 1867, 1868, 1869, Chassis R-186			
Chassis R-186W			
"Magic Keyboard" for models 1861 to 1889, Chassis R-186, 1886, 1887, 1888, 1889, Chassis R-188	Alignment .....10-45 Trimmers, phone, data, "Magic Keyboard" data, parts 10-46 Schematic, socket, voltage, parts, tuner data, speaker data .....9-19, 20 Alignment .....9-21 AFC data, trimmers, tuner, parts .....9-22 Phonograph data .....9-22 See "Magic Keyboard" models 1845 etc. Schematic, socket, voltage, parts .....9-23 Alignment, trimmers, circuit data .....9-24 Schematic, voltage, socket, notes .....10-47 Alignment, trimmers, battery connections .....10-48 Schematic, voltage, socket .....10-49 Alignment, trimmers, circuit data .....10-50 Schematic, voltage, socket .....10-51 Alignment, trimmers .....10-52 Schematic, voltage, socket .....10-53 Alignment, trimmers, drive cord data, notes .....10-54		
1901, 1902, 1903, 1904, 1905, 1906, 1907, 1908, 1909, Chassis R-190D			
1911, 1912, 1913, 1914, 1915, 1916, 1917, 1918, 1919, Chassis R-191D			
1921, 1922, 1923, 1924, 1925, 1926, 1927, 1928, 1929, Chassis R-192D			
3041, 3042, 3043, 3044, 3045, 3046, 3047, 3048, 3049, Chassis R-304, R-304A			
38, 43, 51, O-108 Clock model			
STORY & CLARK RADIO CORP.			
See ELECTRIC SPECIALTIES EXPORT CO.			
STROMBERG-CARLSON TEL. MFG. CO.			
Compact Police Receiver			
Wiring, socket .....41 Schematic .....44			
2859, 2860			
*590, *591			

STROMBERG-CARLSON TEL. MFG. CO.—(Cont.)		RADIOTRON	
MODEL	REVISION	EARLY COMPLETE PAGE	REVISION
Multiple-Record Phonograph	1-17	Chassis wiring	2-1
Phonograph Pick-up	1-17	Schematic, socket, voltage	1-16
1-A	1-1	Schematic, socket	1-17
1-B	1-1	Schematic, socket	1-17
10, 11	1-14	Schematic, socket, voltage	1-1
	1-15	Chassis wiring	1-15
		Voltage, socket, resistance	2-1
12, 14	2-1	Schematic, socket, voltage	1-16
16, 17 DO	1-17	Chassis wiring	1-17
18, 20 AO	1-18	Schematic, socket	1-17
	1-18	Schematic	1-18
	1-19	Chassis wiring	1-19
	1-20	Voltage, parts values	1-19
22, 22-A	1-20	Chassis views	1-20
	1-21	Chassis wiring	1-21
	2-4	Chassis wiring	2-4
	2-5	Schematic, socket	2-5
25, 26 AO	2-6	Voltage, values	2-6
	2-7	Chassis wiring	2-7
	2-8	Chassis wiring	2-8
	2-9	Schematic, socket	2-9
	2-10	Voltage	2-10
27 AO	2-11	Condenser and resistor values	2-11
	2-12	Chassis wiring	2-12
	2-13	Schematic	2-13
29	2-14	Voltage, parts list	2-14
	2-15	Chassis wiring	2-15
	2-16	Schematic, socket, data	2-16
	2-17	Parts list, voltage	2-17
38	2-18	Additional data	2-18
	4-3	Schematic, alignment	4-3
	4-4	Voltage, resistance data	4-4
	4-5	Chassis wiring	4-5
	4-6	Parts list	4-6
38-A	6-14	Schematic	6-14
37	3-8	Schematic, socket	3-8
	3-4	Voltage, parts list	3-4
38, 39, 40, 41 (1st type)	2-18	Schematic, socket, data	2-18
	2-19	Chassis wiring, data	2-19
	2-20	Parts list, voltage	2-20
38, 39, 40, 41 (2nd type)	3-5	Schematic, socket, data	3-5
	3-6	Chassis wiring, data	3-6
48, 49, 50, 51	3-7	Parts list, voltage	3-7
	3-8	Alignment data, notes	3-8
	3-9	Schematic	3-9
	3-10	Chassis wiring	3-10
52, 54	3-11	Voltage, resistance data	3-11
	4-7	Schematic, alignment data	4-7
	4-8	Voltage, circuit notes	4-8
55, 56	4-9	Chassis wiring	4-9
	4-10	Schematic, voltage	4-10
	4-11	Socket, voltage	4-11
	4-12	Resistance data	4-12
	4-13	Chassis wiring	4-13
	4-14	Selector notes	4-14
	4-15	Additional data	4-15
56L, 58LB, 58T, 58TB, 58W, 58WB	7-18	Schematic, voltage, trimmers, chassis	7-18
	6-1	Chassis wiring, list of models	6-1
60	6-2	Alignment	6-2
	7-10	Specifications, schematic	7-10
	6-1	Chassis wiring	6-1
	6-2	Chassis views	6-2
61L, 61LB, 61T, 61TB, 61W, 61WB	6-3	Socket, voltage, parts	6-3
	6-4	Schematic, socket, trimmers, voltage	6-4
61X, 61Z	7-1	Alignment	7-1
	7-2	Schematic, socket, trimmers	7-2
62, 68, 62B, 68B	7-3	Chassis wiring	7-3
	7-4	Schematic, chassis assembly	7-4
	6-5	Chassis wiring	6-5
	6-6	Socket, trimmers, parts	6-6
	6-8	Circuit data, voltage	6-8
64	7-10	Alignment	7-10
	4-16	Schematic, notes	4-16
	4-17	Voltage, parts list	4-17
	4-18	Chassis wiring	4-18
STROMBERG-CARLSON TEL. MFG. CO.—(Cont.)		RADIOTRON	
MODEL	REVISION	EARLY COMPLETE PAGE	REVISION
64	4-19	Chassis assembly	4-19
	4-20	Selector notes	4-20
65, 66, 67	7-5	Schematic, socket, voltage	7-5
	7-6	Chassis wiring	7-6
68	5-5	Specifications, parts	5-5
	5-6	Schematic, voltage	5-6
	5-7	Socket layout, chassis views	5-7
68 Amplifier	5-9	Chassis wiring	5-9
	5-10	Chassis views	5-10
68 Selector	5-8	Chassis wiring	5-8
69 All Wave Selector	5-11	Data	5-11
	5-12	Schematic, notes	5-12
	5-13	Chassis wiring	5-13
	5-14	Socket layout, voltage, parts list	5-14
70, 70B, 72, 72B, 72D, 74, 74B, 74D	5-15	Chassis views	5-15
	6-7	Circuit data, parts, speaker data	6-7
	6-8	Chassis assembly	6-8
	6-9	Schematic	6-9
	6-10	Chassis wiring	6-10
	6-11	Voltage	6-11
	6-12	Trimmers	6-12
80	6-13	Alignment	6-13
	7-7	Schematic, voltage	7-7
	7-8	Chassis wiring	7-8
82, 82-B	7-9	Socket, trimmers, parts list	7-9
	6-15	Circuit data, voltage	6-15
	6-16	Chassis assembly	6-16
	6-17	Schematic, chassis wiring	6-17
	6-18	Socket, trimmers, parts	6-18
	7-10	Alignment	7-10
88, 88-B	6-19	Circuit data, voltage	6-19
	6-20	Chassis wiring	6-20
	6-21	Schematic, chassis assembly	6-21
	6-22	Socket, trimmers, parts	6-22
84, 84-B	7-10	Alignment	7-10
	7-11	Schematic, voltage	7-11
	7-12	Chassis wiring	7-12
	7-13	Chassis views, circuit data, trimmers	7-13
116	7-14	Alignment	7-14
	7-15	Schematic, socket, trimmers, voltage	7-15
125AO-DO	7-16	Chassis wiring	7-16
	7-17	Chassis views, alignment, parts	7-17
136H, 136L	7-18	Schematic, parts	7-18
	8-1	Alignment, voltage	8-1
	8-2	Socket, trimmers, chassis	8-2
	8-3	Chassis wiring	8-3
	8-5	Schematic, parts	8-5
127H, 127M	8-4	Socket, trimmers, chassis	8-4
	8-6	Alignment, voltage	8-6
	10-12	Chassis wiring	10-12
180H, 180HB, 190L, 190LB, 190M, 190MB, 190R, 190RB, 190U, 190UB	7-19	Schematic, socket, trimmers, sensitivity control data	7-19
	7-20	Chassis wiring	7-20
	7-21	Voltage, alignment	7-21
	7-22	Socket, trimmers, parts, circuit data	7-22
	8-15	Schematic, parts	8-15
140H, 140HB, 140K, 140L, 140KB, 140LB, 140P, 140PB	8-16	Voltage, alignment, trimmers	8-16
	8-17	Socket, trimmers, chassis, notes	8-17
145L, 145LB, 145P, 145PB	9-1	Chassis wiring	9-1
	7-23	Schematic, socket, trimmers	7-23
	7-24	Chassis wiring	7-24
	7-25	Circuit data, chassis, alignment, voltage	7-25
	8-7, 8-8	Parts list	8-7, 8-8
150L, 150LB	8-9	Schematic, parts	8-9
	8-9	Socket, trimmers, chassis	8-9

# STROMBERG-CARLSON

STROMBERG-CARLSON TEL. MFG. CO.—(Cont.)	RADIOTRON EARLY COMPLETE PAGE	REVISED PAGE
STROMBERG-CARLSON TEL. MFG. CO.—(Cont.)	MODEL	MODEL
150L, 150LB	255L, 255LB	255L, 255LB
160L, 160LB, 160P, 160PB	260L, 260LB, 260P, 260PB	260L, 260LB, 260P, 260PB
180L, 180LB		
225 AC-D0		
228H, 228HB, 228L, 228LB		
239P		
230H, 230HB, 230L, 230LB, 230P, 230PB, 231R, 231RB, 231P, 231PB		
230H, 230HB, 230L, 230LB, 230P, 230PB, 231R, 231RB, 231P, 231PB		
235H, 235HB, 235L, 235LB		
240H, 240HB, 240L, 240LB, 240P, 240PB, 240R, 240RB, 240S, 240SB, 240W, 240WB, 240P, 240PB		
245L, 245LB, 245M, 245MB, 245R, 245RB, 245P, 245PB		
250L, 250LB		
255L, 255LB		
Alignment ..... 8-10	Alignment, Part 1 ..... 10-7	Alignment, Part 1 ..... 10-7
Data ..... 8-10	Alignment, Part 2; Parts list ..... 10-8	Alignment, Part 2; Parts list ..... 10-8
Chassis views ..... 9-2	Schematic, specifications ..... 9-31	Schematic, specifications ..... 9-31
Circuit data, chassis wiring ..... 8-11, 8-12	Chassis wiring, phonograph ..... 9-32	Chassis wiring, phonograph ..... 9-32
Alignment ..... 8-10	Chassis wiring, phonograph, tuner ..... 9-33	Chassis wiring, phonograph, tuner ..... 9-33
Socket, trimmers, chassis ..... 8-13	Voltage, alignment ..... 9-33, 34	Voltage, alignment ..... 9-33, 34
Voltage, chassis ..... 8-14	Alignment, concluded, AFC ..... 9-35	Alignment, concluded, AFC ..... 9-35
Circuit data, chassis wiring ..... 8-15	Tuner data ..... 9-36	Tuner data ..... 9-36
Schematic ..... 8-19	Tuner assemblies and parts ..... 9-37	Tuner assemblies and parts ..... 9-37
Socket, trimmers, chassis ..... 8-18	Socket, trimmers, parts ..... 9-38	Socket, trimmers, parts ..... 9-38
Alignment, voltage ..... 8-20	Schematic ..... 1-8	Schematic ..... 1-8
Parts ..... 8-21	Chassis, socket, trimmers ..... 10-9	Chassis, socket, trimmers ..... 10-9
Chassis wiring ..... 9-7, 8	Chassis, wiring, voltage ..... 10-10	Chassis, wiring, voltage ..... 10-10
Chassis views ..... 9-9	Alignment, parts ..... 10-11	Alignment, parts ..... 10-11
Schematic, parts ..... 8-23	Schematic, socket, trimmers ..... 10-13	Schematic, socket, trimmers ..... 10-13
Socket, chassis ..... 8-22	Chassis wiring ..... 10-14	Chassis wiring ..... 10-14
Voltage, alignment, trimmers, notes ..... 8-24	Voltage, alignment, phono- graph data ..... 10-15	Voltage, alignment, phono- graph data ..... 10-15
Chassis wiring ..... 9-10	Electric tuning data ..... 10-16	Electric tuning data ..... 10-16
Schematic, socket, trimmers ..... 8-25	Alignment ..... 10-16	Alignment ..... 10-16
Voltage, alignment, parts ..... 8-26	Schematic ..... 10-17	Schematic ..... 10-17
Chassis wiring ..... 9-11	Chassis wiring ..... 10-18	Chassis wiring ..... 10-18
Chassis views ..... 9-12	Electric tuning data ..... 10-16	Electric tuning data ..... 10-16
Schematic, socket, trimmers ..... 8-27	Voltage, socket, trimmers ..... 10-30	Voltage, socket, trimmers ..... 10-30
Voltage, alignment ..... 8-28	Chassis wiring ..... 10-20	Chassis wiring ..... 10-20
Socket, chassis, notes ..... 8-29	Alignment, phonograph, tuner data ..... 10-21	Alignment, phonograph, tuner data ..... 10-21
Parts ..... 8-30	Voltage, socket, trimmers ..... 10-22	Voltage, socket, trimmers ..... 10-22
Chassis wiring, specifications ..... 8-31	Schematic ..... 10-23	Schematic ..... 10-23
Schematic ..... 8-31		
Socket, chassis, parts ..... 8-32	Chassis wiring ..... 10-24	Chassis wiring ..... 10-24
Trimmers ..... 8-35	Voltage, socket, trimmers, cir- cuit data ..... 10-25	Voltage, socket, trimmers, cir- cuit data ..... 10-25
Alignment, voltage ..... 8-36	Alignment ..... 10-26	Alignment ..... 10-26
Chassis wiring ..... 8-33	Electric tuning data ..... 10-16	Electric tuning data ..... 10-16
Chassis wiring ..... 8-34	Schematic ..... 10-27	Schematic ..... 10-27
Schematic, specifications ..... 9-13	Chassis wiring ..... 10-28	Chassis wiring ..... 10-28
Chassis wiring ..... 9-14	Voltage, alignment ..... 10-29	Voltage, alignment ..... 10-29
Socket, trimmers, voltage, alignment ..... 9-15	Socket, trimmers, bass re- sponse data ..... 10-30	Socket, trimmers, bass re- sponse data ..... 10-30
Alignment, phonograph data, tuner adjustments ..... 9-16	Electric tuning data ..... 10-31	Electric tuning data ..... 10-31
Tuner adjustments, concluded, parts ..... 9-17	Schematic ..... 10-32	Schematic ..... 10-32
Continuity test ..... 10-34	Chassis wiring ..... 10-33	Chassis wiring ..... 10-33
Schematic, circuit data, specifications ..... 9-19	Voltage, socket, trimmers ..... 10-33	Voltage, socket, trimmers ..... 10-33
Chassis wiring ..... 9-20	Electric tuning data ..... 10-16	Electric tuning data ..... 10-16
Voltage, socket, trimmers ..... 9-21	Chassis wiring ..... 10-35, 36	Chassis wiring ..... 10-35, 36
Chassis views, specifications ..... 9-22	Voltage, socket, trimmers ..... 10-39	Voltage, socket, trimmers ..... 10-39
Alignment, trimmers ..... 9-23	Tuner data ..... 10-40	Tuner data ..... 10-40
Parts list ..... 9-24	Schematic ..... 10-41, 42	Schematic ..... 10-41, 42
Schematic, specifications ..... 9-26	Alignment, Part 1 ..... 10-43	Alignment, Part 1 ..... 10-43
Chassis wiring, tuner ..... 9-27, 28	Alignment, Part 2, voltage, tuner ..... 10-44	Alignment, Part 2, voltage, tuner ..... 10-44
Socket, trimmers, voltage, alignment ..... 9-29	Socket, trimmers, circuit data ..... 10-39	Socket, trimmers, circuit data ..... 10-39
Alignment, concluded, tuner, parts ..... 9-30	Schematic ..... 1-3	Schematic ..... 1-3
Schematic ..... 8-37	Schematic, socket ..... 1-3	Schematic, socket ..... 1-3
Voltage, trimmers, phono, data ..... 8-38	Power Unit, Schematic ..... 1-11	Power Unit, Schematic ..... 1-11
Alignment ..... 8-39	Schematic, socket ..... 1-1	Schematic, socket ..... 1-1
Chassis, parts ..... 8-40	Schematic, socket ..... 1-2	Schematic, socket ..... 1-2
Continuity test ..... 10-5	Schematic, socket ..... 1-4	Schematic, socket ..... 1-4
Chassis wiring ..... 10-1	Schematic, socket, voltage ..... 1-5	Schematic, socket, voltage ..... 1-5
Chassis views ..... 10-2	Chassis wiring ..... 1-6	Chassis wiring ..... 1-6
Chassis wiring ..... 10-3, 4	Schematic, socket, voltage ..... 1-7	Schematic, socket, voltage ..... 1-7
Socket, trimmers, voltage, continuity ..... 10-5		
Flash tuner assembly, phono- graph data ..... 10-6		



STROMBERG-CARLSON TEL. MFG. CO.—(Cont.)			RADIOTRON		
MODEL	EARLY PAGE	REVISED PAGE	EARLY PAGE	COMPLETE PAGE	PAGE
638 DO					
641, 642, 652, 654					
641	*603	1-7			
641	*605	1-8			
642	Front	2-21			
645 DO	*607	1-9			
		3-1			
652, 654		2-22			
	*605	1-8			
784	*608	1-10			
744	*609	1-11			
840 AO	*612	1-12			
	*618	1-18			
		2-23			
STUDEBAKER					
See PHILCO RADIO AND TELEVISION CORP.					
STUDEBAKER LABORATORIES					
31					
		Misc. 3-8			
SUPERTONE					
A-31					
		Misc. 5-20			
SUPERTONE PRODUCTS CO., INC.					
Juperba					
		Misc. 5-21			
SUPREME INSTRUMENTS CORP.					
"Master" Diagonometer					
Output Meter					
AAA-1 (8-14-31) Diag-					
nometer					
19 Revised Tube Checker					
33 Ohmmeter					
35					
40 Tube Checker					
44 Volt-Ohmmeter					
55					
56 Analyzer (Weston					
Metered)					
60 Oscillator					
61					
62 Tube Tester					
70 Oscillator					
75 AC-DO Volt-Ohm-Mil					
Meter					
85					
85-PL					
89-C Tube Tester					
89-D Tube Tester					
90 Analyzer					
90 Analyzer (Weston					
Metered 6-J)					
91					
99-A Analyzer					
111					
145					
180					
189 Signal Generator					
222					
"833" Free Reference					
Point Tester					
833 Revised					
833 Deluxe					
839-D Deluxe Analyzer					
400-A Diagonometer					
400-B (No. 4 Series) Di-					
agonometer					
444					
SUPREME RADIO					
Supreme 1931					
		Misc. 4-12			
SYNCHROPHASE					
See A. H. GREBE AND CO.					
L. TATRO PRODUCTS CORP.			RADIOTRON		
MODEL	EARLY PAGE	REVISED PAGE	EARLY PAGE	COMPLETE PAGE	PAGE
A, B					
EN-6-4					
IN-25					
EQ-39, FQ-39					
HQ-39					
NH-44, K-54, M-54					
AK-54, AM-54 (Mayor					
and Senator)					
P-54 (Recorder)					
L-54, N-54					
NO-65, OO-65					
SP-67, TP-67					
AQ-69, BQ-69					
CQ-69, DQ-69					
L-74, N-74 (Lieut. Gov-					
ernor and Governor)					
084					
094 (President)					
H-465, I-465					
A-525, B-525					
L-525					
C-625, D-625					
J-665, K-665					
F-725					
F-913					
M-4616					
O-4626, P-4626					
U-5226, V-5226					
Q-5636, R-5636, S-5636					
T-6216					
W-6236, X-6236, Y-6236					
TEMPLE CORP.			RADIOTRON		
8-60, 8-80, 8-90					
8-61, 8-81, 8-91					
THORDARSON ELEC. MFG. CO.			RADIOTRON		
Eliminator					
R-171					
PP-171					
210 Power Amplifier					
R-210					
213					
250 Power Amplifier					
TIFFANY TONE			RADIOTRON		
See HERBERT H. HORN					
TODD ELECTRIC CO.			RADIOTRON		
Schematic					
TRANSFORMER CORP. OF AMERICA			RADIOTRON		
TO1, TO2					
TO-6					
O-10					

# TRANSFORMER TRAV-LER

TRANSFORMER CORP. OF AMERICA—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
MODEL			
TRANSFORMER CORP. OF AMERICA—(Cont.)			
200 Series (SW Converter)			
AO 220, 25-220	3-4	2463	
AO 240	3-5	2464	
241	3-6	2465	
AO-260, 25-260	3-7	2466	
AO 280, 25-280	3-8	2467	
AC-800	3-9	2468	
AC-820	3-10	2469	
AC-840	3-11	2470	
890	3-12	2471	
AO 420	3-13	2472	
422, 428	3-14	2473	
435	3-15	2474	
440	3-16	2475	
450	3-17	2476	
470, 473	3-18	2477	
480	3-19	2478	
500	3-20	2479	
See I ELCO RADIO & TELEVISION CORP.			
TRAV-ER RADIO AND TELEVISION CORP.			
Air Chief	1-2	2480	
Q SG-DX	1-3	2481	
K	1-4	2482	
SG-DG	1-5	2483	
Trav-Lette	1-6	2484	
5-tube AC-DC Superhet	1-7	2485	
5-tube Battery	1-8	2486	
5-tube, 6-volt Battery	1-9	2487	
6-tube Auto	1-10	2488	
6-tube Battery or A-C	1-11	2489	
6 Tube TRF	1-12	2490	
6, 7 AO Power Pack	1-13	2491	
6, 7 DO Power Pack	1-14	2492	
8-tube Battery or A-C	1-15	2493	
8-9	1-16	2494	
11-tube A-C Superhet	1-17	2495	
41, 46R, 50-A, 442	1-18	2496	
46R, Air Chief	1-19	2497	
50-A	1-20	2498	
51, 511	1-21	2499	
53	1-22	2500	
54	1-23	2501	
56	1-24	2502	
60-A	1-25	2503	
63-A	1-26	2504	
76	1-27	2505	

# TRAVLER RADIO AND TELEVISION CORP.—(Cont.)

MODEL EARLY COMPLETE PAGE

131	Schematic, socket, trimmers, parts	9-1
168	See model 638	
173, 738	Schematic, socket	7-2
400	Schematic, alignment	10-2
415	Socket, trimmers	10-3
420A, 420S	Schematic, alignment	10-7
425	Socket, trimmers	10-8
	Schematic, alignment	10-5
426	Socket, trimmers	10-6
	Tuner	10-12
	Schematic, alignment	10-12
	Socket, trimmers	10-6
	Tuner	10-12
431, 431SW	Schematic, socket	9-2
436M	Schematic	10-7
	Socket, trimmers	10-8
437M	Alignment, tuner	10-12
	Schematic	10-7
	Socket, trimmers	10-6
	Alignment, tuner	10-12
442	See model 41	
455L	Schematic, alignment	10-7
465M	Socket, trimmers	10-8
	Schematic	10-9
	Socket, trimmers	10-2
466M	Alignment, tuner	10-12
	Schematic	10-9
	Socket, trimmers	10-8
501	Alignment, tuner	10-12
	Schematic	10-10
A502	Socket, trimmers	10-8
	Schematic	10-9
511	Socket, trimmers	10-8
512	See model 51	
521	Schematic, socket	7-1
522	Schematic, socket	8-1
525, 6-Volt DO	Schematic	7-1
536M	Schematic	10-11
	Socket, trimmers	10-6
539M	Alignment	10-12
	Schematic	10-11
542	Socket, trimmers	10-6
552B	Alignment	10-12
560	Schematic, alignment	10-11
	Socket, trimmers	10-6
622, 623	Schematic, alignment	10-5
633, 634, 168	Schematic, alignment	10-5
635M	Socket, trimmers	10-6
642	Schematic	7-8
645E	Schematic, socket	8-2
	Schematic, notes	7-4
733	Alignment	10-12
	See model 173	

## TRIANGLE ELECTRIC COMPANY

6P, Imperial	Schematic, parts list	7-1
	Alignment, notes, socket, trimmers	7-3

## TRIPLETT ELECTRICAL INSTRUMENT CO.

1126	Schematic	4-1
1150	Schematic	4-1
1151 Oscillator	Schematic	5-1
1166	Schematic	4-2
1166A, 1220A	Schematic	7-1
1200 Tester	Schematic	5-2
1210, Above Serial 100,000	Schematic	Misc. 6-33
1210, Below Serial 100,000	Schematic	Misc. 6-33
1210A Tube Tester	See model	1166A
1220A	Schematic	7-2
1231 Signal Generator	Schematic	7-1
1502 Tester	Schematic	7-3
1508 Tester	Schematic	7-4

# RADIOTRON

EARLY COMPLETE PAGE

131	Schematic, socket, socket, trimmers, parts	9-1
168	See model 638	
173, 788	Schematic	7-2
400	Schematic, socket	10-2
415	Schematic, alignment	10-5
	Socket, trimmers	10-6
420A, 420S	Schematic, alignment	10-7
	Socket, trimmers	10-8
425	Schematic, alignment	10-5
	Socket, trimmers	10-6
	Tuner	10-12
426	Schematic, alignment	10-5
	Socket, trimmers	10-6
	Tuner	10-12
431, 431SW	Schematic, socket	9-2
436M	Schematic	10-7
	Socket, trimmers	10-8
	Alignment, tuner	10-12
437M	Schematic	10-7
	Socket, trimmers	10-6
	Alignment, tuner	10-12
442	See model 41	
455L	Schematic, alignment	10-7
	Socket, trimmers	10-8
465M	Schematic	10-9
	Socket, trimmers	10-2
	Alignment, tuner	10-12
466M	Schematic	10-9
	Socket, trimmers	10-8
	Alignment, tuner	10-12
501	Schematic	10-10
	Socket, trimmers	10-8
A502	Schematic	10-9
	Socket, trimmers	10-8
511	See model 51	
512	Schematic	7-1
521	Schematic, socket	8-1
522	Schematic, socket	8-1
525, 5-Volt DO	Schematic	7-1
536M	Schematic	10-11
	Socket, trimmers	10-6
	Alignment	10-12
	Schematic	10-11
	Socket, trimmers	10-6
539M	Alignment	10-12
	Schematic	10-11
	Socket, trimmers	10-6
542	Alignment	10-12
542	Schematic	7-2

## TRUEVALUE See WESTERN AUTO SUPPLY CO.

6-U	Schematic	Misc. 5-33
-----	-----------	------------

## TURNER CO.

Crystal Microphone	Schematic	5-2
G Amplifier	Schematic	Misc. 7-1
PDQ, B-5-Series A	Schematic, cable connections, data	8-1
3S5, 3S9 Automatic Control	Schematic connections, installation data	8-3
	Station cable and switch connections, color code	8-4
B-5-Series A	See model PDQ	
M-8	Schematic	Misc. 6-34
PR-15, PR-19	Schematic, stations connections	8-2
MC-16	Schematic	5-1
M-16	Schematic	Misc. 6-34
FB-1000	Schematic	5-1
5780	Schematic	5-2

## TYRMAN ELECTRIC CORP.

Shield Grid-7	Schematic	Misc. 1-20
Tyrman 10	Schematic	Misc. 1-20
Imperial 80	Schematic	Misc. 1-20

EARLY RADIOTRON COMPLETE	PAGE
*42	2505
*43, 44	2506
*44-A	2507
*44-B	2508
*29	2585
*46	2509
*47	2510
*49	2512
*45	2511
*49, 51	2514
*45	2513
*30	2485
*31, 2, 8	2486
*800-B, C	2516
*800-A, C	2515

MODEL	ULTRAMAR MFG. CORP.	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
306, 316	Schematic, socket, trimmers, alignment	10-4		
307, 317	Schematic, socket, trimmers, alignment	9-1		
309, 319	Schematic, socket, trimmers, alignment	9-2		
456	Schematic, trimmers	10-1		
	Sockets, trimmers	10-2		
465	Alignment, tuner	10-4		
	Schematic, alignment	10-1		
477	Socket, trimmers	10-2		
	Tuner data	10-4		
	Schematic	10-1		
	Socket, trimmers	10-2		
	Alignment, tuner	10-4		
487	Schematic, socket, trimmers	10-3		
	Alignment	10-4		
801, 802	Schematic, voltage, parts	8-1		
	Socket, trimmers, alignment	8-2		
856	Schematic	10-1		
	Socket, trimmers	10-2		
	Alignment, tuner	10-4		
877	Schematic	10-3		
	Socket, trimmers	10-2		
889	Alignment, tuner	10-4		
UNITED AIR CLEANERS				
See SENTINEL RADIO CORP.				
UNITED AMERICAN BOSCH CORP.				
BAN Power Units	Schematic, values	1-1	2481	
BDN Power Units	Schematic, values	1-1	2481	
Amoroda	See model 16 & 27			
Cruisers	See model 35			
Essex	See model 4 & 10			
Police Auto	See model 108			
Police Motorcycle	See model 119			
MMU-6 (Edition 1 Mag-Motor)	Schematic, data	3-3		
04	Applications	3-8		
4	Schematic, voltage, parts	6-8		
4 Essex	Schematic, voltage	3-5		
05	Schematic, voltage, parts	6-20		
5 A	Schematic, socket, voltage	1-3	2486	52-A
5-A	Parts, values	1-3	2487	52-B
7 DO	See model 205			
7 DO	Schematic	3-4	2488	
7-0 DO	Schematic	3-4	2488	
9-20	See model 100			
10 Essex	Schematic, voltage, data	3-6	2490	
116 Amoroda	Data	Changes 9-6		
20-K, 20-L	Schematic, socket, voltage	1-4	2484	28
27 Amoroda	Schematic, socket, voltage	2-1	2491	52-O
28 AO (2 Types)	Chassis, values, data	2-2	2492	52-D
28 AO Power Pack	Schematic, socket, voltage	1-4	2484	28
29 AO	Schematic, socket, voltage	1-5	2493	35
29 AO	Chassis, parts, values	1-6	2494	38
29 AO, 825 Power Pack	Schematic, voltage	1-5	2495	36
31, 32 AO	Schematic, chassis, voltage	1-7	2495	36
35 Cruisers	Schematic, socket, chassis data	2-3	2497	52-E
87 AO	Voltage, parts list	2-4	2498	52-F
	Schematic, socket, voltage	1-4	2498	29
	Schematic, socket, data	3-7	2499	
	Alignment data, voltage, values	3-8	2500	
40, 41 AO	Schematic, chassis	4-1		
45-A, 45-O	Electrical, values, voltage	4-2		
	Schematic, color code	5-1		
	Alignment data	5-2		
	Test data, parts list	5-3		
	Chassis view, data	5-4		
	Voltage, resistance chart	5-5		
46 AO, 126, 146, 166, 176	Schematic, socket, voltage	1-4	2484	28
48 AO	Schematic, socket, voltage	1-8	2496	34
48 AO	Schematic, socket, voltage data	1-8	2503	39
	Chassis wiring views	1-10	2504	40, 41

UNITED AMERICAN BOSCH CORP.—(Cont.)			RADIOTRON		
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
260, 261	Alignment data, socket, trimmers	5-22			
305 Ed. 1, 305-A	Schematic, resistor color code	3-13	2535		
	Voltage, alignment, data	3-14	2586		
305 Ed. 2, 405	Socket, chassis, trimmers	7-3			
306	Socket, trimmers, alignment	7-3			
	Schematic, voltage, resistor	7-4			
	Circuit data, socket, trimmers, chassis	8-1, 8-2			
307	Alignment, parts	8-3			
	Schematic	8-4			
310, 310A	Socket, trimmers, voltage, alignment	5-23			
	Schematic	7-7			
	Socket, voltage, parts	5-25			
312, 313 (AO)	Socket, trimmers, alignment	5-26			
350	Schematic, socket, voltage	7-7			
	Adjustments	3-1			
	Schematic, voltage, socket, parts	2-16			
352	Socket, trimmers, voltage, alignment	4-9			
355	Schematic, socket, voltage	7-22			
357	Alignment, parts	5-27			
	Schematic, voltage, parts list	5-28			
	Socket, trimmers, voltage, alignment	4-10			
360	Schematic	7-22			
	Socket, trimmers, voltage, alignment	5-24			
360 Late, 361, 364	Alignment data, part 1	7-22			
	Alignment data, part 2	5-29			
370	Schematic, socket, voltage, parts	5-30			
	Schematic, data	4-11			
376	Socket, trimmers, alignment, parts, voltage	7-5			
376BT, 376F, 376S	Schematic, voltage, socket, parts	7-6			
385	Alignment data, part 1	4-12			
386	Alignment data, part 2	5-31			
	Schematic	5-32			
	Schematic, parts	5-33			
	Socket, trimmers, alignment, voltage	6-1			
402, Ed. 1, 2, 3	Speaker data, trimmers, parts	6-2			
	Data	10-6			
402	Schematic, voltage, parts	6-3			
405	Socket, trimmers, alignment	6-4			
420	Schematic, voltage	6-5			
420, 421	Socket, trimmers, alignment	6-6			
	Speaker data, trimmers, parts	6-7			
	Schematic, socket, trimmers, data	6-9			
430, 430J, 430T	Alignment, voltage, parts	6-10			
431, 431J, 431T	Schematic	5-34			
434, 434J, 434T	See model 305, Ed. 2	5-35			
440C, 440T, 441C, 441T, 444C, 444T	Schematic, parts, socket, trimmers, voltage, alignment, parts	6-11			
	Schematic, resistors	6-12			
450L, 450H, 451L, 451H, 454L, 454H	Trimmers, socket, parts, alignment	6-13			
	Schematic, voltage	6-14			
	Socket trimmers, parts, alignment	6-15			
	Schematic, voltage	6-16			
460	Socket, trimmers, resistance data	6-17			
460 A, B, R; 461 A, B, R; 464 A, B, R, Ed. 1	Socket, trimmers, parts	6-18			
	Alignment, parts	6-19			
	Schematic	5-36			
	Circuit data, schematic	6-21			
UNITED AMERICAN BOSCH CORP.—(Cont.)			RADIOTRON		
MODEL		REVISED PAGE	EARLY COMPLETE PAGE		
460 A, B, R; 461 A, B, R; 464 A, B, R, Ed. 1	Socket, trimmers, alignment, voltage, parts	6-22			
460 A, B, R, Ed. 2	Schematic, resistances	6-23			
462A, 462Y	Socket, trimmers, alignment, parts	6-24			
	Schematic, voltage	7-8			
470 G, U; 471 G, U; 474 G, U	Socket, trimmers, chassis	7-9			
480, Ed. 1; 480, Ed. 2; 481, 484	Alignment, parts	7-10			
	Schematic, voltage, resistor data	6-27			
	Schematic	6-25, 6-26			
480, Ed. 3	Socket, trimmers, alignment, parts	6-28			
500	Chassis wiring	7-2			
	Schematic	5-45			
501, 502, AO-DO	Socket, chassis, trimmers	7-2			
502	Schematic, socket	5-37			
	Voltage, alignment data	5-38			
	Schematic, socket	5-39			
	Voltage, parts	5-40			
	Socket, trimmers, alignment	7-2			
	Schematic, socket	5-41			
508	Voltage, parts	5-42			
505	Socket, trimmers, alignment	7-2			
	Schematic, socket	5-43			
	Voltage, notes	5-44			
	Schematic, voltage	6-29			
510, 510E	Socket, trimmers, alignment, parts	6-30			
515	Schematic, voltage, socket	6-31			
	Trimmers, alignment	6-32			
524A, Ed. 1, 2, 2D, 2G	Schematic, voltage	8-5			
	Service data, parts, alignment, notes	8-6			
536	Schematic, voltage, socket, trimmers, resistance data	6-34			
565K, 565W	Schematic, parts list	6-33			
575F, 575Q	Socket, trimmers, chassis, alignment, vibrator data, notes	7-11			
585 (Preliminary)	Schematic, voltage, parts list	7-12			
585Y, 585Z	Socket, trimmers, chassis, alignment	7-13			
	Schematic, voltage, coil data	7-14			
595M, 595P	Socket, trimmers, alignment, parts list	7-15			
	Schematic, voltage, resistor data	7-17			
	Schematic, voltage, resistor data	6-35, 6-36			
	Schematic, voltage, resistor data	6-37, 6-38			
600 (Preliminary)	Centr-O-Matic data, alignment, trimmers	6-39			
600 (Final)	Socket, trimmers, parts list	6-40			
601 (Preliminary)	Schematic, voltage, resistor data	6-41, 6-42			
602 (Preliminary)	Centr-O-Matic data, socket trimmers, alignment	6-43			
602C, 602T (Final)	Trimmers, parts	6-44			
604 (Preliminary) (Final)	Schematic, voltage, parts	7-19			
604B	Socket, trimmers, alignment, chassis, notes	9-2			
	Schematic, voltage, parts	7-20			
	Socket, trimmers, alignment, ment, change	8-6			
	Schematic, voltage, parts	7-21			
	Socket, trimmers, chassis, alignment, notes	9-3			
	Schematic, voltage	7-23			
	Socket, trimmers, chassis, parts, alignment	7-24			
605, 605C (Preliminary)	Schematic, voltage	8-7			
	Socket, trimmers, chassis, alignment, parts	8-8			
	Schematic, voltage	7-25			
	Socket, trimmers, parts list	7-26			

# UNITED AMERICAN UNITED MOTORS

UNITED AMERICAN BOSCH CORP.—(Cont.)	REVISID PAGE	RADIOTRON EARLY COMPLETE PAGE
MODEL		
605, 605C (Preliminary)	Final schematic data...Changes 8-6	
610 (Preliminary)	Schematic, voltage, parts .....7-38	
610, 610A (Final)	Socket, trimmers, alignment, notes .....9-4	
620, 625 (Preliminary)	Schematic, voltage .....7-27	
(Final)		
684A	Socket, trimmers, alignment, parts .....7-38	
	Schematic, voltage, resistor data .....6-45	
686, 687	Socket, trimmers, alignment, parts .....6-46	
	Schematic, voltage, coil data, parts .....7-39	
	Socket, trimmers, chassis, alignment, vibrator adjustment .....7-30	
640 (Preliminary)	Schematic, voltage .....7-31	
	Socket, trimmers, alignment, parts .....7-32	
650 (Preliminary)	Final schematic data...Changes 8-6	
	Schematic, voltage .....7-33	
	Socket, trimmers, alignment, parts .....7-34	
660C, 660T (Preliminary)	Final schematic data...Changes 8-6	
	Schematic, voltage, coil resistances .....7-35, 7-36	
	Socket, trimmers, circuit data, parts, alignment .....7-37	
660C, 660T (Final)	Socket, trimmers, chassis .....9-5	
670C, 670S	Schematic, voltage, coil resistances .....7-39, 7-40	
	Parts list .....7-41	
	Socket, trimmers, alignment, data .....7-42	
670C, 670 (Final)	Chassis, notes .....9-6	
680 (Preliminary)	Schematic, voltage, parts list .....7-43, 7-44	
680 (Final)	Schematic data, circuit data, alignment, specifications, notes .....9-7	
	Socket, trimmers, chassis, parts 9-8	
788A2, 787A2, 788A2	Schematic, voltage, coil resistances, parts list .....7-47	
	Socket, trimmers, circuit data, changes, alignment, notes .....7-48	
812	Schematic, parts, voltage, alignment .....7-45	
825 Power Pack	See model 29 AC	
885 (Preliminary)	Schematic, voltage, parts, coil resistances .....7-46	
UNITED MOTORS SERVICE		
66	Schematic, voltage .....8-1	
500	Socket, trimmers, resistance .....8-2	
636 Delco	See model 680 Delco	
	Schematic, voltage .....6-1	
	Alignment, circuit notes .....6-2	
	Socket, trimmers, chassis layout .....6-3	
	Parts list .....6-4	
627 Delco	Schematic .....7-4	
	Socket, trimmers, chassis .....7-5	
628 Delco	Alignment, voltage .....7-6	
	Schematic .....7-7	
	Socket, trimmers, voltage, chassis .....7-8	
	Alignment .....7-9	
629, Below Serial #40100	Schematic .....8-17	
	Socket, trimmers, chassis, voltage .....8-18	
	Alignment .....8-21	
629, Above Serial #40100	Schematic .....8-19	
	Socket, trimmers, chassis, voltage .....8-20	
	Alignment .....8-21	
680, 500, Delco	Schematic .....7-10	
	Socket, trimmers, chassis, voltage .....7-11	
681	Alignment .....7-12	
	Schematic, voltage .....8-3	
UNITED MOTORS SERVICE—(Cont.)		
MODEL		
631	Socket, trimmers, chassis, alignment .....8-4	
631-A	Schematic, voltage .....8-5	
632	Socket, trimmers, alignment .....8-6	
633	Schematic, voltage .....8-7	
634	Socket, trimmers, alignment .....8-8	
635	Schematic, voltage .....8-9	
R 640 Delco	Socket, trimmers, alignment .....8-10	
	Schematic, voltage .....8-11	
R 641 Delco	Socket, trimmers, alignment .....8-12	
	Schematic, voltage .....8-13	
R 642 Delco	Socket, trimmers, alignment .....8-14	
	Parts list .....9-1	
R 643 Delco	Schematic .....9-4	
	Socket, trimmers, chassis, voltage, alignment .....9-5	
R 644 Delco	Socket, trimmers, chassis, alignment, voltage .....9-6	
	Schematic, alignment .....9-2	
R 645 Delco	Socket, trimmers, chassis, voltage, parts .....9-3	
	Schematic .....9-7	
R 646 Delco	Socket, trimmers, chassis, voltage, alignment .....9-8	
	Schematic, voltage .....9-9	
R 663 Delco	Socket, trimmers, chassis, voltage, alignment .....9-10	
	Schematic, voltage .....10-1	
R 664 Delco	Socket, trimmers, alignment, chassis .....10-2	
	Schematic, change .....10-3	
R 665 Delco	Voltage .....10-4	
	Socket, trimmers, chassis .....10-5	
	Alignment .....10-2	
	Schematic .....10-6	
	Socket, trimmers, chassis .....10-5	
	Alignment .....10-2	
	Voltage .....10-4	
R 666, R-667 Delco	Schematic, socket, changes, trimmers, chassis .....10-7	
	Alignment .....10-2	
	Voltage .....10-4	
	Delco-Matic Tuner (for model R-667 only) schematic, parts .....10-8	
	Delco-Matic Tuner parts layout .....10-9	
	Delco-Matic Tuner operating service notes, Part 1 .....10-10	
	Delco-Matic Tuner service notes, Part 2 .....10-11	
	Schematic, socket, trimmers, chassis .....10-12	
	Alignment .....10-2	
	Voltage .....10-4	
	Delco-Matic Tuner (for Model R-669 only) schematic, parts .....10-8	
	Delco-Matic Tuner parts layout .....10-9	
	Delco-Matic Tuner operating service notes, Part 1 .....10-10	
	Delco-Matic Tuner service notes, Part 2 .....10-12	
R 673 Delco	Schematic .....10-13	
	Voltage, socket, trimmers, chassis .....10-14	
	Alignment .....10-15	
1101 Delco	Schematic .....6-5	
	Alignment, data, socket, trimmers, voltage, parts .....6-6	
1102 Delco, Above Serial 781400	Schematic .....6-8	
1102 Delco, Below Serial 781400	Schematic .....6-7	
1102, 1103, Delco	Socket, trimmers, chassis layout .....6-9	
1103 Delco, Above Serial 805120	Alignment, voltage, parts .....6-10	
1103 Delco, Below Serial 805120	Schematic .....6-8	

UNITED MOTORS SERVICE—(Cont.)			RADIOTRON		
MODEL	REVISIONS	REVISIONS	MODEL	REVISIONS	REVISIONS
MODEL	REVISIONS	REVISIONS	MODEL	REVISIONS	REVISIONS
1104 Delco	Schematic ..... 6-11	Alignment, voltage, socket trimmers, chassis, parts ..... 6-12	R-1143	Alignment, tuner ..... 10-22	Socket, trimmers, voltage, chassis ..... 10-26
1105 Delco	Schematic ..... 7-13	Socket, trimmers, chassis, voltage ..... 7-14	R-1144 Delco	Socket, trimmers, chassis, voltage ..... 10-28	Schematic, notes ..... 10-27
1106 Delco	Alignment ..... 7-15	Schematic ..... 7-16	R-1145 Delco	Tuner data ..... 10-22	Alignment ..... 10-29
1107 Delco	Socket, trimmers, chassis ..... 7-17	Alignment, voltage ..... 7-18	2035 (Below serial #1,207,605)	Socket, trimmers, chassis, voltage ..... 10-30	Alignment ..... 10-29
1108 Delco, Glass Tubes	Schematic ..... 7-19	Voltage, socket, trimmers, chassis ..... 7-20	2035 Revised	Schematic, changes ..... 3-1	Schematic ..... 3-1
1109 Delco	Alignment ..... 7-21	Schematic, voltage ..... 7-22	R-2050 Delco	Resistance data ..... 3-2	Schematic, voltage, socket, notes ..... 9-39
1110 Delco	Alignment ..... 7-23	Schematic, voltage ..... 7-24	R-2055 Delco	Socket, trimmers, chassis, alignment ..... 9-40	Schematic, voltage, changes, battery, notes ..... 9-41
R-1115 Delco, Below Serial 100,000	Socket, trimmers, chassis, dial ..... 7-26	Alignment ..... 7-27	3201, 3202, Delco, Above Serial 800,000	Socket, trimmers, chassis, alignment ..... 9-42	Schematic, voltage ..... 6-15
R-1115 Delco, Above Serial 100,000	Socket, trimmers, chassis, dial ..... 7-28	Alignment ..... 7-29	3201, 3202, Delco, Below Serial 800,000	Alignment data, socket, trimmers, chassis ..... 6-16	Schematic, voltage ..... 6-13
R-1116, R-1117 Delco	Socket, trimmers, chassis, voltage, trans-former and phonograph connections ..... 9-15	Alignment, notes ..... 9-16	3203, 3204, Delco	Alignment, socket, trimmers, parts ..... 6-14	Schematic ..... 6-17
R-1118 Delco	Schematic, chassis, voltage, changes ..... 9-17	Socket, trimmers, alignment, notes ..... 9-18	3205 Delco	Socket, trimmers, chassis, parts ..... 6-19	Schematic, voltage ..... 7-31
R-1119 Delco	Schematic, voltage ..... 9-19	Socket, trimmers, chassis, alignment ..... 9-20	3206, 3207 Delco	Socket, trimmers, chassis, parts ..... 7-32	Schematic ..... 7-33
R-1120 Delco	Schematic, voltage ..... 9-21	Socket, trimmers, chassis, alignment ..... 9-22	R-3208, R-3209 Delco	Socket, trimmers, chassis, parts ..... 7-34	Schematic, voltage ..... 7-35
R-1125 Delco	Schematic, socket, trimmers, chassis, voltage, alignment ..... 9-23	Schematic, voltage, alignment ..... 9-24	R-3210 Delco	Schematic, socket, trimmers, chassis, notes, voltage ..... 9-43	Alignment ..... 9-44
R-1126 Delco	Schematic, voltage, alignment ..... 9-25	Schematic, trimmers ..... 9-26	R-3212 Delco	Schematic, socket, trimmers, chassis, voltage, alignment ..... 9-14	Schematic, voltage ..... 9-15
R-1127 Delco	Schematic, trimmers ..... 9-27	Voltage, alignment, socket, trimmers, chassis ..... 9-28	R-3215 Delco	Notes ..... 9-46	Alignment ..... 9-47
R-1128, R-1129 Delco	Voltage, alignment ..... 9-29	Schematic, voltage ..... 9-30	4036, B-O-P	Schematic ..... 10-33	Voltage ..... 10-30
R-1130 Delco	Trimmers, alignment ..... 9-31	Schematic, voltage ..... 9-32	4037	Alignment ..... 10-34	Socket, trimmers, chassis ..... 10-34
R-1131 Delco	Trimmers, alignment ..... 9-33	Schematic ..... 9-34	4038, 600249	Schematic ..... 10-35	Resistance data ..... 4-1
R-1132 Delco	Voltage, trimmers, alignment notes, dial drive data ..... 9-35	Adjustments, notes ..... 9-36	4048	Schematic, voltage ..... 4-5	Alignment, hints ..... 4-6
"Delcomatic" Tuner for model R-1132	Switch data ..... 9-37	Assembly views ..... 9-38	4049, 4050	Alignment, changes ..... 4-7	Alignment, changes ..... 4-8
R-1134, R-1135, R-1139 Delco	Schematic, voltage, socket, trimmers, chassis ..... 10-16	Alignment, tuner ..... 10-17	4051, 32 Volt	Schematic, voltage ..... 4-9	Schematic, alignment ..... 4-10
R-1140 Delco	Alignment, socket, trimmers, chassis ..... 10-18	Voltage, alignment, tuner data ..... 10-19	4052 AO-DO	Schematic, voltage, alignment ..... 7-37	Schematic, voltage, alignment ..... 7-38
R-1141 Delco	Schematic ..... 10-20	Voltage, socket, trimmers, chassis ..... 10-21	6010 Delco	Alignment, voltage ..... 5-1	Alignment, voltage ..... 5-2
R-1142 Delco	Alignment, tuner ..... 10-22	Schematic, notes ..... 10-23	R-6011 Delco	Socket, trimmers, chassis ..... 7-39	Socket, trimmers, chassis ..... 7-40
R-1143 Delco	Socket, trimmers, chassis, voltage ..... 10-24	Alignment, tuner ..... 10-25	R-6012 Delco	Alignment, voltage ..... 7-41	Socket, trimmers, chassis, changes ..... 9-48
				Notes ..... 9-49	Alignment, voltage, changes ..... 9-50
				Schematic, voltage, changes ..... 9-51	Socket, trimmers, chassis, notes ..... 9-52
				Voltage, alignment ..... 9-53	

**RADIOTRON  
COMPLETE  
PAGE**

MODEL	UNITED MOTORS SERVICE—(Cont.)	REVISED PAGE	EARLY PAGE
90101177 Chevrolet, Late Above Serial 1748809	Schematic, voltage	.....9-64	
901574 Chevrolet	Socket, trimmers, chassis, changes	.....9-65	
	Alignment	.....9-66	
	Schematic, voltage	.....6-33	
	Parts layout	.....6-34	
	Circuit data	.....6-35	
	Alignment, parts	.....6-36	
	Changes	.....Changes 9-6	
601586 Chevrolet	See model 405046 Olds		
601662 Chevrolet	Schematic	.....7-1	
	Socket, trimmers, chassis	.....7-2	
	Alignment, voltage	.....7-3	
601814 Chevrolet	Schematic, voltage, socket, trim- mers, alignment	.....8-22	
958200 Chevrolet	Schematic	.....8-29	
9580393 B-O-P	Alignment, voltage, parts	.....8-30	
	Schematic, voltage, alignment	.....8-31	
	Data	.....Changes 9-6	
980441	Similar to 4037		
980455 B-O-P	Schematic, voltage	.....6-37	
980459 B-O-P	Alignment, service notes, parts	.....6-38	
	Schematic	.....6-39	
980507, 980508 Buick	Alignment, voltage, parts	.....6-40	
980509, Buick	Schematic, voltage, alignment	.....9-67	
	Schematic, voltage	.....9-68	
	Alignment	.....9-67	
980525, 980529, Buick	Schematic, voltage	.....9-67	
	Socket, trimmers, chassis, alignment	.....9-69	
980526, Buick	Schematic, voltage	.....9-70	
	Alignment	.....9-71	
	Socket, trimmers, chassis	.....9-70	
	Schematic, voltage	.....9-72	
	Socket, trimmers, chassis	.....9-73	
	Chassis wiring	.....9-72	
	Alignment	.....9-74	
	Schematic, voltage	.....8-33	
	Alignment, change	.....8-32	
	Socket, trimmers, chassis, note	.....8-34	
	Schematic, voltage	.....8-35	
	Alignment, change	.....8-36	
	Socket, trimmers, chassis	.....8-37	
	Schematic, voltage, alignment	.....8-38	
	Socket, trimmers, chassis	.....9-54	
	Schematic, voltage, alignment	.....8-39	
	Socket, trimmers, chassis	.....9-54	
	Schematic, voltage	.....9-77	
	Socket, trimmers, chassis, alignment	.....9-78	
	Schematic, voltage, socket, trimmers, chassis	.....9-79	
	Alignment	.....9-80	
	Schematic	.....9-81	
	Socket, trimmers, chassis, voltage, alignment	.....9-82	
	Schematic, vibrator, condenser data	.....9-83	
	Socket, trimmers, chassis	.....9-84	
	Schematic, voltage	.....8-41	
	Alignment	.....8-40	
	Socket, trimmers, chassis, notes	.....8-42	
	Schematic, socket, trimmers, chassis	.....9-85	
	Alignment, voltage	.....9-86	
	Schematic, voltage, socket, trimmers, chassis	.....9-87	
	Alignment	.....9-88	
	Schematic, voltage, socket, trimmers, chassis	.....9-89	
	Alignment, notes	.....9-90	
	Schematic	.....9-91	
	Socket, trimmers, chassis, voltage, tuner assembly	.....9-92	
	Schematic, socket, chassis, trimmers, voltage	.....9-93	
	Schematic, socket, chassis, trimmers, condenser data	.....9-94	
	See model 985252		
	Schematic, voltage	.....8-43	
	Alignment	.....8-40	
985252, 985286, Chevrolet			
985253, Chevrolet			
985255, Chevrolet			
985283, Chevrolet			
985284, Chevrolet			
985285, Chevrolet			
985286			
985300 Chevrolet			

MODEL	UNITED MOTORS SERVICE—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
R-6015 Delco	Schematic, chassis, notes	.....9-55	
	Socket, trimmers, voltage, alignment	.....9-56	
364441 Chevrolet	Schematic, voltage, service, notes	.....6-21	
	Alignment, parts	.....6-20	
393884 Oldsmobile	Socket, trimmers, chassis	.....6-22	
	Alignment, circuit notes, parts	.....6-26	
	Parts layouts, changes	.....6-25	
	Schematic, voltage	.....6-23	
	Schematic, changes	.....6-24	
	Schematic, voltage, note	.....8-15	
405045 Oldsmobile	Socket, trimmers, alignment, changes	.....8-16	
44289 Late	Schematic	.....7-42	
405046 Olds, Above Serial #1791092	Socket, trimmers, chassis	.....7-43	
	Alignment, voltage	.....7-44	
	Schematic, voltage	.....8-23	
405057, 405062, Olds Early and Late 544290, 544291, 544297, 544298 Pontiac	Socket, trimmers, chassis, alignment, changes	.....8-24	
	Schematics	.....8-25	
405063, Early, Late Oldsmobile	Socket, trimmers, voltage, chassis, alignment	.....8-26	
	Schematic, socket, chassis, trimmers, voltage, changes	.....9-57	
	Alignment, parts	.....9-58	
	Parts layouts, changes	.....6-25	
44245 Buick-Pontiac 1291345 Buick	Alignment, circuit notes, parts	.....6-26	
	Schematic, voltage	.....6-28	
44245 Buick-Pontiac, Below Serial 1748809	Schematic, changes	.....6-24	
544245 Buick-Pontiac, Above Serial 1748809	See model 393885 Olds		
1291345 Buick	See model 405046 Olds		
544245 Buick-Pontiac	Schematic	.....7-42	
544267 (Above Serial #1750000)	Socket, trimmers, chassis	.....7-43	
544268 Pontiac	Alignment, voltage	.....7-44	
544289 Pontiac (Early)	See model 405045		
544289 Pontiac (Late)	Schematic, socket, chassis, trimmers, voltage	.....9-59	
544290, 544291 Pontiac Serials with prefix "A"	Alignment, data, parts	.....9-60	
544290, 544291 Pontiac Serials with prefix "O"	See model 405057 Olds		
544297, 544298 Pontiac 600153 Chevrolet	Schematic	.....7-45	
	Alignment, voltage	.....7-46	
	Same as 4038		
600249	Schematic	.....9-61	
600565, Chevrolet	Voltage, alignment, trimmers	.....9-62	
600566 Chevrolet	Schematic, voltage	.....6-27	
	Alignment, notes	.....6-28	
601038 Chevrolet	Schematic, voltage	.....6-29	
	Parts locations, data	.....6-30	
	Alignment, test data	.....6-31	
	Socket, test data, parts	.....6-32	
	Schematic, voltage	.....8-27	
	Socket, trimmers, chassis, alignment, changes	.....8-28	
	Schematic, voltage	.....9-63	
601176, 601525 Chevrolet	Socket, trimmers, chassis, changes	.....9-65	
601177 Chevrolet Below Serial 1748809	Alignment	.....9-66	





EARLY PAGE	BADIOTRON COMPLETE PAGE
---------------	-------------------------------

WALGREEN CO.—(Cont.)			REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON COMPLETE PAGE		
MODEL							
41, 42	Schematic		10-2		Schematic, voltage, socket, trimmers, chassis, tuner assembly		
41A, 42A	Schematic		10-2		Tuner data	10-4	
55-RS	Schematic, socket, trimmers, alignment, parts		8-2		Alignment, wave-trap notes, tuner data	10-5	
57-RS	Schematic, socket, trimmers, alignment, parts		8-3		Schematic, voltage, socket, alignment, trimmers	10-7	
166 R1S	Schematic, voltage, alignment, notes, parts		10-6		Schematic, voltage, socket, trimmers, chassis	10-6	
255	Schematic, socket, notes, parts		9-1		Alignment, tuner data	10-5	
308, Chassis 801, 802	Schematic, voltage, alignment, parts		10-7		Schematic, socket, trimmers, alignment	10-8	
360, Chassis HE	Schematic		10-3		Schematic, voltage, socket, trimmers, alignment	10-9	
370	Schematic, socket, trimmers, alignment, parts		8-4		Schematic, socket, trimmers	10-10	
400	Schematic, socket		10-8		Schematic, voltage, socket, trimmers, alignment	10-11	
401	Schematic, voltage, alignment		10-9		Schematic, voltage, socket, alignment, trimmers	10-12	
500 (2 and 3 Bands)	Schematic, voltage, alignment		10-10		Schematic, voltage, socket, alignment, trimmers	10-12	
540	Schematic, socket, alignment, trimmers		10-11		Schematic, socket, trimmers, voltage, alignment	10-12	
550 Auto	Schematic, alignment		10-11		Schematic, voltage, socket, trimmers, alignment	10-11	
550 A-O	Schematic, socket, trimmers, alignment		10-12		Schematic, socket, trimmers, alignment	9-2	
575	Schematic, socket, alignment, trimmers, voltage		10-13		Schematic, socket, alignment, trimmers	10-13	
585, Series A	Schematic, socket, alignment, trimmers, voltage		10-14		Schematic, socket, alignment, trimmers	10-13	
630, 635, 652	Schematic, voltage, alignment, trimmers		9-1		Schematic, socket, alignment, trimmers	10-14	
651	Schematic, voltage, alignment, trimmers		10-15		Schematic, socket, alignment, trimmers	7-3	
660 Auto	Schematic, voltage, socket, trimmers		10-8		Schematic, voltage, socket, trimmers, alignment	10-15	
675	Schematic, voltage, socket, trimmers, alignment		10-16		Schematic, socket, alignment, trimmers	8-1	
700	Schematic, alignment		9-2		Schematic, voltage, socket, trimmers, alignment, parts	10-14	
800	See model M-8				Schematic, socket	8-2	
801, 802 chassis	Schematic, socket, alignment, voltage		10-17		Schematic, socket, trimmers, alignment	9-3	
1050	Schematic, voltage, socket, alignment		10-18		Schematic, voltage, socket, trimmers, alignment	7-4	
4154	Schematic, voltage, socket, alignment		10-18		Schematic, voltage, socket, trimmers, alignment, parts	8-2	
					Schematic, socket, trimmers, alignment	10-10	
					Schematic, socket, alignment, trimmers	10-13	
					Schematic, socket, trimmers, alignment	8-1	
					Schematic, voltage, socket, trimmers, alignment	10-19	
					Tuner data	10-30	
<b>GEO. W. WALKER CO.</b>							
Victoreen "Standard"	Chassis wiring	Misc. 1-23			See model 453	8-1	
Victoreen "Universal"	Chassis wiring	Misc. 1-23			Schematic, voltage, socket, alignment, trimmers	10-16	
					Tuner data	10-30	
					Schematic, socket, trimmers, alignment	9-4	
					Schematic, voltage, socket, trimmers, alignment, parts	8-3	
					Schematic, voltage, socket, alignment, trimmers	10-17	
					Schematic, voltage, socket, trimmers, alignment, parts	8-3	
					Schematic, voltage, socket, trimmers, alignment, parts	10-18	
					Schematic, voltage, socket, trimmers, alignment, parts	8-4	
					Schematic, socket, trimmers, alignment	8-1	
					Schematic, voltage, socket, trimmers, alignment	10-19	
					Tuner data	10-30	

MODEL	WARWICK MFG. CO.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
651	Schematic, voltage, socket, trim- mers, alignment, parts .....8-4		
653	See model 604		
654	Schematic, voltage, socket, trimmers, alignment .....10-20		
655B	See model 648		
659	Schematic, socket, trimmers, voltage, alignment .....10-21		
668, 668B	Tuner data .....10-21		
688	Schematic, voltage, socket, trimmers, alignment .....10-22		
700	Tuner data .....10-30		
701	Schematic, socket, trimmers, alignment, parts .....10-23		
725	Schematic, socket, trimmers, alignment .....9-5		
741	Schematic, socket, trimmers, voltage, alignment, parts .....9-6		
746	Schematic, socket, trimmers, voltage, alignment .....10-24		
747	Schematic, socket, trimmers, voltage, alignment .....10-25		
749	Schematic, socket, trimmers, voltage, tuner adjustments .....9-9		
749, 749B Late	Schematic, socket, trimmers, voltage, alignment .....10-26		
751	Tuner data .....10-30		
761	Schematic, socket, trimmers, alignment, parts .....9-10		
768, 768B	Schematic, socket, trimmers, alignment .....10-27		
846	Alignment, voltage .....10-27		
872	Alignment, socket, trimmers, tuner data .....10-30		
872	Schematic, socket, alignment, trimmers .....10-28		
872	Schematic, voltage, socket, trimmers, alignment .....10-29		
650	Schematic, alignment.....Misc. 8-2		
<b>WEBSTER CO.</b>			
B	Communication System	Schematics, notes .....8-1	
OC-2 and OC-2A Am- plifiers			
C	Communication System, OXO and OXM	Schematics, notes .....8-2	
D	Communication System, OC-3 to OC-10	Schematics, notes .....8-2	
PA-17		Schematic .....5-1	
PA-43		Schematic .....5-1	
B-53		Schematic .....5-2	
A-66		Schematic .....5-2	
B-79		Schematic .....5-3	
WR-86		Schematic .....5-3	
K-358-A		Schematic .....5-4	
K-359-A		Schematic .....5-4	
HG-417		Schematic .....Misc. 6-33	
<b>WEBSTER ELECTRIC CO.</b>			
HMS, HMT, Teletalk		Schematic .....Misc. 8-10	
MS		Schematic .....Misc. 8-10	
B-37-50 AO		Schematic .....Misc. 8-2	
IOS-1241		Schematic .....Misc. 8-10	
6005		Schematic .....3-1	
6009		Schematic .....3-1	
6013		Schematic .....3-1	
6025-JD		Schematic .....3-2	
6080-JE		Schematic .....3-2	
<b>WELLS-GARDNER &amp; CO.</b>			
5 Tube AC-DO Models		Data .....Changes 9-6	
14, 15, 16 Electric Drive Dials		Service notes .....9-4	
		Notes, changes, replacement data .....9-5	
<b>WELLS-GARDNER &amp; CO.—(Cont.)</b>			
MODEL		REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
14, 15, 16 Electric Drive Dials	Motor connections, motor- silencer spring data .....9-6		
	Motor notes, Part 2, gear train data .....9-7		
	Discs and buttons adjustments, Part 1 .....9-8		
	Discs and buttons adjustments, Part 2 .....9-9		
	Motor switch, drive cable data 9-10		
	Cable data, Part 2, clutch as- sembly and electric-manual lever data .....9-11		
	Electric-manual lever notes, Part 2, locking plate and re- versing switch notes .....9-12		
	Parts list .....9-13		
17-Button Telephone Dial and Phantom Light Dial	Adjustments .....9-1		
	Replacement data .....9-2		
	Data, parts list .....9-3		
1936 Receiver	Changes 8-7		
Q, OG (1st and 2nd types)	Schematic, socket .....1-1		
O-C (Series (2005))	Voltage, socket, data .....1-2		
	Schematic, parts list .....5-1		
	Alignment, socket, voltage .....5-2		
ODM Series	Schematic .....7-1		
	Voltage, socket, trimmers, coil data .....7-2		
	Alignment, data, resistance, phono .....7-8		
OEL	Additional data .....Changes 7-12		
	Schematic, sensitivity .....8-1		
	Socket, trimmers, voltage, coils .....8-2		
	Alignment, phono, data, notes .....8-3		
	Notes, parts .....8-4		
	Dial and drive parts data .....8-33		
OF	Dial and drive parts list .....8-34		
	Schematic, sensitivity .....8-5		
	Socket, trimmers, voltage, coils, notes .....8-6		
00A	Alignment, parts, notes, data .....8-7		
	Schematic, layout, voltage, notes .....4-1		
A-1 Series	Coils, phonograph socket notes, parts .....9-14		
	Schematic, specifications, sensitivity, phonograph data 9-15		
B1 Series	Alignment, trimmers, circuit data, voltage .....9-16		
S1 Series	Schematic, voltage, socket, trimmers, alignment .....10-9		
02A	Schematic, voltage .....10-10		
A-2 Series	Alignment, trimmers .....10-11		
	Schematic, layout, voltage, notes .....4-2		
	Schematic, specifications, sensi- tivity, phonograph data .....9-21		
	Trimmers, alignment, circuit data, coils .....9-22		
A2 Series, 7-Station Auto- matic Tuning Panel	Socket, voltage, changes, data, parts .....9-23		
	Installation data, panel view, details .....10-1, 2		
2B Series (22B5)	Installation data .....10-5, 6		
	Schematic, socket, trimmers, parts .....6-1		
	Alignment, voltage, resistance data .....6-2		
B2A Series	Circuit data, parts .....6-3		
	Schematic, specifications .....10-13		
S2 Series	Alignment, voltage, socket, trimmers, coils .....10-14		
	Schematic, socket, voltage, coils, notes .....10-12		
T2 Series	Alignment, trimmers, tuner .....10-11		
	Drive data .....10-42		
	Schematic, voltage, socket, coils, notes .....10-15		
20M Series	Tuner data .....10-42		
	Alignment, trimmers .....10-16		
	Schematic .....7-4		

\*640  
\*640  
3627  
3628

# WELLS-GARDNER

WELLS-GARDNER & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY COMPLETE PAGE	REVISID PAGE	
2CM Series	Socket, trimmers, voltage, coil data	7-5			
2CM-3A Series	Alignment, resistance	7-6			
3DL Series	Changes data	8-7			
	Schematic	7-7			
	Socket, trimmers, coil data, phono	7-8			
	Alignment, voltage, drive, phono, notes	7-9			
	Dial and drive parts data	8-33			
	Dial and drive parts list	8-34			
	Changes	8-7			
A-3, A-6 Series	Schematic, coils, phonograph and speaker connections, specifications, sensitivity 9-17, 18	9-19			
	Voltage, trimmers, alignment, notes	9-20			
	Circuit data, socket, parts	9-17			
A3 Series, 7-Station Automatic Tuning Panel	Installation data, panel view, details	10-1, 2			
B3 Series (Portable)	Installation data	10-1, 2			
T3 Series	Schematic, voltage, socket, trimmers, alignment, coils	10-19			
	Schematic, voltage, socket, trimmers, coils, notes	10-17			
A-4 Series	Alignment, drive cord data	10-18			
	Phonograph data, coils, parts	9-24			
	Schematic, specifications, sensitivity	9-25			
	Trimmers, alignment, circuit data, socket	9-26			
A4 Series, 7-Station Automatic Tuning Panel	Installation data, panel view, details	10-1, 2			
B4 Series (Table Models)	Installation data	10-1, 2			
4B5 Series	Schematic, voltage, socket, alignment, trimmers, coils	10-19			
08A	Schematic, voltage, alignment, socket, trimmers	10-20			
08AA	Schematic, layout, voltage	4-8			
A-5 Series	Schematic, voltage	4-4			
	Schematic, specifications, sensitivity, phonograph data	9-27			
	Trimmers, alignment, circuit data, voltage	9-28			
A5 Series, 7-Station Automatic Tuning Panel	Socket, coils, data, parts	9-29			
	Installation data, panel view, details	10-1, 2			
08BA	Installation data	10-1, 2			
5B	Schematic, layout, voltage	4-5			
C6, 6CH5 Series	Schematic, layout, voltage	4-12			
5C10 Series	Schematic, socket, trimmers, alignment	10-22			
	Schematic, voltage, socket, alignment, trimmers	10-21			
5D Series	Tuner data	10-24			
	Schematic, voltage, parts	6-4			
	Alignment, socket, trimmers, resistances, drive cord data, notes	6-5			
6-E Series (25Y1, 26E6)	Schematic, socket, parts	5-3			
5F, 5FL	Voltage, alignment	5-4			
	Schematic, sensitivity	8-9			
	Alignment, parts	8-8			
5G Series (85G510, 85G560)	Socket trimmers, voltage, coils	8-10			
	Schematic	6-6			
	Voltage, alignment, battery data	6-7			
5H	Socket, trimmers, resistance data, parts	6-8			
	Schematic, data	8-11			
	Socket, trimmers, voltage, coils, resistance	8-12			
	Alignment, notes	8-13			
5K, 5KL	Schematic, sensitivity	8-14			
	Alignment, parts	8-15			
5Y Series (25Y1)	Socket, trimmers, voltage, coils	8-16			
	Schematic, voltage, socket, trimmers, parts	6-9			
	Alignment, resistances, drive cord data	6-10			
WELLS-GARDNER & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY COMPLETE PAGE	REVISID PAGE	
5Y Series (25Y1)	Mounting, notes	6-11			
06A	Schematic, layout, notes	4-6			
6B Series (26B1, 26B5)	Schematic, socket, parts, data	6-12			
	Voltage, circuit data, resistances, parts	6-13			
6C Series	Alignment, notes	6-14			
	Circuit data, voltage, alignment	6-15			
	Schematic	6-16			
	Socket, trimmers, condenser data, parts	6-17			
C-6 Series	Parts, changes	9-30			
	Schematic, coils, specifications	9-31			
	Socket, circuit data, drive cord data, alignment	9-32			
6CH5	See model C5				
6C1	Schematic, socket, trimmers, voltage	8-17			
	Coils, mounting data	8-18			
	Alignment, parts, notes	8-19			
	Changes	9-6			
6C9 Series	Schematic, voltage, socket, trimmers	10-23			
	Alignment, tuner	10-24			
6D Series	Schematic, alignment	7-10			
	Socket, trimmers, voltage, coil and drive data	7-11			
6F Series	R-F chassis schematic	7-12			
	A-F chassis schematic	7-13			
	Socket, trimmers, coil data, phono, changes	7-14			
	Voltage, trimmers, chassis views	7-15			
	Circuit data, alignment	7-16			
6G Series	Resistance, parts	7-17			
	Schematic, trimmers	7-18			
	Voltage, alignment, socket, coil data, parts lists	7-19			
6J Series	Schematic, notes, speaker connections	9-33			
	Socket, trimmers, alignment, changes	9-34			
6K Series	Schematic, socket, coil data	7-20			
	Voltage, alignment, data, parts list	7-21			
6L Series	Schematic, socket, coil data	7-22			
	Alignment, voltage, parts list	7-23			
6N Series	Changes	8-7			
	Schematic, socket, trimmers	7-24			
	Voltage, coil data, resistance, notes	7-25			
6R Series	Alignment, notes	7-26			
	Schematic, alignment	7-27			
	Voltage, socket, trimmers, coil data, resistance	7-28			
6S	Changes	8-7			
	Schematic, parts	8-21			
	Mounting data	8-20			
	Alignment, voltage, socket, trimmers, resistance, notes	8-22			
6-U Series (26U1)	Schematic	5-5			
	Alignment, wiring instructions	5-6			
06W	Installation data	5-7			
V6Z2	Schematic, layout, voltage	4-7			
Z6Z1	Alignment, speaker data	4-8			
	Schematic, voltage	4-13			
07A	Schematic, layout, voltage, alignment data	4-14			
	Schematic, voltage, alignment data	4-9			
C7, C11 Series	Additional data	Changes 7-14			
	Schematic, voltage, socket, alignment, trimmers	10-29			
7O Series (27O1, 27O5)	Schematic, socket, voltage, trimmers	6-18			
	Alignment, resistances, drive cord data	6-19			
7-D Series (27D1, 27D5)	Schematic, socket, alignment	5-9			
	Voltage, parts, circuit changes	5-10			

WELLS-GARDNER & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY	COMPLETE	PAGE
7E	Schematic .....	8-23			
	Socket, trimmers, voltage, data .....	8-24			
	Alignment, coils, drive cord .....	8-25			
7F, 7FL	Resistances, parts .....	8-26			
	Schematic, sensitivity, phono .....	8-27			
	Socket, trimmers, voltage, coils .....	8-28			
	Alignment, phono, data, parts .....	8-29			
7GM Series (87G508, 87G556)	Schematic, trimmers, parts .....	8-30			
	Voltage, trimmers, coil data, changes .....	8-31			
	Resistances, data .....	8-32			
	Circuit data, alignment .....	8-33			
	Additional data .....	8-34			
7H Series (87H508, 87H556)	Schematic .....	8-35			
	Voltage, socket, trimmers, coil data .....	8-36			
	Drive cord data, resistances .....	8-37			
	Schematic .....	8-38			
	Phono, connections, parts .....	8-39			
	Alignment, socket, trimmers, voltage, resistance, coils, changes .....	8-40			
7J	Schematic .....	8-41			
	Socket, voltage, trimmers, coil data .....	8-42			
	Alignment, phono, resistance .....	8-43			
	Dial and drive parts data .....	8-44			
	Dial and drive parts list .....	8-45			
A8 Series	Schematic, socket, phono, data .....	8-46			
	Alignment, trimmers, voltage, parts .....	8-47			
9-B Series (29B5)	Parts .....	8-48			
	Schematic, socket .....	8-49			
	Service notes, parts .....	8-50			
9C Series	Voltage, alignment .....	8-51			
	Schematic .....	8-52			
	Voltage, socket, coil data, trimmers .....	8-53			
A10 Series	Alignment, resistance .....	8-54			
	Schematic .....	8-55			
	Alignment, trimmers, voltage, socket, tuner, drive cord .....	8-56			
A11 Series	Schematic, voltage, alignment .....	8-57			
C11 Series	See C7 series .....	8-58			
A-12 Series	Schematic, socket, phonograph data, voltage, specifications, coils .....	8-59			
	Circuit data, alignment, trimmers .....	8-60			
	Tuner and drive cord data, phonograph data .....	8-61			
A12 Series, Late	Parts list .....	8-62			
	Schematic, voltage, socket, trimmers, changes, tuner switches .....	8-63			
A13 Series	Tuner data .....	8-64			
	Schematic, voltage, socket .....	8-65			
	Alignment, trimmers, coils, specifications .....	8-66			
A-14 Series	Tuner data .....	8-67			
	Schematic, voltage, coils, socket, phonograph data, specifications, sensitivity .....	8-68			
	Circuit, tuner data, changes, phonograph data, notes, parts .....	8-69			
A15 Series	Trimmers, alignment, parts .....	8-70			
	Schematic, voltage, socket, coils, phono, data .....	8-71			
	Alignment, trimmers, specifications .....	8-72			
A16 Series	Tuner data .....	8-73			
	Schematic, voltage, socket, alignment notes .....	8-74			
	Alignment, trimmers, changes, phono, data, movie dial data .....	8-75			
WELLS-GARDNER & CO.—(Cont.)			RADIOTRON		
MODEL			EARLY	COMPLETE	PAGE
A17 Series	Schematic, socket, voltage, phono, data .....	10-40			
	Alignment, trimmers, coils, notes .....	10-41			
A20 Series	Schematic, voltage, socket, coils, specifications .....	10-42			
	Alignment, phono, data, trimmers, drive cord data .....	10-43			
2005 Chassis	See O-G Series .....	10-44			
022	Schematic, layout, voltage .....	10-45			
A22 Series	Schematic, voltage, socket, coils, phono, data .....	10-46			
	Tuner data .....	10-47			
22B5 Chassis	Alignment, trimmers .....	10-48			
A23 Series	See 2B Series .....	10-49			
	Schematic, voltage, phono, data .....	10-50			
	Alignment, trimmers .....	10-51			
	Tuner data .....	10-52			
A24 Series	Drive data .....	10-53			
	Schematic, voltage, phono, data .....	10-54			
	Tuner data .....	10-55			
	Socket, coils, phono, data .....	10-56			
	Alignment, trimmers .....	10-57			
25E1, 25E5 Chassis	See 5-E Series .....	10-58			
25Y1 Chassis	See 5Y Series .....	10-59			
26B1, 26B5 Chassis	See 6B Series .....	10-60			
26U1 Chassis	See 6U Series .....	10-61			
27O1, 27C5 Chassis	See 7O Series .....	10-62			
27D1, 27D5 Chassis	See 7D Series .....	10-63			
29B5 Chassis	See 9B Series .....	10-64			
35G510, 35G560 Chassis	See 5-G Series .....	10-65			
37G508, 37G566 Chassis	See 7GM Series .....	10-66			
37H508, 37H566 Chassis	See 7H Series .....	10-67			
40, 40-A	Schematics .....	10-68			
50	Alignment, socket, voltage .....	10-69			
052 Series	Schematic, layout, voltage .....	10-70			
	Schematic, chassis layout .....	10-71			
062 Auto Set	Voltage .....	10-72			
	Schematic, assembly wiring, voltage .....	10-73			
062-A	Schematic .....	10-74			
72	Schematic, socket .....	10-75			
078	Schematic, layout, voltage .....	10-76			
80, 82-A	Schematic, socket, data .....	10-77			
092 Series, Battery	Schematic, chassis, voltage .....	10-78			
92, 98	Schematic, socket, voltage .....	10-79			
502	Schematic, layout, voltage .....	10-80			
572 AO	Schematic, chassis layout, data .....	10-81			
	Parts list, voltage, alignment data .....	10-82			
WESTERN AUTO SUPPLY CO.			RADIOTRON		
MODEL			EARLY	COMPLETE	PAGE
6-U	Schematic .....	5-2			
26Z1	Schematic, voltage .....	5-3			
	Alignment, parts .....	5-4			
062	Schematic, voltage, assembly wiring .....	5-5			
670	Schematic, socket, trimmers .....	5-6			
D689	Alignment, service notes .....	5-7			
	Schematic, voltage, coils, socket, sensitivity .....	5-8			
	Alignment, trimmers, parts .....	5-9			
	Circuit and tuner data, changes, phono .....	5-10			
D690	Schematic, socket, trimmers .....	5-11			
D691	Alignment, tuner data .....	5-12			
	Schematic, socket, trimmers, alignment .....	5-13			
S-691	Tuner data, alignment .....	5-14			
D692 Early	Schematic .....	5-15			
	Alignment, trimmers .....	5-16			
D692 Late	Schematic, alignment .....	5-17			
	Socket, trimmers, antenna data .....	5-18			

# WESTERN AUTO WESTINGHOUSE ELECTRIC

RADIOTRON  
EARLY COMPLETE  
PAGE

REVISOR  
PAGE

WESTERN AUTO SUPPLY CO.—(Cont.)

MODEL

S-719

D-721, S-721

D-724, S-724 (1934)

D-725, S-725, S-726

D-727, S-727, (1934)

S-732, S-733

D-734 (1936-37)

S-735, D-736 (1934)

D-740, S-740 (1934) (with Mallory 53 or Radiart 3264 Vibrator)

D-743, S-743, 1312 (1934)

Schematic, socket, trimmers, voltage

See model D701 (1936)

Schematic, socket, trimmers, changes

Voltage, parts, alignment

Schematic, socket, parts

Circuit data, alignment, voltage, resistance

Schematic, socket, trimmers, alignment

Alignment, part 2, voltage, changes, parts

Schematic, parts

Voltage, alignment, resistance, trimmers, change

Schematic, voltage, data

Alignment, parts

Schematic, socket, voltage, trimmers, parts

Alignment, notes

Drive cord notes

Schematic, voltage, socket, trimmers, parts

Alignment, notes, test data, parts

Schematic

Schematic, voltage, socket, parts

Alignment, parts, circuit data

WESTERN ELECTRIC CO.

Schematic

Schematic

Schematic

Schematic

# WESTINGHOUSE ELECTRIC WESTINGHOUSE INTERNATIONAL

WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)			RADIOTRON		
			MODEL	REVISION	EARLY COMPLETE
				PAGE	PAGE
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)	WR-28, WR-29	Voltage, socket, alignment data, part 1	WR-472	Alignment, phono. data	10-12
		Schematic, alignment, part 2	WR-500	Schematic	6-15
	WR-30	Schematic	WR-501	Schematic, voltage	6-16
		Voltage, socket, alignment, parts	WR-601	Schematic	6-4
		Schematic, socket, trimmers, parts	WR-603, WR-606	Chassis, socket, parts, alignment, trimmers	10-13
	WR-100	Schematic, changes, parts	WR-604, WR-607	Schematic, voltage	10-14
	WR-101	Alignment, voltage		Alignment, trimmers, socket, chassis, parts	10-15
	WR-101, Chassis UGF	Schematic, voltage	WR-608	Schematic, voltage	10-16
		Alignment, parts		Alignment, socket, trimmers, chassis, parts	10-17
	WR-102-A	Schematic, socket, trimmers, voltage, alignment, chassis	WR-700 Television	Data, parts	10-18
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)	WR-103, WR-103-A	Schematic, voltage		For other data see RCA Model TT-5	10-20
	WR-116, WR-316	Socket, trimmers, chassis	WR-701 Television	Data, parts	10-20
		Alignment, parts		For other data see RCA Model TRK-5	10-20
	WR-154	Schematic, voltage	WR-702 Television	Data, parts	10-20
	WR-201	Alignment, specifications, parts		For other data see RCA Model TRK-9	10-20
	WR-203, WR-303	Schematic, voltage	WR-703 Television	Data, parts	10-20
		Alignment, data, parts		For other data see RCA Model TRK-12	10-20
	WR-204, WR-304	Schematic, voltage, resistance data			
		Alignment, service notes			
	WR-205, WR-305	Socket, trimmers, parts			
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)		Schematic, voltage, resistance data			
	WR-208	Socket, trimmers, data			
		Alignment, service notes, parts			
	WR-211	Schematic, voltage, color coding			
		Alignment, changes, parts			
	WR-212, WR-312	Schematic, socket, trimmers, chassis, alignment, voltage			
		Alignment, voltage, resistance			
	WR-214, WR-314	Socket, trimmers, chassis			
		Alignment, parts			
	WR-222	Schematic, voltage, resistance			
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)		Alignment, specifications, parts			
	WR-226, WR-326, WR-338	Schematic, voltage, resistance			
		Socket, trimmers, alignment, parts			
	WR-228, WR-328	Schematic, voltage, resistance			
		Socket, trimmers, alignment, parts			
	WR-256	Schematic, voltage, alignment, socket, data, trimmers			
	WR-264	Schematic, socket, trimmers, speaker, drive cord data			
		Chassis wiring, voltage			
	WR-306	Alignment, phono. data, tuner, lead dress			
		Schematic, voltage, resistance			
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)		Alignment, parts			
	WR-315	Circuit data, socket, trimmers, chassis			
		Schematic, voltage, resistance			
		Socket, trimmers, chassis			
	WR-326	Alignment, data, alignment			
	WR-328	Parts			
	WR-330	See model WR-226			
		Schematic, voltage, resistance			
	WR-338	Socket, trimmers, alignment, parts			
	WR-472	See model WR-226			
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)		Schematic, voltage, socket, trimmers, pick-up, transformer data, motor coils			
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)					
WESTINGHOUSE ELECTRIC SUPPLY CO., INC.—(Cont.)					

## WESTINGHOUSE INTERNATIONAL

WR-6-R	See RCA 82-R
WR-7-R	See RCA 86-R
WR-18	See RCA RE-16
WR-18-A	See RCA RE-16-A
WR-14-OB	See RCA R-5-X
WR-15-A	See RCA R-10
WR-16	See RCA R-23
WR-17	See RCA R-4
WR-18	See RCA R-8
WR-19	See RCA R-71
WR-20	See RCA R-70 & R-70-N
WR-21	See RCA R-74
WR-22	See RCA R-73 (47)
WR-23	See RCA RE-80
WR-24	See RCA R-24-A
WR-25	See RCA RE-80-SW
WR-26	See RCA R-27
WR-26-M	See RCA R-17-M
WR-27	See RCA R-28-P (A to G)
WR-28	See RCA R-27-P
WR-29	See RCA RE-40-P
WR-30	See RCA 140 & 140-E
WR-31	See RCA 141 & 141-E
WR-32	See RCA 100
WR-33	See RCA M-84
WR-34	See RCA 112
WR-35	See RCA 111
WR-36	See RCA 120
WR-37	See RCA 321
WR-38	See RCA 340
WR-39	See RCA 340-E
WR-40	See RCA M-105
WR-41	See RCA M-116
WR-42	See RCA 143
WR-43	See RCA-Victor 143 (Revised)
WR-44	See RCA 128
WR-45-A	See RCA-Victor 128 (Revised)
WR-46	See RCA 135-B
WR-47	See RCA 118
WR-48	See RCA-Victor 118 (Revised)
WR-48-A	See RCA 322
WR-49	See RCA 128-E
WR-50	See RCA-Victor R-93
WR-102 (Preliminary)	Schematic, voltage
WR-102	Alignment, socket, trimmers, chassis
WR-102	Schematic, voltage
WR-116, WR-116X	Alignment, parts
WR-316, WR-316X	Schematic, voltage
WR-209 (Preliminary)	Schematic, voltage, alignment
WR-209, WR-209X Final	Schematic, voltage, alignment

# WESTINGHOUSE INTERNATIONAL WILCOX-GAY

WESTINGHOUSE INTERNATIONAL—(Cont.)			RADIOTRON	
MODEL	REVISION	EARLY COMPLETE	PAGE	PAGE
WR209	Alignment, socket, trimmers, chassis	10-2		
WR-210, WR-310	Schematic, voltage	7-3		
WR-211, WR-211A, WR-211X	Schematic, voltage	8-8		
WR-211U, WR-311, WR-311X, Final	Alignment, parts	8-4		
WR-212, WR-212X, WR-312, WR-312X	Schematic, voltage, resist- ance	8-5, 8-6		
WR-214X, WR-314X	Alignment, parts	8-7		
WR-310	Schematic, voltage, resist- ance	9-1, 2		
WR-311	Socket, trimmers, chassis	9-3		
WR-314X	Alignment, specifications, parts	9-4		
WR-316, WR-316X	Schematic, voltage, resist- ances	10-3, 4		
	Socket, trimmers, chassis	10-5		
	Alignment, parts	10-6		
	See model WR-210			
	Schematic, voltage	7-4		
	See model WR-214X			
	See model WR-116			
WESTON ELECTRIC INSTRUMENT CORP.				
Jewell Test Panel	Schematic	1-1	2643	
Jewell 133	Schematic	1-2	2644	
Jewell 133-A	Schematic	1-3	2645	
Jewell 137	Schematic	1-3	2646	
Jewell 198, 199 (2nd type)	Schematic	2-1	2647	
Jewell 209	Schematic	2-1	2648	
Jewell 214	Schematic	2-2	2649	
Jewell 408, 409 (1st type)	Schematic	1-5	2650	
Jewell 408, 409 (2nd type)	Schematic	1-6	2651	
Jewell 444	Schematic	2-3	2652	
444, Type 2	Schematic	5-1	2653	
444, Type 3	Schematic	5-2	2654	
Weston 526, Type 7	Schematic	1-7	2655	
Jewell 533	Schematic	2-4	2656	
Jewell 534	Schematic	2-4	2657	
Weston 537	Schematic	1-8	2658	
Jewell 538	Schematic	2-5	2659	
Jewell 540	Schematic	2-6	2660	
540 Type 2	Schematic	5-7	2661	
Weston 547	Schematic	1-10	2662	
Weston 555	Schematic	1-11	2663	
Jewell 560	Schematic	2-6	2664	
563, Type 2	Schematic	5-8	2665	
Weston 564	Schematic	1-11	2666	
Weston 565	Schematic	1-12	2667	
Weston 566	Schematic	1-14	2668	
Jewell WD-566	Schematic	3-1	2669	
Weston 566, Type 8	Schematic	3-2	2670	
571	Schematic	5-4	2671	
Weston 660	Schematic	5-5	2672	
660, Type 3	Schematic	5-6	2673	
691, 672	Schematic	3-4	2674	
Weston 662	Schematic	5-7	2675	
662, Type 2	Schematic	5-8	2676	
Weston 663	Schematic	3-4	2677	
664 Capacity-Voltmeter	Schematic	4-1	2678	
665 Selective Analyzer	Schematic	4-1	2679	
665, Type 2	Schematic	5-4	2680	
672, Type 2	Schematic	5-8		
673	See model	661		
674 Tube Checker	Schematic	4-2		
674, Type 2	Schematic	5-9		
675 Tube Checker	Schematic	4-2		
Weston 676	Schematic	2-7		
676	Schematic	5-10		
676-R, 677-R, 678-R	Schematic	5-11		
677, 678	Schematic	5-12		
692 Oscillator, Type 1	Schematic	6-1		
694	Schematic	5-6		
695	Schematic	5-8		
770 Tube Checker	Schematic	6-2		
780 Capacity Meter	Schematic	6-1		
WESTON RADIO CORP.				
11, 12	See model 70			
20, 4-Tubes	Schematic	6-2		
34, 5-Tubes	Schematic	6-1		
40	Schematic	6-1		
70, 700, 11, 12	Schematic	Misc. 8-3		
WEXTARK RADIO CORP.				
	See Allied Radio & Knight Radio			
WHOLESALE RADIO SERVICE CO., INC.				
Auto Radio Superhet	Schematic, socket, voltage, assembly wiring	3-4	2676	
Duo-Symphonic 1930	Schematic, socket, voltage, data 1-2	1-1	2677	
Duo-Symphonic Junior 1931	Schematic, socket, voltage	1-1	2678	
Great Duo-Symphonic L-1 AO	Schematic, socket, voltage	1-1	2679	
05A Series, AC-DO, L-20 AO	Schematic, chassis layout, voltage	3-1	2680	
M-36, 87, 53 AO	Schematic, voltage, parts list	3-2	2681	
	Schematic	3-3		
WILCOX-GAY CORP.				
Road Mate	See 4-B-26			
Thin Man	See model A53			
2-8-5	Schematic	3-1	2877	
2-T-6	Schematic	3-2	2878	
2-VA-7	Schematic	4-1	2879	
2-VB-7	Schematic	4-2		
A3, A4, Chassis 5A6	Schematic, socket	9-1		
3-D-5	Schematic	4-3		
3-F-7	Schematic	4-4		
3-J-5	Schematic, socket, parts list	7-4		
3-J-5, 8-K-5	Alignment	7-3		
3-J-5, 8-K-5	Schematic, socket, parts	7-1		
3-J-5, 8-K-5	Schematic, socket, voltage, parts	6-1		
3-J-5, 8-K-5	Schematic, socket, voltage	7-1		
3-J-5, 8-K-5	Schematic, socket, voltage	6-2		
3-J-5, 8-K-5	See model 3JD5			
3-J-5, 8-K-5	Schematic, voltage, socket, parts	7-2		
3-K-5	Alignment	7-3		
3-KD-5	See model 3-J-5			
3KE5	Schematic, voltage, socket	5-1		
3-LB-7	Schematic	6-2		
3-PA-6-66	Schematic	4-5		
3-R-6	Schematic	4-7		
3-SB-66	Schematic	4-6		
3-SB-5	Schematic	4-8		
3-TB-66	Schematic, voltage, socket	5-2		
3-VB-6	Schematic	4-8		
3-VB-6	Schematic, voltage, socket	5-3		
3-VB-6	Schematic, socket, voltage	5-4		
3-VB-6	See model A3			
A4	Schematic, voltage, alignment	5-5		
4-B6, Road Mate	Schematic, voltage, socket	5-6		
4-C-5, 4-CB-5 (BO & SW), 4-CA-5 (BO Only)	Schematic	5-7		
4-OD-5	Schematic, voltage, socket	5-9		
4-D-10	Schematic, voltage, socket	5-8		
4-DB-10	Schematic, voltage, socket	5-10		
4-E-6	Schematic, socket, voltage, parts	6-5		
4G7	Alignment data	Changes 7-5		
4H11	Schematic, socket, voltage, parts	6-6		
4JA6, 4JB6	Alignment data	Changes 7-5		
4J6, 4J06	Schematic, socket, voltage, parts	6-3		
	Alignment data	Changes 7-5		
	Alignment data	Changes 7-5		



WILCOX-GAY CORP.—(Cont.)			THE RUDOLPH WURLITZER CO.—(Cont.)			RADIOTRON		
MODEL		REVISED PAGE	MODEL		REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON	PAGE
A5, A6, Chassis 5F8	Schematic, socket	9-2	SA-91-A	Schematic, data	4-9			
5B5, 5B05	Schematic, socket, parts list	7-4	SA-120	Alignment data	5-14			
5BA5	Schematic, socket, parts	7-5	SA-138	Schematic, data	4-10			
5BC5	See model 5B5			Schematic, details	4-11			
5BE6	Schematic, socket, parts	7-6		Alignment data	5-17			
5E7	Schematic, socket, voltage, parts	6-7		Schematic, data	5-18			
5EA7	Schematic, socket, voltage, parts	6-8	316, 416, 616, 716 AC	Schematic, voltage, parts	8-1			
5E8, 5E9	Schematic, socket, parts	7-5	316, 416, 616, 716 DO	Schematic, voltage, parts	8-2			
5F8, Chassis A6	See model A5		400, Serial #110001 to 111000	Schematic, voltage, parts	8-3			
6A5	Schematic, voltage, socket, alignment, parts	8-1	400, Serial #111001 to 111500	Schematic, voltage, parts	8-4			
6B8	Schematic, voltage, socket, alignment, parts	8-2	416	See model 816				
6D6	Schematic, voltage, alignment, socket, parts	8-3	450	Schematic, socket, voltage	5-1			
6F6, 6FB6	Schematic, voltage, socket, alignment, parts	8-4	453 Amplifier	Alignment, parts	5-2			
6T11	Schematic, socket, parts	9-3		Schematic, socket, circuit details	5-3			
7E5	Alignment, trimmers, voltage	9-4	454	Schematic	5-4			
	Schematic, voltage, alignment, socket, trimmers	10-1	460	Schematic, socket, voltage	5-5			
7R5 chassis	See model A41		470	Alignment data	5-6			
7S5 chassis	See model A48		471	Schematic, socket, voltage	5-7			
7T5 chassis	See model A49		480	Schematic	5-8			
8E5 chassis	See model A50		480	Schematic, data	4-12			
8E5 chassis	See model A52		500	Schematic, parts data	Misc. 6-40			
8J5 chassis	See model A53		500 Sound System	See model 316				
8L7 chassis	See model A54			Schematic, parts, voltage, Misc.	7-12			
8N7 chassis	See model A55			See model 816				
A41, A42, Chassis 7R5	Schematic, voltage, socket, alignment	10-2						
A48, Chassis 7S5	Schematic, voltage, socket, alignment	10-3						
A49, Chassis 7T5	Schematic, voltage, socket, alignment	10-4						
A50, Chassis 8D5	Schematic, voltage, socket, alignment	10-5						
A52, Chassis 8E5	Schematic, voltage, socket, alignment	10-6						
A53, Thin Man, Chassis 8J5	Schematic, voltage, socket, alignment	10-7						
A54, Chassis 8L7, A55, Chassis 8N7	Schematic, voltage, socket, alignment	10-8						
WILLARD STORAGE BATTERY CO.			ZENITH RADIO CORP.					
B Unit 3095	Schematic	2-1	4 Tube 2 volt Receivers	Data	Changes 9-5			
AB 3301 G. E. Charger	Schematic	2-2	5 Tube 2 volt Receivers	Data	Changes 9-5			
AB 3301 Westinghouse	Schematic	2-2	5-Tube Zenette, Type 2009-C, L Chassis	Schematic, parts list	1-27			
B Unit 3310, 4310	Schematic	2-1	6-tube Zenette, Chassis A, B, C, D (2004)	Schematic, socket, parts list	1-26			
B Unit 4095	Schematic	2-1		Changes	7-32			
AB 6301	Schematic	2-2	15 Tube Receivers AC-DO Models	Data	Changes 9-6			
WINGS			Automatic Tuner	Schematic, notes	9-43			
See GOODYEAR SERVICE			Chassis A, B, C, D	Push-button ranges, alignment data, service hints	9-44			
WORRITTE MFG. CO.			AH, CH, RH, Chassis 2012 Series	See model 6 tube Zenette				
See U. S. ELECTRIC CORP.				Schematic, socket, chassis, voltage	1-23			
THE RUDOLPH WURLITZER CO.			BH (2021)	Service data, parts list	1-24			
Also see ALL-AMERICAN MOHAWK CORP.			I Chassis	Notes	7-22			
			LH, MH, WH (2022)	Schematic, socket, parts list	2-11			
			LP, 2009-C-P Chassis Hudson	See model 5 tube Zenette				
			Hypermetron	Schematic, socket, parts list	2-12			
			Phonograph pickup	Schematic, socket, parts list	1-25			
			Remote Control	See model 680				
			Stratosphere (16 Tubes)	Circuit changes	10-40			
			Super Zenith Battery	Schematic diagrams	9-10			
			Terraplane Hudson	See model 16-A-61				
			ZE-3	See model 1000Z				
			4-B-106, 4-B-131, 4-B-132, Chassis 5406	Schematic	2-14			
			4-B-231, Chassis 5409	See model 650-HD				
			4B313, 4B355, Chassis 5410	Schematic	2-1			
			4B314, 4B317, Chassis 5411	Schematic	7-1			
				Voltage, socket, trimmers	7-2			
				Schematic, voltage, socket, trimmers, alignment, parts	8-1			
				Phono, circuit	8-6			
				Schematic, parts	9-1			
				Socket, trimmers, voltage, alignment	9-2			
				Circuit changes for phono	10-40			
				Pickup	9-3			
				Schematic, parts	9-3			
				Socket, trimmers, voltage, alignment	9-2			

MODEL	ZENITH RADIO CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE
4-F-133, Chassis 5407	Schematic, voltage, socket, trimmers, alignment, parts, battery connections.....	8-2	
4-F-227, Chassis 5408	Schematic, socket, trimmers, voltage, alignment, parts.....	8-3	
4K310, 4K331, 4K355, Chassis 5412	Phono. circuit.....	8-6	
4K329, Chassis 5413	Schematic, voltage, alignment, socket, trimmers.....	10-5	
4P26, 4T26, 4P51, 4T51 Chassis 5401	Schematic, voltage, alignment, socket, trimmers.....	10-6	
4T26, 4T51, Chassis 5403 Early	Schematic, parts.....	6-17	
4T26, 4T51, Chassis 5403	Voltage, socket, trimmers, alignment, parts.....	6-18	
4T26, 4T51, Chassis 5403 Late with Improved Short Wave	Schematic.....	10-7	
4V31, 4V69 Chassis 5405	Alignment, voltage, socket, trimmers.....	10-8	
ZE-4 5A119, 5A126, 5A127, 5A151, Chassis 5517A	Schematic, parts.....	6-19	
5A318, 5A325, Chassis 5532A	Voltage, socket, trimmers, alignment, parts.....	6-20	
5-F-134, 5-F-166, Chassis 5518	Schematic.....	2-1	
5-F-233, 5-F-251, Chassis 5522	Schematic.....	10-15	
5-J-217, 5-J-247, 5-J-255, Chassis 5524	Voltage.....	10-39	
5J217T, Chassis 5524T	Alignment, socket, trimmers, socket, voltage, alignment, parts, trimmers, alignment, parts, battery connections.....	10-28	
5L528, 5L237, Chassis 5525A	Schematic.....	10-13	
5-M-90, Chassis 5510	Voltage, tuner, socket.....	10-12	
5-M-191, Chassis 5520	Alignment, socket, trimmers, voltage, alignment.....	10-14	
5M239, Chassis 5530	Schematic, voltage, socket, trimmers, alignment, parts.....	8-4	
5-R-123, 5-R-135, 5-R-165, Chassis 5519	Schematic, voltage, socket, trimmers, alignment, parts.....	8-5	
5-R-216, 5-R-226, 5-R-236, Chassis 5526	Phono. circuit.....	8-6	
5R303, 5R312, 5R316, 5R317, 5R337, Chassis 5528	Data.....	9-5	
	Changes.....	8-7	
	Schematic, parts.....	8-7	
	Phono. circuit.....	8-6	
	Voltage, socket, trimmers, alignment.....	8-8	
	Schematic, parts.....	9-5	
	Socket, trimmers, voltage, alignment.....	9-6	
	Schematic.....	10-15	
	Alignment, socket, trimmers.....	10-30	
	Voltage.....	10-39	
	Schematic, parts.....	7-3	
	Voltage, socket, trimmers, alignment.....	7-4	
	Schematic, voltage, changes, parts.....	8-9	
	Socket, trimmers, chassis, drive data.....	8-10	
	Alignment, notes.....	8-11	
	Parts.....	8-12	
	Schematic.....	10-9	
	Socket, trimmers, voltage, alignment.....	10-10	
	Schematic, voltage.....	10-11	
	Alignment, tuner data.....	10-10	
	Schematic, socket, voltage, trimmers, alignment, parts.....	8-13	
	Schematic, voltage, parts, socket, trimmers, parts.....	8-14	
	Phono. circuit.....	8-6	
	Schematic, parts.....	9-7	
	Socket, trimmers, voltage, alignment.....	9-8	
	Circuit changes for phono. pickup.....	10-40	

MODEL	ZENITH RADIO CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIO TELEPHONE
5-S-29, 5-S-56, Chassis 5613, 5613A	Schematic, socket, trimmers, parts ..... 7-5 Voltage, alignment ..... 7-6 Schematic, parts ..... 7-7 Voltage, socket, trimmers ..... 7-2 Alignment ..... Changes 10-3 Schematic, socket, trimmers, alignment, voltage, parts ..... 8-22 Phono, circuit ..... 8-6 Schematic, parts ..... 9-9			
5-S-201, 5-S-218, 5-S-220, 5-S-238, 5-S-237, 5-S-250, 5-S-252, Chassis 5521	Socket, trimmers, voltage, alignment ..... 9-10 Schematic ..... 10-13 Socket, voltage ..... 10-12 Alignment, trimmers, socket ..... 10-14 Schematic, parts ..... 9-11			
5S218AT, 5S228AT, 5S237AT, Chassis 5521AT	Socket, trimmers, voltage, alignment ..... 9-12 Circuit changes for phono, pickup ..... 10-40 Schematic, alignment, socket, trimmers ..... 10-16 Voltage ..... 10-10 Schematic ..... 1-4 Schematic ..... 10-19			
ZE-5 6A203, 6A223, 6A229, 6A239, 6A241, Chassis 5640AT	Voltage ..... 10-39 Alignment, socket, trimmers ..... 10-18 Schematic, parts ..... 7-8 Voltage, socket, trimmers ..... 7-9			
6-B-107, 6-B-139, 6-B-164, Chassis 5635	Alignment ..... 8-36 Schematic, parts, voltage ..... 9-18 Socket, trimmers, alignment ..... 9-17 Circuit changes for phono, pickup ..... 10-40 Schematic, parts ..... 7-10 Voltage, socket, trimmers ..... 7-11 Schematic, parts ..... 8-15			
6-D-202, 6-D-219, 6-D-221, 6-D-238, Chassis 5639	Phono, circuit ..... 8-6 Voltage, alignment, socket, trimmers ..... 8-16 Schematic, parts, voltage, socket, trimmers, alignment ..... 9-4 Circuit changes for phono, pickup ..... 10-40 Schematic, socket, trimmers, parts ..... 9-13 Voltage, alignment ..... 9-15 Circuit changes for phono, pickup ..... 10-40 Schematic, voltage, socket, alignment, trimmers ..... 10-17 Schematic ..... 10-19			
6D312, 6D316, 6D317, 6D337, Chassis 5647	Voltage ..... 10-39 Alignment, socket, trimmers ..... 10-20 Schematic, parts ..... 8-17 Phono, circuit ..... 8-6 Voltage, alignment, socket, trimmers ..... 8-18 Schematic, parts ..... 9-19 Voltage, socket, trimmers, alignment ..... 9-20 Circuit changes for phono, pickup ..... 10-40 Schematic, parts list ..... 7-12 Socket, trimmers, voltage, alignment ..... 7-18			
6-M-90S, 6-M-90D, Chassis 5680				
6-J-230, 6-J-257, Chassis 5642				
6D336, 6D360, Chassis 5646				
6D382, 6D385, Chassis 5657				
6DL120, 6DL121, 6DL122, Chassis 5636 AC-DC				

ZENITH RADIO CORP.—(Cont.)			ZENITH RADIO CORP.—(Cont.)		
MODEL	REVISION	REVISION	MODEL	REVISION	REVISION
6-M-91D, 6-M-91S, Chassis 5691	7-14	7-14	7-D-119, 7-D-126, 7-D-127, Schematic, parts	7-18	7-18
Socket, trimmers, voltage	7-13	7-13	7-D-138, 7-D-151, 7-D-148, 7-D-162, 7-D-168, Chassis 5707		
Alignment	7-4	7-4			
Schematic, parts	7-15	7-15			
Socket, trimmers, voltage	7-13	7-13			
Alignment	7-4	7-4			
Schematic, voltage, changes, parts	8-19	8-19			
Alignment, notes	8-11	8-11			
Socket, trimmers, chassis	8-21	8-21			
Parts	8-12	8-12			
Schematic, voltage, changes, parts	8-20	8-20			
Alignment, notes	8-11	8-11			
Socket, trimmers, chassis	8-21	8-21			
Parts	8-12	8-12			
Schematic, voltage	10-21	10-21			
Alignment, socket, trimmers	10-22	10-22			
Schematic, voltage	10-23	10-23			
Alignment	10-22	10-22			
Socket, trimmers, antenna, data, tuner	10-24	10-24			
Schematic, voltage, socket, trimmers	10-25	10-25			
Alignment, trimmers, tuner data	10-26	10-26			
Schematic, socket, trimmers, parts	7-16	7-16			
Alignment, voltage	7-20	7-20			
Schematic, parts	7-17	7-17			
Voltage, socket, trimmers	7-9	7-9			
Alignment	10-3	10-3			
Schematic, parts	8-23	8-23			
Phono, circuit	8-6	8-6			
Voltage, alignment, socket, trimmers	8-24	8-24			
Schematic, voltage, socket, trimmers, alignment, parts	8-33	8-33			
Phono, circuit	8-6	8-6			
Schematic, parts	9-21	9-21			
Voltage, socket, trimmers, alignment	9-22	9-22			
Schematic, socket, trimmers, parts	9-15	9-15			
Voltage, alignment	9-14	9-14			
Circuit changes for phono, pickup	10-40	10-40			
Installation, operation	10-1	10-1			
Adjustments, notes	10-2	10-2			
Chassis, details	10-3	10-3			
Details, notes	10-4	10-4			
Schematic, socket, trimmers, parts	9-16	9-16			
Voltage, alignment	9-17	9-17			
Circuit changes for phono, pickup	10-40	10-40			
Voltage, socket, trimmers, alignment	9-23	9-23			
Circuit changes for phono, pickup	9-24	9-24			
Schematic, socket, trimmers, parts	10-40	10-40			
Voltage, alignment, parts	6-21	6-21			
Schematic, voltage	10-27	10-27			
Alignment, socket, trimmers	10-28	10-28			
Schematic	2-1	2-1			
Schematic, socket, voltage, alignment	5-3	5-3			
6-M-91D, 6-M-91S, Chassis 5691			7-D-119, 7-D-126, 7-D-127, Schematic, parts	7-18	7-18
6-M-92, Chassis 5692			7-D-138, 7-D-151, 7-D-148, 7-D-162, 7-D-168, Chassis 5707		
6-M-192, Chassis 5697					
6-M-193, 6-M-194, Chassis 5697					
6M292, 6M293, Chassis 5645					
6M295, Chassis 5650					
6M390					
6-S-27, 6-S-52, Chassis 5619					
6-S-128, 6-S-137, 6-S-147, 6-S-152, 6-S-157, Chassis 5634					
6-S-203, 6-S-222, 6-S-223, 6-S-229, 6-S-239, 6-S-241, Chassis 5638					
6-S-254, 6-S-256, Chassis 5644					
6S254AT, 6S256AT, Chassis 5644AT					
6S301, 6S304, 6S305, 6S306, 6S321, 6S322, 6S340, Chassis 5651					
6S306, Automatic Record Changer Model 169-31					
6S330, 6S361, Chassis 5648					
6S341, 6S362, Chassis 5649					
6V27, 6V62 Chassis 5631					
6VA27, 6VA62, Chassis 5629					
ZE-6 7, 7-JB					

## ZENITH

MODEL	ZENITH RADIO CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
9-S-30, 9-S-54, 9-S-55 Chassis 5903	Schematic, socket, trimmers, parts	6-27		
9-S-203, 9-S-232, 9-S-242, 9-S-244, 9-S-262, 9-S-268, 9-S-264, Chassis 5905	Voltage, alignment, parts	6-28		
	Schematic, parts	8-35		
9S204AT, 9S232AT, 9S244AT, 9S262AT, 9S264AT, Chassis 5905AT	Phono, circuit	8-6		
9S307, 9S324, 9S344, 9S367, 9S369, Chassis 5907	Voltage, alignment, socket, trimmers	8-42		
	Schematic, parts	9-33		
9S307, 9S324, 9S344, 9S367, 9S369, Chassis 5907	Voltage, socket, trimmers, alignment	9-36		
9S307, Automatic Record Changer Model 169-51	Circuit changes for phono, pickup	10-40		
	Installation, operation	10-1		
9S365, Chassis 5906	Adjustments, notes	10-2		
	Chassis, details	10-3		
	Details, notes	10-4		
	Voltage, socket, trimmers, alignment	9-37		
	Circuit changes for phono, pickup	9-38		
ZE-9 10, 11, 12, 102, 112, 123	Schematic, data	10-40	654-A, B	
	Schematic, voltage, parts list	2-9	674-Q	2698
	Balancing notes, SPU notes and schematic	2-10	674-R	2716
10-S-130, 10-S-147, 10-S-153, 10-S-155, 10-S-156, 10-S-157, 10-S-160, Chassis 1004	Schematic, voltage, socket, trimmers, phono, data, parts	8-37, 8-38		
ZE-10 11, 12 11, 12, 14 (1st type)	Alignment	8-36	658, 9	2691
	Schematic	1-5, 1-8		
	See model 10			
11-E, 14-E ZE-11	Schematic, socket	1-2	*653	2686
	Power Pack—See ZE-9			
	Schematic, socket	1-3	*654	2687
	Schematic	1-7	*681, 8	2693
	Schematic	1-10	*669	2696
12 (2nd type)	Schematic, socket	1-2	*653	2686
12-L-57, 12-A-57, 12-A-58, 12-L-57, 12-L-58, Chassis 1202 & 1202A	Schematic, parts	7-29, 7-24		
12-S-205, 12-S-232, 12-S-245, 12-S-266, 12-S-266, 12-S-267, 12-S-268, Chassis 1204	Voltage, alignment, socket, trimmers	7-25		
	Schematic, parts	8-41		
12S2345, 12S370, 12S371, Chassis 1206	Phono, circuit	8-6		
	Voltage, alignment, socket, trimmers	8-42		
	Schematic, parts	9-39		
12-U-158, 12-U-159, Chassis 1208	Voltage, socket, trimmers, alignment	9-40		
	Schematic, voltage, socket, trimmers, parts, phono, data	8-39, 8-40		
ZE-12	Alignment	8-36	*665	2698
	Schematic	1-12		
ZE-13	Notes	7-22	*658, 9	2694
14 14-E ZE-14	Schematic	1-5, 1-8		
	See model 11			
	See model 11-3			
15, 16 15-E, 16 15-E, 16-E, 15-EP, 16-E, 15S308, 15S346, 15S372, 15S373, Chassis 1502	Schematic	1-7	*661	2698
	Schematic	1-10	*663	2696
	Schematic, socket	7-26	*665	2689
	Schematic, socket	7-26	*665	2689
	Schematic, parts	9-41		
	Voltage, socket, trimmers, alignment	9-42		
MODEL	ZENITH RADIO CORP.—(Cont.)	REVISED PAGE	EARLY COMPLETE PAGE	RADIOTRON
15S308, 15S346, 15S372, 15S373, Chassis 1502	Circuit changes for phono, pickup	10-40		
15S308, Automatic Record Changer Model 169-31	Installation, operation	10-1		
15-U-246, 15-U-269, 15-U-270, 15-U-271, 15-U-272, 15-U-273, Chassis 1501	Adjustments, notes	10-2		
	Chassis, details	10-3		
	Details, notes	10-4		
	Schematic, parts	8-43		
ZE-15 16 16-A-51, 16-A-63 Strato-sphere, Chassis 1601-C, 1601-P	Phono, circuit	8-6		
	Voltage, alignment, socket, trimmers	8-44		
	Schematic	1-12	*665	2698
	See model 15			
	Schematic, parts	7-27, 7-28		
16-E, 16-EP ZE-16	Voltage, socket, trimmers, alignment	7-29		
	See model 15-E			
ZE-17	Filter, schematic	1-12	*665	2698
18-E	Schematic, socket	1-12	*656	2690
	Data	Changes 8-8		2743
ZE-18	Schematic	1-9	*662	2695
27 Super-Zenith (Series Filament)	Schematic	1-30	656-A	2744
	Schematic, socket	1-6	*657	2692
31, 32 Battery	Schematic, socket	1-6	*657	2692
33, 34, 35, 35-A, 342, 352, 352-A, 362	Schematic, socket, voltage	1-8	*658	2694
33-X, 33-X, 34, 35, 35A	Power Pack—See ZE-10			
33-X, 363-X	Schematic, socket, voltage	1-6	*659	2691
34-P, 342-P	Schematic, socket, voltage	1-7	*661	2698
34-P, 35-P, 35-AP	Power Pack—See ZE-11			
35-P, 35-AP, 352-P, 352-AP	Schematic, socket, voltage	1-10	*668	2696
35-PX, 35-APX, 352-PX, 352-APX	Schematic, socket, voltage	1-9	*662	2695
35-PX, 35-APX	Power Pack—See ZE-18			
37-A	Schematic	1-9	*663	2695
39, 39-A, 392, 392-A	Power Pack—See ZE-11 & ZE-18			
39, 39-A	Schematic, voltage	1-11	*664	2697
40-A	Power Pack—See model ZE-12			
	Schematic, socket	1-11	*664	2697
41, 42	Power Pack—See ZE-12			
50	Schematic, socket, voltage	1-18	*666	2699
ZE-50	See model 60			
P51 Chassis	Schematic	1-15	*668	2701
52, 53	See model M-601			
52, 58	Schematic, socket	1-14	*667	2700
54	Voltage data	1-15	*667	2700
60, 61, 62, 64, 67, 603, 612, 613, 622, 642, 672, 50 (1929 Chassis)	Schematic, socket, voltage	1-16	*670	2702
ZE-60	Schematic	1-17	*671	2703
ZE-70	Schematic	1-17	*671	2703
70, 71, 72, 73, 77, 713, 722, 732, 772	Schematic, socket, voltage	1-18	*672	2704
80 Hypermetron	Tone control installation	1-19	*674-L	2705
	Schematic, socket	1-20	*674-K	2706
	Parts list	1-23	*674-I	2708
	Schematic, parts list	1-21	*674-J	2707
	Data	7-22		
90, 90, V-8, Chassis 2012-4J	Schematic, socket, data	2-3	674-M	2709
91, 92 (1st type)	Schematic	2-4	674-P-1	2710
91, 92 (2nd type)	Schematic	2-5	674-P-2	2711
91, 92 (3rd type)	Circuit data	2-6	674-P-3	2712
91, 92	Balancing notes	2-7	674-O	2713
	Chassis view, voltage, parts list	2-8	674-N	2714
	Notes	7-22		
103 (2017) Serials	See model 10			
#450,001-#450,450	Schematic, notes	2-16	674-P-4	2724
103 (2017) Above Serial #450,451	Schematic	2-15	674-P-5	2725
103 (2017) Above Serial #451,260	Schematic, socket	2-18	674-P-9	2728


ZENITH RADIO CORP.—(Cont.)			ZENITH RADIO CORP.—(Cont.)			ZENITH RADIO CORP.—(Cont.)			ZENITH RADIO CORP.—(Cont.)		
MODEL	REVIS	EARLY	MODEL	REVIS	EARLY	MODEL	REVIS	EARLY	MODEL	REVIS	EARLY
	ED PAGE	COMPLETE PAGE		ED PAGE	COMPLETE PAGE		ED PAGE	COMPLETE PAGE		ED PAGE	COMPLETE PAGE
103	Chassis view, parts list	2727	462	Changes	215	463	Changes	215	464	Changes	215
112, 122	Chassis layout, voltage	2728	470	See model 250		471	See model 250		472	See model 250	
169-31 Automatic Record Changer	See model 10	2730	473	See model 250		474	See model 250		475	See model 250	
200	See models 6S306, 9S307, 15S308		476	Schematic, socket, voltage	4-8	477	Schematic, socket, voltage	4-8	478	Schematic, socket, voltage	4-8
210, 211, 220, 221, 270, A & B	Schematic	2730	479	Schematic, socket, voltage	4-11	480	Schematic, socket, voltage	4-11	481	Schematic, socket, voltage	4-11
210-5, 211-5, 270-5	Schematic, socket	2730	482	Schematic, socket, voltage	4-12	483	Schematic, socket, voltage	4-12	484	Schematic, socket, voltage	4-12
215, 216, 217, 225, 263, 470, Chassis 2044	Socket, trimmers, voltage	2729	485	Schematic	4-13	486	Schematic	4-13	487	Schematic	4-13
215, 216, 225, Chassis 2044	See model 210		488	Voltage, socket	4-14	489	Voltage, socket	4-14	490	Voltage, socket	4-14
220, 221	Schematic, socket	2731	491	See model 258		492	See model 258		493	See model 258	
230, 240, 241, 244, 245, 271, Chassis 2036	Schematic	2732	494	Parts list, voltage	2-21	495	Parts list, voltage	2-21	496	Parts list, voltage	2-21
250, 251, 252, 259, 260, 261, 262, 269, 272, 299, 472, 516, 517, 518, Chassis 2031	Socket, trimmers, voltage	2733	497	Schematic, socket	2-22	498	Schematic, socket	2-22	499	Schematic, socket	2-22
250, 260, 272, Standard and SW	See model 210		500	Schematic, socket, voltage, trimmers, alignment	8-48	501	Schematic, socket, voltage, trimmers, alignment	8-48	502	Schematic, socket, voltage, trimmers, alignment	8-48
258, 268, 278, 280, 281, 288, 289, 478, 558, 568, 578, 589, 590 Early, Chassis 2051 Early	Voltage, parts list	2734	503	Schematic, socket, voltage, trimmers, alignment	8-50	504	Schematic, socket, voltage, trimmers, alignment	8-50	505	Schematic, socket, voltage, trimmers, alignment	8-50
258, 268, 278, 280, 281, 288, 289, 478, 558, 568, 578, 589, 590 Revised, Chassis 2051 Late	Schematic, data	2735	506	Parts	8-49	507	Parts	8-49	508	Parts	8-49
261, 262	Alignment, voltage, socket, trimmers	2736	509	See model 258		510	See model 258		511	See model 258	
263	Schematic	2736	512	Schematic, socket	8-50	513	Schematic, socket	8-50	514	Schematic, socket	8-50
268	Schematic, voltage, socket, trimmers, alignment	2736	515	See model 258		516	See model 258		517	See model 258	
268, 272	Parts	2736	518	See model 258		519	See model 258		520	See model 258	
270-5	Schematic, voltage, socket, trimmers, alignment	2736	521	See model 258		522	See model 258		523	See model 258	
271	Parts	2736	524	See model 258		525	See model 258		526	See model 258	
273, 410, 411, 412, 414, 420, 448, 478, Chassis 2030-2043	Schematic, socket	2736	527	See model 258		528	See model 258		529	See model 258	
277, 281, 288, 293, 478, 577, 588, 598, Chassis 2056	Voltage, electrical values	2736	530	See model 258		531	See model 258		532	See model 258	
278, 280, 281	Schematic, socket, voltage, alignment	2736	533	See model 258		534	See model 258		535	See model 258	
281	See model 258	2736	536	See model 258		537	See model 258		538	See model 258	
288, 289	See model 258	2736	539	See model 258		540	See model 258		541	See model 258	
288, 293	See model 277	2736	542	See model 258		543	See model 258		544	See model 258	
291, 292	See model 210	2736	545	See model 258		546	See model 258		547	See model 258	
299	See model 250	2736	548	See model 258		549	See model 258		550	See model 258	
333, 358-A DO	Schematic, socket	2736	551	See model 258		552	See model 258		553	See model 258	
342-P, 352-A	See model 33 & ZE-13	2736	554	See model 258		555	See model 258		556	See model 258	
352-P, 352-AP	See model 34-P & ZE-14	2736	557	See model 258		558	See model 258		559	See model 258	
352-PX, 352-APX	See model 35-P & ZE-14	2736	560	See model 258		561	See model 258		562	See model 258	
353-A	See model 35-PX	2736	563	See model 258		564	See model 258		565	See model 258	
362-X	See model 33	2736	566	See model 258		567	See model 258		568	See model 258	
392, 392-A	See model 33 & ZE-13	2736	569	See model 258		570	See model 258		571	See model 258	
410, 411, 412, 414, 420	See model 39, ZE-15 & ZE-16	2736	572	See model 258		573	See model 258		574	See model 258	
422	See model 273	2736	575	See model 258		576	See model 258		577	See model 258	
430, 440, 441, 442, 444, 619, Chassis 2033	Schematic, socket, voltage	2736	578	See model 258		579	See model 258		580	See model 258	
448	Schematic, socket	2736	581	See model 258		582	See model 258		583	See model 258	
460, Chassis 2047	Voltage	2736	584	See model 258		585	See model 258		586	See model 258	
462, 650, Chassis 2057	Schematic, voltage	2736	587	See model 258		588	See model 258		589	See model 258	
	Layout, trimmers, alignment	2736	590	See model 258		591	See model 258		592	See model 258	
	Schematic	2736	593	See model 258		594	See model 258		595	See model 258	
	Voltage, socket, alignment	2736	596	See model 258		597	See model 258		598	See model 258	
	data	2736	599	See model 258		600	See model 258		601	See model 258	
		2736	602	See model 258		603	See model 258		604	See model 258	
		2736	605	See model 258		606	See model 258		607	See model 258	
		2736	608	See model 258		609	See model 258		610	See model 258	
		2736	815	See model 258		816	See model 258		817	See model 258	
		2736	818	See model 258		8					

MODEL	ZENITH RADIO CORP.—(Cont.)	REVISED PAGE	RADIOTRON EARLY COMPLETE PAGE
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	Schematic, socket, alignment.....5-5		
Schematic, alignment, socket, trimmers .....	Schematic, alignment, socket, trimmers .....	10-34	
Schematic, socket, voltage, alignment .....	Schematic, socket, voltage, alignment .....	5-6	
Schematic .....	Schematic .....	5-7	
Voltage, socket, alignment.....5-8	Voltage, socket, alignment.....5-8		
Schematic .....	Schematic .....	5-9	
Voltage, socket, alignment.....5-10	Voltage, socket, alignment.....5-10		
Schematic, voltage, socket, parts .....	Schematic, voltage, socket, parts .....	6-5	
Alignment, socket .....	Alignment, socket .....	7-22	
Schematic .....	Schematic .....	5-11	
Voltage, socket, alignment.....5-12	Voltage, socket, alignment.....5-12		
Schematic, socket, parts .....	Schematic, socket, parts .....	6-6	
Schematic .....	Schematic .....	5-13	
Voltage, socket, alignment.....5-14	Voltage, socket, alignment.....5-14		
Schematic, parts .....	Schematic, parts .....	6-23	
Voltage, socket, trimmers, alignment .....	Voltage, socket, trimmers, alignment .....	6-24	
Schematic .....	Schematic .....	10-38	
Alignment, notes .....	Alignment, notes .....	10-33	
Schematic .....	Schematic .....	5-15	
Voltage, socket, alignment, notes .....	Voltage, socket, alignment, notes .....	5-16	
See model 805	See model 805		
See model 806	See model 806		
See model 808	See model 808		
See model 810	See model 810		
See model 814	See model 814		
See model 825	See model 825		
See model S-827	See model S-827		
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-15	
Voltage, socket, trimmers, parts .....	Voltage, socket, trimmers, parts .....	6-16	
Schematic, parts .....	Schematic, parts .....	6-25	
Voltage, socket, trimmers, alignment, parts .....	Voltage, socket, trimmers, alignment, parts .....	6-26	
Schematic .....	Schematic .....	6-7	
Voltage, alignment, socket, trimmers, parts .....	Voltage, alignment, socket, trimmers, parts .....	6-8	
See model 908	See model 908		
See model S-908	See model S-908		
See model 812	See model 812		
See model 810	See model 810		
Schematic .....	Schematic .....	6-9	
Voltage, alignment, socket, trimmers .....	Voltage, alignment, socket, trimmers .....	6-10	
See model 835	See model 835		
Schematic, parts .....	Schematic, parts .....	6-11, 6-12	
Voltage, socket, trimmers .....	Voltage, socket, trimmers .....	6-13	
Alignment, service notes.....6-14	Alignment, service notes.....6-14		
Schematic, parts .....	Schematic, parts .....	6-29, 6-30	
Stratosphere 1000Z	Stratosphere 1000Z		
Chassis 2501-C, 2501-P	Chassis 2501-C, 2501-P		
See model 475	See model 475		
See model 476	See model 476		
See model 476-B	See model 476-B		
See model 70 Series	See model 70 Series		
See model 476-B	See model 476-B		
See model 476	See model 476		
See model 474	See model 474		
Schematic, socket, alignment.....5-5	S		




# RIDER

## Publications

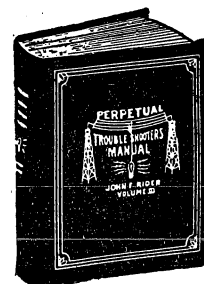

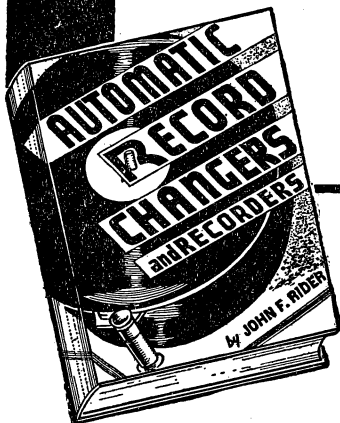*Just what  
the Servicing Industry  
ordered!—*



### RIDER'S "Automatic Record Changers and Recorders"

800,000 record changers are providing an important source of profit for the wide-awake service shops of the country and creating a need for adequate and ready reference data to speed up trouble shooting and repair. Rider anticipated this need and has prepared—just when you need it—a sturdily bound volume containing everything you need know on any automatic record changer or recorder coming to your shop.

Heretofore, the serviceman's prime interest has revolved around the invisible defects which accompany the operation of electrical devices. Mechanics in radio receivers was limited to a lesser degree. However, with the introduction of the automatic record changer, some knowledge of the development of motion by means of gears, levers and cams has become necessary. Hence the birth of Automatic Record Changers and Recorders. Printed on 8½ x 11 paper, the same size as Rider Manuals, the book covers, by means of explanatory text, mechanical and electrical diagrams, all the information you must have to service these high cost instruments quickly and profitably.

#### CONTENTS

Chapter I—MOTORS AND DRIVES. D-C Motors. A-C Motors. Universal Motors. Maintenance of Motors. Commonplace Troubles. SPEED REGULATORS and REDUCTION DRIVES. Chapter II—RECORDERS AND PHONOGRAPHS. The Cutting Head. The Groove. Recording Needles. Pick-ups. Phonograph Needles. Chapter III—AUTOMATIC RECORD CHANGERS. Mechanisms. Troubles. Chapter IV—ANALYSIS OF RCA MODEL RP-152-C RECORD CHANGER. MANUFACTURERS' SERVICE DATA.

744 PAGES . . . . . BOUND IN BUCKRAM . . . . . \$7.50

## SERVICING BY SIGNAL TRACING



Signal Tracing is destined to become the universally adopted method of locating defects in communication systems, no matter what the nature of the system—if it is a home broadcast receiver, auto-radio receiver, police receiver, commercial, marine, navy or army receiver. Every public address system, every centralized radio system comes within the capabilities of signal tracing. . . . Television receivers, facsimile receivers and other systems intended for special application can be serviced with equal ease. . . . Signal Tracing, founded upon the signal itself, is the most basic, most fundamental method of trouble shooting ever devised. . . . It is free of every limitation which in the past has

hindered speedy service operations. . . .

You can't afford to be without this book. . . . We mean every word of this statement. . . . It is vital to your immediate welfare—to your future. . . . Get your copy today—NOW!

#### CONTENTS

Chapter I—Introduction to Signal Tracing. Chapter II—Amplifier Operation and The Signal. Chapter III—Diode Detector Tube Systems. Chapter IV—Multi-Element Detector Systems. Chapter V—Oscillator Tube Systems. Chapter VI—Mixer Tube Systems. Chapter VII—Control Circuits and Voltages. Chapter VIII—Coupling Devices. Chapter IX—The T-R-F Receiver. Chapter X—The Superheterodyne Receiver. Chapter XI—Television and Facsimile Receivers. Chapter XII—Public Address Systems. Chapter XIII—Localizing Defects by Signal Tracing. Chapter XIV—Signal Tracing in Receiver Design.

360 PAGES . . . 188 ILLUSTRATIONS . . . \$4.00

SPANISH EDITION . . . \$4.00

## VACUUM TUBE VOLTMETERS

The vacuum-tube voltmeter has been rapidly forging to the front as a favorite tool of engineers, research workers and servicemen. By its proper use, dynamic measurements can be made under any and all conditions with a minimum of effort and time. Here is a book that is a perfect mine of information for everybody who wants to know all about these important instruments. Not only is the theory explained upon which the functioning of the different types of v-t voltmeters is based, but the practical applications of these instruments are completely described. Like nearly all types of voltmeters, multipliers and shunts are employed with vacuum-tube voltmeters to extend their ranges. These and their uses are explained, as is the calibration of the different types.

For those men who are interested in the construction of v-t voltmeters, adequate information will be found for v-t voltmeters were built in the author's laboratory, and constants are given for the components of many types, as well as a wealth of other useful data.



#### CONTENTS

Chapter I. Fundamentals of Vacuum-Tube Voltmeter. Chapter II. Diode Vacuum-Tube Voltmeters. Chapter III. Triode Vacuum-Tube Voltmeters. Chapter IV. Slide-Back Vacuum-Tube Voltmeters. Chapter V. Rectifier-Amplifier Vacuum-Tube Voltmeters. Chapter VI. Tuned Vacuum-Tube Voltmeters. Chapter VII. Audio-Frequency and Logarithmic Vacuum-Tube Voltmeters. Chapter VIII. Vacuum-Tube Voltmeters for D-C Voltage, Current, and Resistance Measurements. Chapter IX. Design and Construction of Vacuum-Tube Voltmeters. Chapter X. Calibration and Testing of V-T Voltmeters. Chapter XI. Applications of V-T Voltmeters. Bibliography.

180 PAGES . . . 111 ILLUSTRATIONS . . . \$2.50



---

# *Rider's Manuals* **HAD TO** **BE BETTER**

*to become the "standard"*

Vol. XIV . 1376 Pages . \$12.50

Vol. XIII . 1672 Pages . \$12.50

Vol. XII . 1648 Pages . \$12.50

Vol. XI . 1652 Pages . \$12.50

Vol. X . 1664 Pages . \$12.50

Vol. IX . 1672 Pages . \$12.50

Vol. VIII . 1650 Pages . \$12.50

Vol. VII . 1600 Pages . \$12.50

Vol. VI . 1240 Pages . \$ 9.50

Vols. I to V abridged . 2000 Pages . \$15.00

Vol. I, II, III, IV, and V out of print — no longer available



**John F. Rider Publisher, Inc.**

404 Fourth Avenue, New York 16, N. Y.

---



# ADV Plans, LLC

## Copyright Notice:

The entire contents of this CD/DVD are copyright 2014 by ADV Plans, LLC. All Rights Reserved.

Reproduction or distribution of this disk, either free or for a fee is strictly prohibited. We actively monitor and remove listings on eBay thru Vero.

You are free to copy or use individual images in your own projects, magazines, brochures or other school projects.

Only the sellers listed here are authorized distributors of this collection:  
[www.theclassicarchives.com/authorizedsuppliers](http://www.theclassicarchives.com/authorizedsuppliers)

Please view our other products at  
[www.theclassicarchives.com](http://www.theclassicarchives.com),  
or our ebay stores:

[TheClassicArchives](#)  
[ADVPlans](#)  
[SuperShedPlans](#)

